

# Processor Data Paths - ALU and Registers

---

Incorporating the ALU into a Processor Data Path




# L4 – Incorporate ALU into data path

---

- Building up the data path
- Control of the data path
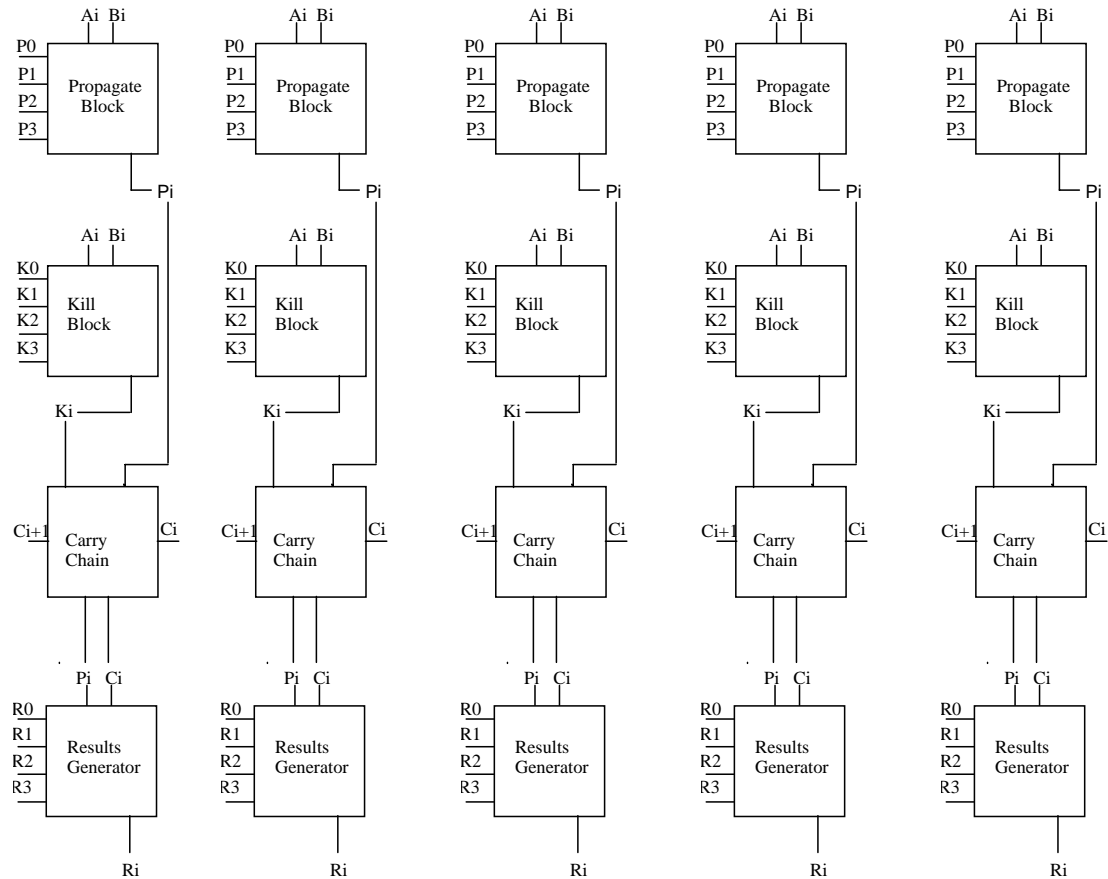
# Have our multifunction ALU


- Will now put an interface around the ALU and build up a data path


 
# The wrapper


---

- Establish an interface to the ALU slices
- Have the data inputs
- Have a Carry in
- Have control in
- Produce
  - The result R
  - A carry out



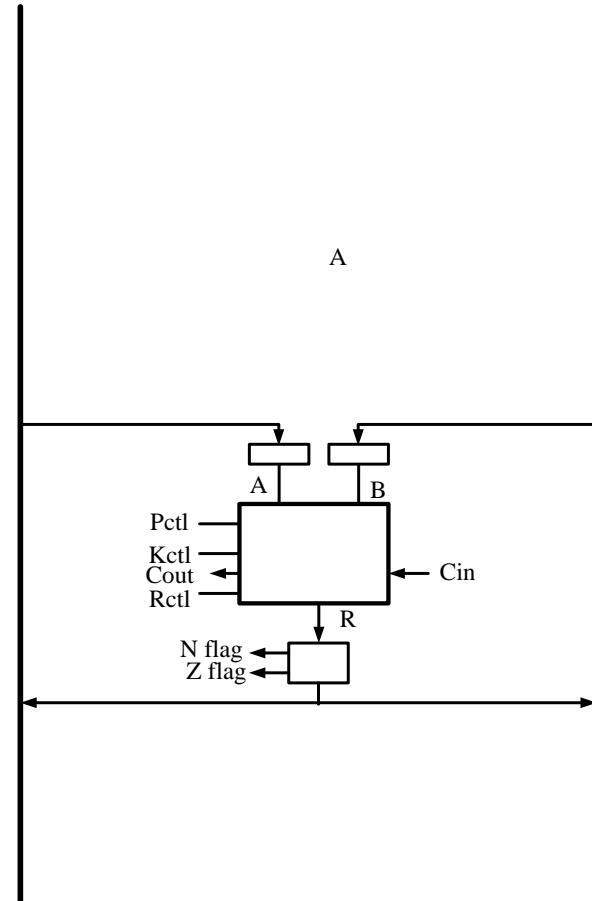
# Build up step 1

- Add input and output latches/bus drivers
- Add 2 internal data busses
- Add flag generation
- Inputs & control – A,B,Cin,Pctl, Kctl, Rctl
- Outputs – Cout, R, Nflag, Zflag


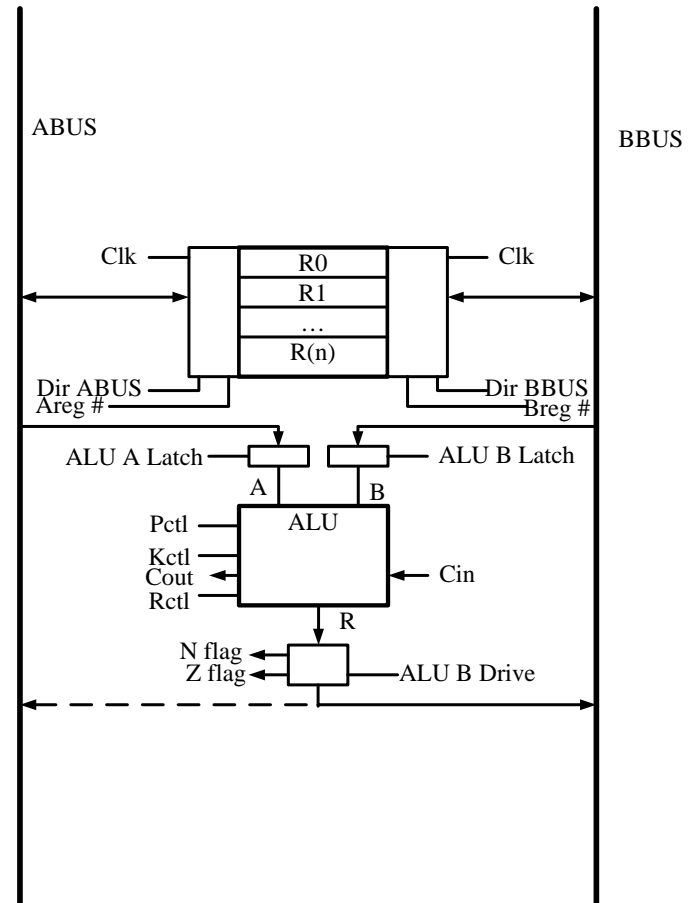
# Build up step 2

- Now add a general purpose registers
- These are dual ported registers
- Loading or driving of registers on the bus is controlled by the clock
- Busses are tristate






# Dual Ported Registers

---

- Register are dual ported
  - Registers can be loaded from or drive a value onto both the A Bus and B Bus simultaneously
  - Possible combinations on same cycle
    - Drive both the A Bus and B Bus
    - Load from both the A Bus and B Bus
      - Must be different registers!!!!!!!!!!
      - Register bank does not check for this – responsibility of the controller
    - Load from one Bus and drive the other
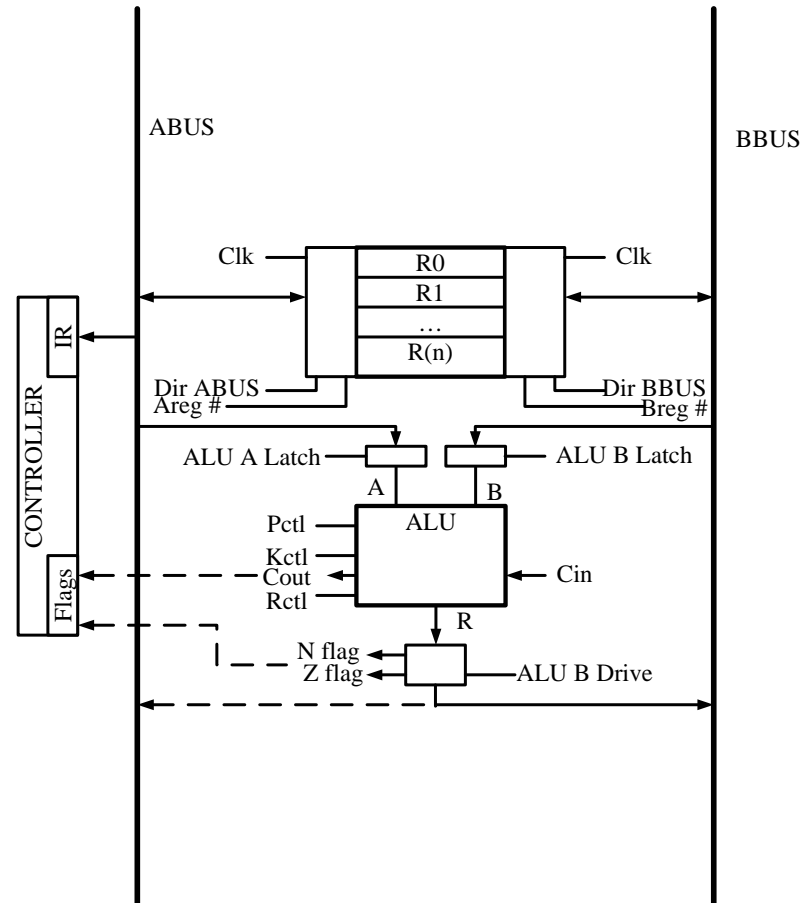
# Now add the controller


- Note the Instruction Register and Flags register





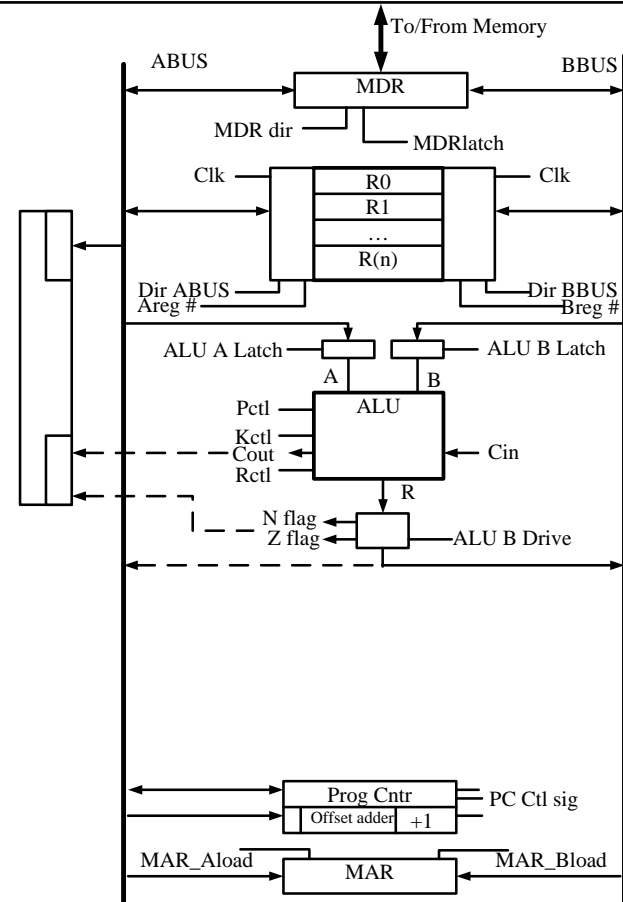
# Program Counter and MDR, MAR

- MDR – Memory Data Register
- MAR – Memory Address Register
- PC Register increment and offset integrated into register design


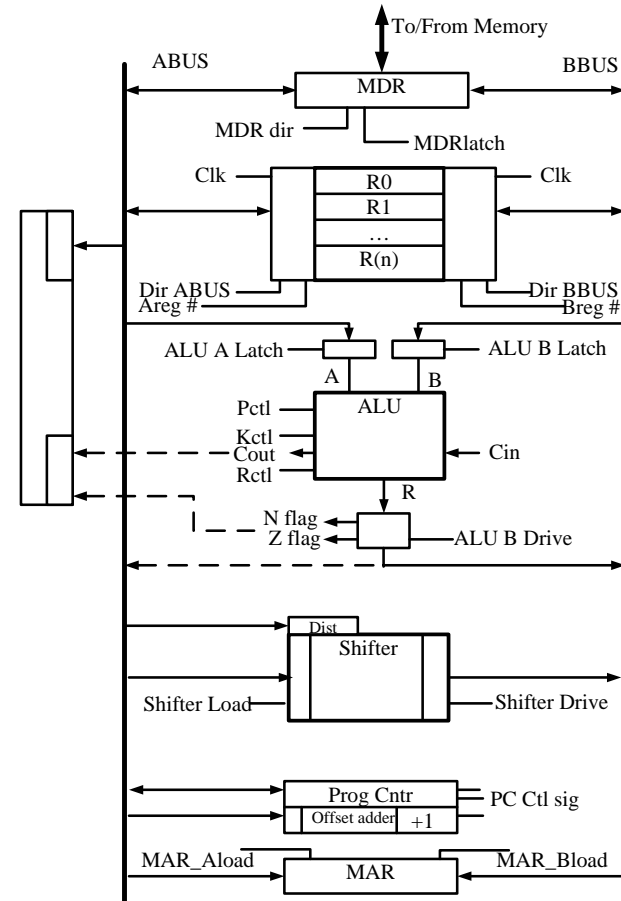
# Other Functional Units

- May want to incorporate
  - Shifter
  - Floating Point Units
  - Index addressing registers
  - Etc.




# General Operation of a Datapath

---

- Datapaths are generally synchronous
- Internal clock most likely higher than bus clock
- Typical RTL of datapath
  - Cyc 1: Mem(PC)  $\rightarrow$  IR
  - PC + 1  $\rightarrow$  PC
  - Cyc 2: RS1+RS2  $\rightarrow$  ALUout
  - Cyc 3: ALU out  $\rightarrow$  RS1

# Datapath Control Evolution


- Finite State Machine (FSM)
  - Fixed and unvarying action of a datapath
  - FSM implemented with PLA

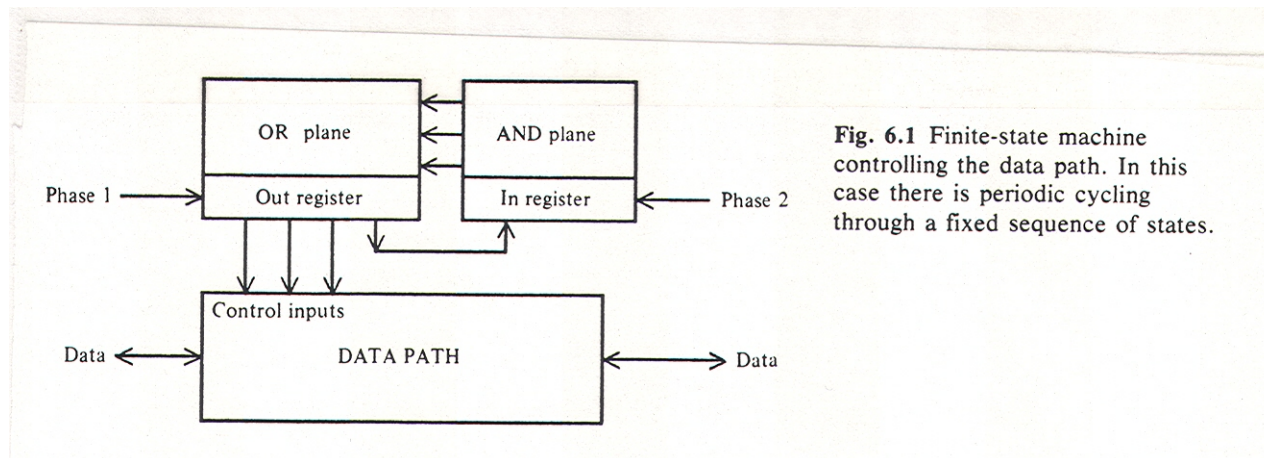

**Fig. 6.1** Finite-state machine controlling the data path. In this case there is periodic cycling through a fixed sequence of states.

# Use of flags


- Here the current data can affect the action of the controller

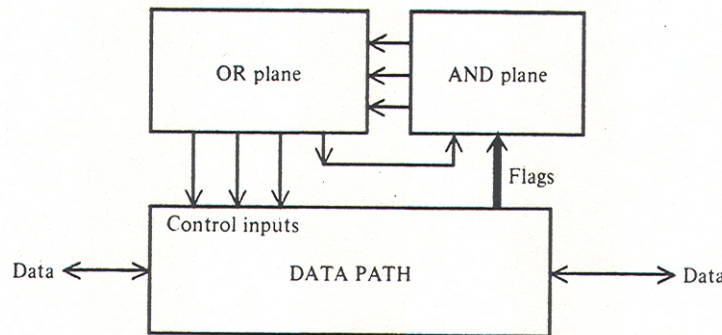

**Fig. 6.2** Finite-state machine controlling the data path. In this case the next state can be a function of the previous operation's outcome.

# Load flags

- By loading a flags register can use them to affect the controller only at specific points in the “program”

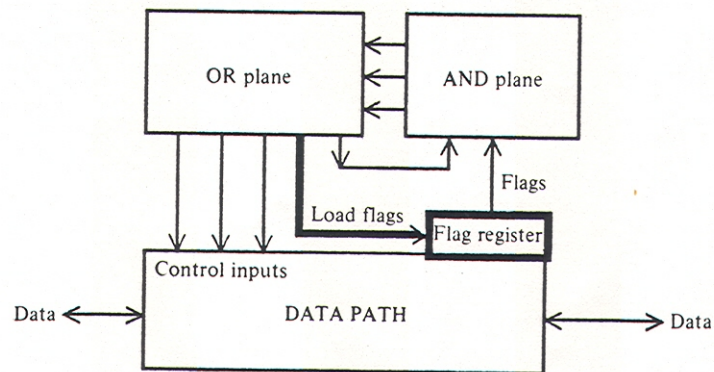

**Fig. 6.3** Finite-state machine controlling the data path. In this case a data path operation result may control machine sequencing for a number of later cycles.

# Data from memory used

- In addition to flags, data from memory can affect the state and the datapaths action

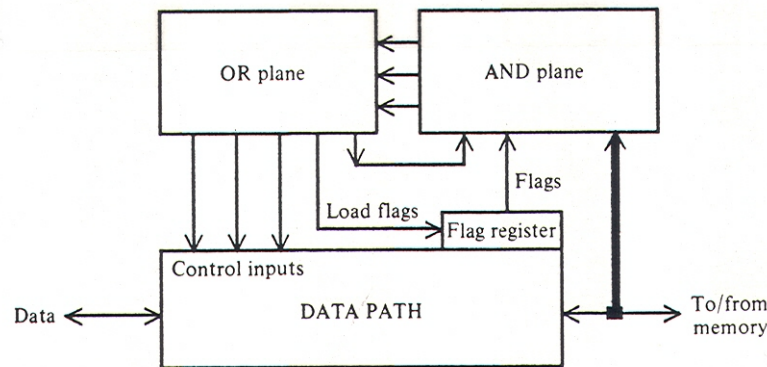
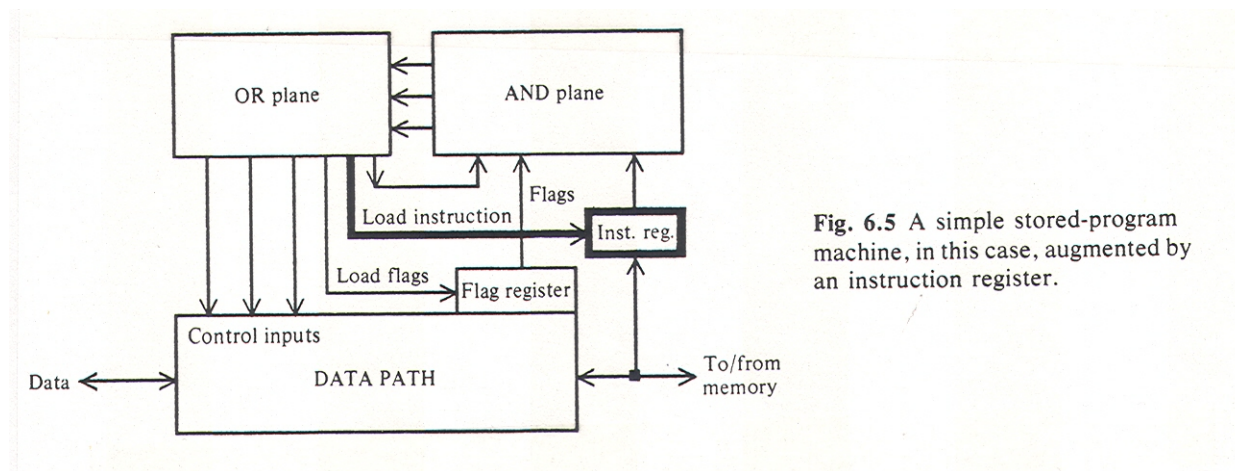


Fig. 6.4 A simple stored-program machine, where data read from a memory can affect machine sequencing.

# Instruction Reg

- Have now progressed to a “stored” program

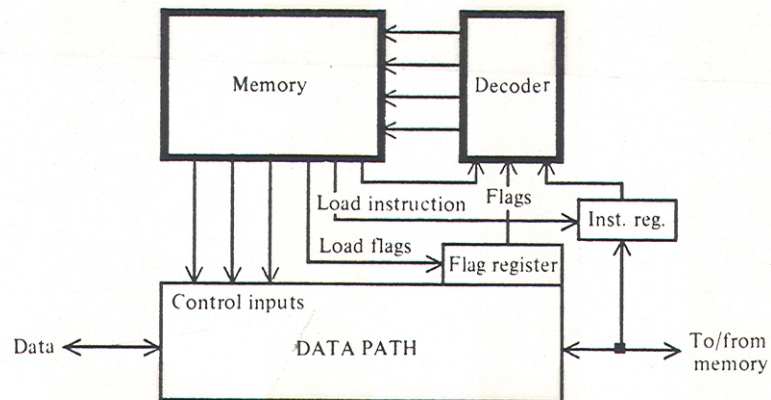


**Fig. 6.5** A simple stored-program machine, in this case, augmented by an instruction register.



# Alternative form

- Here use a ROM rather than a PLA finite state machine



**Fig. 6.7** An alternative form of stored-program machine, illustrating the use of a decoder and memory to implement the state machine controlling the data path.

# Another alternative

- Use a microprogram counter

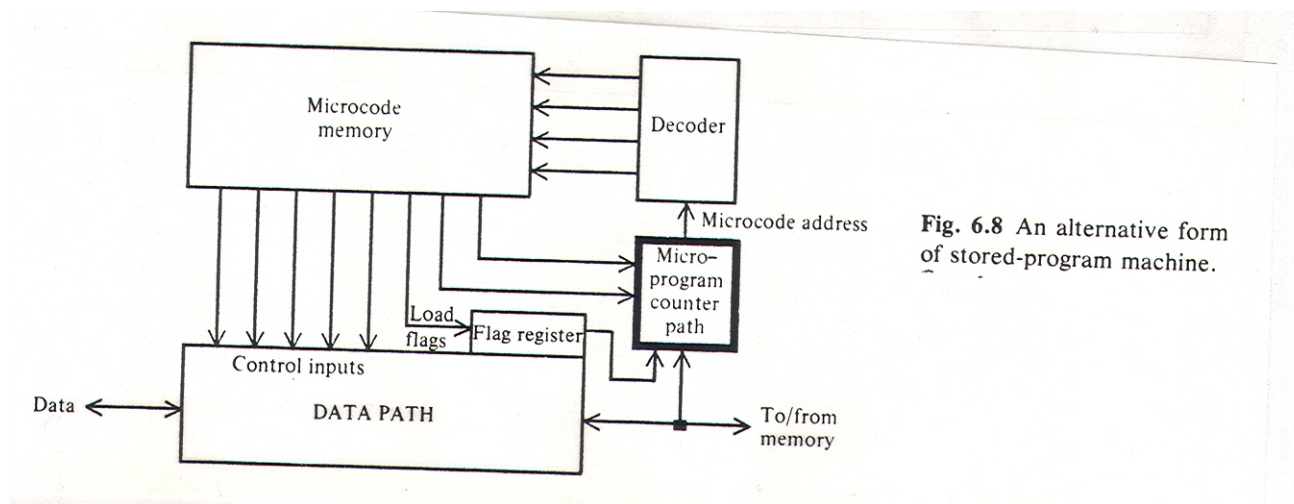


Fig. 6.8 An alternative form of stored-program machine.

# A different slice

- Just a different visualization

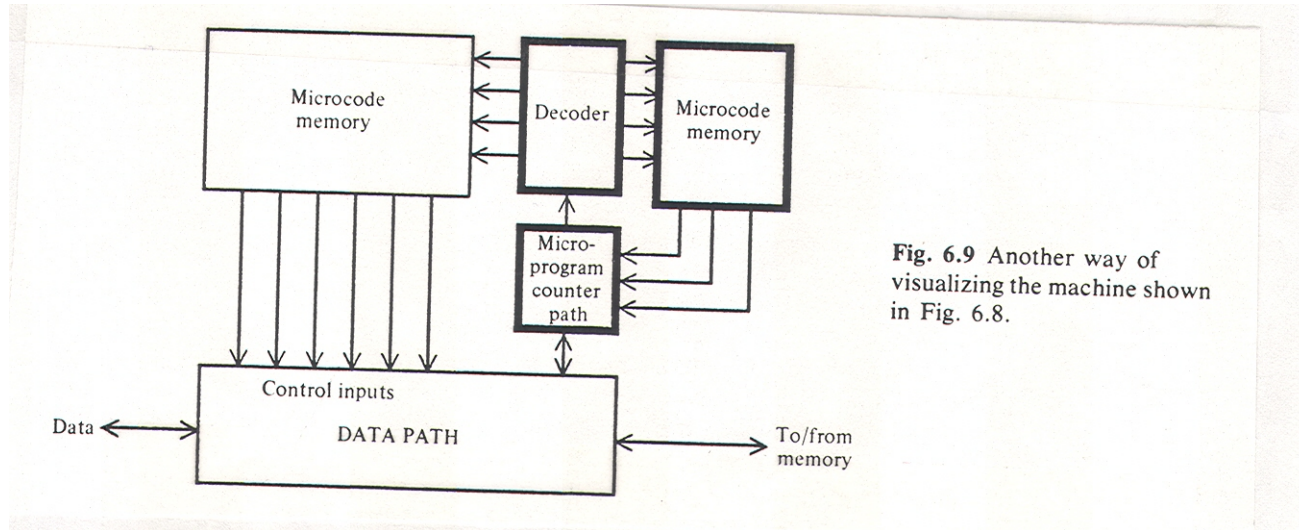


Fig. 6.9 Another way of visualizing the machine shown in Fig. 6.8.

# Operation

- Shows steps the controller would go through to execute the instructions

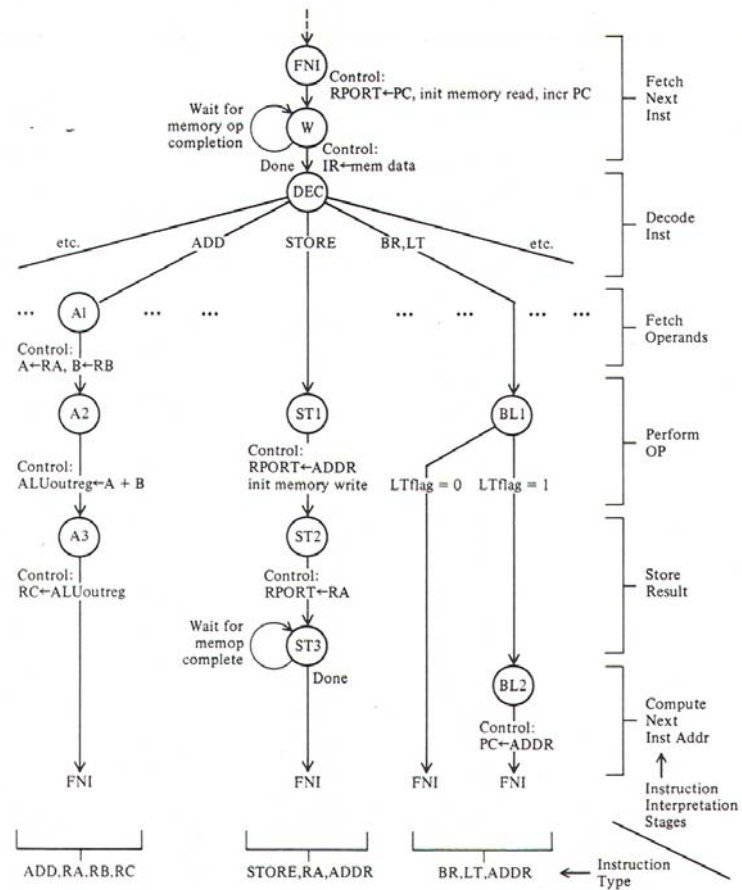


Fig. 6.6 A portion of the state diagram for the controller of a stored-program machine, illustrating some typical instruction interpretation state sequences and their associated control outputs.

# Operation Examples – ALU op

Function of sub-sequence	Control [& State] sequence	Comments
Fetch Next Inst:	$RPORT \leftarrow PC$ read memory $PC \leftarrow PC + 1$ [Y' = fcn(memop complete)] - $IR \leftarrow \text{mem data}$	Place next instr. address in right port. Raise control line to initiate memory read. Increment PC, overlapping incr. with fetch. Loop here till memory read completes. Load IR with inst, when read completed.
Decode Instruction:	[Y' = fcn(IR)]	Set machine state as fcn of instruction.
Fetch Operands:	$A \leftarrow R7$ $B \leftarrow R2$	Load ALU input registers with operands.
Perform Operation:	$ALUoutreg \leftarrow A + B$	Add A and B, store in output register.
Store Result:	$R5 \leftarrow ALUoutreg$ [Y' = FNI]	Send result address to R5. Inst. not a branch, so simply return to FNI state.



# Store result back to memory

Function of sub-sequence	Control [& State] sequence	Comments
Fetch Next Inst:	RPORT $\leftarrow$ PC read memory PC $\leftarrow$ PC + 1 [Y' = fcn(memop complete)] IR $\leftarrow$ mem data	Place next instr. address in right port. Raise control line to initiate memory read. Increment PC. Loop here till memory read completes. Load IR with inst, when read completed.
Decode Instruction:	[Y' = fcn(IR)]	Set machine state as fcn of instruction.
Perform Operation:	RPORT $\leftarrow$ IR(ADDRESS) write memory	Send the contents of IR address field to memory. Raise write control line to init. memory write.
Store Result:	RPORT $\leftarrow$ R3 [Y' = fcn(memop complete)] [Y' = FNI]	Place data in right output port. Loop here till memory write completes. Inst. not a branch, so simply return to FNI state.