



The Ohio State University
Department of Electrical and Computer Engineering

ECE 205
Spring 2009

Quiz #3

May 8, 2009

Name (print) _____


Grade _____

- Note -

- There is 1 problem on the following pages.
- Please read the questions carefully.

“No aid is given, received or observed”

Signature _____

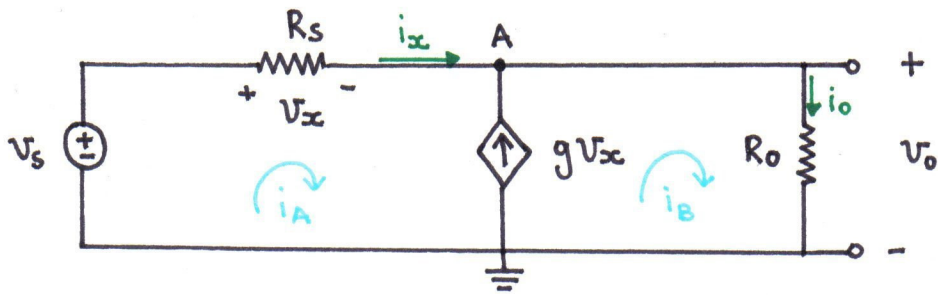

Find an expression for the voltage gain v_o/v_s

SOLUTION 1 NODE VOLTAGE ANALYSIS

$$\left\{ \begin{array}{l} \frac{V_A - V_s}{R_s} + \frac{V_A}{R_o} = gV_x \quad \text{NODE EQUATION} \\ V_x = V_s - V_o \quad \text{CONTROLLING VARIABLE IN TERMS OF THE OTHER UNKNOWNNS} \\ V_A = V_o \end{array} \right.$$

$$\Rightarrow \frac{V_o}{R_s} + \frac{V_o}{R_o} = \frac{V_s}{R_s} + g(V_s - V_o)$$


$$\left(\frac{1}{R_s} + \frac{1}{R_o} + g \right) V_o = \left(\frac{1}{R_s} + g \right) V_s$$

$$\left(\frac{R_o + R_s + gR_sR_o}{R_sR_o} \right) V_o = \left(\frac{1 + gR_s}{R_s} \right) V_s$$

$$\boxed{\frac{V_o}{V_s} = \frac{R_o(1 + gR_s)}{R_o + R_s + gR_sR_o}}$$

SOLUTION 2

SOURCE TRANSFORMATION

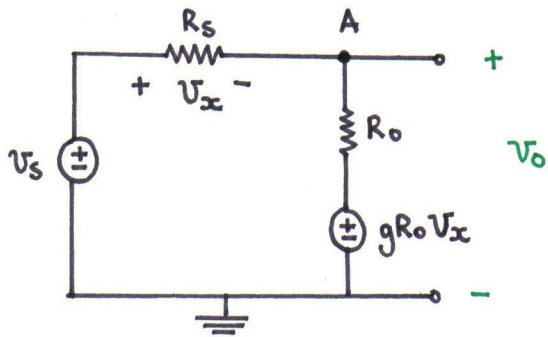

$$V_A = V_o \quad (2)$$

$$\frac{V_A - V_s}{R_s} + \frac{V_A - gR_o V_x}{R_o} = 0 \quad (1)$$

$$V_x = V_s - V_o \quad (3)$$

Combining (1), (2) and (3) \Rightarrow $(V_o - V_s) R_o + R_s [V_o - gR_o(V_s - V_o)] = 0$

$$(R_o + gR_s R_o) V_s = (R_o + R_s + gR_s R_o) V_o$$

$$\boxed{\frac{V_o}{V_s} = \frac{R_o + gR_s R_o}{R_o + R_s + gR_s R_o}}$$

SOLUTION 3

MESH CURRENT ANALYSIS

$$\begin{cases} gV_x = i_B - i_A & (1) \text{ CONSTRAINT IMPOSED BY THE CURRENT SOURCE} \\ R_s i_A + R_o i_B = V_s & (2) \text{ SUPERMESH EQUATION} \\ V_x = R_s i_A & (3) \text{ CONTROLLING VARIABLE IN TERMS OF THE OTHER UNKNOWN} \end{cases}$$

(1) and (3) \Rightarrow $gR_s i_A + i_A = i_B \quad \Rightarrow \quad i_A = \frac{1}{1 + gR_s} i_B$

substitute in (2) \Rightarrow $\frac{R_s}{1 + gR_s} i_B + R_o i_B = V_s$


$$\frac{R_s + R_o(1 + gR_s)}{1 + gR_s} i_B = V_s \quad \Rightarrow \quad i_B = \frac{1 + gR_s}{R_s + R_o(1 + gR_s)} V_s$$

$$\boxed{V_o = R_o i_B}$$

\Rightarrow


$$\boxed{\frac{V_o}{V_s} = \frac{R_o i_B}{V_s} = \frac{R_o(1 + gR_s)}{R_s + R_o(1 + gR_s)}}$$

SOURCE TRANSFORMATION

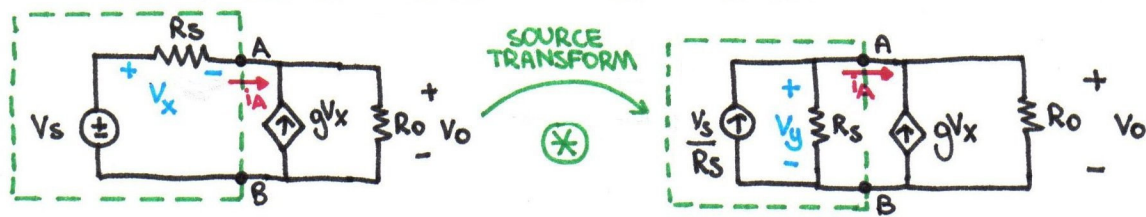

if you transform the independent voltage source into a current source you "lose" the info about V_x . NOTE THAT $V_x \neq V_y$ (in general)

SIMPLE EXAMPLE

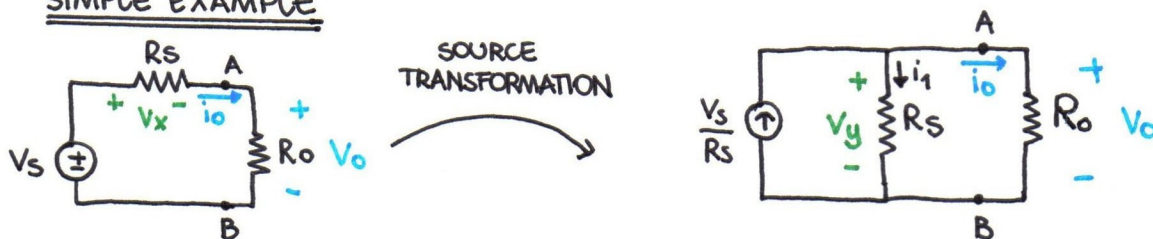

$$i_o = \frac{V_s}{R_s + R_o}$$

$$V_o = \frac{R_o}{R_s + R_o} V_s$$

$$V_x = \frac{R_s}{R_s + R_o} V_s$$

using current division rule

$$i_1 = \frac{R_o}{R_s + R_o} \cdot \frac{V_s}{R_s}$$

$$i_o = \frac{R_s}{R_s + R_o} \cdot \frac{V_s}{R_s} = \frac{V_s}{R_s + R_o}$$

$$V_o = R_o i_o = \frac{R_o}{R_s + R_o} V_s$$

$$V_y = V_o \neq V_x$$

i_o and V_o do not change but the potential difference across R_s changes (if $R_s \neq R_o$)

WHEN YOU USE SOURCE TRANSFORMATION THE TWO CIRCUITS WILL HAVE THE SAME i - v CONSTRAINTS AT THE TERMINALS A-B THAT IS, EITHER MODEL DELIVERS THE SAME VOLTAGE AND CURRENT TO THE REST OF THE CIRCUIT, HOWEVER

- EQUIVALENT SOURCES DO NOT HAVE THE SAME INTERNAL POWER LOSS
- IN THE TRANSFORMATION YOU "LOSE THE INFO" ABOUT THE CURRENT AND POTENTIAL DIFFERENCE ACROSS R_s . So if you want to apply source transformation (*), you have to derive first an expression for V_x : $V_x = R_s \cdot i_A$ then you can change the source and consider the "equivalent current i_A " (= current through the terminal A) But you CAN'T SAY $V_x = V_y$