

Problem#1: Problem 1-3 textbook

An ampere-hour (Ah) measures the time integral of the current. The recording of this meter in an 8-hour period is 3300 Ah. Find the number of coulombs that flowed through the meter during the recording time period.

$$1 \text{ ampere} = \frac{1 \text{ coulomb}}{\text{second}}$$


$$i = \frac{\Delta q}{\Delta t}$$

$$1 \text{ hour} = 60 \cdot 60 = 3600 \text{ seconds} \quad \Rightarrow \quad 1 \text{ Ah} = 3600 \text{ coulombs}$$


$$3300 \text{ Ah} = 3300 \cdot 3600 = 11.88 \cdot 10^6 \text{ coulombs} = \boxed{11.88 \text{ MC}}$$

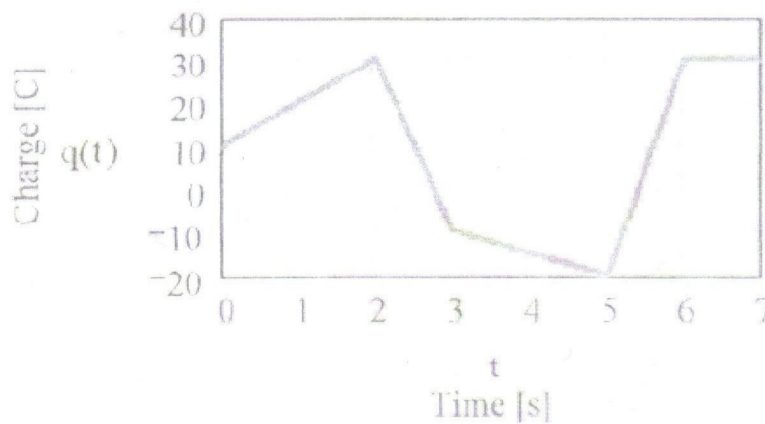Problem#2: Problem 1-8 textbook

The Figure shows the plot of the net positive charge flowing in a wire. Using MATLAB sketch the plot of the current during the same time period.


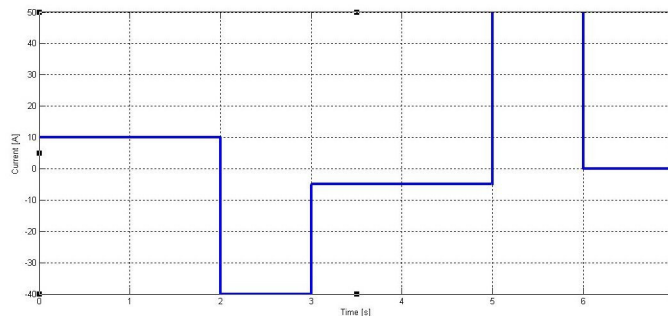
```
>> stairs([0,1,2,3,4,5,6,7],[10,10,-40,-5,-5,50,0,0])  
>> grid  
>> xlabel('Time [s]')  
>> ylabel('Current [A]')
```



Problem#3: Problem 1-9 textbook

The net positive charge flowing through the device varies with the equation $q(t) = 3t^2$ C. Find the current through the device at $t=0, t=1$ and $t=3$ sec.

$$i = \frac{dq}{dt} \quad \Rightarrow \quad i(t) = \frac{d(3t^2)}{dt} = 6t \text{ A}$$

$$i(0) = 0 \text{ A}$$

$$i(1) = 6 \text{ A}$$

$$i(3) = 18 \text{ A}$$

t [s]	i [A]
0	0
1	6
3	18

Problem#4: Problem 1-17 textbook

The i - v relationship of a photocell is $i = e^v - 10$ A. For $v=-2, 2$ and 3 V find the device power and state if it is absorbing power or delivering power.

(i) $v = -2$ $i = e^{-2} - 10 = -9.865 \text{ A}$
 $p = v \cdot i = (-2) \cdot (-9.865) = \underline{\underline{19.73 \text{ W}}}$ ABSORBING ($p > 0$)

(ii) $v = 2$ $i = e^2 - 10 = -2.611 \text{ A}$
 $p = v \cdot i = (2) \cdot (-2.611) = \underline{\underline{-5.222 \text{ W}}}$ DELIVERING ($p < 0$)

(iii) $v = 3$ $i = e^3 - 10 = 10.086 \text{ A}$
 $p = v \cdot i = (3) \cdot (10.086) = \underline{\underline{30.258 \text{ W}}}$ ABSORBING ($p > 0$)

Problem#5: Problem 1-14 textbook

An incandescent lamp absorbs 60 W when connected to 120-V source.

- Find the current through the lamp.
- Find the cost of operating the lamp for 24 hours when electricity cost is 6.8 cents/kWh.

$$(a) \quad i = \frac{P}{V} = \frac{60 \text{ W}}{120 \text{ V}} = \boxed{0.5 \text{ A}}$$

(b) NOTE the watt-hour (Wh) is a unit of energy. Recall that $1 \text{ watt} = \frac{1 \text{ joule}}{1 \text{ second}}$

therefore $1 \text{ Wh} = 1 \text{ W} \cdot 3600 \text{ s} = 3600 \text{ J}$
 $1 \text{ kWh} = 1000 \text{ Wh} = 3.6 \cdot 10^6 \text{ J}$

$$60 \text{ W} \cdot 24 \text{ hr} = 1440 \text{ Wh} = 1.44 \text{ kWh}$$

$$\text{cost} = 6.8 \frac{\text{cents}}{\text{kWh}} \cdot 1.44 \text{ kWh} = 9.792 \text{ cents} = \boxed{0.09792 \text{ \$}}$$


Problem#6: Problem 1-19 textbook

The maximum power a device can dissipate is 0.5 W. Determine the maximum current allowed by the device power rating when voltage is 15 V.

$$i_{\max} = \frac{P_{\max}}{V} = \frac{0.5 \text{ W}}{15 \text{ V}} = 0.0333 \text{ A} = \boxed{33.3 \text{ mA}}$$

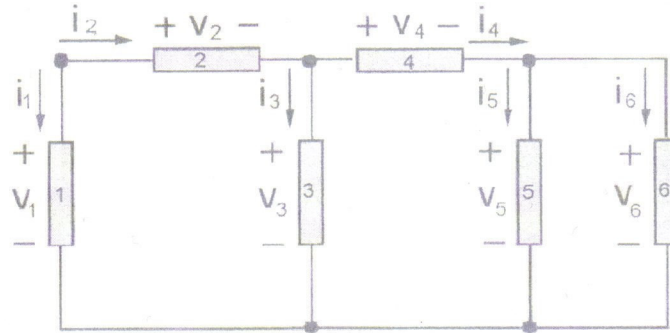Problem#7: Problem 1-23 textbook

The Figure shows a circuit with voltage and current variable assigned to each of the six devices. Use power balance to find v_4 when $v_1=20$ V, $i_1=-2$ A, $p_2=20$ W, $p_3=10$ W, $i_4=1$ A, and $p_5=p_6=2.5$ W. Is device 4 absorbing or delivering power?



$$P_1 = v_1 \cdot i_1 = (20) \cdot (-2) = -40 \text{ W}$$

POWER BALANCE : $P_1 + P_2 + P_3 + P_4 + P_5 + P_6 = 0$

$$P_4 = - (P_1 + P_2 + P_3 + P_5 + P_6) = - (-40 + 20 + 10 + 2.5 + 2.5) = -(-5) = \boxed{5 \text{ W}}$$

$$P_4 = 5 \text{ W} > 0 \Rightarrow \text{device 4 is } \underline{\text{ABSORBING POWER}}$$

$$v_4 = \frac{P_4}{i_4} = \frac{5 \text{ W}}{1 \text{ A}} = \boxed{5 \text{ V}}$$

Problem#8: Problem 2-2 textbook

A $6.2 \text{ k}\Omega$ resistor dissipates 12 mW . Find the current through the resistor.


$$R = 6.2 \text{ k}\Omega = 6.2 \cdot 10^3 \Omega$$

$$p = 12 \text{ mW} = 12 \cdot 10^{-3} \text{ W}$$

$$p = i^2 R \Rightarrow i = \sqrt{\frac{P}{R}} = \sqrt{\frac{12 \cdot 10^{-3}}{6.2 \cdot 10^3}} = \sqrt{\frac{12 \cdot 10^{-6}}{6.2}} = \boxed{1.39 \text{ mA}}$$

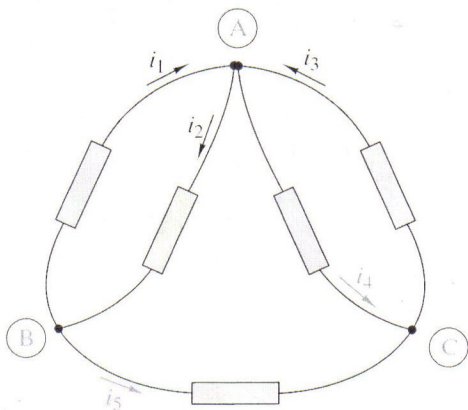Problem#9: Problem 2-17 textbook

In Figure $i_2=2$ A, $i_3=-5$ A, and $i_4=4$ A. Find i_1 and i_5 .



NODE (A) $i_1 + i_3 = i_2 + i_4$

$i_1 = i_2 + i_4 - i_3 = 2 + 4 - (-5) = 11$ A



NODE (B) $i_1 + i_5 = i_2$

$i_5 = i_2 - i_1 = 2 - (11) = -9$ A

Problem#10: Problem 2-22 textbook

- Use the passive sign convention to assign a voltage and current to every element
- Use KVL to find the voltage across each resistor.
- By using Ohm's law find the current through each resistor.
- Use KCL to find the current through each voltage source.

PASSIVE SIGN CONVENTION

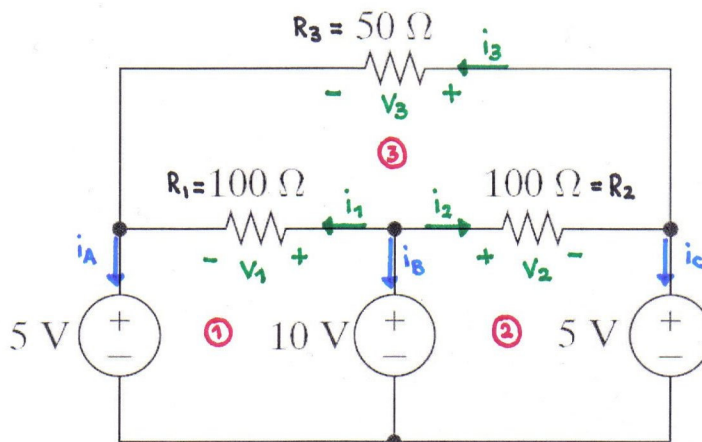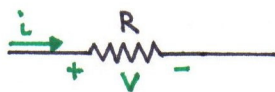

(b) KVL

LOOP ①	$5 + V_1 = 10$	$\Rightarrow V_1 = 5V$
LOOP ②	$10 = V_2 + 5$	$\Rightarrow V_2 = 5V$
LOOP ③	$V_1 = V_2 + V_3$	$\Rightarrow V_3 = V_1 - V_2 = 0V$

(c) $i = \frac{V}{R}$

$i_1 = \frac{5}{100} = 0.05A = 50$ mA

$i_2 = \frac{5}{100} = 50$ mA

$i_3 = 0$ A

(d) $i_A = i_1 = 50$ mA

$i_B = -i_1 - i_2 = -100$ mA

$i_C = 50$ mA

NOTE: voltage sources do not necessarily deliver power (think about what happens when we charge batteries)