

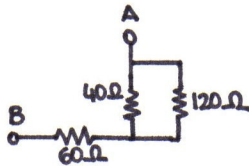
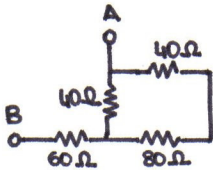
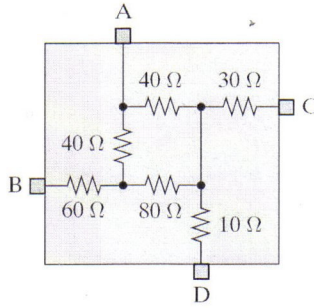


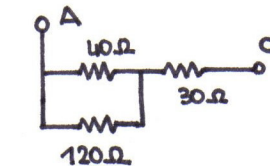Problem#1: Problem 2-31 textbook



Find the equivalent resistance between terminals A-B, A-C, A-D, B-C, B-D, and C-D.




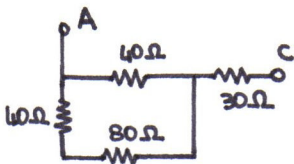
$$\begin{aligned} \underline{\underline{R_{AB}}} &= (60 + 40 // 120) \Omega \\ &= 60 + \frac{40 \cdot 120}{40 + 120} = \underline{\underline{90 \Omega}} \end{aligned}$$



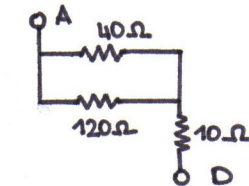
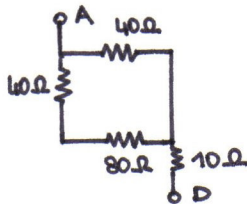
$$\begin{aligned} \underline{\underline{R_{AC}}} &= (30 + 40 // 120) \Omega \\ &= 30 + \frac{40 \cdot 120}{40 + 120} = \underline{\underline{60 \Omega}} \end{aligned}$$



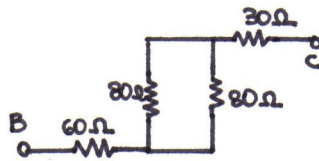
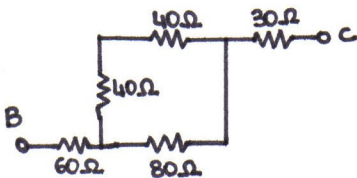
$$\begin{aligned} \underline{\underline{R_{AD}}} &= (10 + 40 // 120) \Omega \\ &= 10 + \frac{40 \cdot 120}{40 + 120} = \underline{\underline{40 \Omega}} \end{aligned}$$


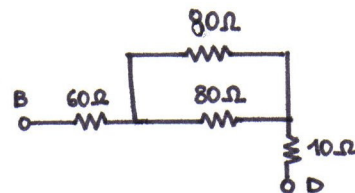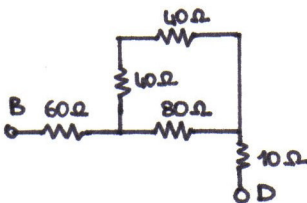
$$\begin{aligned} \underline{\underline{R_{BC}}} &= (60 + 80 // 80 + 30) \Omega \\ &= 60 + \frac{80 \cdot 80}{80 + 80} + 30 = \underline{\underline{130 \Omega}} \end{aligned}$$



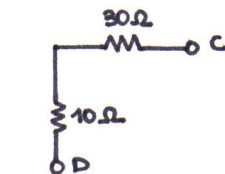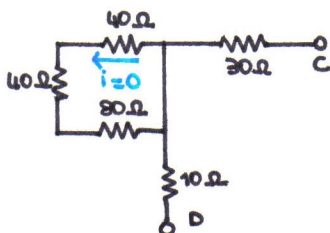
$$\begin{aligned} \underline{\underline{R_{BD}}} &= (60 + 80 // 80 + 10) \Omega \\ &= 60 + \frac{80 \cdot 80}{80 + 80} + 10 = \underline{\underline{110 \Omega}} \end{aligned}$$




$$\underline{\underline{R_{CD}}} = 30 + 10 = \underline{\underline{40 \Omega}}$$

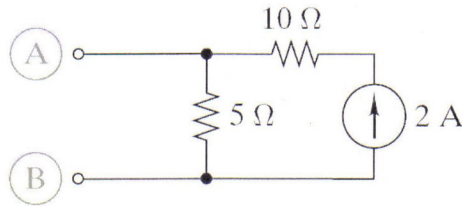Problem#2: Problem 2-34 textbook


Find the equivalent practical voltage source at terminals A and B.



EQUIVALENT →

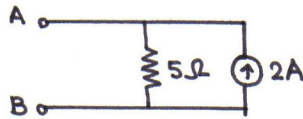


EQUIVALENT →

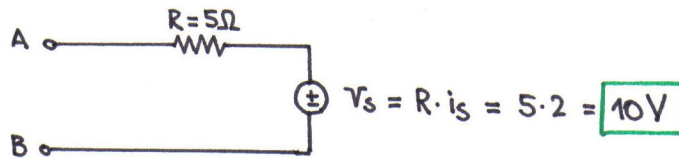


Problem#3: Problem 2-39 textbook

What is the range of R_{EQ} ?

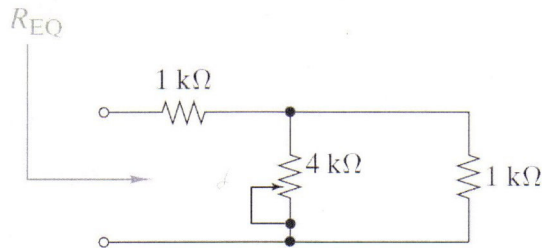

CASE 1

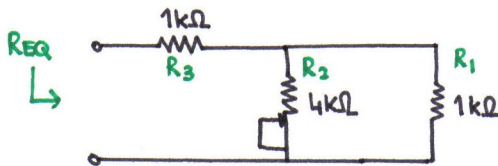


$$R_{EQ} = R_3 + (R_1 // R_2)$$


$$R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{4 \cdot 1}{4 + 1} = \frac{4}{5}$$

$$R_{EQ} = 1 + \frac{4}{5} = \frac{9}{5} = 1.8 \Omega$$

CASE 2

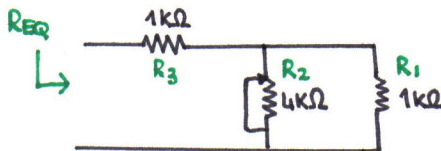


→

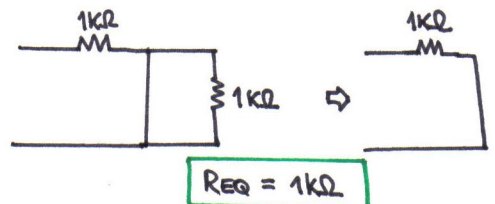

The range of R_{EQ} is $[1, 1.8] \Omega$

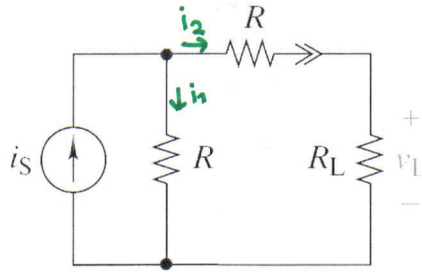Problem#4: Problem 2-42 textbook

Use the current division to obtain an expression for V_L in terms of R and R_L and i_s .





$$R_{EQ} = R + R_L$$

$$i_2 = \frac{R}{R_{EQ}} i_s = \frac{R}{R + R_L} i_s$$

$$V_L = R_L \cdot i_2 = \frac{R R_L}{R + R_L} i_s$$


Problem#5: Problem 2-43 textbook

Find i_x in the given circuit.

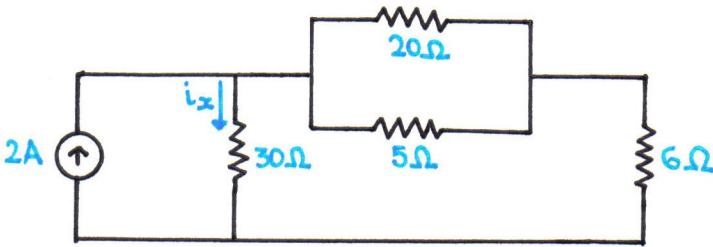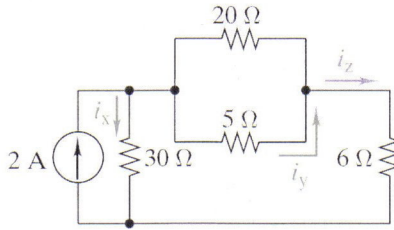


$$R_1 = 6 + 20 // 5$$
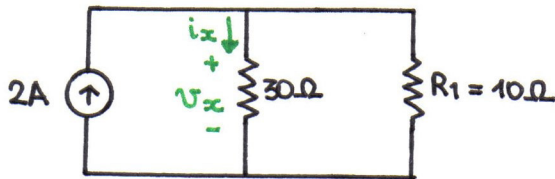
$$= 6 + \frac{5 \cdot 20}{20 + 5} = 6 + 4 = 10 \Omega$$



$$i_x = \frac{V_x}{30} \text{ A}$$
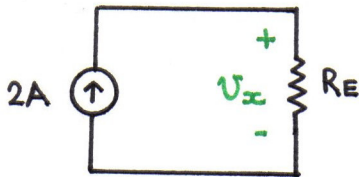
$$R_E = 30 // 10 = \frac{30 \cdot 10}{30 + 10} = \frac{30}{4} = 7.5 \Omega$$




$$V_x = R_E \cdot 2 = 15 \text{ V}$$

$$\underline{\underline{i_x = \frac{V_x}{30} = \frac{15}{30} = \underline{\underline{0.5 \text{ A}}}}}$$

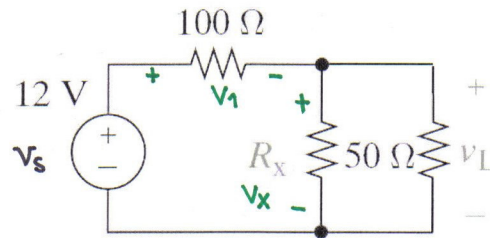Problem#6: Problem 2-50 textbook

Select a positive value for R_x so that $v_L = 6\text{ V}$.




$$v_x = v_L = 6\text{ V}$$

Since $v_s = 12\text{ V}$ then $v_1 = 6\text{ V}$

Let $R_{EQ} = R_x \parallel 50\Omega$, then
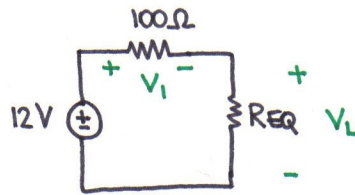
$$\underline{v_L = 6\text{ V}} \iff \underline{R_{EQ} = 100\Omega}$$




$$R_{EQ} = \frac{R_x \cdot 50\Omega}{R_x + 50} = 100\Omega$$

$$\Rightarrow 100^2 (R_x + 50) = 50 R_x$$

$$R_x = -100\Omega$$

UNFEASIBLE !!

NOTE ON PARALLEL CONNECTION

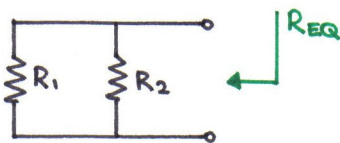

$$R_{EQ} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} < \min \{ R_1, R_2 \}$$

In fact, since $R_1 > 0$, $R_2 > 0$

$$R_1 R_2 < R_1 R_2 + R_1^2 = R_1 (R_1 + R_2) \Rightarrow \frac{R_1 R_2}{R_1 + R_2} < R_1$$

$$R_1 R_2 < R_1 R_2 + R_2^2 = R_2 (R_1 + R_2) \Rightarrow \frac{R_1 \cdot R_2}{R_1 + R_2} < R_2$$

NOTE THAT, IF $R_1 = R_2$, THEN $R_{EQ} = R_1/2 = R_2/2$

We want $R_{EQ} = R_x \parallel 50 = 100\Omega$ but using the previous note


we have that $R_{EQ} < 50\Omega$ for every $R_x > 0$

as a result, the problem does not have a feasible solution.

↓
positive R_x

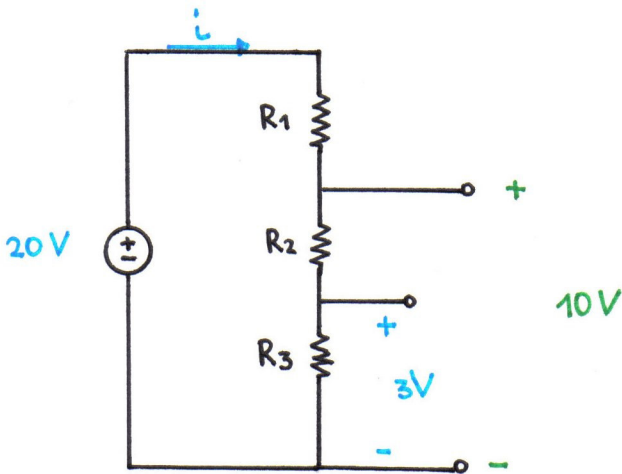Problem#7: Problem 2-48 textbook

Select the values of R_1 and R_2 and R_3 so that the voltage divider produces the shown output voltages.



$$i = \frac{V}{R} = \frac{20}{R_1 + R_2 + R_3}$$

$$(R_2 + R_3) \cdot i = 10 \text{ V}$$

\Rightarrow

$$\frac{(R_2 + R_3) 20}{R_1 + R_2 + R_3} = 10$$

$$20 (R_2 + R_3) = 10 (R_1 + R_2 + R_3)$$

$$10 R_1 - 10 R_2 - 10 R_3 = 0$$

(A)

$$R_3 \cdot i = 3 \text{ V}$$

\Rightarrow

$$\frac{R_3 \cdot 20}{R_1 + R_2 + R_3} = 3$$

$$3 R_1 + 3 R_2 - 17 R_3 = 0$$

(B)

You have

2 EQUATIONS ((A) & (B)) = 2 CONSTRAINTS

3 UNKNOWNNS (R_1, R_2, R_3)

\rightarrow you have 1 degree of freedom ; for instance choose $R_1 = 10 \Omega$.

Then (A) becomes

$$R_2 + R_3 = 10$$

(B) becomes

$$3 R_2 - 17 R_3 = 30$$

$$\begin{cases} R_2 + R_3 = 10 & (1) \\ 3 R_2 - 17 R_3 = 30 & (2) \end{cases}$$

$$(2) - 3 \cdot (1) \Rightarrow -17 R_3 - 3(R_3) = -30 - 3 \cdot (10)$$

\Rightarrow

$$\underline{\underline{R_3 = 3 \Omega}}$$



substituting in (1)

\Rightarrow


$$\underline{\underline{R_2 = 7 \Omega}}$$

Problem#8: Problem 2-56 textbook

Use source transformation to find i_x .

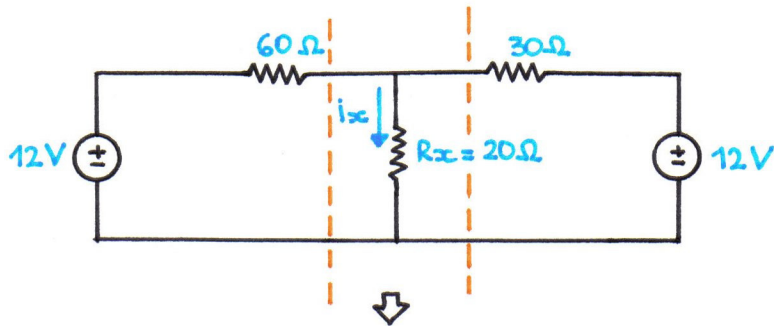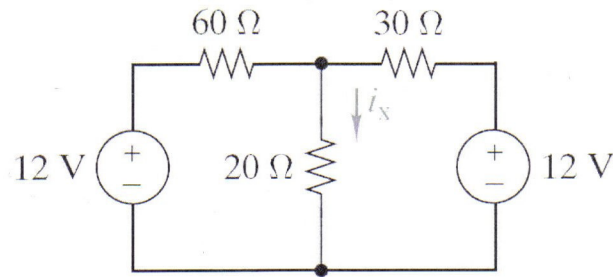


Use source transformation to find i_x

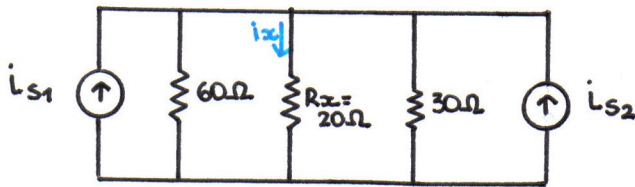

source transformation

$$i_{s1} = \frac{12}{60} \text{ A} = 0.2 \text{ A}$$
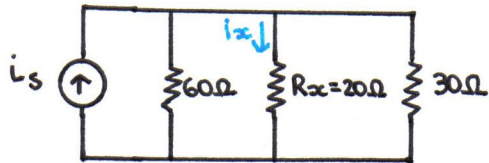
$$i_{s2} = \frac{12}{30} \text{ A} = 0.4 \text{ A}$$




composite source

$$i_s = i_{s1} + i_{s2} = 0.2 + 0.4 = 0.6 \text{ A}$$

Since $30 \parallel 60 = \frac{30 \cdot 60}{30 + 60} = 20 \Omega$



then $R_E = R_x$ and thus
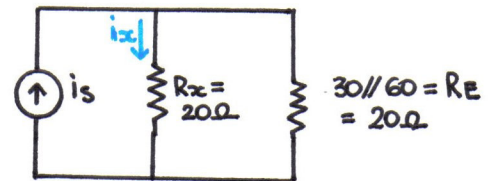
$$\underline{i_x = \frac{i_s}{2} = 0.3 \text{ A}}$$



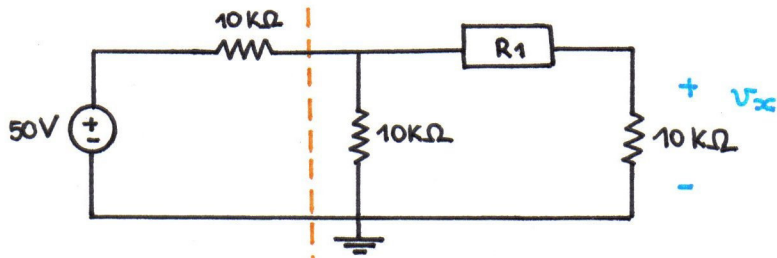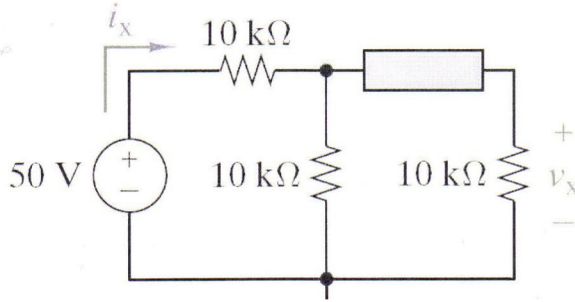Problem#9: Problem 2-60 textbook

The box in the circuit is a resistor whose value can be anywhere between $8\text{ k}\Omega$ and $80\text{ k}\Omega$. Write a MATLAB program to find the range of values of v_x using circuit reduction.




$$8\text{ k}\Omega \leq R_1 \leq 80\text{ k}\Omega$$

Use circuit reduction to find the range of values of v_x


↓ SOURCE TRANSFORMATION
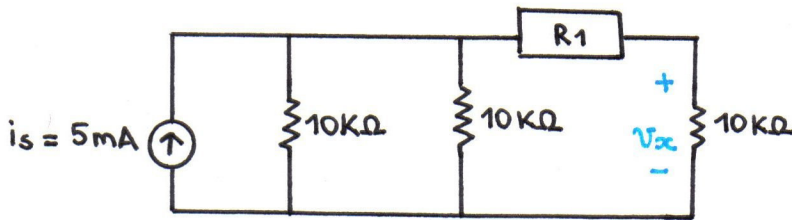
$$i_s = \frac{50\text{V}}{10\text{k}\Omega} = 5\text{mA}$$




$$10 // 10 = \frac{10 \cdot 10}{10 + 10} = 5\text{k}\Omega$$

↓ RESISTORS CONNECTED IN //

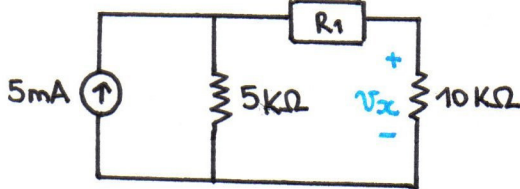

↓ SOURCE TRANSFORMATION
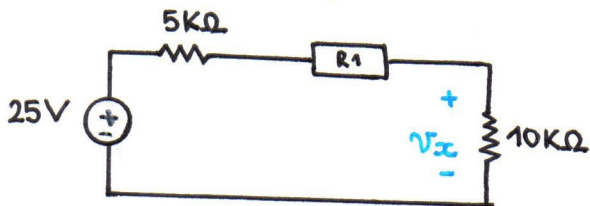
$$v = 5 \cdot 10^{-3} \cdot 5 \cdot 10^3 = 25\text{V}$$



$$8\text{ k}\Omega \leq R_1 \leq 80\text{ k}\Omega$$

Applying the voltage division rule

$$R_1 = 8\text{ k}\Omega \quad \Rightarrow \quad \underline{\underline{v_x}} = \left(\frac{10}{5+8+10} \right) \cdot 25 = \underline{\underline{10.87\text{ V}}}$$

$$R_1 = 80\text{ k}\Omega \quad \Rightarrow \quad \underline{\underline{v_x}} = \left(\frac{10}{5+80+10} \right) \cdot 25 = \underline{\underline{2.6316\text{ V}}}$$