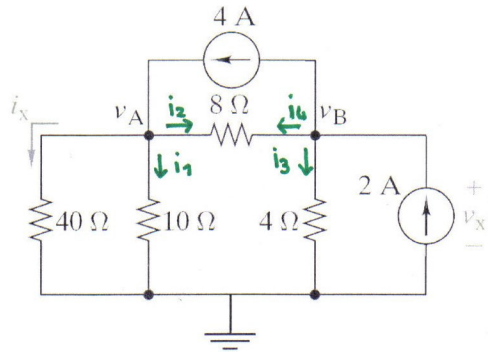


Problem#1: Problem 3-2 textbook

- Formulate node voltage equations for the circuit.
- Solve these equations and find v_x and i_x .



(a) $i_x + i_1 + i_2 = 4$ KCL @ NODE A

$$\frac{V_A}{40} + \frac{V_A}{10} + \frac{V_A - V_B}{8} = 4$$

$$V_A + 4V_A + 5(V_A - V_B) = 4$$

$$\boxed{10V_A - 5V_B = 160} \quad (1)$$

$i_4 + i_3 + 4 = 2$ KCL @ NODE B

$$i_4 + i_3 = -2$$

$$\frac{V_B - V_A}{8} + \frac{V_B}{4} = -2$$

$$V_B - V_A + 2V_B = -16$$

$$\boxed{V_A - 3V_B = 16} \quad (2)$$

(b) Node Voltage equations $\begin{cases} 10V_A - 5V_B = 160 & (1) \\ V_A - 3V_B = 16 & (2) \end{cases}$

(2) $\rightarrow V_A = 16 + 3V_B$

substituting in (1) $\rightarrow 10(16 + 3V_B) - 5V_B = 160$

$$160 + 30V_B - 5V_B = 160 \quad \Rightarrow \quad V_B = 0$$


$$V_A = 16$$

$$\boxed{v_x = V_B = 0V}$$

$$\boxed{i_x = \frac{4V_A}{40} = \frac{16}{40} = 0.4A}$$

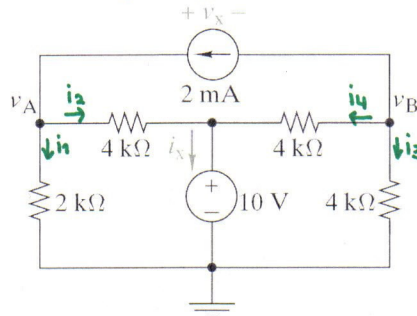Problem#2: Problem 3-4 textbook

- Formulate node voltage equations for the circuit.
- Solve these equations and find v_x and i_x .



(a) $i_1 + i_2 = 2 \text{ mA}$ KCL @ NODE A

$$\frac{V_A}{2 \cdot 10^3} + \frac{V_A - 10}{4 \cdot 10^3} = 2 \cdot 10^{-3}$$

$$2V_A + V_A - 10 = 8$$

$$3V_A = 18$$

$$V_A = 6 \text{ V}$$

$i_3 + i_4 = -2 \text{ mA}$ KCL @ NODE B

$$\frac{V_B}{4 \cdot 10^3} + \frac{V_B - 10}{4 \cdot 10^3} = -2 \cdot 10^{-3}$$

$$V_B + V_B - 10 = -8$$

$$2V_B = 2$$


$$V_B = 1 \text{ V}$$

(b) $V_x = V_A - V_B = 5 \text{ V}$

$$i_x = i_2 + i_4 = \frac{V_A - 10}{4 \cdot 10^3} + \frac{V_B - 10}{4 \cdot 10^3} = \frac{-4}{4 \cdot 10^3} + \frac{-9}{4 \cdot 10^3} = -\frac{13}{4} \text{ mA} = -3.25 \text{ mA}$$

Problem#3: Problem 3-7 textbook

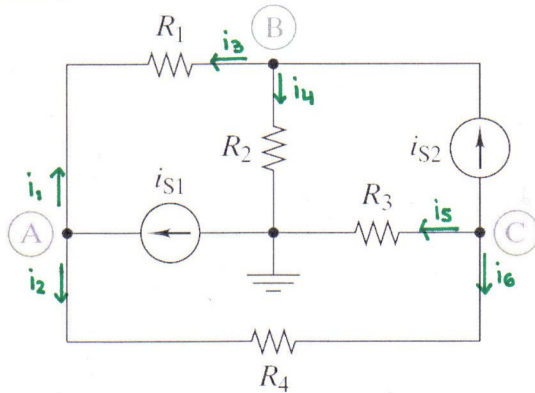- a) Formulate the node voltage equations for the circuit.
 b) Use **MATLAB** to solve for v_A , v_B , v_C when $R_1=1\text{ k}\Omega$, $R_2=2\text{ k}\Omega$, $R_3=4\text{ k}\Omega$, $R_4=2\text{ k}\Omega$, and $i_{s1}=i_{s2}=2\text{ mA}$.



3 UNKNOWNNS

(a) $i_1 + i_2 = i_{s1}$ KCL @ NODE A

$$\frac{V_A - V_B}{R_1} + \frac{V_A - V_C}{R_4} = i_{s1} \quad (1)$$

$i_3 + i_4 = i_{s2}$ KCL @ NODE B

$$\frac{V_B - V_A}{R_1} + \frac{V_B}{R_2} = i_{s2} \quad (2)$$

$i_5 + i_6 + i_{s2} = 0$ KCL @ NODE C

$$\frac{V_C}{R_3} + \frac{V_C - V_A}{R_4} = -i_{s2} \quad (3)$$

(b) Using the numerical values

$$\frac{V_A - V_B}{1} + \frac{V_A - V_C}{2} = 2 \quad \Leftrightarrow \quad 3V_A - 2V_B - V_C = 4$$

$$\frac{V_B - V_A}{1} + \frac{V_B}{2} = 2 \quad \Leftrightarrow \quad -2V_A + 3V_B = 4$$

$$\frac{V_C}{4} + \frac{V_C - V_A}{2} = -2 \quad \Leftrightarrow \quad -2V_A + 3V_C = -8$$

Let $A := \begin{bmatrix} 3 & -2 & -1 \\ -2 & 3 & 0 \\ -2 & 0 & 3 \end{bmatrix}$ $B := \begin{bmatrix} 4 \\ 4 \\ -8 \end{bmatrix}$ $x := \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix}$


then (1)-(2)-(3) can be written as

$$Ax = B \quad x = A^{-1}B \quad \text{using Matlab} \quad x = A \setminus B = \begin{bmatrix} 4 \\ 4 \\ 0 \end{bmatrix}$$

$$V_A = 4V \quad V_B = 4V \quad V_C = 0V$$

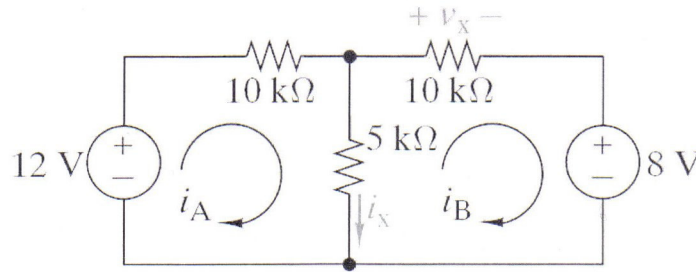Problem#4: Problem 3-9 textbook

- Formulate the mesh-current equations for the circuit.
- Use equations to find v_x and i_x .



(a) Resistor unit = kΩ , I drop the 10^3 factor but I know the current unit = mA

$$10 i_A + 5 (i_A - i_B) = 12$$

$$10 i_B + 8 + 5 (i_B - i_A) = 0$$

$$\begin{cases} 15 i_A - 5 i_B = 12 & (1) \\ -5 i_A + 15 i_B = -8 & (2) \end{cases} \quad \text{MESH CURRENT EQUATIONS}$$

$$(2) \Rightarrow i_A = 3 i_B + \frac{8}{5} \quad (*)$$

$$(1) \Rightarrow 15 \left(3 i_B + \frac{8}{5} \right) - 5 i_B = 12$$

$$45 i_B + 24 - 5 i_B = 12$$

$$40 i_B = -12$$


$$i_B = \frac{-12}{40} = -0.3 \text{ mA}$$

$$\text{using } (*) \quad i_A = -0.9 + 1.6 = 0.7 \text{ mA}$$

$$(b) \quad v_x = 10 \cdot 10^3 \cdot (-0.3 \cdot 10^{-3}) = -3 \text{ V}$$

$$i_x = i_A - i_B = 0.7 - (-0.3) = 1 \text{ mA}$$


sanity check

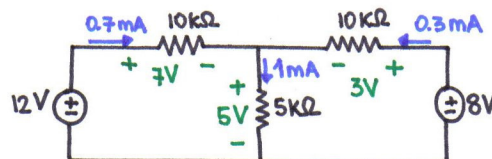

OK!!

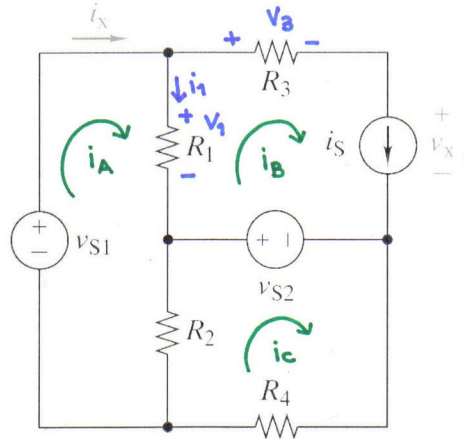Problem#5: Problem 3-13 textbook

- Formulate mesh-current equations for the given circuit.
- Solve these equations with **MATLAB** to find v_x and i_x when $R_1=$, $R_2=10\text{ k}\Omega$, $R_3=2\text{ k}\Omega$, $R_4=1\text{ k}\Omega$, $i_s=2.5\text{ mA}$, $v_{s1}=12\text{ V}$ and $v_{s2}=0.5\text{ V}$.
- Find the power supplied by v_{s1} .



$$i_x = i_A$$

RESISTOR UNIT = $\text{k}\Omega$
 I DROP THE 10^3 FACTOR
 AND I KNOW THE UNIT
 FOR i_A, i_B, i_C IS mA

(a) A: $R_1 (i_A - i_B) + R_2 (i_A - i_C) = v_{s1}$

B: $i_B = i_s$

C: $R_4 i_C + R_2 (i_C - i_A) = -v_{s2}$

$$\begin{cases} (R_1 + R_2) i_A - R_2 i_C = v_{s1} + R_1 i_s \\ -R_2 i_A + (R_2 + R_4) i_C = -v_{s2} \\ i_B = i_s \end{cases}$$

MESH-CURRENT EQUATIONS

(b) $20 i_A - 10 i_C = 12 + 10 \cdot 2.5 = 37$

$-10 i_A + 11 i_C = -0.5$

$$\underbrace{\begin{bmatrix} 20 & -10 \\ -10 & 11 \end{bmatrix}}_A \underbrace{\begin{bmatrix} i_A \\ i_C \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 37 \\ -0.5 \end{bmatrix}}_B$$

$Ax = B$
 using Matlab

$$x = A \setminus B = \begin{bmatrix} 3.35 \\ 3 \end{bmatrix}$$

(c) $i_x = i_A = \boxed{3.35\text{ mA}}$


$$\boxed{\begin{matrix} i_A = 3.35\text{ mA} \\ i_C = 3\text{ mA} \end{matrix}}$$

$v_x = v_1 - v_3 = R_1 i_1 - R_3 i_B = R_1 (i_A - i_B) - R_3 i_B$

$= R_1 i_A - (R_1 + R_3) i_B = 33.5 - 12 \cdot 2.5 = \boxed{3.5\text{ V}}$

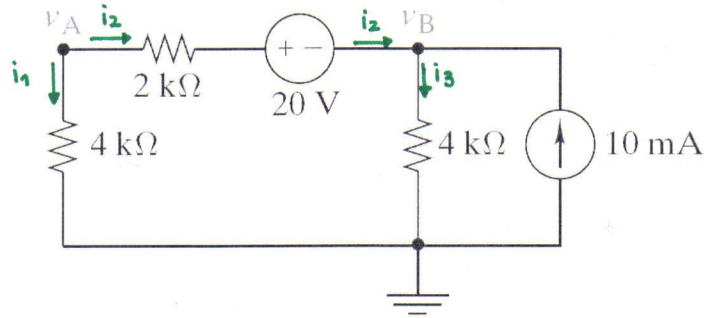Problem#6: Problem 3-19 textbook

Find the node voltages v_A and v_B in the Figure.



$$A : \quad \frac{v_A}{4 \cdot 10^3} + \frac{v_A - (20 + v_B)}{2 \cdot 10^3} = 0$$

$$v_A + 2 [v_A - 20 - v_B] = 0$$

$$\boxed{3v_A - 2v_B = 40}$$

$$B : \quad \frac{v_A - 20 - v_B}{2 \cdot 10^3} + 10 \cdot 10^{-3} = \frac{v_B}{4 \cdot 10^3}$$

$$2(v_A - 20 - v_B) + 40 = v_B$$

$$\boxed{2v_A - 3v_B = 0}$$

$$\begin{cases} 3v_A - 2v_B = 40 & (1) \\ 2v_A - 3v_B = 0 & (2) \end{cases}$$

$$(2) \Rightarrow v_A = \frac{3}{2}v_B$$

$$(1) \Rightarrow \frac{9}{2}v_B - 2v_B = 40$$


$$\frac{5}{2}v_B = 40 \quad \Leftrightarrow$$

$$\boxed{v_B = \frac{80}{5} = 16 \text{ V}}$$

$$\boxed{v_A = \frac{3}{2} \cdot 16 = 24 \text{ V}}$$

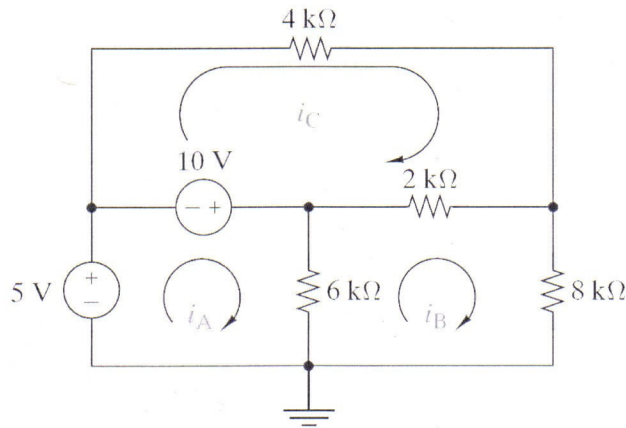Problem#7: Problem 3-20 textbook

Find the mesh currents i_A , i_B and i_C in the circuit.



RESISTOR UNIT = $k\Omega$

I DROP THE 10^3 FACTOR
AND I KNOW THAT
THE UNIT FOR i_A, i_B, i_C
IS mA

$$A: \quad 5 + 10 = 6(i_A - i_B)$$

$$B: \quad 8i_B + 6(i_B - i_A) + 2(i_B - i_C) = 0$$

$$C: \quad 4i_C + 2(i_C - i_B) + 10 = 0$$

$$\underbrace{\begin{bmatrix} 6 & -6 & 0 \\ 6 & -16 & 2 \\ 0 & 2 & -6 \end{bmatrix}}_A \underbrace{\begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 15 \\ 0 \\ 10 \end{bmatrix}}_B$$

$$Ax = B$$

using Matlab

$$x = A \setminus B = \begin{bmatrix} 3.75 \\ 1.25 \\ -1.25 \end{bmatrix}$$

$$\begin{aligned} i_A &= 3.75 \text{ mA} \\ i_B &= 1.25 \text{ mA} \\ i_C &= -1.25 \text{ mA} \end{aligned}$$