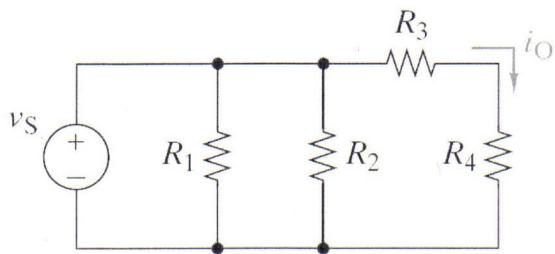


### Problem#1: Problem 3-22 textbook

Find the proportionality constant  $K = i_o / v_s$  for the given circuit.




$$R_{EQ} = R_3 + R_4$$

$$i_o = \frac{v_s}{R_{EQ}} = \frac{v_s}{R_3 + R_4}$$


$$K = \frac{i_o}{v_s} = \frac{1}{R_3 + R_4}$$
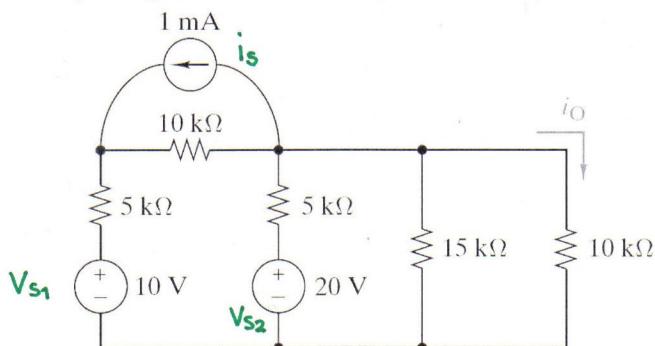
### Problem#2: Problem 3-29 textbook

Use the superposition principle to find the output current  $i_o$ .



① CONSIDER ONLY  $V_{S1}$

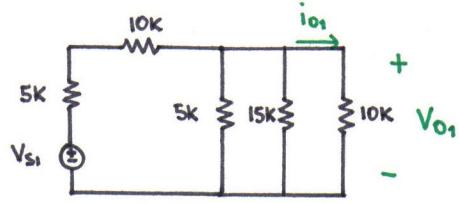


$$i_{o1} = \frac{V_{o1}}{10k\Omega}$$

$$R_{EQ} = 5k\Omega // 15k\Omega // 10k\Omega$$

$$\frac{1}{R_{EQ}} = \frac{1}{5} + \frac{1}{15} + \frac{1}{10} = \frac{11}{30}$$


$$R_{EQ} = \frac{30}{11} k\Omega$$

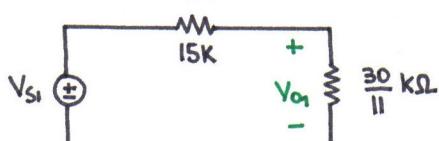

$$V_{o1} = \frac{R_{EQ} \cdot V_{S1}}{(5k\Omega + 10k\Omega) + R_{EQ}} = \frac{30/11}{15 + 30/11} \cdot 10 = \frac{20}{13} = 1.538V$$

$$i_{o1} = \frac{V_{o1}}{10k\Omega} = \frac{2}{13} mA = 0.154 mA$$


(2) CONSIDER ONLY  $V_{S2}$

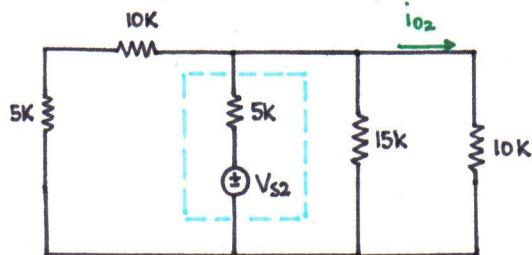

$$\text{SERIES } 10\text{K} + 5\text{K} = 15\text{K}$$

SOURCE TRANSFORMATION

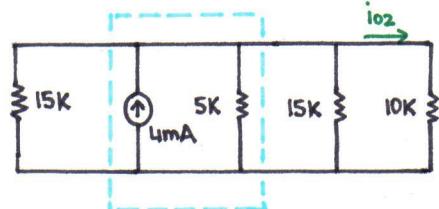
$$i_{S2} = \frac{V_{S2}}{5\text{K}} = 4\text{mA}$$



$$R_{\text{EQ}} = 15\text{K} // 5\text{K} // 15\text{K}$$




$$\frac{1}{R_{\text{EQ}}} = \frac{1}{15\text{K}} + \frac{1}{5\text{K}} + \frac{1}{15\text{K}} = \frac{1}{3\text{K}}$$

$$R_{\text{EQ}} = 3\text{K}\Omega$$

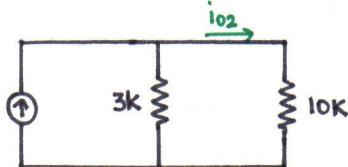

$$i_{02} = \frac{3}{3+10} \cdot 4 \cdot 10^{-3} = \frac{12}{13} \text{ mA} = 0.923 \text{ mA}$$

(3) CONSIDER ONLY  $i_s$

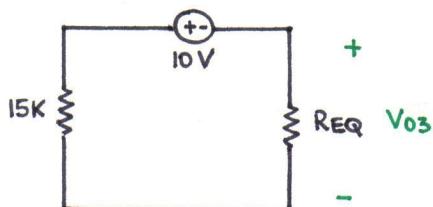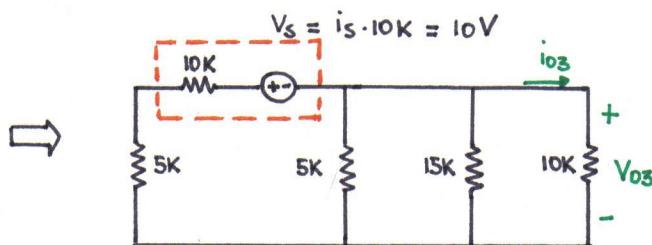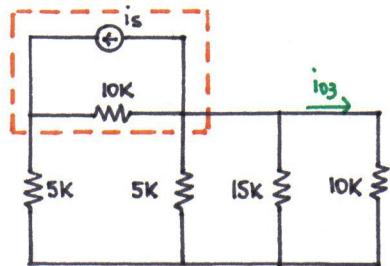

$$i_{03} = \frac{V_{03}}{10\text{K}}$$

$$\text{SERIES } 5\text{K} + 10\text{K} = 15\text{K}$$

$$5\text{K} // 15\text{K} // 10\text{K} := R_{\text{EQ}} = \frac{30}{11} \text{ K}\Omega$$

$$V_{03} = - \left( \frac{\frac{30}{11}}{15 + \frac{30}{11}} \right) \cdot 10 = - \frac{20}{13} \text{ V}$$


$$i_{03} = \frac{V_{03}}{10\text{K}} = - \frac{2}{13} \text{ mA} = - 0.154 \text{ mA}$$

(4) SUM CONTRIBUTIONS


$$i_0 = i_{01} + i_{02} + i_{03} = \frac{2}{13} + \frac{12}{13} - \frac{2}{13} = \frac{12}{13} \text{ mA} = 0.923 \text{ mA}$$
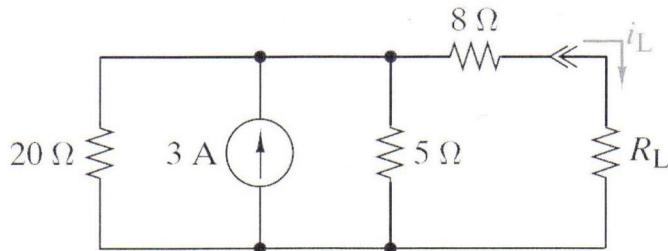
### Problem#3: Problem 3-38 textbook

Find the Norton equivalent circuit seen by  $R_L$ . Find the current when  $R_L=6\Omega$ ,  $12\Omega$ , and  $60\Omega$ .



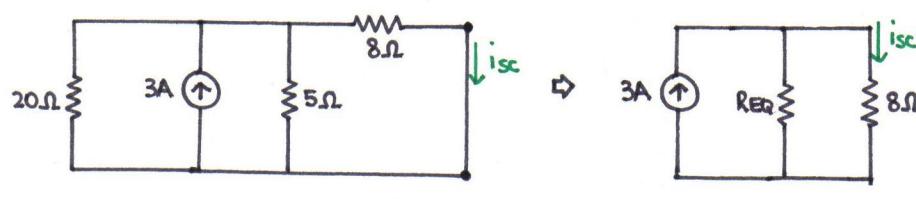- ① COMPUTE THE "SHORT CIRCUIT CURRENT"  $i_{sc} = i_N$




$$R_{eq} = 5 // 20 = \frac{100}{25} = 4\Omega$$

$$\begin{aligned} i_N = i_{sc} &= \frac{R_{eq}}{R_{eq} + 8} \cdot 3A \\ &= \frac{4}{12} \cdot 3A = 1A \end{aligned}$$

- ② COMPUTE THE RESISTANCE  $R_N$ . There are 2 ways to determine it

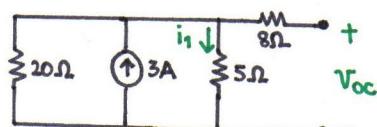(a)  $R_N = V_{oc} / i_{sc}$  where  $V_{oc}$  = "OPEN CIRCUIT VOLTAGE"




$$i_1 = \frac{20}{20+5} \cdot 3 = \frac{60}{25} A$$


$$V_{oc} = 5 \cdot \frac{60}{25} = 12V$$

$$R_N = \frac{V_{oc}}{i_{sc}} = \frac{12}{1} = 12\Omega$$

(b)  $R_N = \text{LOOK BACK RESISTANCE}$

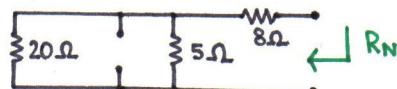

$$R_N = 20 // 5 + 8 = 4 + 8 = 12\Omega$$

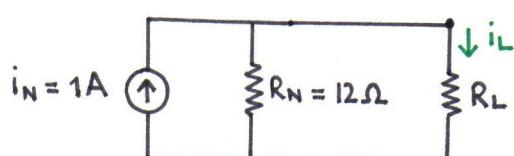

NORTON EQUIVALENT CIRCUIT

$$i_L = \frac{12}{12+R_L} i_N$$


$$R_L = 6\Omega \Rightarrow i_L = \frac{12}{18} = \frac{2}{3} = 0.667A$$

$$R_L = 12\Omega \Rightarrow i_L = \frac{12}{24} = 0.5A$$

$$R_L = 60\Omega \Rightarrow i_L = \frac{12}{72} = \frac{1}{6}A$$
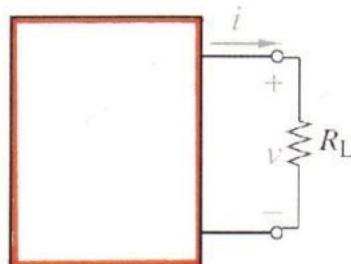
### Problem#4: MATLAB Program



The i-v characteristics of an active circuit is  $3v+300i=60$ . Write a MATLAB program to plot the output voltage versus  $R_L$  curve when the load resistance is changing from  $500 \Omega$  to  $3 k\Omega$ .




$$i = \frac{1}{5} - \frac{V}{100}$$



$$V = 20 - 100i$$

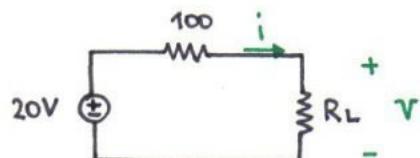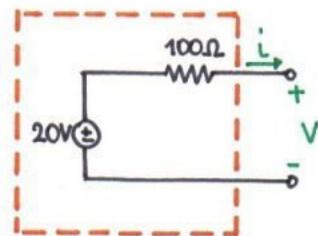

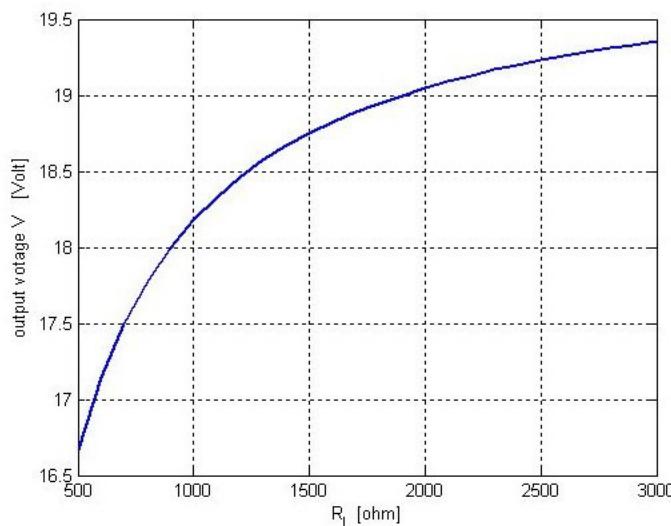
$$\left\{ \begin{array}{l} V = \frac{R_L}{R_L + 100} \cdot 20V \\ \text{for } 500\Omega \leq R_L \leq 3000\Omega \end{array} \right.$$



```
>> RL=(500:100:3000);
>> V=20*RL./(RL+100);
>> plot(RL,V,'LineWidth',2);
>> grid
>> xlabel('R_L [ohm]')
>> ylabel('output votage V [Volt]')
```

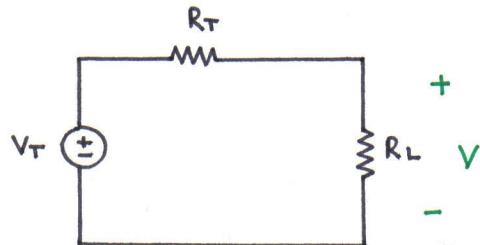**Problem#5: Problem 3-45 textbook**

The Thevenin equivalent parameters of a voltage source are  $v_T=25$  V and  $R_T=150 \Omega$ . Find the smallest load resistance for which the load voltage exceeds 15 V.



$$V = \frac{R_L}{R_L + R_T} v_T$$

$$\frac{R_L}{R_L + R_T} v_T > 15V$$


$$25 R_L > 15 (R_L + 150)$$

$$10 R_L > 2250$$

$$R_L > 225 \Omega$$
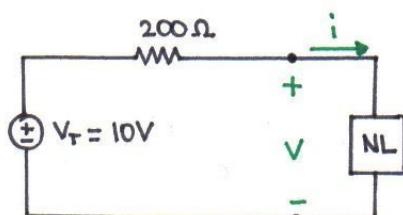
### Problem#6: Problem 3-50 textbook (MATLAB Problem)

A nonlinear resistor is connected across a two terminal source whose Thevenin equivalent is  $V_T=10$  V and  $R_T=200 \Omega$ . The i-v characteristics of the resistor is  $v=4000i^2$ . Plot the i-v characteristics of the source and the resistor with **MATLAB** and graphically determine the voltage across and current through the nonlinear resistor.



$$\text{SOURCE} \quad V = 10 - 200i$$

$$\text{NL RESISTOR} \quad V = 4000i^2$$

i-v characteristics

$$\begin{cases} i = \frac{1}{20} - \frac{V}{200} \\ i = \sqrt{\frac{V}{4000}} \end{cases}$$


```
>> V=(0:0.01:10);
>> i1=1/20-V/200;
>> i2=sqrt(V/4000);
>> plot(V,i1,V,i2,'--','LineWidth',2);
>> grid
>> legend('source','nonlinear resistor')
>> xlabel('v')
>> ylabel('i')
```

$$10 - 200i = 4000i^2$$

$$\begin{cases} 400i^2 + 20i - 1 = 0 \\ i > 0 \\ V = 10 - 200i \end{cases}$$

$$\begin{array}{|c|} \hline i = 0.031 \text{ A} \\ V = 3.8 \text{ V} \\ \hline \end{array}$$



Q-POINT

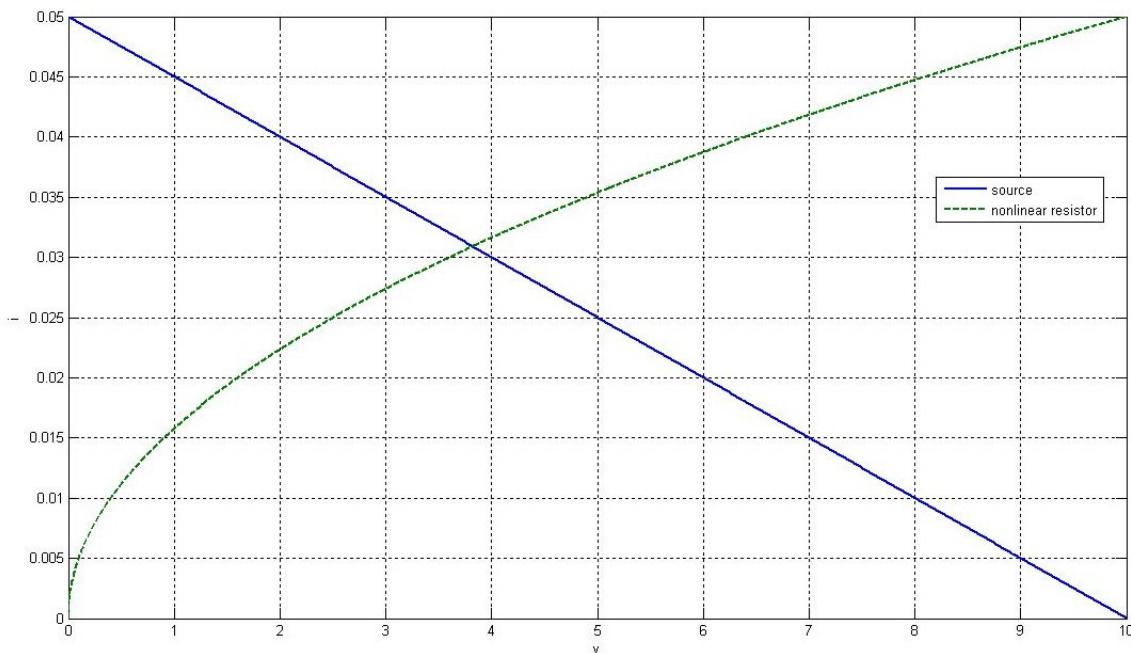

**Problem#7: Problem 3-56 textbook**


Find the value of  $R$  in the circuit so that maximum power is delivered to the  $4\text{k}\Omega$  load.

Find the maximum power.

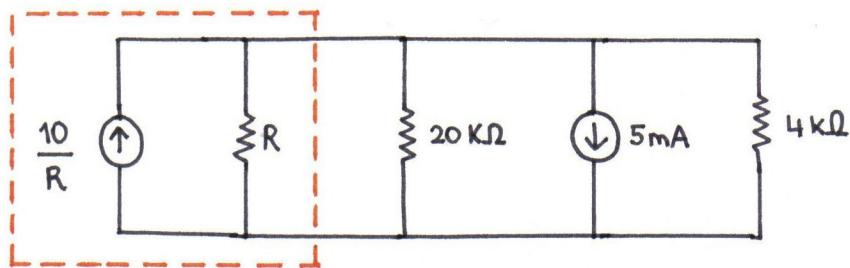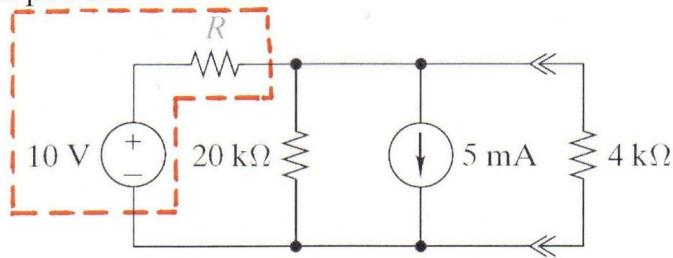

$$R_N = R // 20\text{k}\Omega = \frac{20R}{20+R}$$

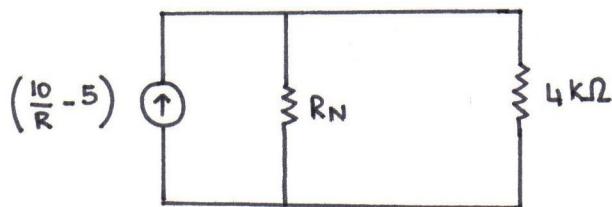( $R$  and  $R_N$  in  $\text{k}\Omega$ )



Since  $R_T = R_N$  and max power delivered  $\leftrightarrow R_T = 4\text{k}\Omega$

then the max power is delivered to the  $4\text{k}\Omega$  load when

$$\frac{20R}{20+R} = 4 \quad \Rightarrow \quad 20R = 80 + 4R$$

$$R = \frac{80}{16} \text{k}\Omega$$


$R = 5\text{k}\Omega$

since  $R_N = R_L$  and  $V_L = V_N \Rightarrow i_L = \left(\frac{10}{R} - 5\right) \cdot \frac{1}{2} = (2-5) \cdot \frac{1}{2} = -1.5\text{mA}$



$$P = R_L i_L^2 = 4 \cdot 10^3 \cdot (1.5 \cdot 10^{-3})^2 = 9 \cdot 10^{-3} = 9\text{mW}$$

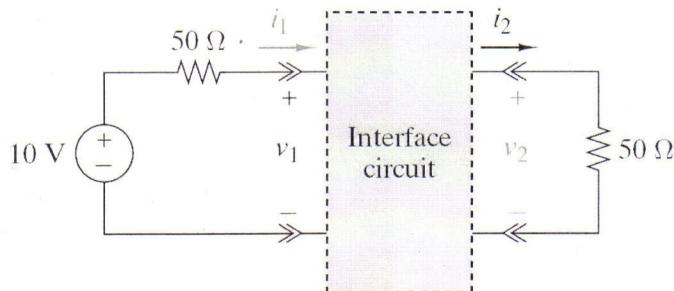**Problem#8: Problem 3-61 textbook**

The output current of the voltage source in the Figure must be less than 100mA. Design an interface circuit so that the load voltage is  $v_2=4$  V and the source current is  $i_1 < 100$  mA.



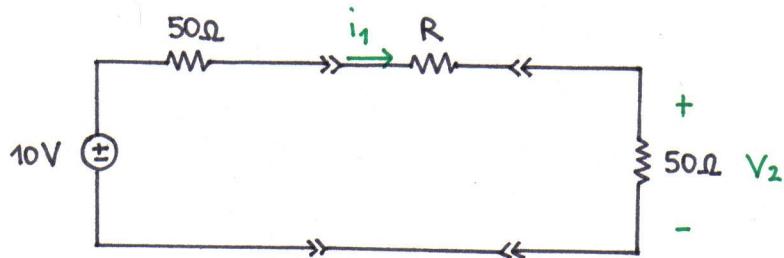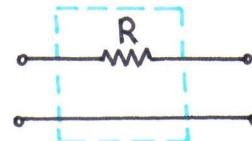Let's start considering the simpler interface



$$V_2 = \frac{50}{100+R} \cdot 10 = 4V$$

$$500 = 400 + 4R \quad \Leftrightarrow \quad R = 25\Omega$$

$$i_1 = \frac{10}{R_{TOT}} = \frac{10}{50+50+25} = \frac{10}{125} = 0.08A < 0.1A$$

R = 25Ω satisfies the specifics