



The Ohio State University  
Department of Electrical Engineering

ECE 205

**Circuit Analysis**


**Home work Set # 5**

**Print Your Name**

---

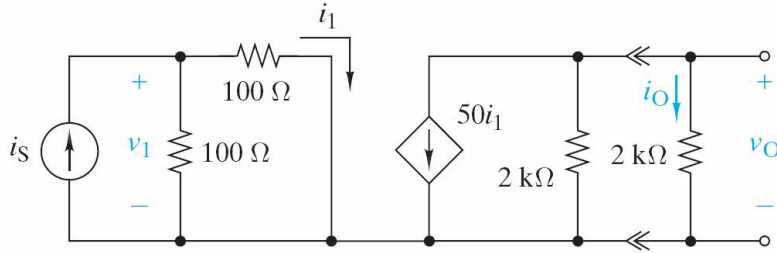
**Problem#1: Problem 4-2 textbook**

Find the voltage gain  $v_o/v_1$  and the current gain  $i_o/i_s$  for the given circuit. If the input current is  $i_s=2\text{mA}$ , find the power supplied by the input current source.




**Problem#2: Problem 4-7 textbook**

Find the output voltage.

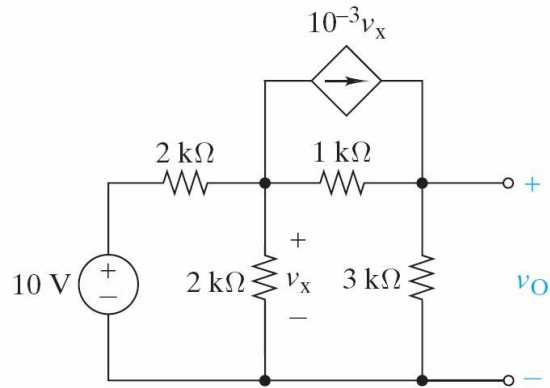


**Problem#3: Problem 4-13 textbook**

Find the input resistance  $R_{IN}$ .

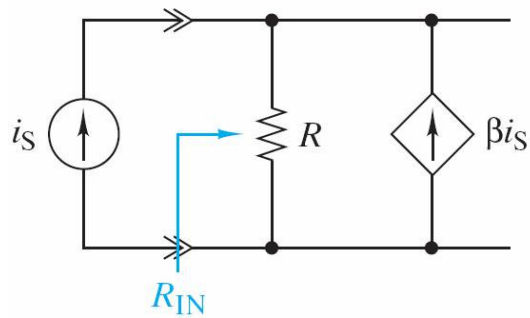

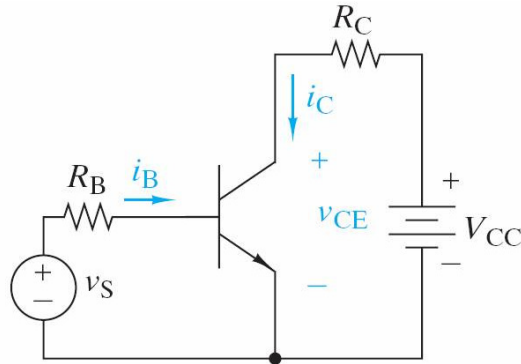**Problem#4: Problem 4-16 textbook**


The circuit parameters are  $R_B=50\text{ k}\Omega$ ,  $R_C=3\text{ k}\Omega$ ,  $\beta=100$ ,  $V_\gamma=0.7\text{ V}$ , and  $V_{CC}=15\text{ V}$ . Find the collector current  $i_C$  and  $V_{CE}$  for  $v_s=2\text{ V}$ .



**Problem#5: MATLAB Program**


The input to the circuit is a series connection of a dc source and signal source  $v_s$ . The parameters of the circuit are  $R_B=500\text{ k}\Omega$ ,  $R_C=5\text{ k}\Omega$ ,  $\beta=100$ ,  $V_\gamma=0.7\text{ V}$ , and  $V_{CC}=15\text{ V}$ .

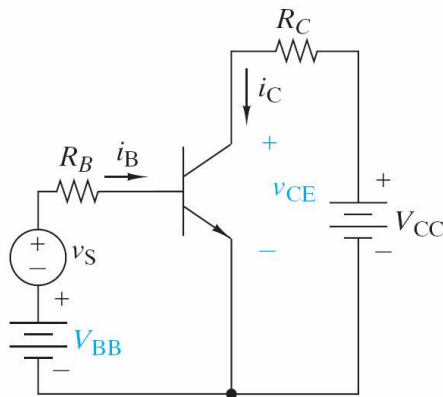- a) With  $v_s=0$  select the value of  $V_{BB}$  so that the circuit is in active mode when  $v_{CE}=V_{CC}/2$ .
- b) Using the same value of  $V_{BB}$  plot the characteristics of  $v_{CE}$  versus  $v_s$  as the signal voltage changes from  $-10\text{V}$  to  $+10\text{V}$ .




**Problem#6: Problem 4-23 textbook**

Find  $v_O$  in terms of  $v_S$ .

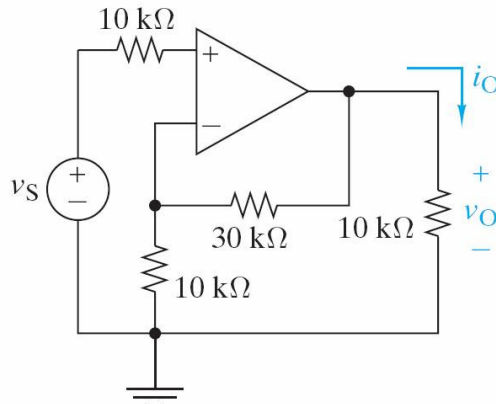

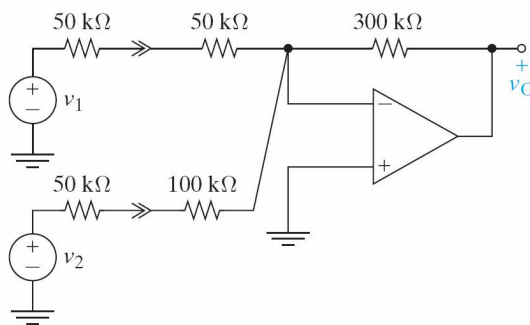
**Problem#7: Problem 4-26 textbook**

Find  $v_O$  in terms of inputs  $v_1$  and  $v_2$ .



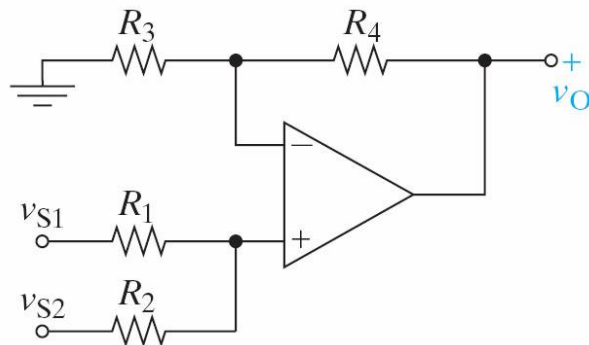
**Problem#8: Problem 4-30 textbook**

Find  $v_O$  in terms of  $v_{S1}$  and  $v_{S2}$ .



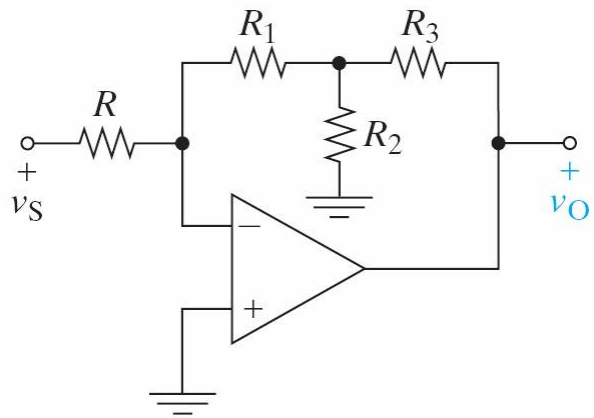**Problem#9: Problem 4-33 textbook**

Using node voltage analysis, find the input- output relationship.



**Problem#10: Problem 4-11 textbook**

Find an expression for  $v_o/v_s$ .

