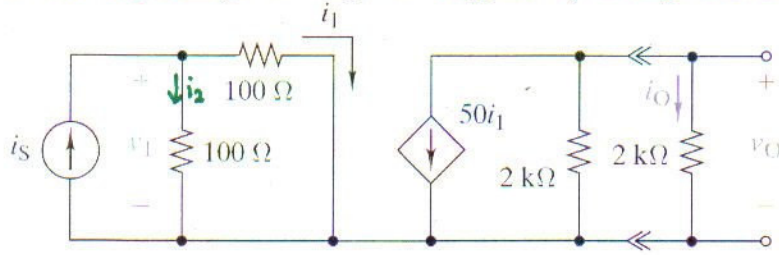


**Problem#1: Problem 4-2 textbook**

Find the voltage gain  $v_o/v_1$  and the current gain  $i_o/i_s$  for the given circuit. If the input current is  $i_s=2\text{mA}$ , find the power supplied by the input current source.



$$i_1 = \frac{100}{100+100} i_s = \frac{i_s}{2} = i_2$$

$$v_1 = 100 i_2 = 50 i_s$$

$$i_s = \frac{v_1}{50}$$


$$i_o = -\frac{2}{2+2} (50 i_1) = -25 i_1 = -12.5 i_s \quad \Rightarrow \quad \boxed{\frac{i_o}{i_s} = -12.5}$$

$$v_o = 2 \cdot 10^3 i_o = 2 \cdot 10^3 (-12.5 i_s) = -25 \cdot 10^3 i_s = -\frac{25 \cdot 10^3}{50} v_1 \quad \Rightarrow \quad \boxed{\frac{v_o}{v_1} = -500}$$

POWER SUPPLIED  $p = |v_1 \cdot i_s| = 50 (2 \cdot 10^{-3}) \cdot 2 \cdot 10^{-3} = 200 \cdot 10^{-6} = \boxed{0.2 \text{ mW}}$

**Problem#3: Problem 4-13 textbook**

Find the input resistance  $R_{IN}$ .

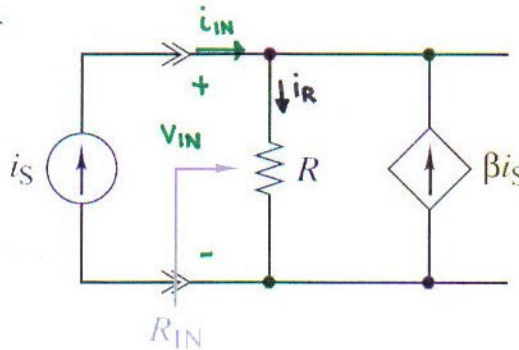

$$R_{IN} = \frac{v_{IN}}{i_{IN}}$$

$$i_{IN} = i_s$$

$$i_R = i_{IN} + \beta i_s = (1 + \beta) i_s$$

$$v_{IN} = R i_R = R(1 + \beta) i_s$$


$$\boxed{R_{IN}} = \frac{v_{IN}}{i_{IN}} = \frac{R(1 + \beta) i_s}{i_s} = \boxed{R(1 + \beta)}$$

**Problem#2: Problem 4-7 textbook**

Find the output voltage.

$$V_A = V_x$$

$$V_B = V_o$$

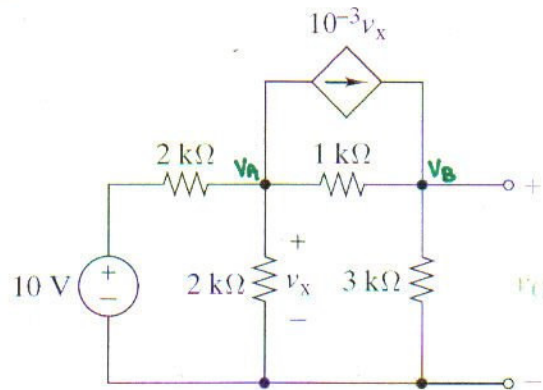

$$\text{NODE A} \quad \frac{V_A - 10}{2k} + \frac{V_A}{2k} + \frac{V_A - V_B}{1k} + 10^{-3} V_x = 0$$

$$V_A - 10 + V_A + 2V_A - 2V_B + 2V_A = 0$$

$$6V_A - 2V_B = 10 \quad (1)$$

$$\text{NODE B} \quad \frac{V_B - V_A}{1k} + \frac{V_B}{3k} = 10^{-3} V_x$$

$$3V_B - 3V_A + V_B = 3V_A$$


$$-6V_A + 4V_B = 0 \quad (2)$$

$$(1) + (2) \Rightarrow 2V_B = 10 \Rightarrow V_B = 5V \Rightarrow \boxed{V_o = 5V}$$

$$\text{substituting in (2)} \Rightarrow 6V_A = 20 \Rightarrow V_A = \frac{10}{3}V \Rightarrow V_x = 3.33V$$

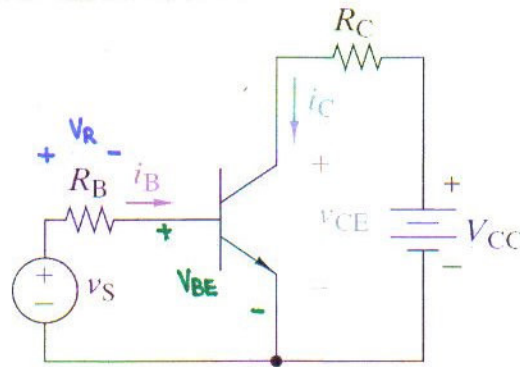**Problem#4: Problem 4-16 textbook**


The circuit parameters are  $R_B=50\text{ k}\Omega$ ,  $R_C=3\text{ k}\Omega$ ,  $\beta=100$ ,  $V_\gamma=0.7\text{ V}$ , and  $V_{CC}=15\text{ V}$ . Find the collector current  $i_C$  and  $V_{CE}$  for  $v_s=2\text{ V}$ .




$$V_R = V_s - V_{BE}$$

$$i_B = \frac{V_R}{R_B} = \frac{V_s - V_{BE}}{R_B}$$

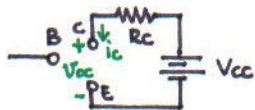(1) COMPUTE THE OPEN-CIRCUIT VOLTAGE AND SHORT-CIRCUIT CURRENT


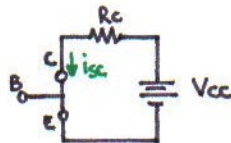
$$i_C = 0 \Rightarrow \underline{V_{oc} = V_{CC} = 15V}$$



$$\underline{i_{sc} = \frac{V_{CC}}{R_C} = \frac{15}{3K} = 5mA}$$

(2) ASSUME THAT THE BJT OPERATES IN ACTIVE MODE AND SOLVE THE CIRCUIT

when the BJT is in active mode  $\begin{cases} i_C = \beta i_B \\ V_{BE} = V_\gamma \end{cases}$

$$i_C = \beta i_B = \beta \left( \frac{V_s - V_{BE}}{R_B} \right) = 100 \left( \frac{2 - 0.7}{50 \cdot 10^3} \right) = 2.6\text{ mA}$$

$$V_{CE} = 15 - R_C i_C = 15 - 3 \cdot 10^3 (2.6 \cdot 10^{-3}) = 7.2\text{ V}$$

(3)

since

$$\begin{aligned} 0 < i_C < i_{sc} = 5\text{ mA} \\ 0 < V_{CE} < V_{oc} = 15\text{ V} \end{aligned}$$

the BJT is indeed operating  
in ACTIVE MODE




Thus the analysis carried in step (2) is correct and

$$\begin{aligned} i_C &= 2.6\text{ mA} \\ V_{CE} &= 7.2\text{ V} \end{aligned}$$

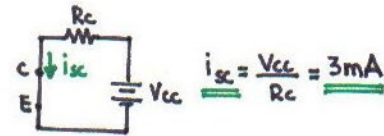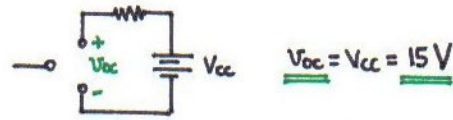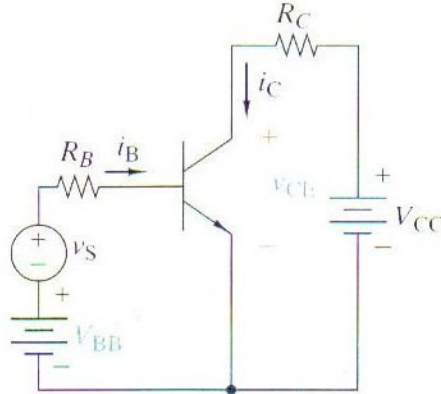
### Problem#5: MATLAB Program

The input to the circuit is a series connection of a dc source and signal source  $v_s$ . The parameters of the circuit are  $R_B=500 \text{ k}\Omega$ ,  $R_C=5 \text{ k}\Omega$ ,  $\beta=100$ ,  $V_\gamma=0.7 \text{ V}$ , and  $V_{CC}=15 \text{ V}$ .

- With  $v_s=0$  select the value of  $V_{BB}$  so that the circuit is in active mode when  $v_{CE}=V_{CC}/2$ .
- Using the same value of  $V_{BB}$  plot the characteristics of  $v_{CE}$  versus  $v_s$  as the signal voltage changes from  $-10\text{V}$  to  $+10\text{V}$ .



(a)

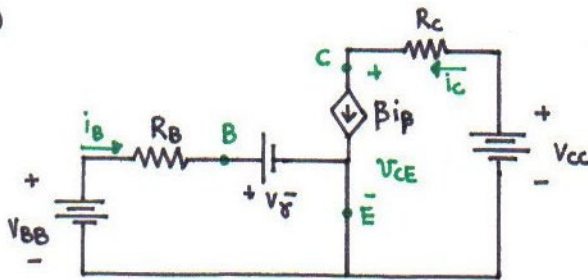

#### ACTIVE MODE

$$\begin{cases} v_{CE} + R_C i_C = V_{CC} \\ V_\gamma + R_B i_B = V_{BB} \end{cases} \quad \begin{cases} i_C = \beta i_B \\ v_{CE} = \frac{V_{CC}}{2} \end{cases}$$

$$\begin{cases} \frac{V_{CC}}{2} + R_C \beta i_B = V_{CC} & (1) \\ i_B = \frac{V_{BB} - V_\gamma}{R_B} & (2) \end{cases}$$

substituting (2) into (1)

$$R_C \beta \left( \frac{V_{BB} - V_\gamma}{R_B} \right) = \frac{V_{CC}}{2} \quad \Leftrightarrow \quad 5\text{K} \cdot 100 \left( \frac{V_{BB} - 0.7}{500\text{K}} \right) = 7.5 \quad \Leftrightarrow \quad \boxed{V_{BB} = 8.2 \text{ V}}$$

(b) the BJT remains in ACTIVE MODE IF

$$0 < v_{CE} < v_{oc} = 15\text{V} \quad (*)$$

$$0 < i_C < i_{sc} = 3\text{mA} \quad (+)$$


$$v_{CE} = V_{CC} - R_C \beta i_B = V_{CC} - \frac{R_C \beta}{R_B} (V_{BB} + v_s - V_\gamma) = V_{CC} - V_{BB} - v_s - V_\gamma = 7.5 - v_s$$

$$(*) \quad 0 < 7.5 - v_s < 15 \quad \Leftrightarrow \quad \boxed{-7.5\text{V} < v_s < 7.5\text{V}}$$

$$i_C = \beta \left( \frac{V_{BB} + v_s - V_\gamma}{R_B} \right) = 0.2 (7.5 + v_s) \cdot 10^{-3}$$


$$v_s = -7.5\text{V} \quad \Leftrightarrow \quad i_C = 0 \quad \Leftrightarrow \quad (+) \text{ is satisfied}$$
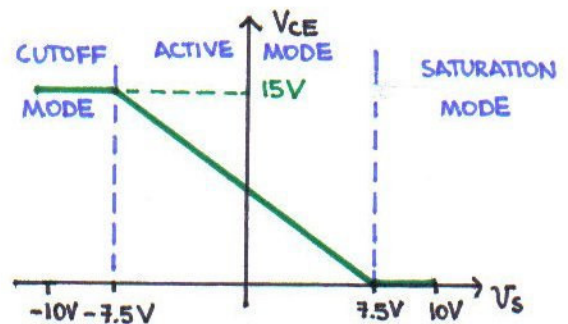
$$v_s = 7.5\text{V} \quad \Leftrightarrow \quad i_C = 3\text{mA}$$



**Problem#6: Problem 4-23 textbook**

Find  $v_o$  in terms of  $v_s$ .

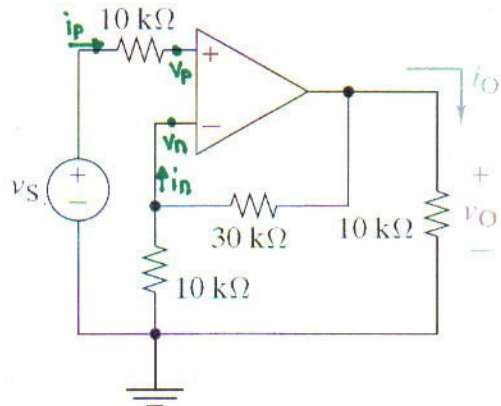

OP AMP  $\Rightarrow$

$$\begin{aligned} v_p &= v_n \\ i_p &= i_n = 0 \end{aligned}$$

$$i_p = 0 \Rightarrow v_p = v_s$$

$$v_n = v_p = v_s$$

$$i_n = 0 \Rightarrow \frac{v_n}{10\text{K}} + \frac{v_n - v_o}{30\text{K}} = 0$$


$$3v_n + v_n - v_o = 0$$

$$4v_n = v_o$$

$$v_o = 4v_s$$

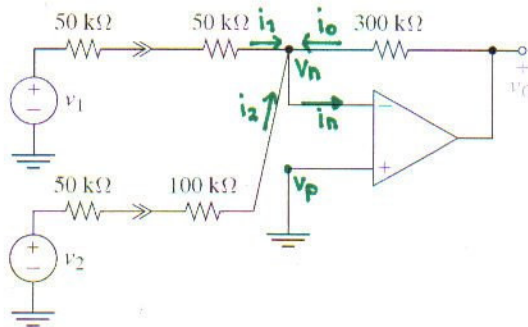**Problem#7: Problem 4-26 textbook**

Find  $v_o$  in terms of inputs  $v_1$  and  $v_2$ .



OP AMP  $\Rightarrow$

$$\begin{aligned} v_p &= v_n \\ i_p &= i_n = 0 \end{aligned}$$

$$v_p = 0 \Rightarrow v_n = 0$$


$$i_n = 0 \Rightarrow i_o + i_1 + i_2 = 0$$

$$\frac{v_o - v_n}{300k} + \frac{v_1 - v_n}{100k} + \frac{v_2 - v_n}{150k} = 0$$

$$2v_2 + 3v_1 + v_o = 0$$

$$v_o = -3v_1 - 2v_2$$

NOTE

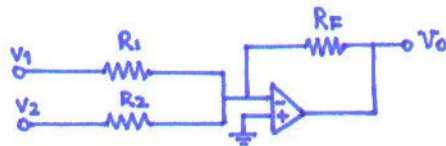

SUMMER

$$v_o = K_1 v_1 + K_2 v_2$$

$$K_1 = -\frac{R_F}{R_1}$$


$$K_2 = -\frac{R_F}{R_2}$$

IN OUR CASE  $R_1 = 100k\Omega$   
 $R_2 = 150k\Omega$   
 $R_F = 300k\Omega$

HENCE  $K_1 = -3$   
 $K_2 = -2$

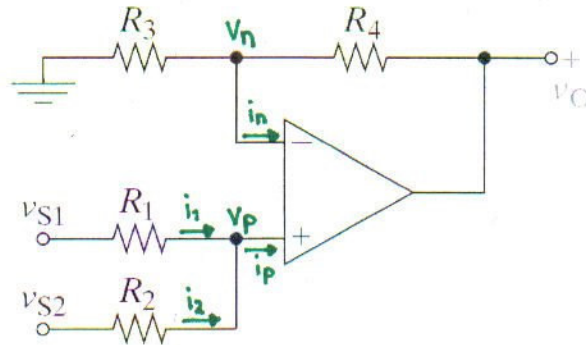**Problem#8: Problem 4-30 textbook**

Find  $v_o$  in terms of  $v_{s1}$  and  $v_{s2}$ .



$$i_n = i_p = 0$$

$$v_n = v_p$$

since  $i_n = 0$  by voltage division rule 
$$v_n = \frac{R_3}{R_3 + R_4} v_o = v_p$$

$$i_p = 0 \Rightarrow i_1 + i_2 = 0$$

$$\frac{v_{s1} - v_p}{R_1} + \frac{v_{s2} - v_p}{R_2} = 0$$

$$R_2 \left( v_{s1} - \frac{R_3 v_o}{R_3 + R_4} \right) + R_1 \left( v_{s2} - \frac{R_3 v_o}{R_3 + R_4} \right) = 0$$


$$R_2 v_{s1} + R_1 v_{s2} = \frac{R_3 (R_1 + R_2)}{R_3 + R_4} v_o$$

$$v_o = \frac{R_3 + R_4}{R_3 (R_1 + R_2)} [R_2 v_{s1} + R_1 v_{s2}]$$

NON INVERTING  
SUMMER AMPLIFIER

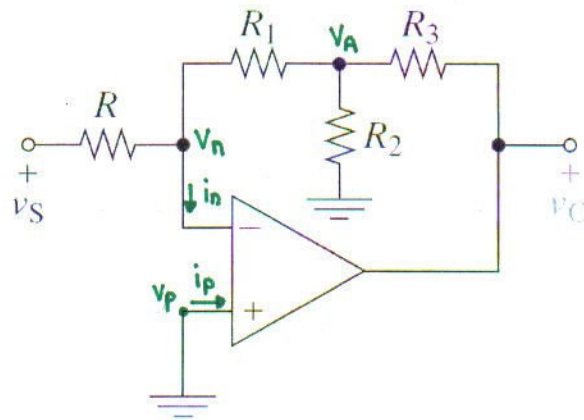**Problem#9: Problem 4-33 textbook**

Using node voltage analysis, find the input- output relationship.



$$v_n = v_p$$

$$i_n = i_p = 0$$

$$v_p = 0 \quad \Rightarrow \quad v_n = v_p = 0$$

$$i_n = 0 \quad \Rightarrow \quad \frac{v_n - v_s}{R} + \frac{v_n - v_A}{R_1} = 0$$

$$R_1 v_s = -R v_A$$

$$v_A = -\frac{R_1}{R} v_s$$

$$\text{KCL @ NODE A} \quad \Rightarrow \quad \frac{v_A - v_n}{R_1} + \frac{v_A}{R_2} + \frac{v_A - v_o}{R_3} = 0$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v_A = \frac{v_o}{R_3}$$


$$\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 R_2 R_3} \left( -\frac{R_1}{R} v_s \right) = \frac{v_o}{R_3}$$

$$v_o = -\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R R_2} v_s$$



**Problem#10: Problem 4-11 textbook**

Find an expression for  $v_o/v_s$ .

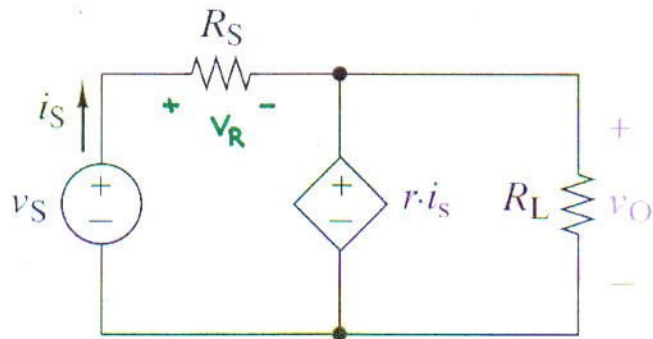

$$v_R = R_s i_s = v_s - r i_s$$

$$(R_s + r) i_s = v_s$$

$$i_s = \frac{v_s}{R_s + r}$$

$$v_o = r i_s = \frac{r}{R_s + r} v_s$$

$$\boxed{\frac{v_o}{v_s} = \frac{r}{r + R_s}}$$