



The Ohio State University
Department of Electrical Engineering

ECE 205

Circuit Analysis

Home work Set # 7


Print Your Name

Problem#1: Problem 6-2 textbook

The voltage across a 3mF capacitor is $v_c(t) = 20 \sin(2\pi 10t)$ V . Derive expressions for $i_c(t)$ and $p_c(t)$. Is the capacitor absorbing or delivering power?

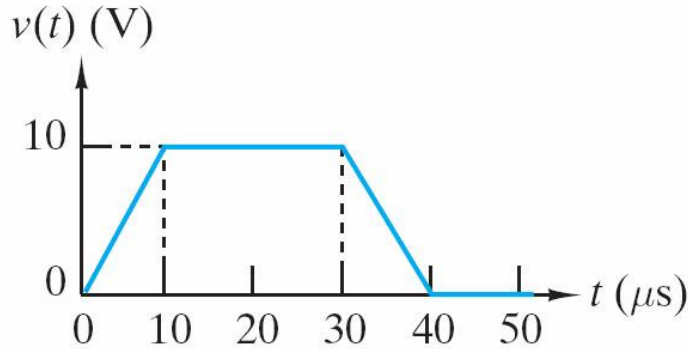Problem#2: Problem 6-6 textbook

The voltage across a 0.5 μ F capacitor is shown in the Figure. Sketch $i_c(t)$ and $p_c(t)$. Is the capacitor absorbing or delivering power?




Problem#3: MATLAB Problem

A voltage of $v_L(t) = 5 \cos(1000t) - 2 \sin(3000t)$ V appears across a 50mH inductor. Derive an expression for $i_L(t)$ assuming $i_L(0)=0$. Discuss the effect of frequency on the relative amplitudes of the sinusoidal components of $i_L(t)$ and $v_L(t)$. Sketch these waveforms in MATLAB.

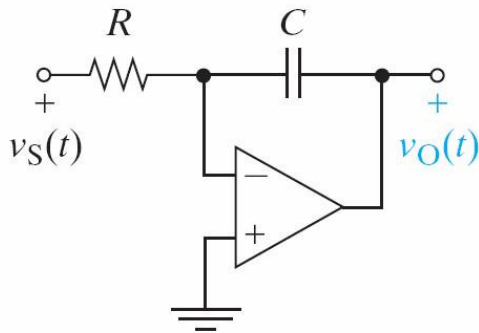
Problem#4: Problem 6-21 textbook

The OP AMP integrator in the Figure has $R=40$ k Ω , $C=50$ nF, and $v_o(0)=10$ V. The input is $v_s(t) = 10e^{-500t}u(t)$ V . Find $v_o(t)$ for $t>0$.



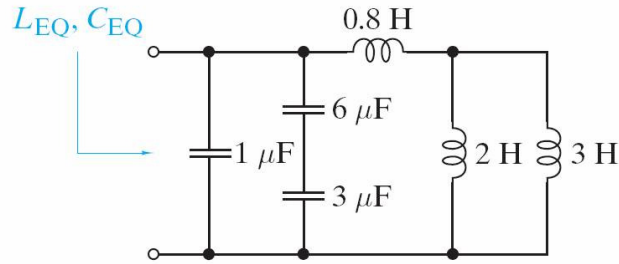
Problem#5: Problem 6-40 textbook

For the circuit given find an equivalent circuit consisting of one inductor and one capacitor.



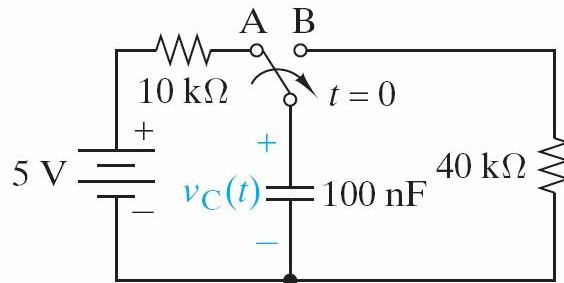
Problem#6: Problem 7-7 textbook

The switch has been in position A for a long time and is moved to position B at $t=0$. Find $v_C(t)$ for $t \geq 0$.



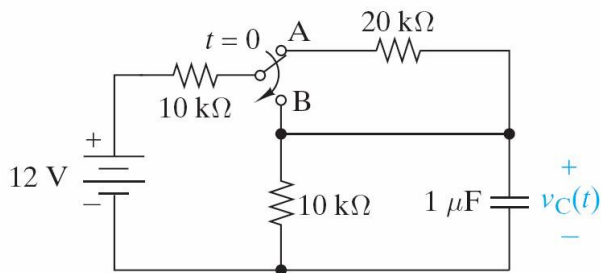
Problem#7: Problem 7-13 textbook

The switch has been in position A for a long time and is moved to position B at $t=0$. Find $v_C(t)$ for $t \geq 0$. Identify t_e forced and natural components in the response.



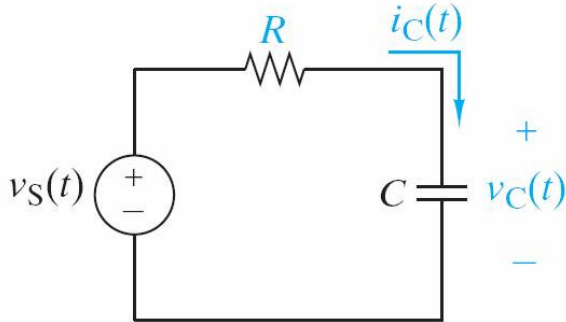Problem#8: Problem 7-26 textbook

For $t \geq 0$ the step response of the current through the capacitor in Figure is $i_C(t) = 20e^{-2000t}$ mA. Find $v_C(t)$ for $t \geq 0$ when $C = 1 \mu\text{F}$ and $v_C(0) = 5$ V.



Problem#9: Problem 7-27 textbook

For $t \geq 0$ the step response of the current through and voltage across the inductor are:

$$i_L(t) = 5 - 10e^{-2000t} \text{ mA} \quad \text{and} \quad v_L(t) = e^{-2000t} \text{ V}$$

- (a) Find v_s , R and L .
- (b) Find the energy stored in the inductor at $t = \ln(2)/2$ ms.

