

Problem#1: Problem 6-2 textbook

The voltage across a 3mF capacitor is $v_c(t) = 20 \sin(2\pi 10t)$ V. Derive expressions for $i_c(t)$ and $p_c(t)$. Is the capacitor absorbing or delivering power?

$$i_c(t) = C \frac{dv_c}{dt} = (3 \cdot 10^{-3}) \cdot 20 \cdot (2\pi 10) \cos(2\pi 10t)$$


$$i_c(t) = 1.2\pi \cos(2\pi 10t) \text{ A}$$

$$p_c(t) = v_c(t) \cdot i_c(t) = 20 \sin(2\pi 10t) \cdot 1.2\pi \cos(2\pi 10t)$$
$$= 24\pi \sin(2\pi 10t) \cdot \cos(2\pi 10t)$$

↓ $\sin\alpha \cos\alpha = \frac{\sin 2\alpha}{2}$ since $\sin(\alpha+\beta) = \sin\alpha \cos\beta + \sin\beta \cos\alpha$
 $\sin(2\alpha) = 2 \sin\alpha \cos\alpha$

$$p_c(t) = 12\pi \sin(2\pi 20t) \text{ W}$$

$$T_0 = \frac{1}{20} = 50 \text{ ms}$$

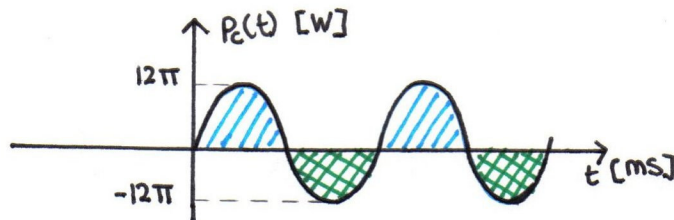


/// ABSORBING
⊗ DELIVERING

The capacitor absorbs and delivers power

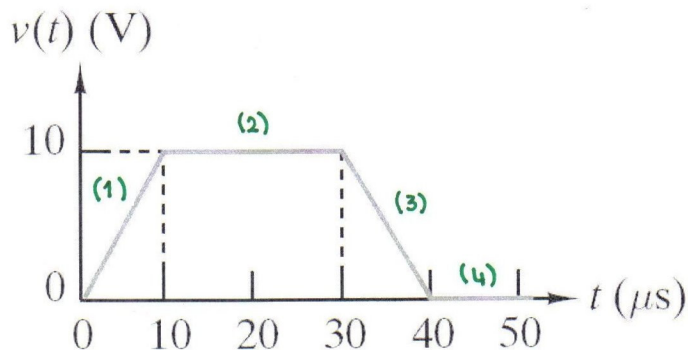Problem#2: Problem 6-6 textbook



The voltage across a $0.5 \mu\text{F}$ capacitor is shown in the Figure. Sketch $i_c(t)$ and $p_c(t)$. Is the capacitor absorbing or delivering power?




(1) slope in $[0, 10] \mu\text{s} = \frac{10}{10^{-5}} = 10^6 \quad \Rightarrow \quad i_c(t) = C \frac{dv_c}{dt} = 0.5 \cdot 10^{-6} \cdot 10^6 = 0.5 \text{ A} \quad t \in [0, 10] \mu\text{s}$

(2)-(4) slope in $[10, 30] \mu\text{s}$ and $[40, 50] \mu\text{s} = 0 \quad \Rightarrow \quad i_c(t) = C \cdot 0 = 0 \text{ A} \quad t \in [10, 30] \mu\text{s}$
 $t \in [40, 50] \mu\text{s}$

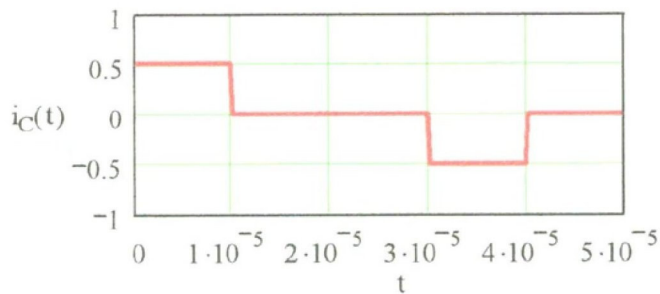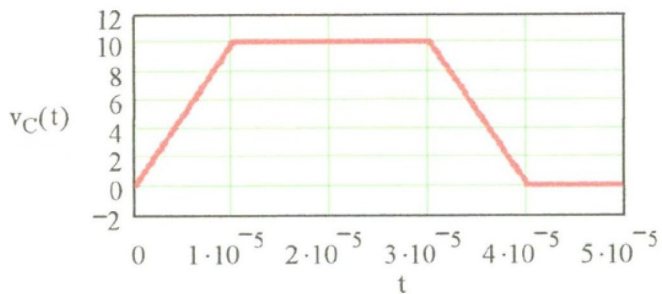(3) slope in $[30, 40] \mu\text{s} = \frac{-10}{10^{-5}} = -10^6 \quad \Rightarrow \quad i_c(t) = 0.5 \cdot 10^{-6} (-10^6) = -0.5 \text{ A} \quad t \in [30, 40] \mu\text{s}$



$$p_c(t) = v_c(t) \cdot i_c(t)$$

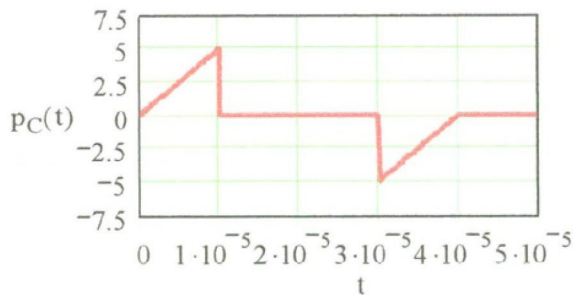

The capacitor absorbs power from $0 < t < 10 \mu\text{s}$ and delivers power in $30 \mu\text{s} < t < 40 \mu\text{s}$.

Problem#3: MATLAB Problem

A voltage of $v_L(t) = 5 \cos(1000t) - 2 \sin(3000t) \text{ V}$ appears across a 50mH inductor. Derive an expression for $i_L(t)$ assuming $i_L(0)=0$. Discuss the effect of frequency on the relative amplitudes of the sinusoidal components of $i_L(t)$ and $v_L(t)$. Sketch these waveforms in MATLAB.

$$L = 0.05 \text{ H}$$

$$v_L(t) = 5 \cos(1000t) - 2 \sin(3000t) \text{ V}$$

$$v_L(t) = L \frac{di_L(t)}{dt} \Rightarrow i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(x) dx$$

$$\begin{aligned} i_L(t) &= 0 + \frac{1}{0.05} \int_0^t [5 \cos(1000x) - 2 \sin(3000x)] dx \\ &= 20 \left[\frac{5}{1000} \sin(1000x) + \frac{2}{3000} \cos(3000x) \right]_0^t \\ &= \frac{1}{10} \sin(1000t) + \frac{1}{75} \cos(3000t) - \frac{1}{75} \text{ A} \end{aligned}$$


NOTE if $v_L(t) = a_1 \cos(\omega_1 t) - a_2 \sin(\omega_2 t)$

$$\begin{aligned} \text{then } i_L(t) &= \frac{1}{L} \left[\frac{a_1}{\omega_1} \sin(\omega_1 t) + \frac{a_2}{\omega_2} \cos(\omega_2 t) - \frac{a_2}{\omega_2} \right] \\ &= \underbrace{-\frac{a_2}{L\omega_2}}_{\text{DC}} + \underbrace{\frac{a_1}{L\omega_1} \sin(\omega_1 t) + \frac{a_2}{L\omega_2} \cos(\omega_2 t)}_{\text{AC}} \end{aligned}$$


in $v_L(t)$ the ratio of the two amplitudes of the 1KHz and 3KHz AC components is

$$\frac{a_1}{a_2} = \frac{5}{2} = \underline{\underline{2.5}}$$

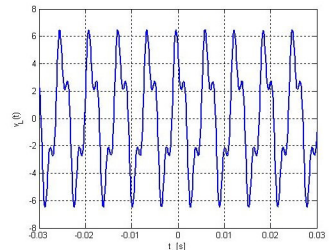in $i_L(t)$ is $\frac{\frac{a_1}{L\omega_1}}{\frac{a_2}{L\omega_2}} = \frac{a_1}{a_2} \cdot \frac{\omega_2}{\omega_1} = \frac{5}{2} \cdot \frac{3000}{1000} = 7.5$




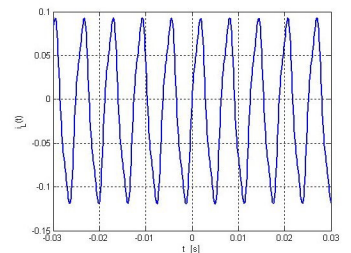Therefore the integration produces a DC component and reduces the amplitude of the higher frequency (3KHz) component relative to the lower frequency component (1KHz)



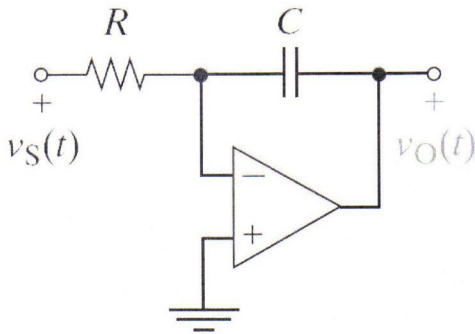Problem#4: Problem 6-21 textbook

The OP AMP integrator in the Figure has $R=40 \text{ k}\Omega$, $C=50 \text{ nF}$, and $v_o(0)=10 \text{ V}$. The input is $v_s(t) = 10e^{-500t} u(t) \text{ V}$. Find $v_o(t)$ for $t > 0$.



$$\begin{aligned} V_n &= V_p \\ i_n &= i_p = 0 \end{aligned}$$

$$V_p = 0 \Rightarrow V_n = 0$$

$$i_n = 0 \Rightarrow \frac{v_s - v_n}{R} + C \frac{d(v_o - v_n)}{dt} = 0$$

$$\frac{dv_o}{dt} = -\frac{1}{RC} v_s$$

$$v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_s(x) dx = 10 - \frac{1}{RC} \int_0^t 10 e^{-500x} dx$$


$$= 10 - \frac{1}{40 \cdot 10^3 \cdot 50 \cdot 10^{-9}} \left[-\frac{e^{-500x}}{50} \right]_0^t$$

$$= 10 - \frac{10}{500} \left(-\frac{e^{-500t}}{50} + \frac{1}{50} \right)$$

$$v_o(t) = 10 e^{-500t} \text{ V} \quad t \geq 0$$


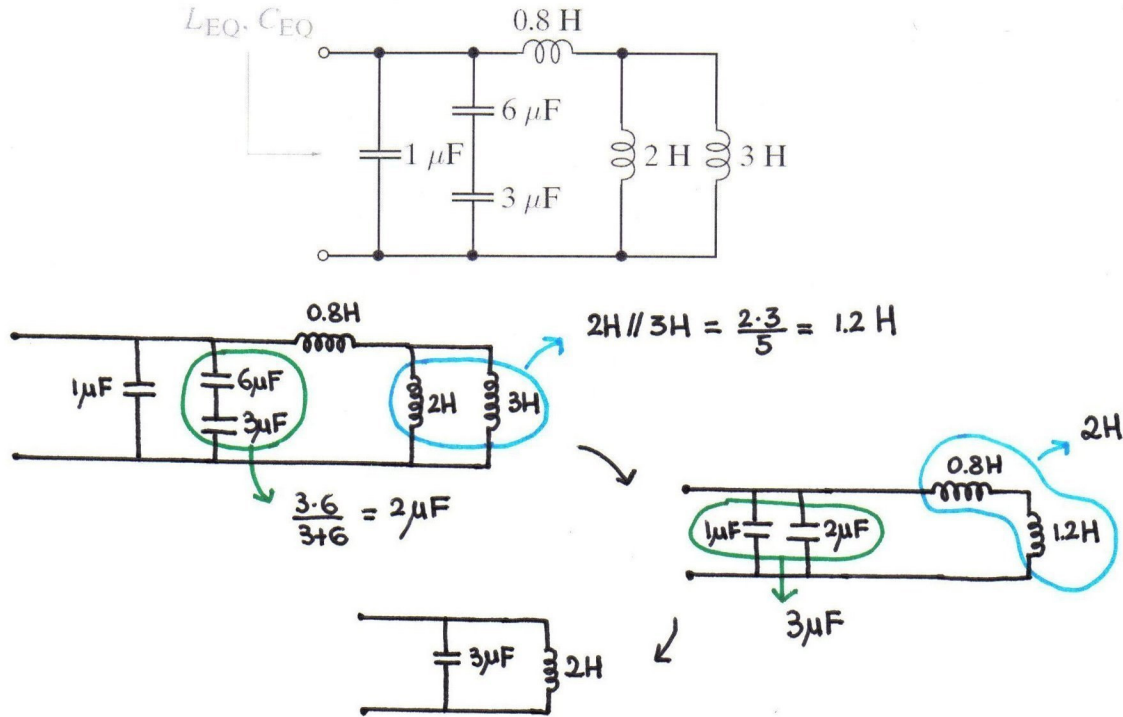
Problem#5: Problem 6-40 textbook

For the circuit given find an equivalent circuit consisting of one inductor and one capacitor.




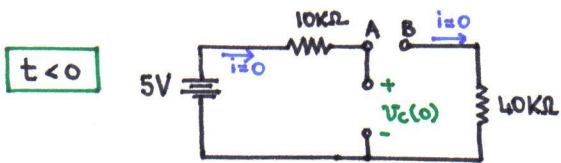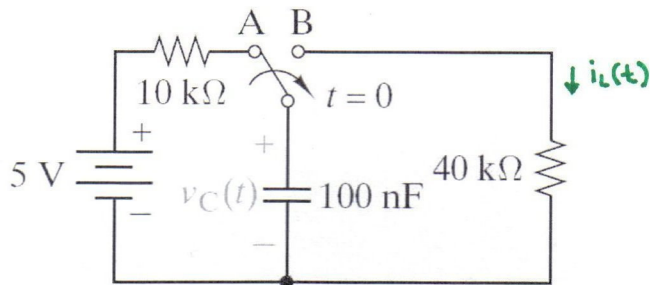Problem#6: Problem 7-7 textbook

The switch has been in position A for a long time and is moved to position B at $t=0$. Find $v_c(t)$ for $t \geq 0$.



$$v_c(0) = \underline{5\ \text{V}}$$

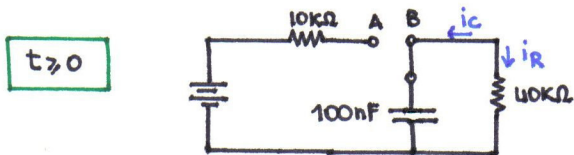

$$\text{KCL } i_c + i_R = 0 \Rightarrow C \frac{dv_c}{dt} + \frac{v_c}{R} = 0$$


$$\frac{dv_c}{dt} = -250 v_c$$

$$v_c(t) = v_c(0) e^{-250t}$$


$$v_c(t) = 5 e^{-250t} \text{ V} \quad t \geq 0$$

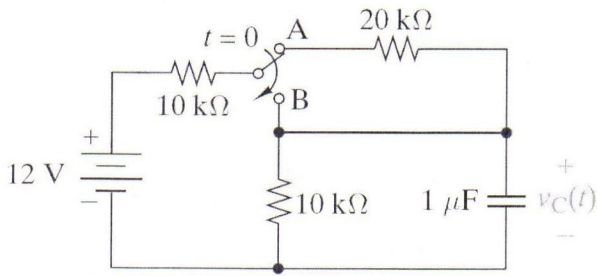Problem#7: Problem 7-13 textbook

The switch has been in position A for a long time and is moved to position B at $t=0$. Find $v_C(t)$ for $t \geq 0$. Identify the forced and natural components in the response.





$t < 0$

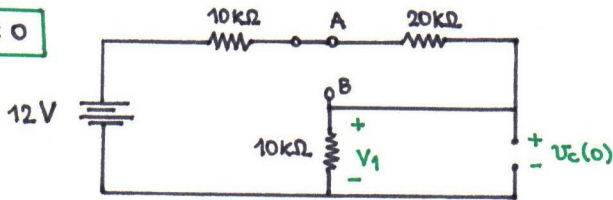

VOLTAGE DIVISION RULE

$$v_C(0) = \frac{10K}{10K + 10K + 20K} \cdot 12V = 3V$$

$t \geq 0$

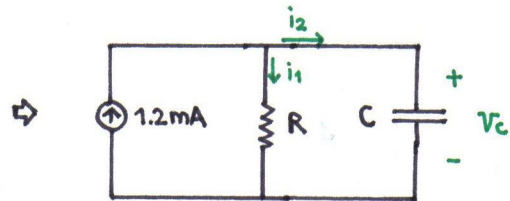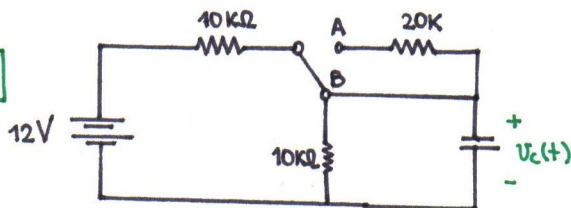

$$i_s = \frac{V_s}{10K} = \frac{12}{10 \cdot 10^3} = 1.2 \text{ mA}$$

$$R = 10K \parallel 10K = 5K\Omega$$

$$i_1 + i_2 = 1.2 \text{ mA}$$

$$\frac{v_C}{R} + C \frac{dv_C}{dt} = 1.2 \cdot 10^{-3}$$

$$\frac{dv_C}{dt} + \frac{1}{RC} v_C = \frac{1.2 \cdot 10^{-3}}{C}$$

$$a = \frac{1}{RC} = \frac{1}{5 \cdot 10^3 \cdot 10^{-6}} = 200$$

$$b = \frac{1.2 \cdot 10^{-3}}{10^{-6}} = 1200$$

$$b/a = 1200/200 = 6$$

$$\begin{cases} \frac{dv_C}{dt} + a v_C = b \\ v_C(0) = v_0 \end{cases}$$


$$v_C(t) = \left(v_0 - \frac{b}{a} \right) e^{-at} + \frac{b}{a}$$

$$v_C(t) = (3 - 6) e^{-200t} + 6 = \underbrace{6}_{\text{NATURAL RESPONSE}} - \underbrace{3 e^{-200t}}_{\text{FORCED RESPONSE}} \text{ V} \quad t \geq 0$$

NATURAL RESPONSE FORCED RESPONSE

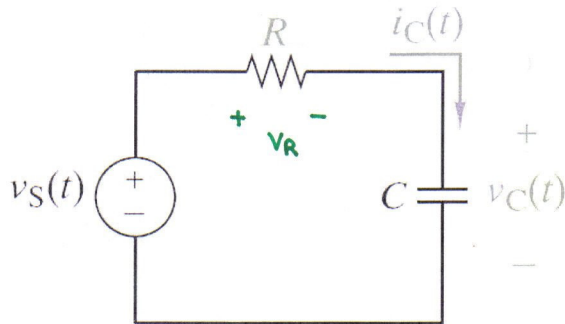Problem#8: Problem 7-26 textbook

For $t \geq 0$ the step response of the current through the capacitor in Figure is $i_C(t) = 20e^{-2000t}$ mA. Find $v_C(t)$ for $t \geq 0$ when $C = 1 \mu\text{F}$ and $v_C(0) = 5$ V.



$$v_C(t) = v_C(0) + \frac{1}{C} \int_0^t i_C(x) dx$$

$$= 5 + \frac{1}{\frac{10^{-6}}{10^{-3}}} \int_0^t 20 \cdot 10^{-3} e^{-2000x} dx$$

$$= 5 + 10^3 \left[-\frac{e^{-2000x}}{100} \right]_0^t = 5 + 10^3 \left[-\frac{e^{-2000t}}{100} + \frac{1}{100} \right]$$

$$= 15 - 10 e^{-2000t} \text{ V} \quad t \geq 0$$


Problem#9: Problem 7-27 textbook

For $t \geq 0$ the step response of the current through and voltage across the inductor are:

$$i_L(t) = 5 - 10e^{-2000t} \text{ mA} \quad \text{and} \quad v_L(t) = e^{-2000t} \text{ V}$$

(a) Find v_s , R and L .

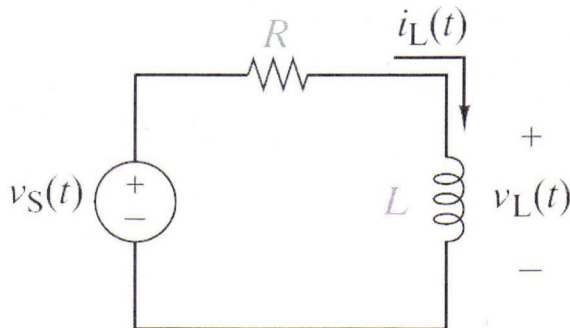(b) Find the energy stored in the inductor at $t = \ln(2)/2$ ms.



$$(a) \quad L = \frac{v_L(t)}{\frac{di_L(t)}{dt}} = \frac{e^{-2000t}}{(-10)(-2000)e^{-2000t} \cdot 10^{-3}} = \frac{1}{20} = \boxed{0.05 \text{ H}}$$

$$v_R + v_L = v_s \quad \Leftrightarrow \quad R i_L(t) + L \frac{di_L(t)}{dt} = v_s$$

$$\frac{di_L(t)}{dt} + \frac{R}{L} i_L(t) = \frac{v_s}{L} \quad \Leftrightarrow \quad i_L(t) = a e^{-\frac{R}{L}t} + b \quad \Leftrightarrow \quad \frac{R}{L} = 2000$$

$$\boxed{R} = 2000 L = \boxed{100 \Omega}$$

since at $t = \infty$ the inductor acts like a short circuit

$$\boxed{v_s} = R i_L(\infty) = 100 \cdot 5 \cdot 10^{-3} = \boxed{0.5 \text{ V}}$$

$$(b) \quad w_L(t) = \frac{1}{2} L i_L^2(t)$$

$$\boxed{w_L \left(\frac{\ln(2)}{2000} \right)} = \frac{1}{2} L \left[5 - 10 \exp \left(-\frac{2000 \ln(2)}{2000} \right) \right]^2 \cdot (10^{-3})^2$$

$$= \frac{1}{2} L \left[\cancel{5} - 10 \exp(-\ln(2)) \right]^2 \cdot 10^{-6} = \boxed{0}$$

$$\exp(-\ln(2)) = \exp(\ln(\frac{1}{2})) = \frac{1}{2}$$