



The Ohio State University  
Department of Electrical Engineering

ECE 205

**Circuit Analysis**

**Home work Set # 8**

**Print Your Name**

---

**Problem#1: Problem 8-1 textbook**

Transform the following sinusoids into phasor form and draw a phasor diagram. Use the additive property of phasors to find  $v_1(t) + v_2(t)$ .

a)  $v_1(t) = 250 \cos(\omega t + 60^\circ) \text{V}$

b)  $v_2(t) = 100 \cos(\omega t) + 150 \sin(\omega t) \text{V}$

**Problem#2: Problem 8-3 textbook**

Convert the following phasors into sinusoidal waveforms.

a)  $\mathbf{V}_1 = 10e^{-j30^\circ} \text{V}, \omega = 10^4 \text{ rad/s}$

b)  $\mathbf{V}_2 = 60e^{-j220^\circ} \text{V}, \omega = 10^4 \text{ rad/s}$

c)  $\mathbf{I}_1 = 5e^{j90^\circ} \text{A}, \omega = 200 \text{ rad/s}$

d)  $\mathbf{I}_2 = 2e^{j270^\circ} \text{A}, \omega = 200 \text{ rad/s}$

**Problem#3: Problem 8-6 textbook**

Convert the following phasors into sinusoids:

a)  $\mathbf{V}_1 = 20 + j25 \text{V}, \omega = 10 \text{ rad/s}$

b)  $\mathbf{V}_2 = 5(8 - j3) \text{V}, \omega = 20 \text{ rad/s}$

c)  $\mathbf{I}_1 = 12 - j5 + \frac{4}{j} \text{A}, \omega = 300 \text{ rad/s}$


d)  $\mathbf{I}_2 = \frac{3 + j8}{2 - j6} \text{A}, \omega = 50 \text{ rad/s}$

**Problem#4: Problem 8-10 textbook**

Given a sinusoid  $v_1(t)$  whose phasor is  $\mathbf{V}_1 = -3 + j4 \text{V}$ , use phasor methods to find the voltage  $v_2(t)$  that leads  $v_1(t)$  by  $90^\circ$  and has an amplitude of  $10 \text{V}$ .

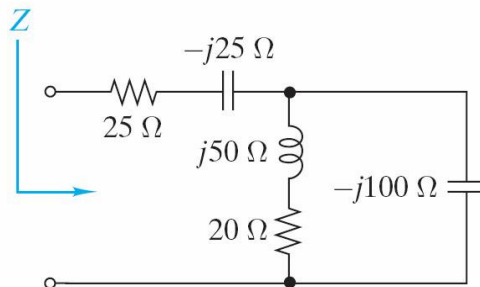
**Problem#5: Problem 8-12 textbook**

Find the equivalent impedance  $Z$  in the circuit. Express the result in both polar and rectangular form.



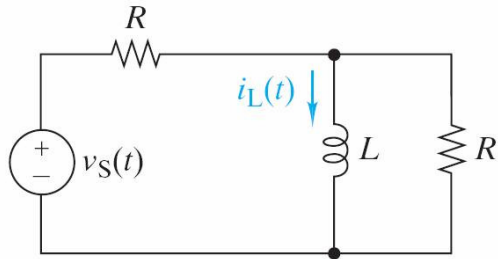
**Problem#6: Problem 8-22 textbook**

The circuit is operating in the sinusoidal steady state with  $v_S(t) = V_A \cos(\omega t)$ . Derive a general expression for the phasor response  $I_L$ .



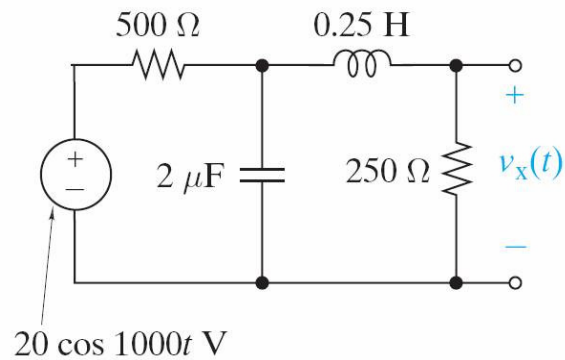
**Problem#7: Problem 8-26 textbook**

The circuit is operating in sinusoidal steady state. Find the steady state response  $v_x(t)$ .



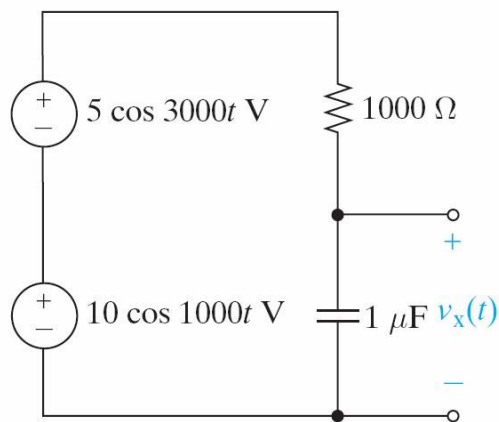
**Problem#8: Problem 8-30 textbook**

The circuit is operating in sinusoidal steady state. Use superposition to find the response  $v_x(t)$ . *Note:* the sources do not have the same frequency.



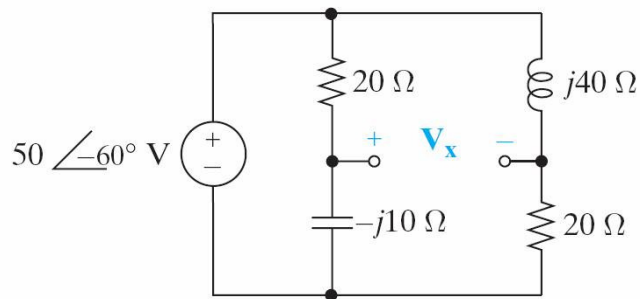**Problem#9: Problem 8-32 textbook**

The circuit is operating in the sinusoidal steady state. Find the phasor response  $V_x$ .



**Problem#10: Problem 8-41 textbook**

The circuit is operating in the sinusoidal steady state with  $\omega=4 \text{ krad/s}$ . Use node-voltage analysis to find the steady-state response  $v_x(t)$ .

