

Problem#1: Problem 8-1 textbook

Transform the following sinusoids into phasor form and draw a phasor diagram. Use the additive property of phasors to find $v_1(t) + v_2(t)$.


a) $v_1(t) = 250 \cos(\omega t + 60^\circ) \text{V}$

b) $v_2(t) = 100 \cos(\omega t) + 150 \sin(\omega t) \text{V}$

$$\boxed{V_1} = 250 \angle 60^\circ = 250 \cos(60^\circ) + j 250 \sin(60^\circ) = \boxed{125 + j 216.5}$$

$$v_2(t) = 100 \cos(\omega t) + 150 \cos(\omega t - 90^\circ)$$
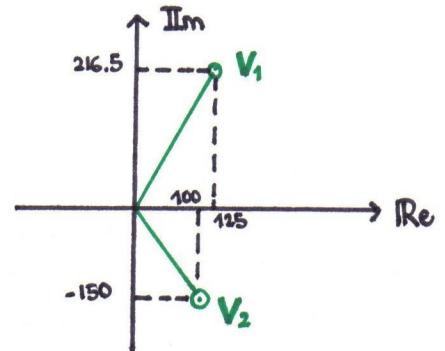
$$\boxed{V_2} = \underbrace{100 \angle 0^\circ}_{100 + j0} + \underbrace{150 \angle -90^\circ}_{0 - j150} = \boxed{100 - j 150}$$



$$\boxed{V_3} = V_1 + V_2 = 225 + 66.5 j$$

$$= \sqrt{225^2 + 66.5^2} \angle \tan^{-1} \left(\frac{66.5}{225} \right) \cdot \frac{180}{\pi} = \boxed{234.62 \angle 16.465^\circ}$$

↳ $\text{Re}\{V\} > 0$
 $\text{Im}\{V\} > 0$
 thus $0 < \theta < 90^\circ$

$$\boxed{v_1(t) + v_2(t) = 234.62 \cos(\omega t + 16.465^\circ) \text{ V}}$$

Problem#2: Problem 8-3 textbook

Convert the following phasors into sinusoidal waveforms.

a) $V_1 = 10e^{-j30^\circ} \text{V}, \omega = 10^4 \text{ rad/s}$

b) $V_2 = 60e^{-j220^\circ} \text{V}, \omega = 10^4 \text{ rad/s}$

c) $I_1 = 5e^{j90^\circ} \text{A}, \omega = 200 \text{ rad/s}$

d) $I_2 = 2e^{j270^\circ} \text{A}, \omega = 200 \text{ rad/s}$

a) $\boxed{v_1(t)} = \text{Re} [10 e^{-j30^\circ} \cdot e^{j10^4 t}] = 10 \text{Re} [e^{j(10^4 t - 30^\circ)}] = \boxed{10 \cos(10^4 t - \frac{\pi}{6})} \text{ V}$
 ↓
 $\cos \theta = \text{Re} [e^{j\theta}]$

b) $\boxed{v_2(t) = 60 \cos(10^4 t - 220 \frac{\pi}{180})} \text{ V}$

c) $\boxed{i_1(t) = 5 \cos(200t + \frac{\pi}{2})} \text{ A}$

$$90^\circ = \frac{\pi}{2}$$

d) $\boxed{i_2(t) = 2 \cos(200t + \frac{3}{2}\pi)} \text{ A}$

$$270^\circ = \frac{3}{2}\pi$$

Problem#3: Problem 8-6 textbook

Convert the following phasors into sinusoids:

a) $V_1 = 20 + j25V, \omega = 10\text{rad/s}$

b) $V_2 = 5(8 - j3)V, \omega = 20\text{rad/s}$

c) $I_1 = 12 - j5 + \frac{4}{j}A, \omega = 300\text{rad/s}$

d) $I_2 = \frac{3 + j8}{2 - j6}A, \omega = 50\text{rad/s}$

a) $V_1 = 20 + j25V \quad M = \sqrt{20^2 + 25^2} = 32.016$

$$\theta = \begin{cases} \tan^{-1}\left(\frac{25}{20}\right) \cdot \frac{180}{\pi} & = 51.34^\circ \\ 0^\circ < \theta < 90^\circ \end{cases}$$

$$V_1 = 32.016 \angle 51.34^\circ$$

$$v_1(t) = 32.016 \cos(10t + 51.34^\circ) \quad V$$

b) $V_2 = 40 - j15V = 42.72 \angle -20.556^\circ \quad V$

$$v_2(t) = 42.72 \cos(20t - 20.556^\circ) \quad V$$

c) $I_1 = 12 - j5 + \frac{4j}{j^2 = -1} = 12 - j9 = 15 \angle -36.87^\circ \quad A$

$$i_1(t) = 15 \cos(300t - 36.87^\circ) \quad A$$

d) $I_2 = \frac{3 + j8}{2 - j6} \cdot \frac{2 + j6}{2 + j6} = \frac{6 + j16 + j18 - 48}{4 + 36} = -\frac{42}{40} + j\frac{34}{40} = 1.35 \angle 141.01^\circ$

$$i_2(t) = 1.35 \cos(50t + 141^\circ) \quad A$$

\downarrow
 $\text{Re}\{I\} < 0$
 $\text{Im}\{I\} > 0$
 $90^\circ < \theta < 180^\circ$

Problem#4: Problem 8-10 textbook

Given a sinusoid $v_1(t)$ whose phasor is $V_1 = -3 + j4$ V, use phasor methods to find the voltage $v_2(t)$ that leads $v_1(t)$ by 90° and has an amplitude of 10 V.

$$V_1 = -3 + j4 = 5 \angle 126.87^\circ$$

$$M_1 = \sqrt{3^2 + 4^2} = 5$$


$$\left\{ \begin{array}{l} \theta_1 = \tan^{-1}\left(\frac{4}{-3}\right) = -53.13 \\ 90^\circ < \theta_1 < 180^\circ \end{array} \right. \Rightarrow \theta_1 = 126.87^\circ$$

$$V_2 = 10 \angle 126.87^\circ + 90^\circ = 10 \angle 216.87^\circ$$

$$v_2(t) = \text{Re} [V_2 e^{j\omega t}] = 10 \cos(\omega t + 216.87^\circ) = 10 \cos(\omega t - 143.13^\circ) \text{ V}$$

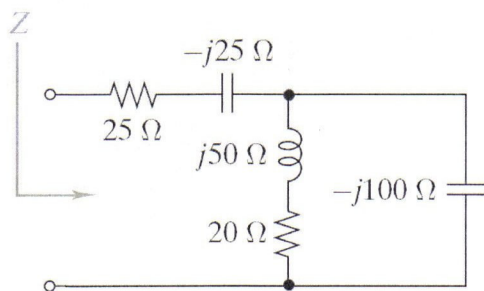Problem#5: Problem 8-12 textbook

Find the equivalent impedance Z in the circuit. Express the result in both polar and rectangular form.



$$Z = 25 - j25 + \frac{(20 + j50)(-j100)}{(20 + j50) + (-j100)}$$

$$= 25 - j25 + \frac{5000 - j2000}{20 - j50}$$

$$= 25 - j25 + (68.966 + j72.414) = 93.966 + j47.414$$



$$|Z| = \sqrt{93.966^2 + 47.414^2} = 105.2506$$

$$\angle Z = \frac{180}{\pi} \tan^{-1}\left(\frac{47.414}{93.966}\right) = 26.775^\circ$$

$$Z = 105.2506 \angle 26.775^\circ$$

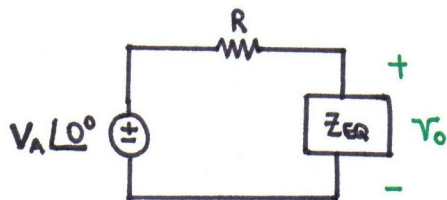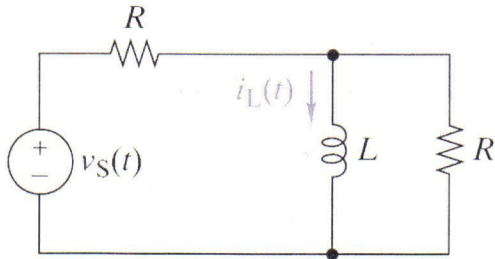Problem#6: Problem 8-22 textbook

The circuit is operating in the sinusoidal steady state with $v_s(t) = V_A \cos(\omega t)$. Derive a general expression for the phasor response I_L .



$$L \Leftrightarrow Z_L = j\omega L$$

$$R \Leftrightarrow Z_R = R$$

$$V_s = V_A \angle 0^\circ$$

$$Z_{EQ} = j\omega L \parallel R = \frac{j\omega RL}{R + j\omega L}$$

$$V_0 = \frac{Z_{EQ}}{R + Z_{EQ}} V_s$$


$$I_L = \frac{V_0}{j\omega L}$$

$$V_0 = \frac{j\omega RL V_s}{R(R + j\omega L) + j\omega RL} = \frac{j\omega L V_A}{R + j2\omega L}$$

$$\boxed{I_L} = \frac{V_A}{R + j2\omega L} = \boxed{\frac{R - j2\omega L}{R^2 + (2\omega L)^2} V_A}$$

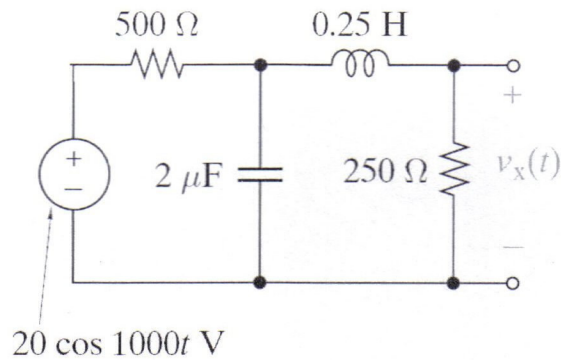Problem#7: Problem 8-26 textbook


The circuit is operating in sinusoidal steady state. Find the steady state response $v_x(t)$.



$$\omega = 1000 \text{ rad/s}$$

$$Z_C = -\frac{j}{\omega C} = -\frac{j}{1000 \cdot 2 \cdot 10^{-6}} = -j 500 \Omega$$
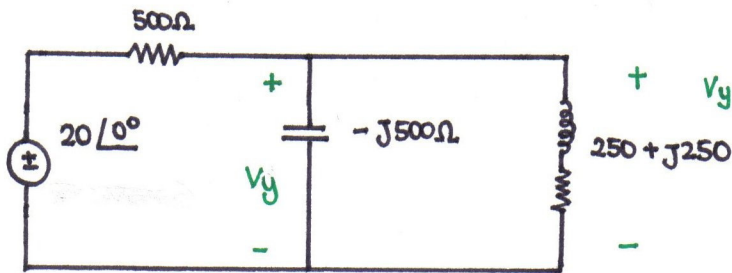
$$Z_L = j\omega L = j \cdot 1000 \cdot 0.25 = j 250 \Omega$$



$$Z_{EQ} = \frac{(-j500)(250 + j250)}{(-j500) + (250 + j250)} = 500 \Omega = \frac{500(250 - j250)}{(250 - j250)}$$

Applying voltage division rule twice:



$$V_y = \frac{Z_{EQ}}{500 + Z_{EQ}} \cdot 20 = 10 \text{ V}$$

$$V_x = \frac{250}{250 + j250} V_y = 5 - j5 \text{ V} = 7.071 \angle -45^\circ \text{ V}$$

$$v_x(t) = 7.071 \cos(1000t - 45^\circ) \text{ V}$$

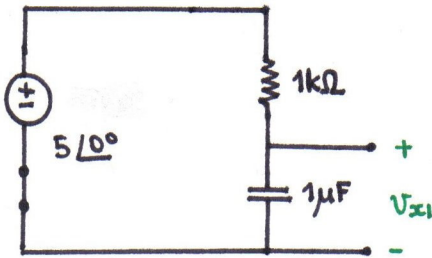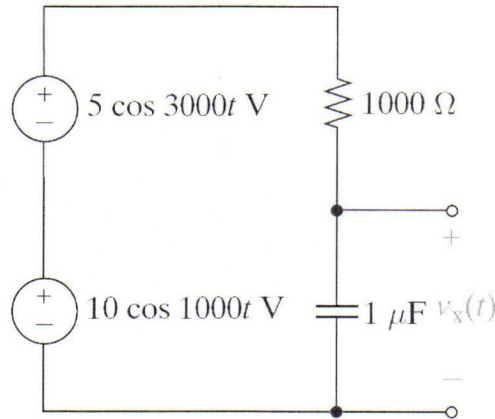Problem#8: Problem 8-30 textbook

The circuit is operating in sinusoidal steady state. Use superposition to find the response $v_x(t)$. *Note:* the sources do not have the same frequency.




$$\omega_1 = 3000 \text{ rad/s}$$

$$Z_{C1} = \frac{-j}{\omega_1 C} = \frac{-j}{3000 \cdot 10^{-6}} = -j \frac{1000}{3}$$

$$V_{x1} = \frac{-j \frac{1000}{3} \cdot 5}{1000 - j \frac{1000}{3}} = 0.5 - j1.5 = 1.581 \angle -71.57^\circ$$
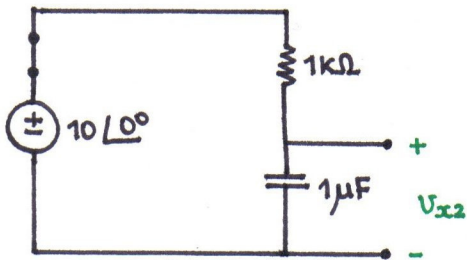
$$v_{x1}(t) = 1.581 \cos(3000t - 71.57^\circ)$$



$$\omega_2 = 1000 \text{ rad/s}$$

$$Z_{C2} = \frac{-j}{\omega_2 C} = -\frac{j}{10^3 \cdot 10^{-6}} = -j 1000$$



$$V_{x2} = \frac{-j 1000 \cdot 10}{1000 - j 1000} = 5 - j5 = 7.071 \angle -45^\circ$$

$$v_{x2}(t) = 7.071 \cos(1000t - 45^\circ)$$

$$v_x(t) = v_{x1}(t) + v_{x2}(t) = 1.581 \cos(3000t - 71.57^\circ) + 7.071 \cos(1000t - 45^\circ)$$

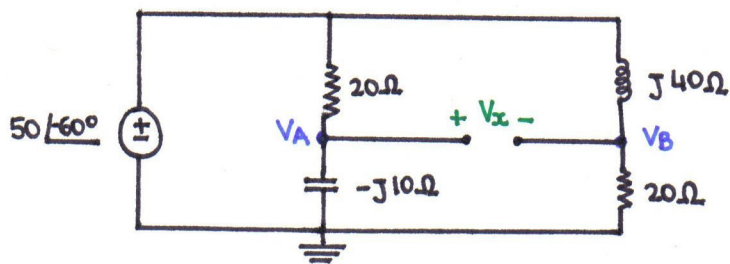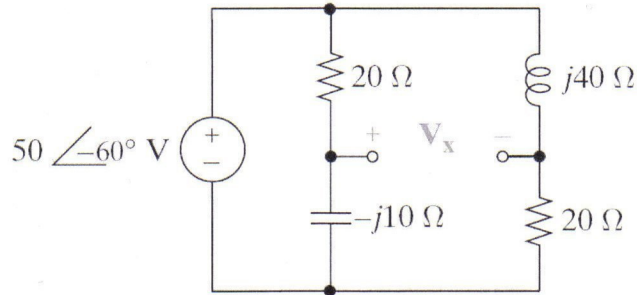Problem#9: Problem 8-32 textbook

The circuit is operating in the sinusoidal steady state. Find the phasor response V_x .




$$\begin{aligned} V_A &= \left(\frac{-j10}{20 - j10} \right) 50 \angle -60^\circ = \left(0.4472 \angle -63.4349^\circ \right) \left(50 \angle -60^\circ \right) \\ &= 22.36 \angle -123.435^\circ = -12.3202 - j18.66 \end{aligned}$$

$$\begin{aligned} V_B &= \left(\frac{20}{20 + j40} \right) 50 \angle -60^\circ \\ &= \left(0.4472 \angle -63.4349^\circ \right) \left(50 \angle -60^\circ \right) \\ &= 22.36 \angle -123.435^\circ = -12.3202 - j18.66 \end{aligned}$$

$$V_x = V_A - V_B = 0$$

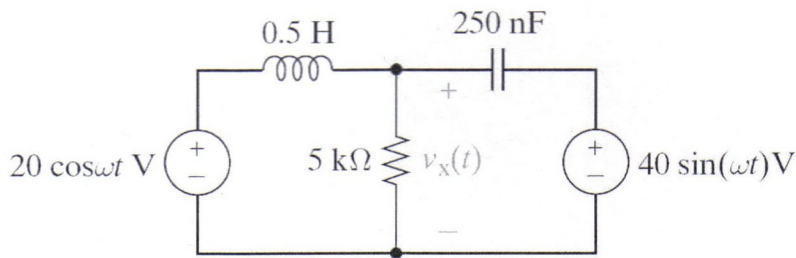
Problem#10: Problem 8-41 textbook

The circuit is operating in the sinusoidal steady state with $\omega=4$ krad/s. Use node-voltage analysis to find the steady-state response $v_x(t)$.



$$z_c = \frac{-j}{\omega C} = \frac{-j}{4000 \cdot 250 \cdot 10^{-9}} = -j 1000 \Omega = 1000 \angle -90^\circ$$
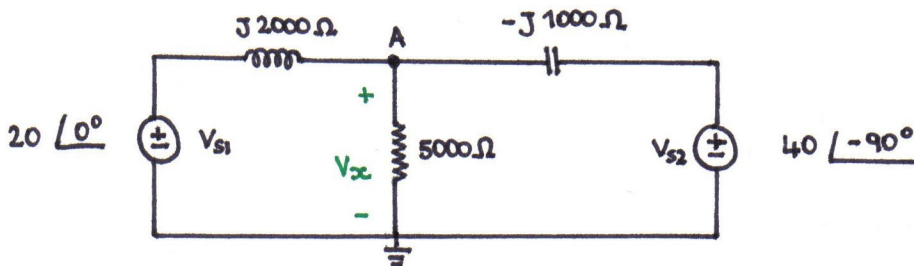
$$z_L = j\omega L = j 4000 \cdot 0.5 = j 2000 \Omega = 2000 \angle 90^\circ$$



$$v_A = v_x$$

$$\frac{v_A - v_{s1}}{z_L} + \frac{v_A - v_{s2}}{z_c} + \frac{v_A}{5K} = 0$$

$$v_A \left(\frac{1}{z_L} + \frac{1}{z_c} + \frac{1}{5K} \right) = \frac{v_{s1}}{z_L} + \frac{v_{s2}}{z_c}$$

$$v_A = \frac{z_L \cdot z_c \cdot 5K}{z_L z_c + z_L 5K + z_c 5K} \cdot \left(\frac{v_{s1}}{z_L} + \frac{v_{s2}}{z_c} \right)$$

$$= \frac{z_c v_{s1} + z_L v_{s2}}{z_L z_c + z_L 5K + z_c 5K} \cdot 5K$$

$$= \frac{20 \angle -90^\circ + 80 \angle 0^\circ}{2 \cdot 10^6 \angle 0^\circ + 5 \cdot 10^6 \angle -90^\circ + 10 \cdot 10^6 \angle 90^\circ} \cdot 5000$$

$$= 5 \frac{20 \angle -90^\circ + 80 \angle 0^\circ}{2 \angle 0^\circ + 5 \angle -90^\circ + 10 \angle 90^\circ} = 5 \frac{80 - j20}{2 - j5 + j10}$$

$$= 5 \frac{80 - j20}{2 + j5} = 10.3448 - j75.8621 = 76.564 \angle -82.235^\circ$$

$$v_x(t) = v_A(t) = 76.564 \cos(4000t - 82.235^\circ)$$