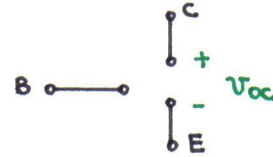



BIPOLAR JUNCTION TRANSISTOR - BJT

(1) Compute


(a) the OPEN-CIRCUIT VOLTAGE V_{oc}



(b) the SHORT-CIRCUIT CURRENT i_{sc}

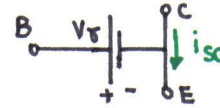

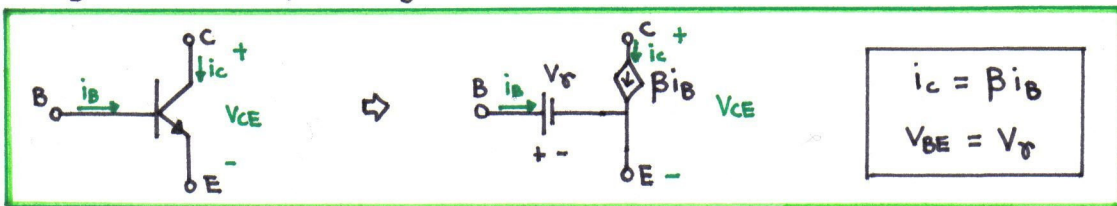(2) You start ASSUMING that the BJT is operating in ACTIVE MODE so you use the following model to solve the circuit




Solve the circuit and determine V_{CE} and i_C

(3)


(a) IF $0 < V_{CE} < V_{oc}$ and $0 < i_C < i_{sc}$ then the BJT is indeed operating in ACTIVE MODE and thus the analysis carried in step (2) is correct (= you are done)

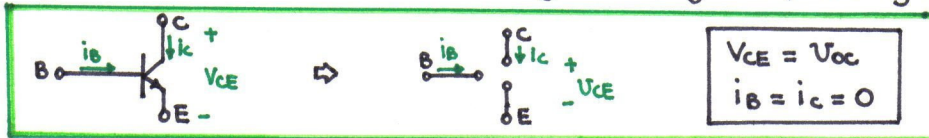(b) IF $V_{CE} > V_{oc}$ or $i_C < 0$ then the BJT is operating in CUTOFF MODE which means that the analysis carried in step (2) is NOT CORRECT so you have to solve the circuit again using the following model




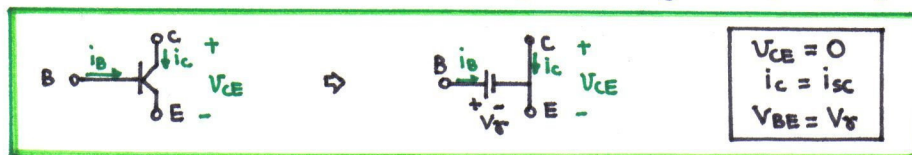(c) IF $V_{CE} < 0$ or $i_C > i_{sc}$ then the BJT is operating in SATURATION MODE

which means that the analysis carried in step (2) is NOT CORRECT so you have to solve the circuit again using the following model




EXAMPLE

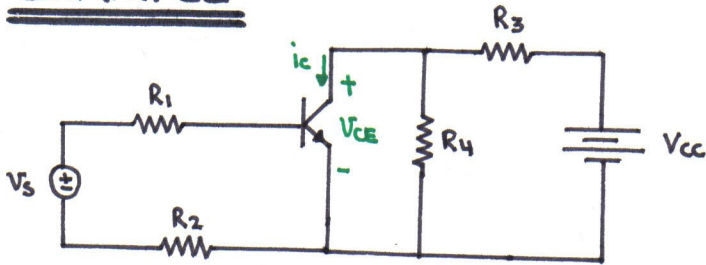


$$\begin{aligned} V_{CC} &= 20\text{ V} \\ R_1 &= R_2 = 25\text{ k}\Omega \\ R_3 &= R_4 = 2\text{ k}\Omega \\ \beta &= 100 \\ V_{\gamma} &= 0.7\text{ V} \end{aligned}$$

Find i_c and V_{CE} for (a) $V_s = 3\text{ V}$
(b) $V_s = 8\text{ V}$

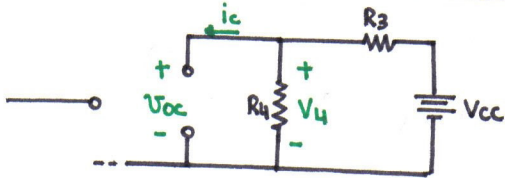(1) Compute the OPEN-CIRCUIT VOLTAGE and SHORT-CIRCUIT CURRENT



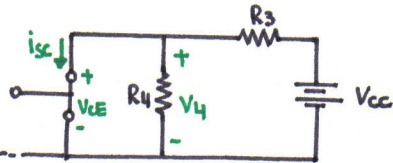
$$i_c = 0 \Rightarrow V_{OC} = V_4 = \frac{R_4}{R_3 + R_4} V_{CC} = 10\text{ V}$$



$$V_{CE} = 0 \Rightarrow V_4 = 0 \Rightarrow i_{sc} = \frac{V_{CC}}{R_3} = 10\text{ mA}$$

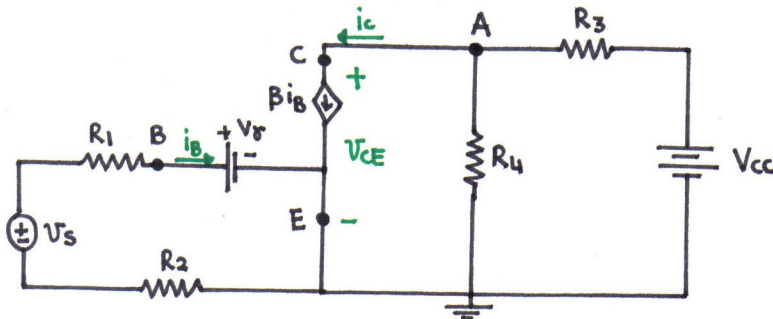(2) ASSUME that the BJT is operating in ACTIVE MODE and solve the circuit



$$i_c = \beta i_B$$

$$V_{BE} = V_{\gamma}$$

KVL @ LOOP 1

$$R_1 i_B + V_{\gamma} + R_2 i_B = V_s \Rightarrow i_B = \frac{V_s - V_{\gamma}}{R_1 + R_2} = \frac{V_s - 0.7}{50\text{ k}}$$

$$i_c = \beta i_B = \beta \frac{V_s - V_{\gamma}}{R_1 + R_2} = 100 \frac{V_s - 0.7}{50\text{ k}} \quad (*)$$

KCL @ NODE A


$$\frac{V_A - V_{CC}}{R_3} + \frac{V_A}{R_4} + i_c = 0$$

$$(R_3 + R_4) V_A = R_4 V_{CC} - i_c (R_3 R_4)$$

since $V_{CE} = V_A$

$$V_{CE} = \frac{R_4}{R_3 + R_4} V_{CC} - \frac{R_3 R_4}{R_3 + R_4} i_c \quad (**)$$

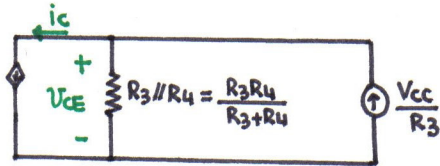NOTE: you can obtain (***) applying a source transformation instead of the KCL @ node A



$$V_{CE} = \frac{R_3 R_4}{R_3 + R_4} \left(\frac{V_{CC}}{R_3} - i_c \right)$$

$$V_{CE} = \left(\frac{2k}{4k} \right) V_{CC} - \left(\frac{4 \cdot 10^6}{4 \cdot 10^3} \right) \left(100 \frac{V_S - 0.7}{50k} \right) = \frac{V_{CC}}{2} - 2(V_S - 0.7)$$

$$i_c = 2(V_S - 0.7) \cdot 10^{-3}$$

$$V_{CE} = 10 - 2(V_S - 0.7)$$

(3)

(a) $V_S = 3V$

$$i_c = 2 \cdot (3 - 0.7) \cdot 10^{-3} = 4.6 \text{ mA} < 10 \text{ mA} = i_{sc}$$

$$V_{CE} = 10 - 2(3 - 0.7) = 5.4 \text{ V} < 10 \text{ V} = V_{oc}$$

since $\begin{cases} i_c < i_{sc} \\ V_{CE} < V_{oc} \end{cases} \Rightarrow$ the BJT is indeed operating in active mode, thus

$$i_c = 4.6 \text{ mA}$$

$$V_{CE} = 5.4 \text{ V}$$

(b) $V_S = 8V$

$$i_c = 2 \cdot (8 - 0.7) \cdot 10^{-3} = 14.6 \text{ mA} > 10 \text{ mA} = i_{sc}$$

since $i_c > i_{sc}$ then the BJT is not operating in active mode

but in SATURATION MODE, thus

$$i_c = i_{sc} = 10 \text{ mA}$$

$$V_{CE} = 0 \text{ V}$$

NOTE: if you have to compute only i_c and V_{CE} you are done.

if you are required to find other quantities (for instance the potential difference across R_3) then you have to solve the circuit again using the BJT model for saturation mode