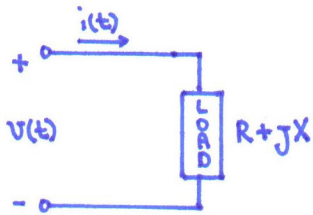


COMPLEX POWER

LISA FIORENTINI
ECE 205 - SP09



$$v(t) = V_A \cos(\omega t + \phi_V)$$

$$V_{rms} = V_A / \sqrt{2}$$

$$i(t) = I_A \cos(\omega t + \phi_I)$$

$$I_{rms} = I_A / \sqrt{2}$$

$$\mathbf{V} = V_{rms} \angle \phi_V$$

$$\mathbf{I} = I_{rms} \angle \phi_I$$

$$\theta = \phi_V - \phi_I$$

POWER FACTOR ANGLE

$$\boxed{P} = \frac{V_A I_A}{2} \cos \theta = \boxed{V_{rms} I_{rms} \cos \theta} \text{ [W]}$$

AVERAGE POWER

$$\boxed{Q} = \frac{V_A I_A}{2} \sin \theta = \boxed{V_{rms} I_{rms} \sin \theta} \text{ [VARs]}$$

REACTIVE POWER

$$p(t) = v(t) \cdot i(t) = \underbrace{P(1 + \cos 2\omega t)}_{\text{NET ENERGY} \neq 0} - \underbrace{Q \sin(2\omega t)}_{\text{TRANSFERS NO ENERGY}}$$

INSTANTANEOUS POWER

$$\begin{aligned} W > 0 \text{ if } P > 0 &\Rightarrow -90^\circ < \theta < 90^\circ && \text{ENERGY FLOW SOURCE} \rightarrow \text{LOAD} \\ W < 0 \text{ if } P < 0 &\Rightarrow 90^\circ < \theta < 270^\circ && \text{ENERGY FLOW LOAD} \rightarrow \text{SOURCE} \end{aligned}$$

$$\begin{aligned} \boxed{S} &= \mathbf{V} \mathbf{I}^* = \boxed{P + jQ} \\ &= \mathbf{Z} |\mathbf{I}|^2 = (R + jX) I_{rms}^2 \end{aligned}$$

COMPLEX POWER


$$R = \frac{P}{I_{rms}^2} \quad X = \frac{Q}{I_{rms}^2}$$

$$|S| = V_{rms} I_{rms} \text{ [VA]} \quad \text{APPARENT POWER}$$

$$\text{pf} = \cos \theta \quad \text{POWER FACTOR}$$


$$\underline{\theta > 0} \Rightarrow \phi_V > \phi_I \quad \text{VOLTAGE LEADS} \Rightarrow \text{lagging power factor}$$
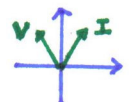
$$\underline{Q > 0}, \quad X > 0 \quad \underline{\text{INDUCTIVE LOAD}}$$




$$\underline{\theta < 0} \Rightarrow \phi_I > \phi_V \quad \text{CURRENT LEADS} \Rightarrow \text{leading power factor}$$

$$\underline{Q < 0}, \quad X < 0 \quad \underline{\text{CAPACITIVE LOAD}}$$

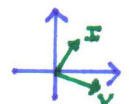

EXAMPLE 1

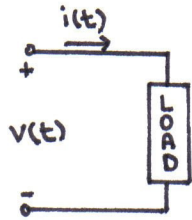


Given $i(t)$ and $v(t)$ calculate the average power and the reactive power. Is the load absorbing or delivering

net energy?
net energy?

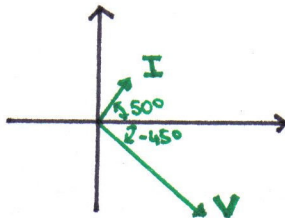(a) $v(t) = 1500 \cos(\omega t - 45^\circ) \text{ V}$
 $i(t) = 2 \cos(\omega t + 50^\circ) \text{ A}$

$$V_A = 1500 \quad \phi_v = -45^\circ \quad V_{\text{rms}} = 1500 / \sqrt{2}$$

$$I_A = 2 \quad \phi_i = 50^\circ \quad I_{\text{rms}} = 2 / \sqrt{2}$$



CURRENT LEADS \rightarrow CAPACITIVE LOAD $\rightarrow Q < 0$

$$\theta = \phi_v - \phi_i = -45^\circ - 50^\circ = -95^\circ$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos \theta = \frac{1500}{\sqrt{2}} \cdot \frac{2}{\sqrt{2}} \cos(-95^\circ) = 1500(-0.087) = \boxed{-130.7 \text{ W}}$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \theta = \frac{1500}{\sqrt{2}} \cdot \frac{2}{\sqrt{2}} \sin(-95^\circ) = 1500(-0.996) = \boxed{-1494.3 \text{ VARs}}$$

Since $P < 0 \Rightarrow W < 0 \Rightarrow$ the load is delivering power

(b) $v(t) = 90 \cos(\omega t + 60^\circ)$
 $i(t) = 10.5 \cos(\omega t - 20^\circ)$


$$\theta = \phi_v - \phi_i = 60^\circ + 20^\circ = 80^\circ$$

$$P = \frac{90}{\sqrt{2}} \cdot \frac{10.5}{\sqrt{2}} \cos 80^\circ = 82.05 \text{ W}$$

$$Q = \frac{90}{\sqrt{2}} \cdot \frac{10.5}{\sqrt{2}} \sin 80^\circ = 465.322 \text{ VARs}$$

Since $P > 0 \Rightarrow W > 0 \Rightarrow$ the load is absorbing power

EXAMPLE 2

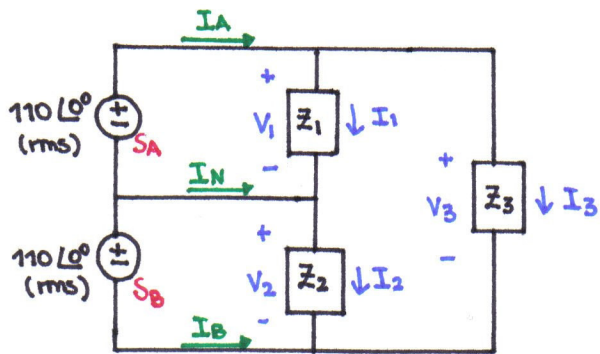

The three loads draw complex powers

$$S_1 = 1250 + j500 \quad \text{VA}$$

$$S_2 = 800 + j0 \quad \text{VA}$$

$$S_3 = 2000 + j400 \quad \text{VA}$$

(a) Find I_A , I_N and I_B

(b) Find the complex power produced by each source

(a) $V_1 = 110 \angle 0^\circ = 110$

$$S_1 = V_1 I_1^* = 1250 + j500$$

$$\Rightarrow I_1^* = \frac{S_1}{V_1} = 11.364 + j4.545$$

$$\boxed{I_1 = 11.364 - j4.545} \quad \text{A}$$

$$V_2 = 110 \angle 0^\circ = 110$$

$$S_2 = V_2 I_2^* = 800 + j0$$

$$\Rightarrow I_2^* = \frac{S_2}{V_2} = 7.273 + j0$$

$$\boxed{I_2 = 7.273} \quad \text{A}$$

$$V_3 = V_1 + V_2 = 220$$

$$S_3 = V_3 I_3^* = 2000 + j400$$

$$\Rightarrow I_3^* = \frac{S_3}{V_3} = 9.09 + j1.818$$

$$\boxed{I_3 = 9.09 - j1.818} \quad \text{A}$$

$$\boxed{I_A = I_1 + I_3 = 20.455 - j6.363} \quad \text{A}$$


$$\boxed{I_B = -(I_2 + I_3) = -16.363 + j1.818} \quad \text{A}$$

$$\boxed{I_N = I_2 - I_1 = -4.092 + j4.545} \quad \text{A}$$

(b) $\boxed{S_A} = -(110) I_A^* = -110 (20.455 + j6.363) = \boxed{-2250 - j699.9} \quad \text{VA}$

$\boxed{S_B} = (110) I_B^* = 110 (-16.363 - j1.818) = \boxed{-1800 - j200} \quad \text{VA}$

EXAMPLE 3

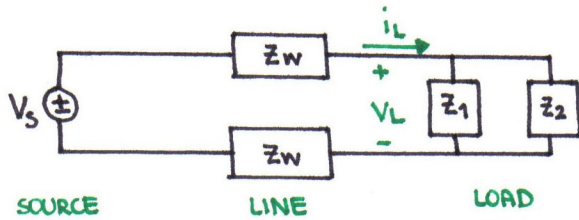

The two loads absorb complex power

- $S_1 = 12 + j6$ kVA

- $|S_2| = 15$ kVA at 0.75 lagging power factor

Then $|V_L| = 4.4$ kV (rms)

$Z_w = 3 + j8 \Omega$

(a) Find the line current and source voltage

Choose $\phi_v = 0$ for the sake of simplicity $\Rightarrow V_L = 4400 \angle 0^\circ$

$$\begin{cases} \text{pf} = \cos \theta = 0.75 \\ \text{pf lagging} \Rightarrow \theta > 0 \end{cases} \quad \begin{cases} \theta = \cos^{-1}(0.75) \\ \theta > 0 \end{cases} \quad \Rightarrow \boxed{\theta = 41.4^\circ}$$

$\phi_{I_2} = \phi_v - \theta = -41.4^\circ$

$S_2 = |S_2| (\cos \theta + j \sin \theta) = 15000 (0.75 + j 0.661) = 11250 + j 9920$

$S_1 = 12000 + j 6000$

$S_{\text{LOAD}} = S_1 + S_2 = 23250 + j 15920 = \boxed{V_L I_L^*}$

$I_L^* = \frac{23250 + j 15920}{4400} = 5.284 + j 3.618$

$I_L = 5.284 - j 3.618 = \boxed{6.404 \angle -34.4^\circ}$

$V_s = 2 Z_w \cdot I_L + V_L = 2(3 + j8)(6.404 \angle -34.4^\circ) + 4400$

$= (10 \angle 53.2^\circ)(6.404 \angle -34.4^\circ) + 4400$

$= 4489.6 + j 62.836 = \boxed{4490.03 \angle 0.8^\circ}$

(b) Find the complex power produced by the source

$S_s = -V_s I_L^* = + (4490.03 \angle 0.8^\circ)(6.404 \angle 34.4^\circ)$

$= \boxed{23495.7 + j 16575.4}$ VA