

EXAMPLE

For $t > 0$ the current through a 2mH inductor is $i_L(t) = 100t e^{-1000t}$ A.

(a) Derive an expression for $v_L(t)$

(b) Is the inductor absorbing power, delivering power or both?

(a) $L = 2\text{mH}$


$$i_L(t) = 100t e^{-1000t} \quad t \geq 0$$

$$v_L(t) = L \frac{di_L(t)}{dt} = (2 \cdot 10^{-3}) \cdot [100 - 1000(100t)] e^{-1000t}$$

$$v_L(t) = (0.2 - 200t) e^{-1000t} \text{ V}$$

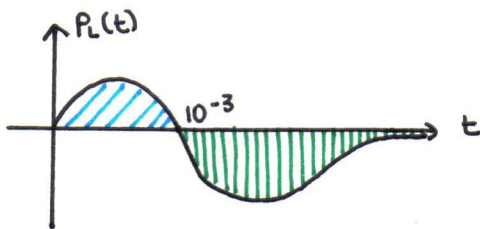(b) $P_L(t) = i_L(t) \cdot v_L(t) = (100t) \cdot e^{-1000t} \cdot (0.2 - 200t) e^{-1000t}$

$$P_L(t) = (20t - 20000t^2) e^{-2000t} \text{ W} \quad t \geq 0$$




/// ABSORBING

||| DELIVERING

The inductor is first absorbing and then delivering power

EXAMPLE

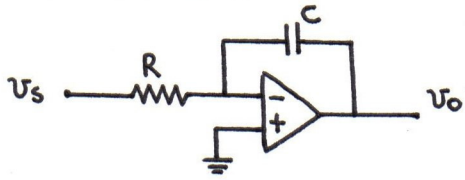

$$R = 20 \text{ k}\Omega$$

$$C = 100 \text{ nF}$$

$$V_o(0) = 0 \text{ V}$$

$$V_s(t) = [5 \sin \omega t] \mu(t)$$

Find $v_o(t)$ for $t > 0$

$$V_p = V_n = 0$$


$$\frac{V_s}{R} + C \frac{dV_o}{dt} = 0$$

$$\int_0^t \frac{dV_o}{dt} = -\frac{1}{RC} V_s(t) = -\frac{1}{20 \cdot 10^3 \cdot 100 \cdot 10^{-9}} = \int_0^t -500 V_s(t)$$

$$V_o(t) + \cancel{V_o(0)}_{=0} = \int_0^t -500 (5 \sin \omega t) dt = 2500 \left[\frac{\cos \omega t}{\omega} \right]_0^t$$


$$V_o(t) = \frac{2500}{\omega} [\cos(\omega t) - 1]$$

EXAMPLE

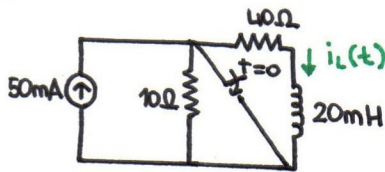

The switch has been open for a long time and is closed at $t=0$
Find $i_L(t)$ for $t \geq 0$.

$t < 0$

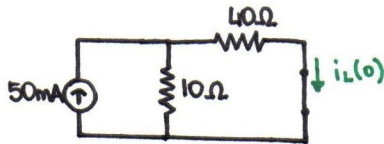


CURRENT DIVISION

$$i_L(0) = \frac{10}{10+40} \cdot 50 \text{ mA} = 10 \text{ mA}$$

$$\underline{i_L(0) = 10 \text{ mA}}$$

$t \geq 0$

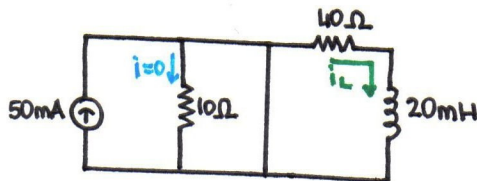

$$\text{KVL} \quad 40 \cdot i_L + 20 \cdot 10^{-3} \frac{di_L}{dt} = 0$$

$$\frac{di_L}{dt} + 2000i_L = 0$$

$$i_L(t) = A e^{-2000t}$$

$$i_L(0) = 10 = A$$

$$\underline{i_L(t) = 10 \cdot e^{-2000t} \text{ mA} \quad t \geq 0}$$