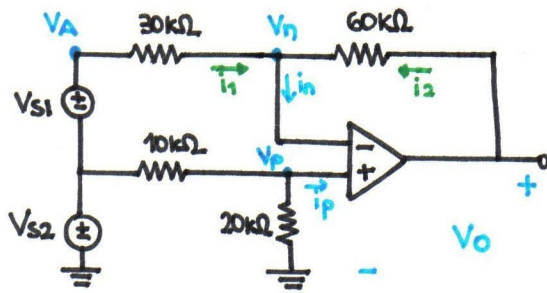


EXAMPLE 1



$$\begin{aligned} V_n &= V_p \\ i_n &= i_p = 0 \end{aligned}$$

Find v_o in terms of the inputs v_{s1} and v_{s2} .

$$i_p = 0 \Rightarrow V_p = \frac{2}{3} V_{s2} \quad (\text{VOLTAGE DIVISION RULE})$$

$$V_n = V_p = \frac{2}{3} V_{s2}$$

$$V_A = V_{s1} + V_{s2}$$

$$i_1 + i_2 = i_n = 0 \Rightarrow \frac{V_A - V_n}{30k} + \frac{V_o - V_n}{60k} = 0$$


$$\begin{aligned} V_A &= V_{s1} + V_{s2} \\ V_n &= \frac{2}{3} V_{s2} \end{aligned}$$

$$2 \left(V_{s1} + V_{s2} - \frac{2}{3} V_{s2} \right) + \left(V_o - \frac{2}{3} V_{s2} \right) = 0$$

$$2 V_{s1} + 2 \left(\frac{1}{3} V_{s2} \right) + V_o - \frac{2}{3} V_{s2} = 0$$

$$\boxed{V_o = -2V_{s1} + 0V_{s2}}$$

EXAMPLE 2

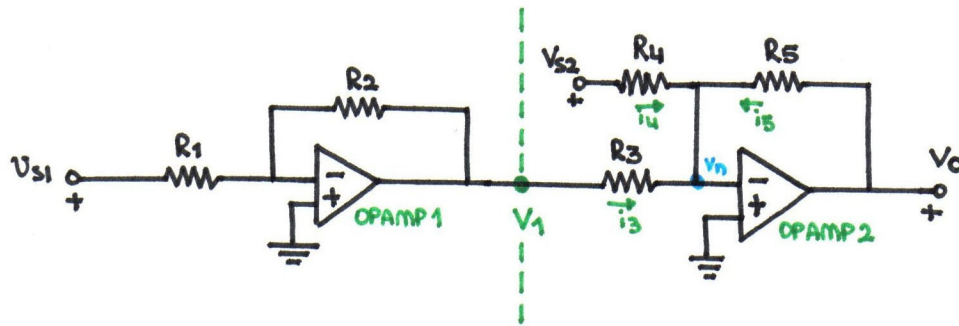

Find v_o in terms of the inputs v_{s1} and v_{s2}

OPAMP 1

$$V_p = V_n = 0$$

$$\frac{V_{s1}}{R_1} + \frac{V_1}{R_2} = 0$$

$$V_1 = -\frac{R_2}{R_1} V_{s1}$$

OPAMP 2

$$V_p = V_n = 0$$

$$i_n = 0 \Rightarrow i_3 + i_4 + i_5 = 0$$

$$\frac{V_1 - V_n}{R_3} + \frac{V_{s2} - V_n}{R_4} + \frac{V_o - V_n}{R_5} = 0$$

$$V_o = -\frac{R_5}{R_3} V_1 - \frac{R_5}{R_4} V_{s2}$$

$$= -\frac{R_5}{R_3} \left(-\frac{R_2}{R_1} V_{s1} \right) - \frac{R_5}{R_4} V_{s2}$$

$$V_o = \frac{R_2 R_5}{R_1 R_3} V_{s1} - \frac{R_5}{R_4} V_{s2}$$