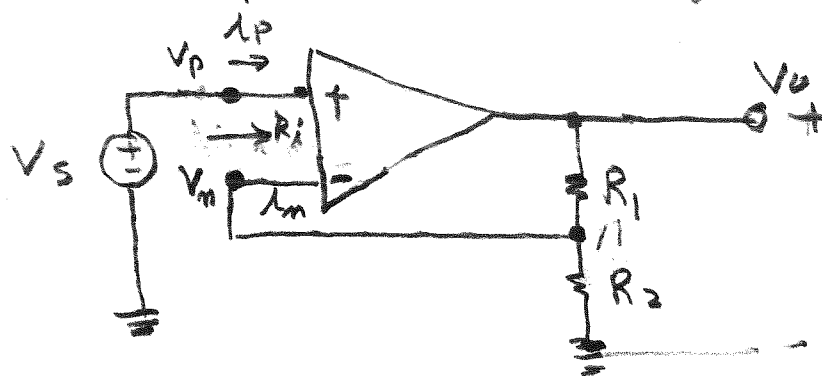


OPAMPS - Problems

①

A. Kuyhand


Problem: Consider the noninverting op AMP with $R_1 = 3 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$ given below:



Find V_o if $V_s = 10 \text{ V}$

$R_i \rightarrow \infty$ (open ckt) $\Rightarrow i_p = 0, i_m = 0$

Eq. ckt.

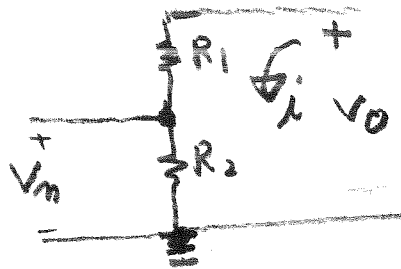

$$V_o = i (R_1 + R_2)$$

$$i = \frac{V_o}{R_1 + R_2}$$

$$V_m = i R_2 = \frac{R_2}{R_1 + R_2} V_o$$

since $R_i \rightarrow \infty \Rightarrow$ open ckt $V_p = V_s$
 (noninverting condition) and since we have
 an ideal OP AMP, we have $V_p = V_m$

$$\therefore V_s = \frac{R_2}{R_1 + R_2} V_o \Rightarrow$$


$$V_o = \frac{R_1 + R_2}{R_2} V_s \quad V_o = 2.5$$

FOR $R_1 = 3 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$ $V_s = 10$

$$\therefore V_o = \left(\frac{3 + 2}{2} \right) V_s = 2.5 V_s$$

$$V_o = 25 \text{ VOLTS}$$

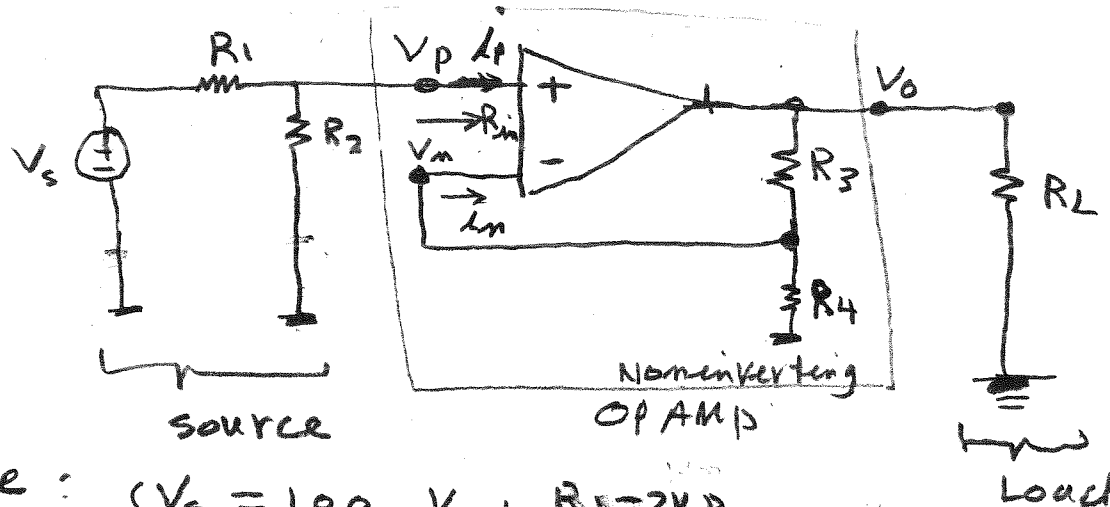Problem. Consider the noninverting OP AMP given below.




ASSUME : source $\left\{ \begin{array}{l} V_s = 100 \text{ V} \\ R_1 = 2 \text{ K}\Omega \\ R_2 = 3 \text{ K}\Omega \end{array} \right.$

OPAMP $\left\{ \begin{array}{l} R_3 = 4 \text{ K}\Omega \\ R_4 = 2 \text{ K}\Omega \end{array} \right.$

Find V_o if $R_L = 1 \text{ K}\Omega$

Solution.

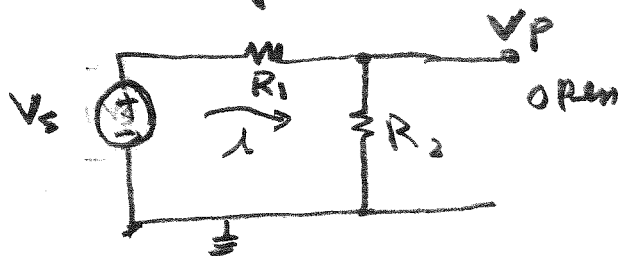$R_i \Rightarrow \infty$ $i_p = 0$, $i_m = 0$ open ckt
source eq. ckt



$$V_s = i(R_1 + R_2) \quad i = \frac{V_s}{R_1 + R_2}$$

$$V_p = R_2 i = \left(\frac{R_2}{R_1 + R_2} \right) V_s \quad \boxed{V_p = K_s V_s}$$

$$K_s = \frac{3}{5} = \frac{6}{10} = 0.6$$

$$V_p = 0.6 (100)$$


$$V_p = 60 \text{ VOLT}$$

Attenuation.

3


since the noninverting OP AMP has Zero output resistance $R_o \Rightarrow$ very small $R_o \Rightarrow 0$

The OP AMP equivalent ckt is

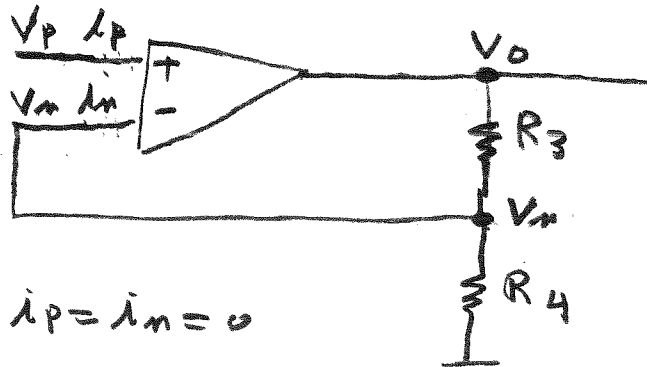

Recall $i_p = i_m = 0$

$$V_p = V_m$$

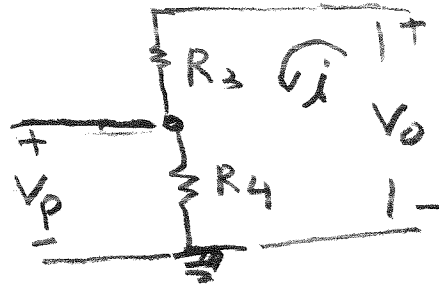

$$V_o = i (R_3 + R_4)$$

$$i = \frac{V_o}{R_3 + R_4}$$

$$V_p = i R_4 \Rightarrow V_p = \left(\frac{R_4}{R_3 + R_4} \right) V_o$$

OR.

$$V_o = \left(\frac{R_3 + R_4}{R_4} \right) V_p$$

$$V_o = K_{AMP} V_p$$

for $R_3 = 4$, $R_4 = 2$

$$K_{AMP} = \frac{R_3 + R_4}{R_4} = \frac{4 + 2}{2} = \frac{6}{2} = 3$$

$$V_o = 3(60) = 180 \text{ V}$$


The overall ckt gain is:

$$K_{ckt} = \frac{V_o}{V_s} = K_s \times K_{AMP} = 0.6(3) = 1.8$$

$$V_o = K_{ckt} V_s \quad V_o = 1.8 \times 100 = 180 \text{ V}$$

4

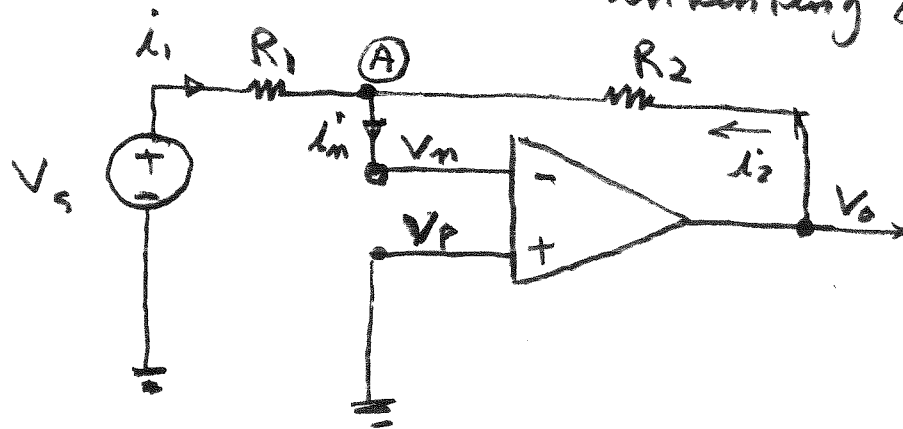Problem 3. Given the interconnection of OP AMP below:



Assume $R_1 = 10 \text{ k}\Omega$ $R_2 = 20 \text{ k}\Omega$
and $V_s = 120 \text{ V}$ find V_o .

Solution.

In this OP-AMP V_p is grounded, therefore

$$V_p = 0$$

Node (A) is at V_m $V_A = V_m$. Write $\sum I_i = 0$ for node (A). We will have:

$$\frac{V_s - V_m}{R_1} + \frac{V_o - V_m}{R_2} - i_m = 0 \quad *$$

RECALL OPAMP constraints:

$$V_p = V_m \text{ and } i_p = i_m = 0$$

However, $V_p = 0 \Rightarrow V_m = 0$ substituting the above in *, we will have:

$$\frac{V_s}{R_1} + \frac{V_o}{R_2} = 0$$

5

Solution Problem 3 cont.

$$\frac{V_s}{R_1} = -\frac{V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_s \quad \text{where } K_v = \frac{R_2}{R_1} \text{ is}$$

the closed-loop gain. since the voltage gain is negative, it indicates a signal inversion.


$$\text{For } R_1 = 10 \text{ k}\Omega \quad R_2 = 20 \text{ k}\Omega, \quad V_s = 120$$

we will have,

$$V_o = -\left(\frac{20}{10}\right)(120) = -60$$

(6)

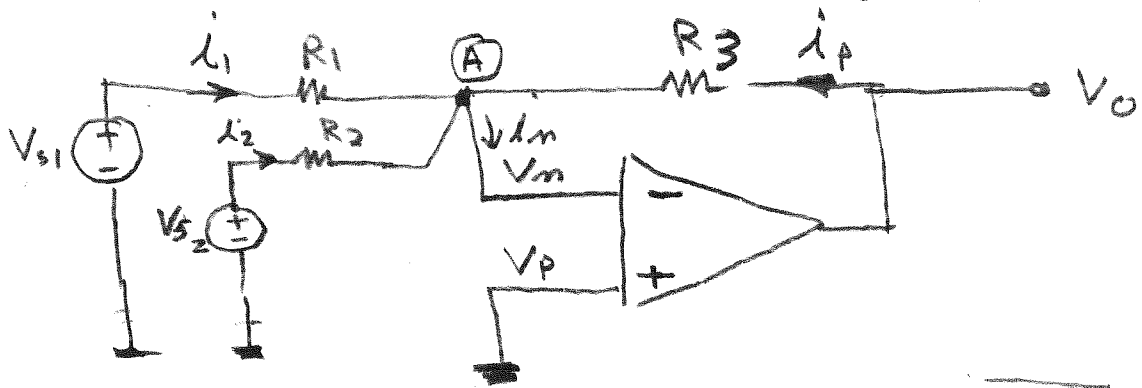Problem 4. Given the summing OP AMPS below



Given $V_{s1} = 100 \text{ V}$, $V_{s2} = 120 \text{ V}$, $R_1 = 10 \text{ k}\Omega$
 $R_2 = 20 \text{ k}\Omega$ and $R_3 = 100 \text{ k}\Omega$
Find V_o

Solution. Write $\sum i_i = 0$ for node (A).

$$(*) \quad \frac{V_{s1} - V_A}{R_1} + \frac{V_{s2} - V_A}{R_2} + \frac{V_o - V_A}{R_3} - i_m = 0$$

Node (A) is connected to V_m . $\Rightarrow V_A = V_m$

Also, the noninverting input is grounded.

$$\Rightarrow V_p = 0 \quad \text{op AMP constraints are}$$

$$V_p = V_m = 0 \quad \text{and} \quad i_m = 0$$


We can rewrite * as

$$\frac{V_{s1}}{R_1} + \frac{V_{s2}}{R_2} + \frac{V_o}{R_3} = 0$$

$$\Rightarrow V_o = \underbrace{\left(-\frac{R_3}{R_1}\right)}_{K_1} V_{s1} + \underbrace{\left(-\frac{R_3}{R_2}\right)}_{K_2} V_{s2}$$

(7)
Solution Problem 4. cont.

$$V_o = K_1 v_{s1} + K_2 v_{s2}$$

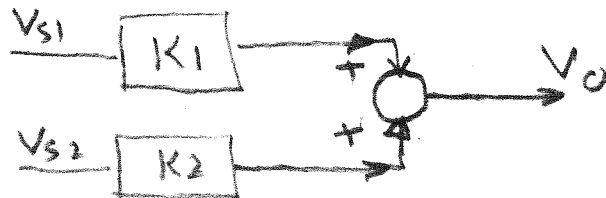


$$K_1 = \frac{100}{10} = 10 \quad K_2 = \frac{100}{20} = 5$$

$$v_o = -10(100) - 5(120)$$

$$= -1000 - 600 = -1600 \text{ V}$$

(8)

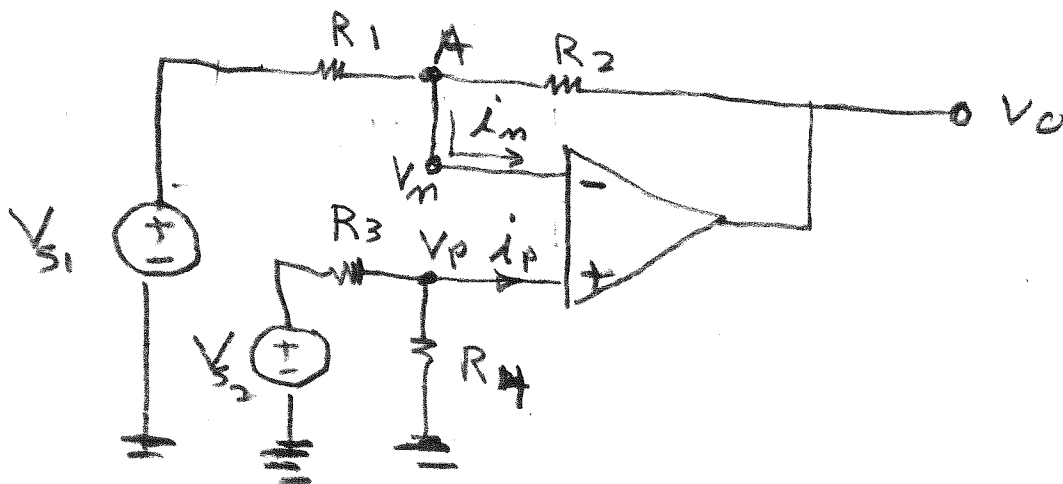Problem 5. Consider the differential OP AMP given below:



Assume $R_1 = 10 \text{ k}\Omega$ $R_2 = 20 \text{ k}\Omega$,
 $R_3 = 30 \text{ k}\Omega$ $R_4 = 40 \text{ k}\Omega$,
 $V_{s1} = 10 \text{ V}$ $V_{s2} = 20 \text{ V}$

Find V_o .


Solution. The op-amp above is called a differential or subtractor. This op-amp has two inputs, one applied at the inverting input and one at the noninverting input.

Use superposition. Apply V_{s1} while V_{s2} is off. This means there is no excitation at noninverting input. $\Rightarrow V_p = 0$

(9)


Problem 5 solution continued.

For this case the ckt is

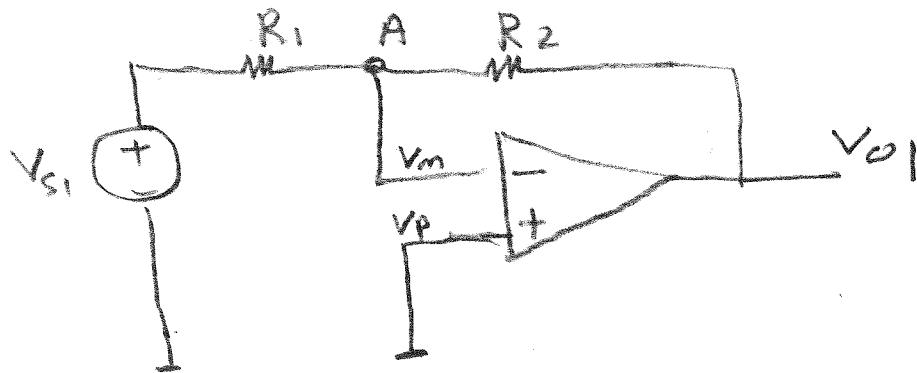

$$V_{o1} = - \frac{R_2}{R_1} V_{s1}$$

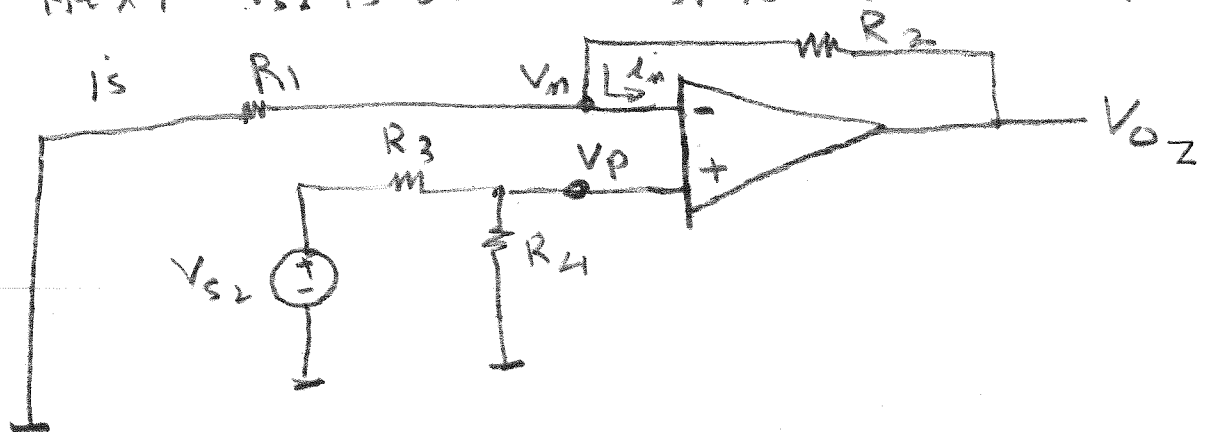Next V_{s2} is on and V_{s1} is off. The eq. ckt



For this eq. ckt, we have:

$$V_{o2} = \left(\frac{R_4}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} \right) V_2$$

Add up V_{o1} and V_{o2} using superposition principle

$$V_o = V_{o1} + V_{o2}$$

10

Problem 5 solution cont.

$$v_o = - \underbrace{\frac{R_2}{R_1}}_{K_1} v_{s1} + \underbrace{\left(\frac{R_4}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} \right)}_{K_2} v_{s2}$$

$$v_o = -K_1 v_{s1} + K_2 v_{s2}$$


$$K_1 = \frac{20}{10} = 2 \quad K_2 = \frac{40}{30+40} + \frac{10+20}{10}$$

$$K_2 = \frac{4}{7} + 3 = 3.57$$

$$v_o = -2(10) + 3.57(20)$$

$$= -20 + 71.4 = 51.4 \text{ V}$$


Problem 6. Consider the OPAMP below:

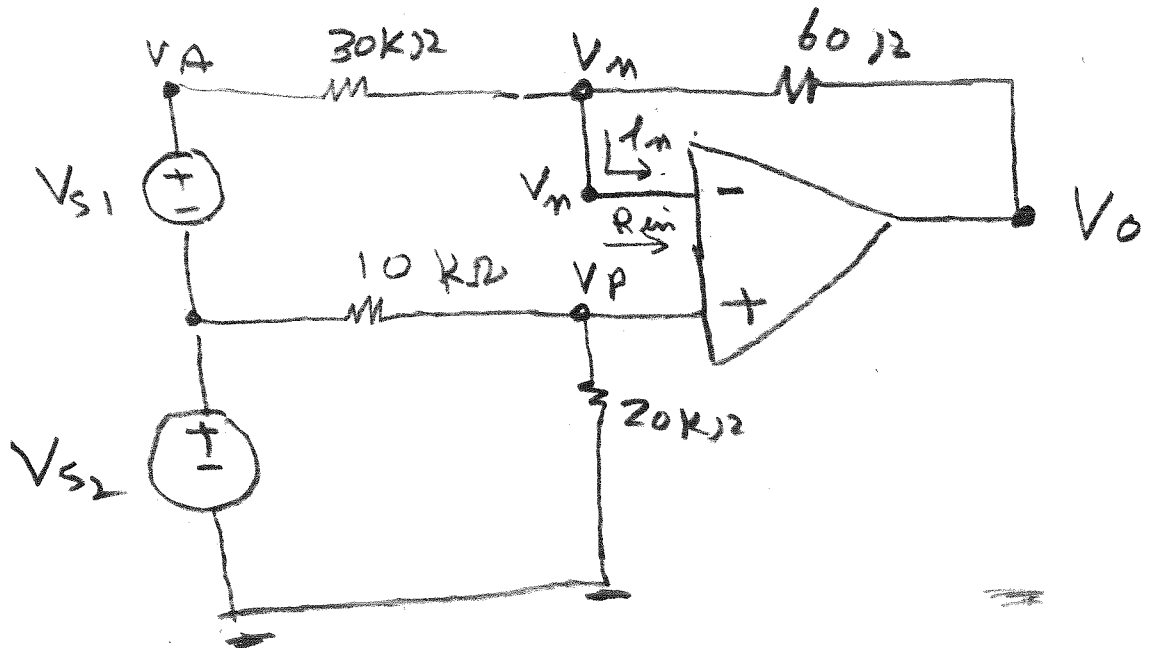

Find V_o in terms of V_{s1} and V_{s2} .

Solution. $R_{in} \rightarrow \infty$ $V_p = V_n$ $i_p = i_n = 0$

Eq. ckt is

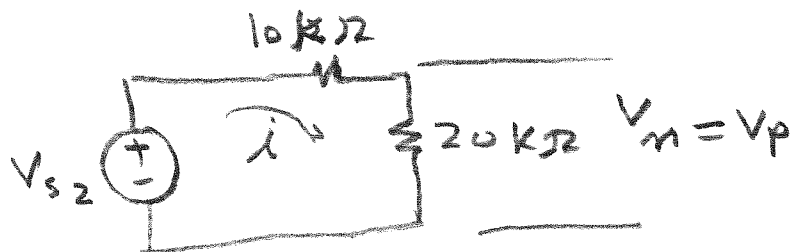


$$V_s = i(10 + 20) = 30i \quad i = \frac{V_s}{30}$$

$$V_p = V_n = i(20k\Omega) = \frac{20}{30} V_{s2} = \frac{2}{3} V_{s2}$$

12

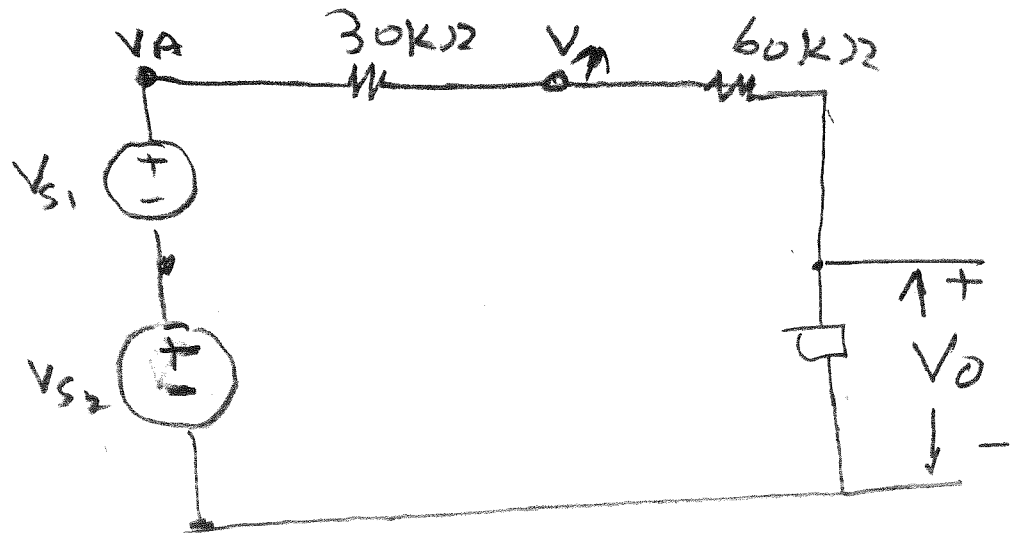problem 6. solution cont.

NOW, we know V_m . To calculate V_o , we have:



$$V_A = V_{s1} + V_{s2}$$

$$\sum i_i = 0 \text{ at node } m$$

$$\frac{V_m - V_A}{30k\Omega} + \frac{V_m - V_o}{60k\Omega} = 0$$

$$\text{or } 2(V_m - V_A) + (V_m - V_o) = 0$$

$$2 \left[\frac{2}{3} V_{s2} - (V_{s1} + V_{s2}) \right] + \left(\frac{2}{3} V_{s2} - V_o \right) = 0$$


$$\frac{4}{3} V_{s2} - 2V_{s1} - 2V_{s2} + \frac{2}{3} V_{s2} - V_o = 0$$

$$V_o = -2V_{s1}$$

$$\frac{V_o}{V_{s1}} = -2$$

OP-AMP Problems.


Problem 7. Consider

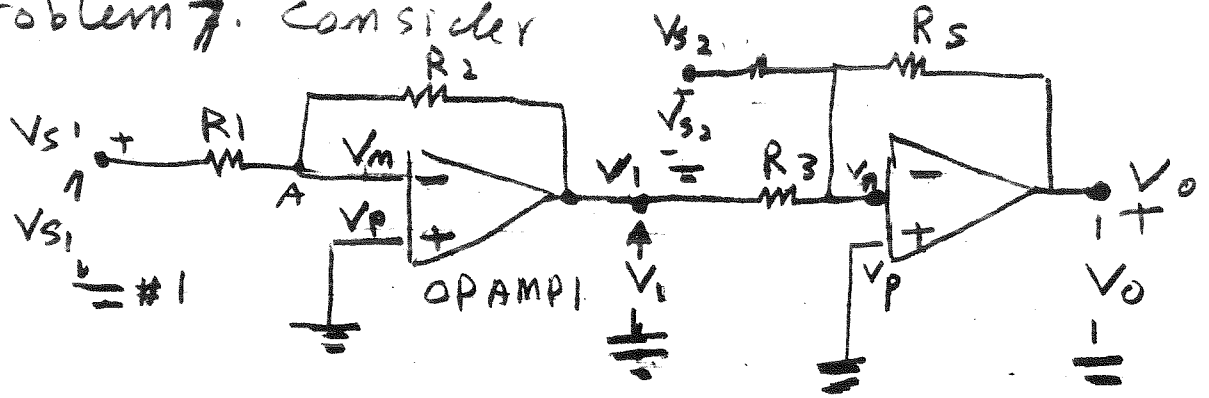

Find v_o in terms of the input v_{s1} and v_{s2}

Solution: Here, we have two OP-AMPS. First, we calculate the voltage V_1 in term of V_{s1} .

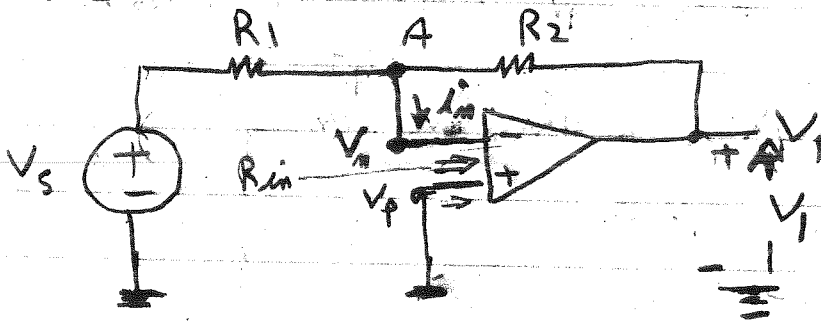
For OP-amp 1) operating in the inverting mode, we will have



$\sum i$ at node A • Note node A is at V_m voltage

$$\frac{V_s - V_m}{R_1} + \frac{V_1 - V_m}{R_2} - i_m = 0$$

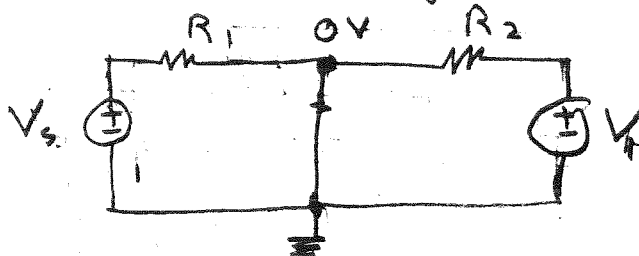However, R_{in} is very high $\Rightarrow i_m \approx 0$ and $V_m = V_p = 0$




$$\frac{V_s}{R_1} + \frac{V_1}{R_2} = 0$$

(14)

Problem 7 solution cont.

$$V_1 = -\frac{R_1}{R_2} V_s$$

For OPAMP2, we will have the following:

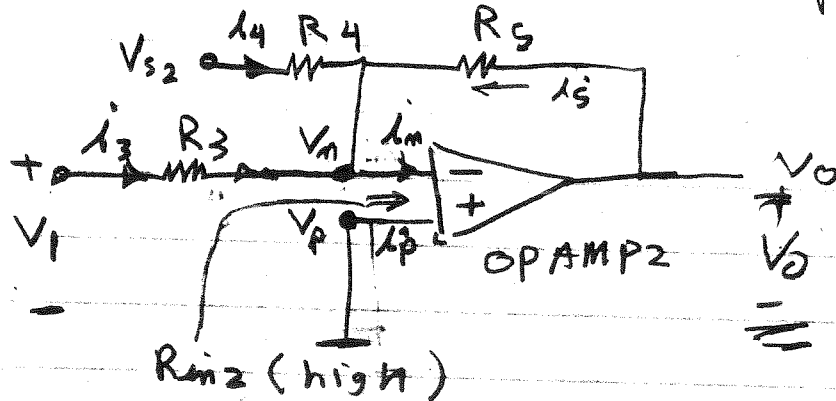

Again OPAMP2 has a very high input resistance,
 $i_p = i_m = 0$ $V_p = V_m = 0$

$$\frac{V_1 - V_m}{R_3} + \frac{V_{s2} - V_m}{R_4} + \frac{V_0 - V_m}{R_5} = 0$$

Note that $V_m = 0$, therefore, we have:

$$\frac{V_1}{R_3} + \frac{V_{s2}}{R_4} + \frac{V_0}{R_5} = 0$$

Multiply the above by R_5 and then rewrite the above as

$$V_0 = -\frac{R_5}{R_3} V_1 - \frac{R_5}{R_4} V_{s2}$$

Recall that $V_1 = -\frac{R_1}{R_2} V_s$, therefore, we will have the following:

(15)

Problem 7 solution cont.

$$V_o = -\frac{R_5}{R_3} \left(-\frac{R_2}{R_1} V_{s1} \right) - \frac{R_5}{R_4} V_{s2}$$

$$V_o = \frac{R_2 R_5}{R_1 R_3} V_{s1} - \frac{R_5}{R_4} V_{s2}$$

$$V_o = K_1 V_{s1} - K_2 V_{s2}$$

$$\text{where } K_1 = \frac{R_2 R_5}{R_1 R_3} \quad \text{and}$$

$$K_2 = \frac{R_5}{R_4}$$

By selecting R_1, R_2, R_3, R_4 and R_5 ,
you can obtain the desired output
voltage.