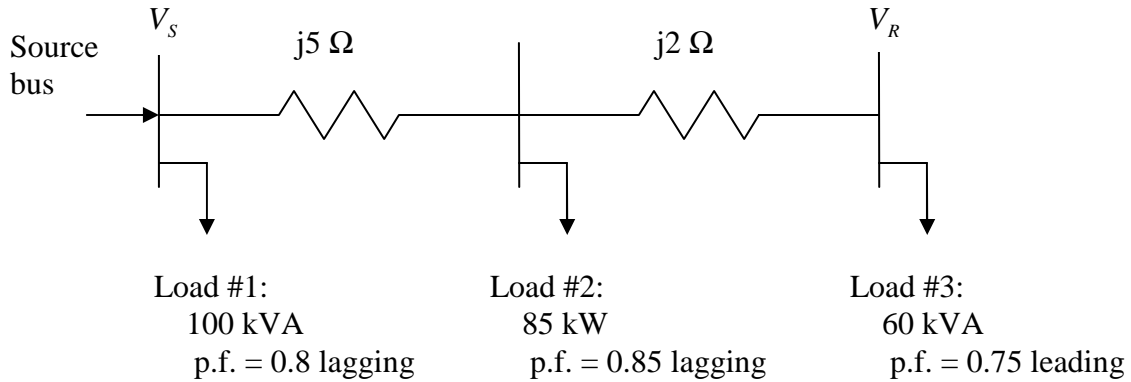


EE341 Homework #2 Solution

Problem 1: Consider a 3- ϕ distribution system as shown below:



Compute the following:

- 1) The source voltage V_S , if V_R is to be maintained at 2.2 kV.
- 2) The source current and power factor at the source.
- 3) The total complex power supplied by the source.
- 4) How much reactive power should be connected to the source bus for obtaining unity power factor at the source bus?
- 5) Write Matlab code to solve the above problems. Please submit the Matlab code and the results.


Solution:

a) load #1: $S_{1,\phi} = \frac{100}{3} (0.8 + j\sqrt{1-0.8^2}) = 33.33 \angle 36.87^\circ \text{ kVA}$

load #2: $S_{2,\phi} = \frac{85/0.85}{3} (0.85 + j\sqrt{1-0.85^2}) = 33.33 \angle 31.79^\circ \text{ kVA}$

load #3: $S_{3,\phi} = \frac{60}{3} (0.75 - j\sqrt{1-0.75^2}) = 20 \angle -41.41^\circ \text{ kVA}$

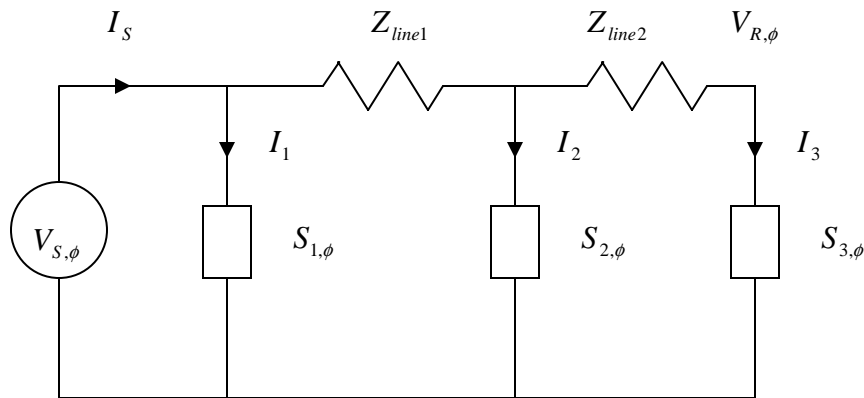b) Single phase equivalent circuit is shown as below:



$$V_{R,\phi} = \frac{2200}{\sqrt{3}} = 1270.2 \angle 0^\circ \text{ V}$$

$$I_3 = \left(\frac{S_{3,\phi}}{V_{R,\phi}} \right)^* = \left(\frac{20 \times 10^3 \angle -41.41^\circ}{1270.2 \angle 0^\circ} \right)^* = 15.75 \angle 41.41^\circ \text{ A}$$

$$V_{2,\phi} = V_{R,\phi} + I_3 Z_{line2} = 1270.2 \angle 0^\circ + 15.75 \angle 41.41^\circ \times j2 = 1249.6 \angle 1.08^\circ \text{ V}$$

$$I_2 = \left(\frac{S_{2,\phi}}{V_{2,\phi}} \right)^* = \left(\frac{33.33 \times 10^3 \angle 31.79^\circ}{1249.6 \angle 1.08^\circ} \right)^* = 26.68 \angle -30.71^\circ \text{ A}$$

$$V_{s,\phi} = V_{2,\phi} + (I_2 + I_3) Z_{line1} = 1249.6 \angle 1.08^\circ + (26.68 \angle -30.71^\circ + 15.75 \angle 41.41^\circ) \times j5 \\ = 1280.67 \angle 8.86^\circ \text{ V}$$

1) So, the source voltage is $|V_{S,L-L}| = \sqrt{3}|V_{S,\phi}| = 2218.18 \text{ V}$

$$2) I_1 = \left(\frac{S_{1,\phi}}{V_{s,\phi}} \right)^* = \left(\frac{33.33 \times 10^3 \angle 36.87^\circ}{1280.67 \angle 8.86^\circ} \right)^* = 26.03 \angle -28.01^\circ \text{ A}$$

The source current is $I_s = I_1 + I_2 + I_3 = 59.75 \angle -14.96^\circ \text{ A}$

The power factor is $pf = \cos \theta = \cos(\theta_{V_s} - \theta_{I_s}) = \cos(8.86^\circ + 14.96^\circ) = 0.91$ lagging.

$$3) S_{s,\phi} = V_{s,\phi} I_s^* = 1280.67 \angle 8.86^\circ \times 59.75 \angle 14.96^\circ = 76.52 \angle 23.83^\circ \text{ kVA}$$

So the total power supplied by the source is

$$S_{s,3\phi} = 3S_{s,\phi} = 229.57 \angle 23.83^\circ \text{ kVA} = 210 + j92.74 \text{ kVA}$$

4) To make $pf=1$, $-j92.74$ kVar reactive power should be connected to source bus.

5) Matlab code: hw2_1.m

```
% hw #2, problem 1

S1ph = 100e3 * exp(j*acos(0.8)) / 3;
fprintf('S1ph = %10.2f /_ %6.2f VA\n', abs(S1ph), angle(S1ph)*180/pi);
S2ph = 85e3/0.85 * exp(j*acos(0.85)) / 3;
fprintf('S2ph = %10.2f /_ %6.2f VA\n', abs(S2ph), angle(S2ph)*180/pi);
S3ph = 60e3 * exp(-j*acos(0.75)) / 3;
fprintf('S3ph = %10.2f /_ %6.2f VA\n', abs(S3ph), angle(S3ph)*180/pi);

Zline1 = j*5;
Zline2 = j*2;

VRph = 2.2e3 / sqrt(3);
fprintf('VRph = %10.2f /_ %6.2f V\n', abs(VRph), angle(VRph)*180/pi);
I3 = conj(S3ph / VRph);
fprintf('I3 = %10.2f /_ %6.2f A\n', abs(I3), angle(I3)*180/pi);
V2ph = VRph + I3 * Zline2;
fprintf('V2ph = %10.2f /_ %6.2f V\n', abs(V2ph), angle(V2ph)*180/pi);
I2 = conj(S2ph / V2ph);
fprintf('I2 = %10.2f /_ %6.2f A\n', abs(I2), angle(I2)*180/pi);
Vsph = V2ph + (I2+I3) * Zline1;
```

```

fprintf('VSph = %10.2f /_ %6.2f V\n', abs(VSph), angle(VSph)*180/pi);
VSL = sqrt(3) * abs(VSph);
fprintf('|VSL| = %10.2f V\n', abs(VSL));

I1 = conj(S1ph / VSph);
fprintf('I1 = %10.2f /_ %6.2f A\n', abs(I1), angle(I1)*180/pi);
IS = I1 + I2 + I3;
fprintf('IS = %10.2f /_ %6.2f A\n', abs(IS), angle(IS)*180/pi);
pf = cos(angle(VSph) - angle(IS));
fprintf('pf = %10.2f lagging\n', pf);

SSph = VSph * conj(IS);
fprintf('SSph = %10.2f /_ %6.2f VA\n', abs(SSph), angle(SSph)*180/pi);
SS3ph = 3 * SSph;
fprintf('SS3ph = %10.2f /_ %6.2f VA\n', abs(SS3ph), angle(SS3ph)*180/pi);
fprintf('SS3ph = (%10.2f) + j*(%10.2f) VA\n', real(SS3ph), imag(SS3ph));

Sc = -imag(SS3ph);
fprintf('Sc = j*(%10.2f) Var\n', Sc);

```


Result:

```

S1ph = 33333.33 /_ 36.87 VA
S2ph = 33333.33 /_ 31.79 VA
S3ph = 20000.00 /_ -41.41 VA
VRph = 1270.17 /_ 0.00 V
I3 = 15.75 /_ 41.41 A
V2ph = 1249.56 /_ 1.08 V
I2 = 26.68 /_ -30.71 A
VSph = 1280.67 /_ 8.86 V
|VSL| = 2218.18 V
I1 = 26.03 /_ -28.01 A
IS = 59.75 /_ -14.96 A
pf = 0.91 lagging
SSph = 76522.47 /_ 23.83 VA
SS3ph = 229567.42 /_ 23.83 VA
SS3ph = ( 210000.00) + j*( 92742.65) VA
Sc = j*( -92742.65) Var

```

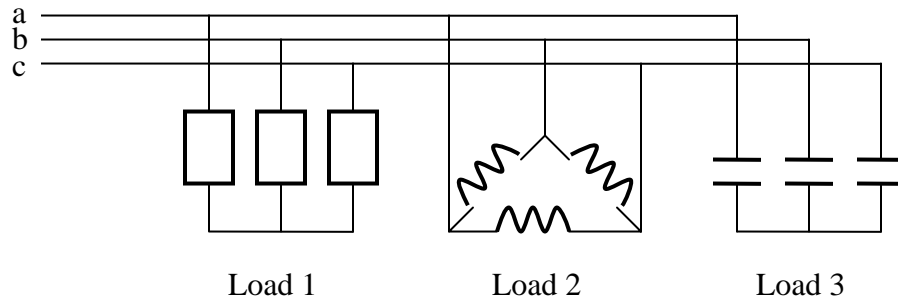Problem 2: A balanced three-phase, three-wire feeder has three balanced loads as shown:



Load 1 are three lamps, each rated 100 watts at 120 volts. Load 2 are three inductors, each having an inductance of 0.1 Henry. Load 3 are three capacitors, each having a capacitance of 100 μF .

The line-to-line voltage on the feeder is 220 volts, and the frequency is 60 Hz. Find the source current in the feeder lines and the power delivered by the source.

Solution:


$$\text{a) load 1: } R = \frac{V_{lamp}^2}{P_{lamp}} = \frac{120^2}{100} = 144\Omega$$

$$\text{load 2: } Z_{L,\Delta} = j\omega L = j2\pi \times 60 \times 0.1 = j37.7\Omega$$

$$Z_{L,Y} = Z_{L,\Delta} / 3 = j12.57\Omega$$

$$\text{load 3: } Z_C = -j \frac{1}{\omega C} = -j \frac{1}{2\pi \times 60 \times 100e-6} = -j26.53\Omega$$

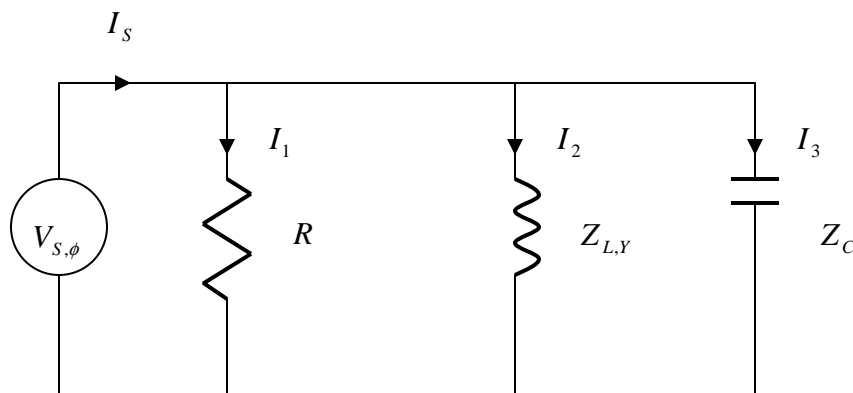b) The single-phase equivalent circuit is shown as below:



$$V_{S,\phi} = \frac{220}{\sqrt{3}} = 127.02 \angle 0^\circ \text{ V}$$

$$\text{c) } I_1 = \frac{V_{S,\phi}}{R} = \frac{127.02 \angle 0^\circ}{144} = 0.8821 \angle 0^\circ \text{ A}$$

$$I_2 = \frac{V_{s,\phi}}{Z_{L,Y}} = \frac{127.02\angle 0^\circ}{j12.57} = 10.11\angle -90^\circ \text{ A}$$

$$I_3 = \frac{V_{s,\phi}}{Z_C} = \frac{127.02\angle 0^\circ}{-j26.53} = 4.788\angle 90^\circ \text{ A}$$


So the source current is $I_S = I_1 + I_2 + I_3 = 5.392\angle -80.58^\circ \text{ A}$

The power delivered by the source is

$$\begin{aligned} S_{S,3\phi} &= 3V_{s,\phi}I_S^* = 3 \times 127.02\angle 0^\circ \times 5.392\angle 80.58^\circ = 336.1 + j2026.9 \text{ VA} \\ &= 2054.6\angle 80.58^\circ \text{ VA} \end{aligned}$$

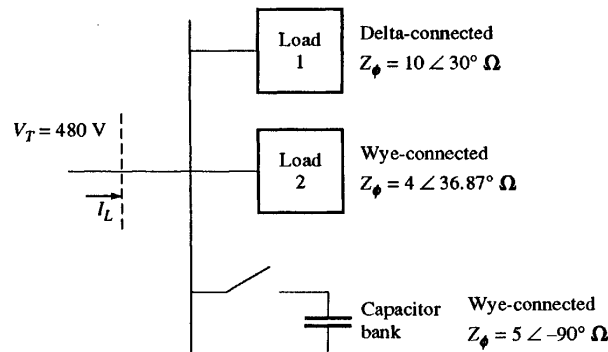Problem 3: Solve problem A-4 (textbook, page 673)

A-4. Figure A-19 shows a small 480-V distribution system. Assume that the lines in the system have zero impedance.



- (a) If the switch shown is open, find the real, reactive, and apparent powers in the system. Find the total current supplied to the distribution system by the utility.
- (b) Repeat part (a) with the switch closed. What happened to the total current supplied? Why?

SOLUTION

(a) With the switch open, the power supplied to each load is

$$P_1 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(480 \text{ V})^2}{10 \Omega} \cos 30^\circ = 59.86 \text{ kW}$$

$$Q_1 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(480 \text{ V})^2}{10 \Omega} \sin 30^\circ = 34.56 \text{ kVAR}$$

$$P_2 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(277 \text{ V})^2}{4 \Omega} \cos 36.87^\circ = 46.04 \text{ kW}$$

$$Q_2 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(277 \text{ V})^2}{4 \Omega} \sin 36.87^\circ = 34.53 \text{ kVAR}$$

$$P_{\text{TOT}} = P_1 + P_2 = 59.86 \text{ kW} + 46.04 \text{ kW} = 105.9 \text{ kW}$$

$$Q_{\text{TOT}} = Q_1 + Q_2 = 34.56 \text{ kVAR} + 34.53 \text{ kVAR} = 69.09 \text{ kVAR}$$

The apparent power supplied by the utility is

$$S_{\text{TOT}} = \sqrt{P_{\text{TOT}}^2 + Q_{\text{TOT}}^2} = 126.4 \text{ kVA}$$

The power factor supplied by the utility is

$$\text{PF} = \cos \left[\tan^{-1} \frac{Q_{\text{TOT}}}{P_{\text{TOT}}} \right] = \cos \left[\tan^{-1} \frac{69.09 \text{ kVAR}}{105.9 \text{ kW}} \right] = 0.838 \text{ lagging}$$

The current supplied by the utility is

$$I_L = \frac{P_{\text{TOT}}}{\sqrt{3} V_T \text{PF}} = \frac{105.9 \text{ kW}}{\sqrt{3} (480 \text{ V})(0.838)} = 152 \text{ A}$$

(b) With the switch closed, P_3 is added to the circuit. The real and reactive power of P_3 is

$$P_3 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(277 \text{ V})^2}{5 \Omega} \cos(-90^\circ) = 0 \text{ kW}$$

$$Q_3 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(277 \text{ V})^2}{5 \Omega} \sin(-90^\circ) = -46.04 \text{ kVAR}$$

$$P_{\text{TOT}} = P_1 + P_2 + P_3 = 59.86 \text{ kW} + 46.04 \text{ kW} + 0 \text{ kW} = 105.9 \text{ kW}$$

$$Q_{\text{TOT}} = Q_1 + Q_2 - Q_3 = 34.56 \text{ kVAR} + 34.53 \text{ kVAR} - 46.06 \text{ kVAR} = 23.03 \text{ kVAR}$$

The apparent power supplied by the utility is

$$S_{\text{TOT}} = \sqrt{P_{\text{TOT}}^2 + Q_{\text{TOT}}^2} = 108.4 \text{ kVA}$$

The power factor supplied by the utility is

$$\text{PF} = \cos \left[\tan^{-1} \frac{Q_{\text{TOT}}}{P_{\text{TOT}}} \right] = \cos \left[\tan^{-1} \frac{23.03 \text{ kVAR}}{105.9 \text{ kW}} \right] = 0.977 \text{ lagging}$$

The current supplied by the utility is

$$I_L = \frac{P_{\text{TOT}}}{\sqrt{3} V_T \text{PF}} = \frac{105.9 \text{ kW}}{\sqrt{3} (480 \text{ V})(0.977)} = 130.4 \text{ A}$$