



The Ohio State University  
Department of Electrical Engineering

EE 341

**Energy Conversion**  
**Home work Set # 3**

**Print Your Name**

---

**The Last Four Digits of Your OSU I.D. number :**

---

1. Solve Problem 2-1(text, page 133)

2-1. The secondary winding of a transformer has a terminal voltage of

$v_s(t) = 282.8 \sin 377t$  V. The turns ratio of the transformer is 50:200 ( $a = 0.25$ ). If

the secondary current of the transformer is  $i_s(t) = 7.07 \sin(377t - 36.87^\circ)$  A, what is

the primary current of this transformer? What are its voltage regulation and

efficiency? The impedances of this transformer referred to the primary side are

$$R_{eq} = 0.05\Omega \quad R_C = 75\Omega$$

$$X_{eq} = 0.225\Omega \quad X_M = 20\Omega$$

2. Solve Problem 2-3(text, page 134)

2-3. A 1000-VA 230/115-V transformer has been tested to determine its equivalent circuit. The results of the tests are shown below.

Open-circuit test	Short-circuit test
$V_{OC} = 230 \text{ V}$	$V_{SC} = 13.2 \text{ V}$
$I_{OC} = 0.45 \text{ A}$	$I_{SC} = 6.0 \text{ A}$
$P_{OC} = 30 \text{ W}$	$P_{SC} = 20.1 \text{ W}$

All data given were taken from the primary side of the transformer.

- Find the equivalent circuit of this transformer referred to the low-voltage side of the transformer.
- Find the transformer's voltage regulation at rated conditions and (1) 0.8 PF lagging, (2) 1.0 PF, (3) 0.8 PF leading.
- Determine the transformer's efficiency at rated conditions and 0.8 PF lagging.