



The Ohio State University
Department of Electrical Engineering

EE 341


Energy Conversion
Home work Set # 4

Print Your Name

The Last Four Digits of Your OSU I.D. number :

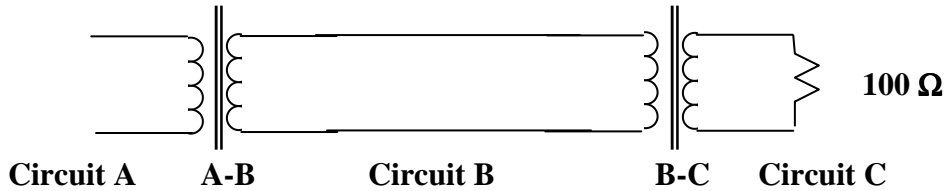Problem No.1:

Three parts of a single-phase electric systems are designated **A**, **B** and **C** , and are connected to each other through transformers, as shown below:



The transformers are rated as follows:

Transformer	kVA	Ratio	Leakage Reactance
A-B	10000	13.8kV/138kV	10%
B-C	10000	138kV/69kV	8%

If the base in **Circuit B** is chosen as 10000kVA, 138kV, answer the following questions:

Question		True	False
a-	Z_{base} in circuit A equals to Z_{base} in circuit B	[]	[]
b-	V_{base} in circuit A is 138 kV	[]	[]
c-	S_{base} in circuit C is 10 000kVA	[]	[]
d-	The 100Ω resistor referred to circuit B is 400Ω	[]	[]
e-	The 100Ω resistor referred to circuit A is 4Ω	[]	[]
f-	The per-unit value of 100Ω resistor is the same in all parts of the circuit	[]	[]

2. Use Matlab to solve problem 2-10 (page 136). Please submit the matlab code, comments and results.

3. Solve problem 2-11 (page 136). Please give detailed steps.