

Homework #4 Solutions

1. (2-18, page 138) Three 25-kVA 24,000/277-V distribution transformers are connected in Δ -Y. The open-circuit test was performed on the low-voltage side of this transformer bank, and the following data were recorded:

$$V_{line,OC} = 480 \text{ V} \quad I_{line,OC} = 4.10 \text{ A} \quad P_{3\phi,OC} = 945 \text{ W}$$

The short-circuit test was performed on the high-voltage side of this transformer bank, and the following data were recorded:

$$V_{line,SC} = 1400 \text{ V} \quad I_{line,SC} = 1.80 \text{ A} \quad P_{3\phi,SC} = 912 \text{ W}$$

- (a) Find the per-unit equivalent circuit of this transformer bank.
- (b) Find the voltage regulation of this transformer bank at the rated load and 0.90 PF lagging.
- (c) What is the transformer bank's efficiency under these conditions?

SOLUTION (a) The equivalent of this transformer bank can be found just like the equivalent circuit of a single-phase transformer if we work on a per-phase bases. The open-circuit test data on the low-voltage side can be used to find the excitation branch impedances referred to the secondary side of the transformer bank. Since the secondary is Y-connected, the per-phase open-circuit quantities are:

$$V_{\phi,OC} = 277 \text{ V} \quad I_{\phi,OC} = 4.10 \text{ A} \quad P_{\phi,OC} = 315 \text{ W}$$

The excitation admittance is given by

$$|Y_{EX}| = \frac{I_{\phi,OC}}{V_{\phi,OC}} = \frac{4.10 \text{ A}}{277 \text{ V}} = 0.01483 \text{ mho}$$

The admittance angle is

$$\theta = -\cos^{-1}\left(\frac{P_{\phi,OC}}{V_{\phi,OC} I_{\phi,OC}}\right) = -\cos^{-1}\left(\frac{315 \text{ W}}{(277 \text{ V})(4.10 \text{ A})}\right) = -73.9^\circ$$

Therefore,

$$Y_{EX} = G_C - jB_M = 0.01483 \angle -73.9^\circ = 0.00411 - j0.01425$$

$$R_C = 1/G_C = 243 \Omega$$

$$X_M = 1/B_M = 70.2 \Omega$$

The *base impedance* referred to the secondary side is

$$Z_{base,S} = \frac{(V_{\phi,S})^2}{S_\phi} = \frac{(277 \text{ V})^2}{25 \text{ kVA}} = 3.069 \Omega$$

so the excitation branch elements can be expressed in per-unit as

$$R_C = \frac{243 \Omega}{3.069 \Omega} = 79.2 \text{ pu}$$

$$X_M = \frac{70.2 \Omega}{3.069 \Omega} = 22.9 \text{ pu}$$

The short-circuit test data can be used to find the series impedances referred to the primary side, since the short-circuit test data was taken on the primary side. Note that the primary is Δ -connected, so $V_{\phi,SC} = V_{SC} = 1400 \text{ V}$, $I_{\phi,SC} = I_{SC} / \sqrt{3} = 1.039 \text{ A}$, and $P_{\phi,SC} = P_{SC} / 3 = 304 \text{ W}$.

$$|Z_{EQ}| = \frac{V_{\phi,SC}}{I_{\phi,SC}} = \frac{1400 \text{ V}}{1.039 \text{ A}} = 1347 \ \Omega$$

$$\theta = \cos^{-1}\left(\frac{P_{\phi,SC}}{V_{\phi,SC} I_{\phi,SC}}\right) = \cos^{-1}\left(\frac{304 \text{ W}}{(1400 \text{ V})(1.039 \text{ A})}\right) = 77.9^\circ$$

$$Z_{EQ} = R_{EQ} + jX_{EQ} = 1347 \angle 77.9^\circ = 282 + j1371 \ \Omega$$


The base impedance referred to the secondary side is

$$Z_{\text{base},P} = \frac{(V_{\phi,P})^2}{S_{\phi}} = \frac{(24,000 \text{ V})^2}{25 \text{ kVA}} = 24,040 \ \Omega$$

The resulting per-unit impedances are

$$R_{EQ} = \frac{282 \ \Omega}{24,040 \ \Omega} = 0.0117 \text{ pu} \qquad X_{EQ} = \frac{1371 \ \Omega}{24,040 \ \Omega} = 0.057 \text{ pu}$$

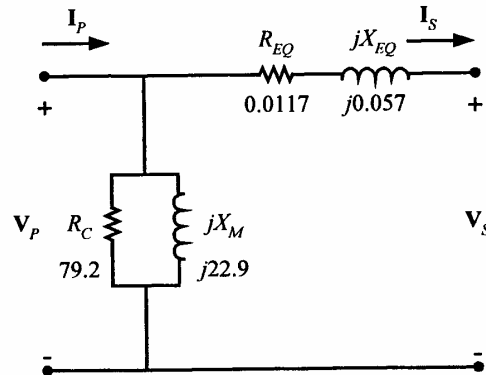The per-unit, per-phase equivalent circuit of the transformer bank is shown below:



(b) If this transformer is operating at rated load and 0.90 PF lagging, then current flow will be at an angle of $-\cos^{-1}(0.9)$, or -25.8° . The voltage at the primary side of the transformer will be

$$V_p = V_s + I_s Z_{EQ} = 1.0 \angle 0^\circ + (1.0 \angle -25.8^\circ)(0.0117 + j0.057) = 1.037 \angle 2.65^\circ$$

The voltage regulation of this transformer bank is

$$\text{VR} = \frac{1.037 - 1.0}{1.0} \times 100\% = 3.7\%$$

(c) The output power of this transformer bank is

$$P_{\text{OUT}} = V_s I_s \cos \theta = (1.0)(1.0)(0.9) = 0.9 \text{ pu}$$

The copper losses are

$$P_{\text{CU}} = I_s^2 R_{EQ} = (1.0)^2 (0.0117) = 0.0117 \text{ pu}$$

The core losses are

$$P_{\text{core}} = \frac{V_p^2}{R_c} = \frac{(1.037)^2}{79.2} = 0.014 \text{ pu}$$


Therefore, the total input power to the transformer bank is

$$P_{\text{IN}} = P_{\text{OUT}} + P_{\text{CU}} + P_{\text{core}} = 0.9 + 0.0117 + 0.014 = 0.9257$$

and the efficiency of the transformer bank is

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100\% = \frac{0.9}{0.9257} \times 100\% = 97.2\%$$

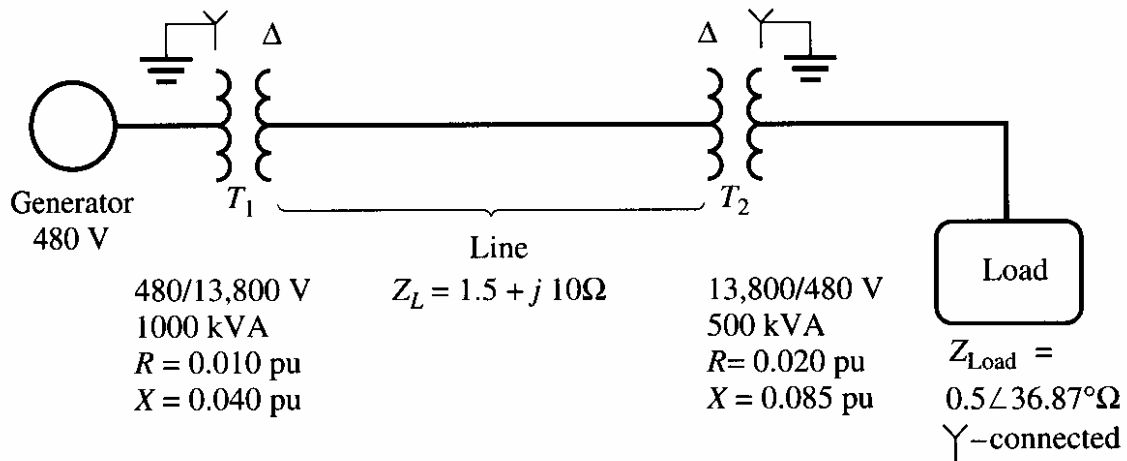2. The following figure shows a power system consisting of a three-phase 480-V 60-Hz generator supplying a load through a transmission line with a pair of transformers at either end.



- (a) Sketch the per-phase equivalent circuit of this power system.
 (b) Find the active power P , reactive power Q , and apparent (complex) power S supplied by the generator. What is the power factor of the generator?

Solution:

<u>Region 1</u>	<u>Region 2</u>	<u>Region 3</u>
$S_{\text{base1}} = 1000 \text{ kVA}$	$S_{\text{base2}} = 1000 \text{ kVA}$	$S_{\text{base3}} = 1000 \text{ kVA}$
$V_{L,\text{base1}} = 480 \text{ V}$	$V_{L,\text{base2}} = 13,800 \text{ V}$	$V_{L,\text{base3}} = 480 \text{ V}$

This problem can best be solved using the per-unit system of measurements. The power system can be divided into three regions by the two transformers. If the per-unit base quantities in Region 1 are chosen to be $S_{\text{base1}} = 1000 \text{ kVA}$ and $V_{L,\text{base1}} = 480 \text{ V}$, then the base quantities in Regions 2 and 3 will be as shown above. The base impedances of each region will be:

$$Z_{\text{base1}} = \frac{3V_{\phi1}^2}{S_{\text{base1}}} = \frac{3(277 \text{ V})^2}{1000 \text{ kVA}} = 0.238 \Omega$$

$$Z_{\text{base2}} = \frac{3V_{\phi2}^2}{S_{\text{base2}}} = \frac{3(7967 \text{ V})^2}{1000 \text{ kVA}} = 190.4 \Omega$$

$$Z_{\text{base3}} = \frac{3V_{\phi3}^2}{S_{\text{base3}}} = \frac{3(277 \text{ V})^2}{1000 \text{ kVA}} = 0.238 \Omega$$

(a) To get the per-unit, per-phase equivalent circuit, we must convert each impedance in the system to per-unit on the base of the region in which it is located. The impedance of transformer T_1 is already in per-unit to the proper base, so we don't have to do anything to it:

$$R_{1,\text{pu}} = 0.010$$

$$X_{1,\text{pu}} = 0.040$$

The impedance of transformer T_2 is already in per-unit, but it is per-unit to the base of transformer T_2 , so it must be converted to the base of the power system.

$$(R, X, Z)_{\text{pu on base 2}} = (R, X, Z)_{\text{pu on base 1}} \frac{(V_{\text{base 1}})^2 (S_{\text{base 2}})}{(V_{\text{base 2}})^2 (S_{\text{base 1}})} \quad (2-60)$$

$$R_{2,\text{pu}} = 0.020 \frac{(7967 \text{ V})^2 (1000 \text{ kVA})}{(7967 \text{ V})^2 (500 \text{ kVA})} = 0.040$$

$$X_{2,\text{pu}} = 0.085 \frac{(7967 \text{ V})^2 (1000 \text{ kVA})}{(7967 \text{ V})^2 (500 \text{ kVA})} = 0.170$$


The per-unit impedance of the transmission line is

$$Z_{\text{line,pu}} = \frac{Z_{\text{line}}}{Z_{\text{base2}}} = \frac{1.5 + j10 \Omega}{190.4 \Omega} = 0.00788 + j0.0525$$

The per-unit impedance of Load is

$$Z_{\text{load,pu}} = \frac{Z_{\text{load1}}}{Z_{\text{base3}}} = \frac{0.5 \angle 36.87^\circ \Omega}{0.238 \Omega} = 1.681 + j1.261$$

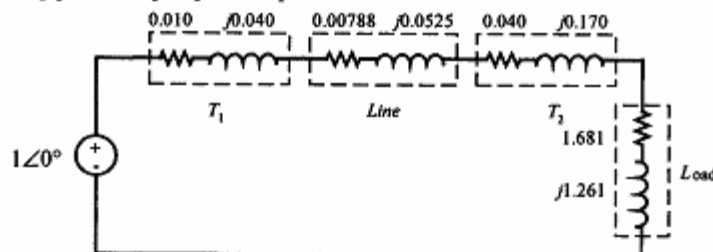The resulting per-unit, per-phase equivalent circuit is shown below:



(b) the equivalent impedance of this circuit is

$$Z_{EQ} = 0.010 + j0.040 + 0.00788 + j0.0525 + 0.040 + j0.170 + 1.681 + j1.261$$

$$Z_{EQ} = 1.7389 + j1.5235 = 2.312 \angle 41.2^\circ$$

The resulting current is

$$\mathbf{I} = \frac{1 \angle 0^\circ}{2.312 \angle 41.2^\circ} = 0.4325 \angle -41.2^\circ$$

The load voltage under these conditions would be

$$\mathbf{V}_{\text{Load,pu}} = \mathbf{I} Z_{\text{Load}} = (0.4325 \angle -41.2^\circ)(1.681 + j1.261) = 0.909 \angle -4.3^\circ$$

$$V_{\text{Load}} = V_{\text{Load,pu}} V_{\text{base3}} = (0.909)(480 \text{ V}) = 436 \text{ V}$$

The power supplied to the load is

$$P_{\text{Load,pu}} = I^2 R_{\text{Load}} = (0.4325)^2 (1.681) = 0.314$$

$$P_{\text{Load}} = P_{\text{Load,pu}} S_{\text{base}} = (0.314)(1000 \text{ kVA}) = 314 \text{ kW}$$

The power supplied by the generator is

$$P_{G,\text{pu}} = VI \cos \theta = (1)(0.4325) \cos 41.2^\circ = 0.325$$

$$Q_{G,\text{pu}} = VI \sin \theta = (1)(0.4325) \sin 41.2^\circ = 0.285$$

$$S_{G,\text{pu}} = VI = (1)(0.4325) = 0.4325$$

$$P_G = P_{G,\text{pu}} S_{\text{base}} = (0.325)(1000 \text{ kVA}) = 325 \text{ kW}$$

$$Q_G = Q_{G,\text{pu}} S_{\text{base}} = (0.285)(1000 \text{ kVA}) = 285 \text{ kVAR}$$

$$S_G = S_{G,\text{pu}} S_{\text{base}} = (0.4325)(1000 \text{ kVA}) = 432.5 \text{ kVA}$$

The power factor of the generator is

$$\text{PF} = \cos 41.2^\circ = 0.752 \text{ lagging}$$