



The Ohio State University
Department of Electrical Engineering

EE 341

Energy Conversion
Home work Set # 5

Print Your Name

The Last Four Digits of Your SSN:

1. A 100-kVA, 240/120 Y-Y three-phase power transformer has a per-unit resistance of 0.01 pu and a per-unit reactance of 0.035 pu. The excitation branch elements are $R_C = 80$ pu and $X_M = 20$ pu.
 - (a) If this transformer supplies a rated load at 0.8 PF lagging, draw the phasor diagram of one phase of the transformer.
 - (b) What is the voltage regulation of the transformer bank under these conditions?
 - (c) Sketch the equivalent circuit referred to the low-voltage side of one phase of this transformer. Calculate all the transformer impedances referred to the low-voltage side.

2. Problem 2-19 on textbook (Chapman)

A 20-kVA, 20,000/480-V 60-Hz distribution transformer is tested with the following results.

Open-circuit test (measured from secondary side)	Short-circuit test (measured from primary side)
$V_{oc} = 480V$	$V_{sc} = 1130V$
$I_{oc} = 1.51A$	$I_{sc} = 1.00A$
$P_{oc} = 271W$	$P_{sc} = 260W$

- (a) Find the per-unit equivalent circuit for this transformer at 60 Hz.
- (b) What would the rating of this transformer be if it were operated on a 50-Hz power system? (Hint: If this transformer were operated at 50 Hz, both the voltage and apparent power would have to be derated by a factor of 50/60.)
- (c) Sketch the equivalent circuit of this transformer referred to the primary side *if it is operating at 50 Hz*. (Hint: when frequency changes, the resistances will be unaffected, but the reactances will be changed because $X = \omega L = 2\pi fL$.