

## 1. Problem 5-3 on textbook (Chapman, page 318)


A 480-V, 200-kVA, 0.8-PF-lagging, 60-Hz, two-pole, Y-connected synchronous generator has a synchronous reactance of  $0.25 \Omega$  and an armature resistance of  $0.04 \Omega$ . At 60 Hz, its friction and windage losses are 6kW, and its core losses are 4kW. Assume that the field current of the generator has been adjusted to a value of 4.5 A (so that the open-circuit terminal voltage of the generator will be about 477 V).

- What will the terminal voltage of this generator be if it is connected to a  $\Delta$ -connected load with an impedance of  $5\sqrt{3}\angle 30^\circ \Omega$ ?
- Sketch the phasor diagram of this generator.
- What is the efficiency of the generator at these conditions?
- Now assume that another identical  $\Delta$ -connected load is to be paralleled with the first one. What happens to the phasor diagram for the generator?
- What is the new terminal voltage after the load has been added?
- What must be done to restore the terminal voltage to its original value?

## SOLUTION

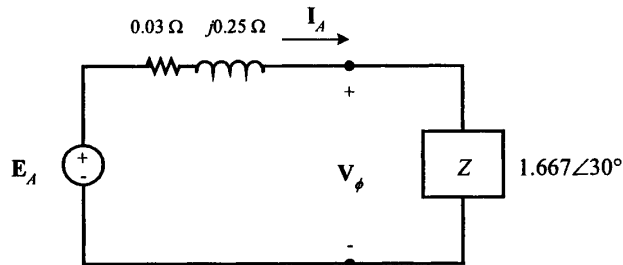(a) If the field current is 4.5 A, the open-circuit terminal voltage will be about 477 V, and the phase voltage in the generator will be  $477/\sqrt{3} = 275 \text{ V}$ .

The load is  $\Delta$ -connected with three impedances of  $5\sqrt{3}\angle 30^\circ \Omega$ . From this Y- $\Delta$  transform, this load is equivalent to a Y-connected load with three impedances of  $1.667\angle 30^\circ \Omega$ . The resulting per-phase equivalent circuit is shown below:



The magnitude of the phase current flowing in this generator is

$$I_A = \frac{E_A}{|R_A + jX_S + Z|} = \frac{275 \text{ V}}{|0.03 + j0.25 + 1.667\angle 30^\circ|} = \frac{275 \text{ V}}{1.829 \Omega} = 150 \text{ A}$$

Therefore, the magnitude of the phase voltage is

$$V_\phi = I_A Z = (150 \text{ A})(1.667 \Omega) = 250 \text{ V}$$

and the terminal voltage is

$$V_T = \sqrt{3} V_\phi = \sqrt{3} (250 \text{ V}) = 433 \text{ V}$$


(b) Armature current is  $I_A = 150\angle -30^\circ \text{ A}$ , and the phase voltage is  $V_\phi = 250\angle 0^\circ \text{ V}$ . Therefore, the internal generated voltage is

$$E_A = V_\phi + R_A I_A + jX_S I_A$$

$$E_A = 250\angle 0^\circ + (0.03 \Omega)(150\angle -30^\circ \text{ A}) + j(0.25 \Omega)(150\angle -30^\circ \text{ A})$$

$$E_A = 275\angle 6.3^\circ \text{ V}$$

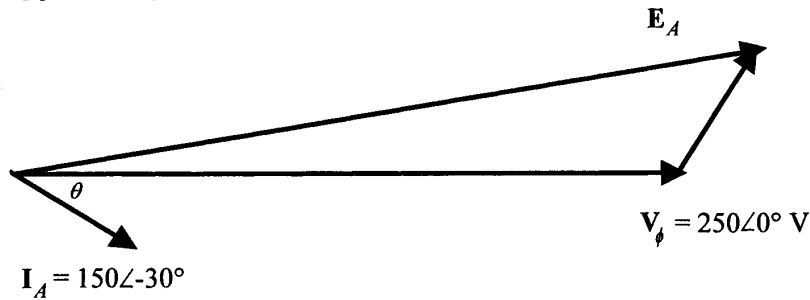The resulting phasor diagram is shown below (not to scale):



(c) The efficiency of the generator under these conditions can be found as follows:

$$P_{\text{OUT}} = 3V_{\phi} I_A \cos \theta = 3(250 \text{ V})(150 \text{ A})(0.8) = 90 \text{ kW}$$

$$P_{\text{CU}} = 3I_A^2 R_A = 3(150 \text{ A})^2 (0.03 \Omega) = 2 \text{ kW}$$

$$P_{\text{F\&W}} = 6 \text{ kW}$$


$$P_{\text{core}} = 4 \text{ kW}$$

$$P_{\text{stray}} = (\text{assumed } 0)$$

$$P_{\text{IN}} = P_{\text{OUT}} + P_{\text{CU}} + P_{\text{F\&W}} + P_{\text{core}} + P_{\text{stray}} = 102 \text{ kW}$$

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100\% = \frac{90 \text{ kW}}{102 \text{ kW}} \times 100\% = 88.2\%$$

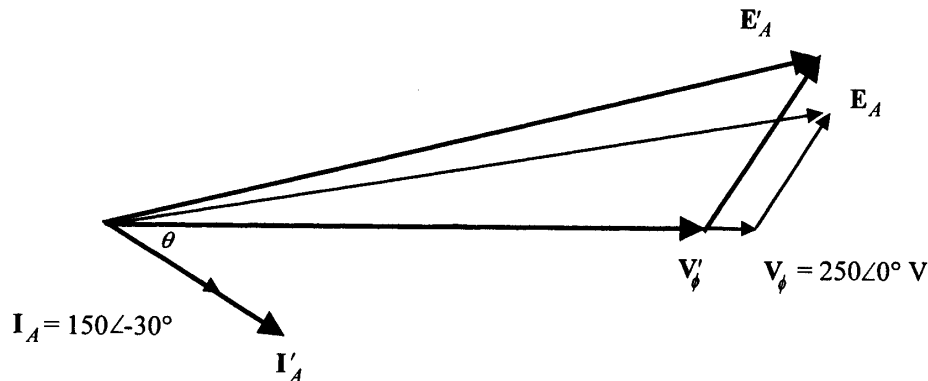(d) When the new load is added, the total current flow increases at the same phase angle. Therefore,  $jX_s I_s$  increases in length at the same angle, while the magnitude of  $E_A$  must remain constant. Therefore,  $E_A$  “swings” out along the arc of constant magnitude until the new  $jX_s I_s$  fits exactly between  $V_{\phi}$  and  $E_A$ .



(e) The new impedance per phase will be half of the old value, so  $Z = 0.8333 \angle 30^\circ \Omega$ . The magnitude of the phase current flowing in this generator is

$$I_A = \frac{E_A}{|R_A + jX_s + Z|} = \frac{275 \text{ V}}{|0.03 + j0.25 + 0.8333 \angle 30^\circ|} = \frac{275 \text{ V}}{1.005 \Omega} = 274 \text{ A}$$

Therefore, the magnitude of the phase voltage is

$$V_{\phi} = I_A Z = (274 \text{ A})(0.8333 \Omega) = 228 \text{ V}$$

and the terminal voltage is

$$V_T = \sqrt{3} V_\phi = \sqrt{3} (228 \text{ V}) = 395 \text{ V}$$

(f) To restore the terminal voltage to its original value, increase the field current  $I_F$ .

2. Problem 5-7 on textbook (Chapman, page 319)

A 13.5-kV, 20-MVA, 0.8-PF-lagging, 60-Hz, two-pole, Y-connected steam-turbine generator has a synchronous reactance of  $5.0 \Omega$  per phase and an armature resistance of  $0.5 \Omega$  per phase. This generator is operating in parallel with a large power system (infinite bus).

- What is the magnitude of  $E_A$  at rated conditions?
- What is the torque angle of the generator at rated conditions?
- If the field current is constant, what is the maximum power possible out of this generator?
- At the absolute maximum power possible, how much reactive power will this generator be supplying or consuming? Sketch the corresponding phasor diagram. (Assume  $I_F$  is still unchanged.)

SOLUTION

(a) The phase voltage of this generator at rated conditions is

$$V_\phi = \frac{V_T}{\sqrt{3}} = 7794 \text{ V}$$

The armature current per phase at rated conditions is

$$I_A = \frac{S}{\sqrt{3} V_T} = \frac{20,000,000 \text{ VA}}{\sqrt{3} (13,500 \text{ V})} = 855 \text{ A}$$

Therefore, the internal generated voltage at rated conditions is

$$\mathbf{E}_A = \mathbf{V}_\phi + R_A \mathbf{I}_A + jX_S \mathbf{I}_A$$

$$\mathbf{E}_A = 7794 \angle 0^\circ + (0.5 \Omega)(855 \angle -36.87^\circ \text{ A}) + j(5.0 \Omega)(855 \angle -36.87^\circ \text{ A})$$

$$\mathbf{E}_A = 11,160 \angle 16.5^\circ \text{ V}$$


The magnitude of  $E_A$  is 11,160 V.

(b) The torque angle of the generator at rated conditions is  $\delta = 16.5^\circ$ .

(c) Ignoring  $R_A$ , the maximum output power of the generator is given by

$$P_{\text{MAX}} = \frac{3 V_\phi E_A}{X_S} = \frac{3(7794 \text{ V})(11,160 \text{ V})}{5 \Omega} = 52.2 \text{ MW}$$

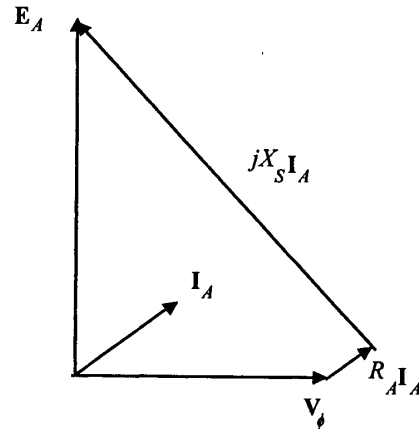(d) The phasor diagram at these conditions is shown below:



Under these conditions, the armature current is

$$I_A = \frac{E_A - V_\phi}{R_A + jX_S} = \frac{11,160 \angle 90^\circ \text{ V} - 7794 \angle 0^\circ \text{ V}}{0.5 + j5.0 \Omega} = 2790 \angle 39.5^\circ \text{ A}$$

The reactive power produced by the generator is

$$Q = 3V_\phi I_A \sin \theta = 3(7794 \text{ V})(2790 \text{ A}) \sin (0^\circ - 39.5^\circ) = -41.5 \text{ MVAR}$$

The generator is actually consuming reactive power at this time.