EE341 Homework #7 Solutions

Chapter 6: Synchronous Motors

- A 480-V, 60 Hz, six-pole synchronous motor draws 80 A from the line at unity power factor and full 6-1. load. Assuming that the motor is lossless, answer the following questions:
 - (a) What is the output torque of this motor? Express the answer both in newton-meters and in pound-
 - (b) What must be done to change the power factor to 0.8 leading? Explain your answer, using phasor
 - (c) What will the magnitude of the line current be if the power factor is adjusted to 0.8 leading?

SOLUTION

If this motor is assumed lossless, then the input power is equal to the output power. The input power to this motor is

$$P_{IN} = \sqrt{3} V_T I_L \cos \theta = \sqrt{3} (480 \text{ V}) (80 \text{ A}) (1.0) = 66.5 \text{ kW}$$


The output torque would be

$$\tau_{\text{LOAD}} = \frac{P_{\text{OUT}}}{\omega_m} = \frac{66.5 \text{ kW}}{\left(1200 \text{ r/min}\right) \left(\frac{1 \text{ min}}{60 \text{ s}}\right) \left(\frac{2\pi \text{ rad}}{1 \text{ r}}\right)} = 529 \text{ N} \cdot \text{m}$$

In English units,

$$\tau_{\text{LOAD}} = \frac{7.04 \, P_{\text{OUT}}}{n_m} = \frac{(7.04)(66.5 \,\text{kW})}{(1200 \,\text{r/min})} = 390 \,\text{N} \cdot \text{m}$$

(b) To change the motor's power factor to 0.8 leading, its field current must be increased. Since the power supplied to the load is independent of the field current level, an increase in field current increases $|\mathbf{E}_A|$ while keeping the distance $E_A \sin \delta$ constant. This increase in E_A changes the angle of the current \mathbf{I}_{A} , eventually causing it to reach a power factor of 0.8 leading.

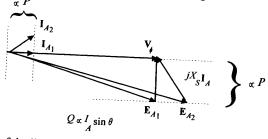

The magnitude of the line current will be

$$I_L = \frac{P}{\sqrt{3} V_T \text{ PF}} = \frac{66.5 \text{ kW}}{\sqrt{3} (480 \text{ V})(0.8)} = 100 \text{ A}$$

6-2. A 480-V, 60 Hz, 400-hp 0.8-PF-leading eight-pole Δ -connected synchronous motor has a synchronous reactance of 1.0 Ω and negligible armature resistance. Ignore its friction, windage, and core losses for the


- (a) If this motor is initially supplying 400 hp at 0.8 PF lagging, what are the magnitudes and angles of \mathbf{E}_A and \mathbf{I}_A ?
- (b) How much torque is this motor producing? What is the torque angle δ ? How near is this value to the maximum possible induced torque of the motor for this field current setting?
- (c) If $|\mathbf{E}_A|$ is increased by 15 percent, what is the new magnitude of the armature current? What is the motor's new power factor?
- (d) Calculate and plot the motor's V-curve for this load condition.

SOLUTION

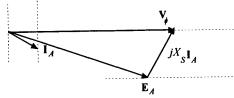(a) If losses are being ignored, the output power is equal to the input power, so the input power will be

$$P_{IN} = (400 \text{ hp})(746 \text{ W/hp}) = 298.4 \text{ kW}$$

This situation is shown in the phasor diagram below:



The line current flow under these circumstances is

$$I_L = \frac{P}{\sqrt{3} V_T \text{ PF}} = \frac{298.4 \text{ kW}}{\sqrt{3} (480 \text{ V})(0.8)} = 449 \text{ A}$$

Because the motor is Δ -connected, the corresponding phase current is $I_A = 449/\sqrt{3} = 259 \,\mathrm{A}$. The angle of the current is $-\cos^{-1}(0.80) = -36.87^\circ$, so $I_A = 259 \angle -36.87^\circ \,\mathrm{A}$. The internal generated voltage \mathbf{E}_A is

$$E_A = V_\phi - jX_S I_A$$

$$E_A = (480 ∠ 0° V) - j(1.0 Ω)(259 ∠ - 36.87° A) = 385 ∠ - 32.6° V$$

(b) This motor has 8 poles and an electrical frequency of 60 Hz, so its rotation speed is $n_m = 900$ r/min. The induced torque is

$$\tau_{\text{ind}} = \frac{P_{\text{OUT}}}{\omega_m} = \frac{298.4 \text{ kW}}{(900 \text{ r/min}) \left(\frac{1 \text{ min}}{60 \text{ s}}\right) \left(\frac{2\pi \text{ rad}}{1 \text{ r}}\right)} = 3166 \text{ N} \cdot \text{m}$$

The maximum possible induced torque for the motor at this field setting is

$$\tau_{\text{ind,max}} = \frac{3 V_{\phi} E_{A}}{\omega_{m} X_{S}} = \frac{3(480 \text{ V})(385 \text{ V})}{(900 \text{ r/min}) \left(\frac{1 \text{ min}}{60 \text{ s}}\right) \left(\frac{2\pi \text{ rad}}{1 \text{ r}}\right) (1.0 \Omega)} = 5882 \text{ N} \cdot \text{m}$$

(c) If the magnitude of the internal generated voltage E_A is increased by 15%, the new torque angle can be found from the fact that $E_A \sin \delta \propto P = \text{constant}$.

$$E_{A2} = 1.15 E_{A1} = 1.15(385 \text{ V}) = 443 \text{ V}$$

$$\delta_2 = \sin^{-1} \left(\frac{E_{A1}}{E_{A2}} \sin \delta_1 \right) = \sin^{-1} \left(\frac{385 \text{ V}}{443 \text{ V}} \sin(-32.6^\circ) \right) = -27.9^\circ$$

The new armature current is


$$I_{A2} = \frac{V_{\phi} - E_{A2}}{jX_{S}} = \frac{480 \angle 0^{\circ} \text{ V} - 443 \angle - 27.9^{\circ} \text{ V}}{j1.0 \Omega} = 225 \angle -23.1^{\circ} \text{ A}$$

The magnitude of the armature current is 225 A, and the power factor is $\cos(-23.1^{\circ}) = 0.920$ lagging.

(d) A MATLAB program to calculate and plot the motor's V-curve is shown below:

```
% M-file: prob6_2d.m
  % M-file create a plot of armature current versus Ea
      for the synchronous motor of Problem 6-2.
  % First, initialize the field current values (21 values
  % in the range 3.8-5.8 A)
  i_f = (38:1:58) / 10;
 % Initialize values
 Ea = (1:0.01:1.70)*385;
 Ear = 385;
                                    % Magnitude of Ea volts
 deltar = -32.6 * pi/180;
                                    % Reference Ea
                                   % Reference torque angle
 Xs = 1.0;
                                    % Synchronous reactance
 Vp = 480;
 Ear = Ear * (cos(deltar) + j * sin(deltar));
                                    % Phase voltage at 0 degrees
 % Calculate delta2
 delta2 = asin ( abs(Ear) ./ abs(Ea) .* sin(deltar) );
 % Calculate the phasor Ea
Ea = Ea .* (cos(delta2) + j .* sin(delta2));
% Calculate Ia
Ia = (Vp - Ea) / (j * Xs);
% Plot the v-curve
figure(1);
plot(abs(Ea),abs(Ia),'b','Linewidth',2.0);
xlabel('\bf\itE_{A}\rm\bf (V)');
ylabel('\bf\itI_{A}\rm\bf (A)');
title ('\bfSynchronous Motor V-Curve');
grid on;
```

The resulting plot is shown below

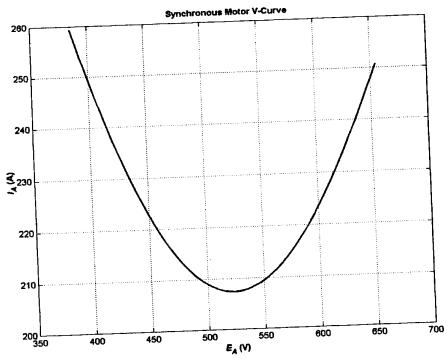

- 6-7. A 208-V Y-connected synchronous motor is drawing 50 A at unity power factor from a 208-V power system. The field current flowing under these conditions is 2.7 A. Its synchronous reactance is 0.8 Ω. Assume a linear open-circuit characteristic.
 - (a) Find the torque angle δ .
 - (b) How much field current would be required to make the motor operate at 0.78 PF leading?
 - (c) What is the new torque angle in part (b)?

SOLUTION

(a) The phase voltage of this motor is $V_{\phi} = 120$ V, and the armature current is $I_A = 50 \angle 0^{\circ}$ A. Therefore, the internal generated voltage is


$$\mathbf{E}_{A} = \mathbf{V}_{\phi} - R_{A} \mathbf{I}_{A} - j X_{S} \mathbf{I}_{A}$$

$$\mathbf{E}_{A} = 120 \angle 0^{\circ} \, \mathbf{V} - j (0.8 \, \Omega) (50 \angle 0^{\circ} \, \mathbf{A})$$

$$\mathbf{E}_{A} = 126.5 \angle -18.4^{\circ} \, \mathbf{V}$$

The torque angle δ of this machine is -18.4° .

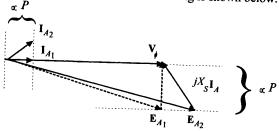(b) The motor operating at a power factor of 0.78 leading is shown below.



Since the power supplied by the motor is constant, the quantity $I_{\mathcal{A}}\cos\theta$, which is directly proportional to power, must be constant. Therefore,

$$I_{A2}(0.78) = (50 \text{ A})(1.00)$$

 $I_{A2} = 64.1 \angle 38.7^{\circ} \text{ A}$

The internal generated voltage required to produce this current would be

$$\begin{aligned} \mathbf{E}_{A2} &= \mathbf{V}_{\phi} - R_{A} \mathbf{I}_{A2} - j X_{S} \mathbf{I}_{A2} \\ \mathbf{E}_{A2} &= 120 \angle 0^{\circ} \, \text{V} - j \big(0.8 \, \Omega \big) \big(64.1 \angle 38.7^{\circ} \, \text{A} \big) \\ \mathbf{E}_{A2} &= 157 \angle - 14.7^{\circ} \, \text{V} \end{aligned}$$

The internal generated voltage E_A is directly proportional to the field flux, and we have assumed that the flux is directly proportional to the field current. Therefore, the required field current is

$$I_{F2} = \frac{E_{A2}}{E_{A1}}I_{F1} = \frac{157 \text{ V}}{126.5 \text{ V}}(2.7 \text{ A}) = 3.35 \text{ A}$$

(c) The new torque angle δ of this machine is -14.7° .