



The Ohio State University  
Department of Electrical Engineering

EE 341

**Energy Conversion  
Midterm**

**Print Your Name**

**Solution**

---

**The Last Four Digits of Your SSN:**


---

“No aid is given, received or observed”

**Signature :** \_\_\_\_\_

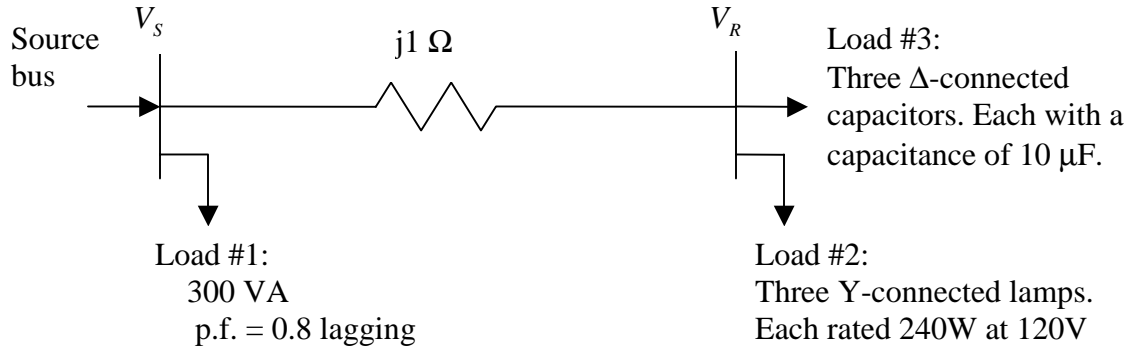**Problem No.1: (30 points)**

Consider a three-phase feeder shown below:



The Source bus voltage  $V_S$  is maintained at 240 V (line-to-line), 60 Hz. Compute the complex power supplied by the source and the power factor of the source.


**Solution:**

load 1:  $S_1 = 300 \angle \cos^{-1}(0.8) = 300 \angle 36.87^\circ \text{ VA}$

load 2:  $R = \frac{V_{lamp}^2}{P_{lamp}} = \frac{120^2}{240} = 60 \Omega$

load 3:  $Z_{C,\Delta} = -j \frac{1}{\omega C} = -j \frac{1}{2\pi \times 60 \times 10e-6} = -j265.3 \Omega$   
 $Z_{C,Y} = Z_{C,\Delta} / 3 = -j88.4 \Omega$

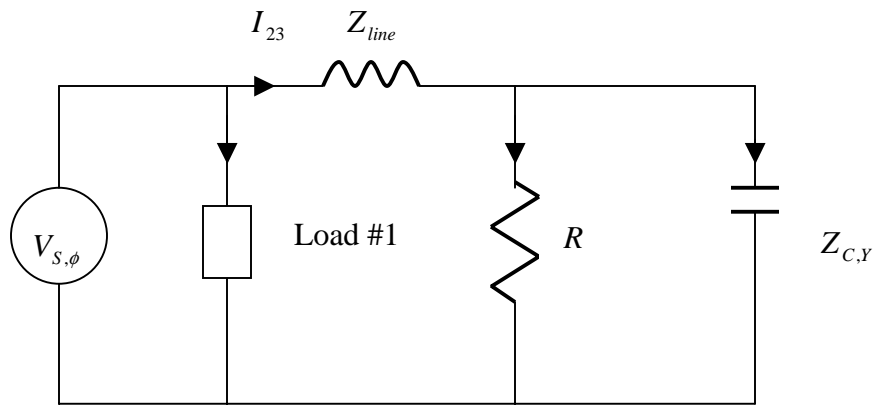The single-phase equivalent circuit is shown as below:



$$V_{S,\phi} = \frac{240}{\sqrt{3}} = 138.56 \angle 0^\circ \text{ V}$$

The equivalent impedance of the line and load #2, #3 is

$$Z_{eq} = Z_{line} + R // Z_{C,Y} = j1 + \frac{(60)(-j88.4)}{60 - j88.4} = 41.08 - j26.88 = 49.09 \angle -33.19^\circ \Omega$$

So the current  $I_{23}$  is

$$I_{23} = \frac{V_{S,\phi}}{Z_{eq}} = \frac{138.56 \angle 0^\circ}{49.09 \angle -33.19^\circ} = 2.82 \angle 33.19^\circ \text{ A}$$

The power delivered by the source is

$$\begin{aligned} S_{S,3\phi} &= 3V_{S,\phi} I_{23}^* + S_1 = 3 \times 138.56 \angle 0^\circ \times 2.82 \angle 33.19^\circ + 300 \angle 36.87^\circ = 1221.8 - j462.3 \text{ VA} \\ &= 1306.4 \angle -20.73^\circ \text{ VA} \end{aligned}$$

And power factor is  $PF = \cos(-20.73^\circ) = 0.935$  leading.

**Problem No.2: (40 points)**

A 10 kVA, 20,000/480-V single-phase transformer is tested on HV side with the following data:

$$\text{Short-circuit test: } V_{SC} = 1130V \quad I_{SC} = 1.00A \quad P_{SC} = 260W$$

- Determine the equivalent circuit of the transformer referred to secondary side.
- If the transformer is supplying a rated load with 0.8 PF lagging under rated voltage. Find the voltage regulation of this transformer.

**Solution:**

- a) From primary side (HV):

$$|Z_{EQ}| = \frac{V_{SC}}{I_{SC}} = \frac{1130}{1.00} = 1130\Omega$$

$$\cos\theta = \frac{P_{SC}}{V_{SC}I_{SC}} = \frac{260}{1130 \times 1.00} = 0.2301 \Rightarrow \theta = 76.7^\circ$$

so  $Z_{EQ} = 1130\angle 76.7^\circ = 260 + j1100\Omega$

converting to secondary side:

$$a = \frac{20000}{480} = 41.67$$

$$Z'_{EQ} = \frac{Z_{EQ}}{a^2} = 0.15 + j0.63\Omega$$

- b)  $S = 10\angle \cos^{-1}(0.8) = 10\angle 36.87^\circ \text{ kVA}$

$$V_S = 480\angle 0^\circ V$$

$$I_S = \left(\frac{S}{V_S}\right)^* = \left(\frac{10000\angle 36.87^\circ}{480\angle 0^\circ}\right)^* = 20.83\angle -36.87^\circ \text{ A}$$


$$V'_P = V_S + I_S Z'_{EQ} = 480\angle 0^\circ + 20.83\angle -36.87^\circ \times (0.15 + j0.63) = 490.5\angle 1.01^\circ V$$

the voltage regulation is:

$$VR = \frac{|V'_P| - |V_S|}{|V_S|} \times 100\% = \frac{490.5 - 480}{480} \times 100\% = 2.19\%$$

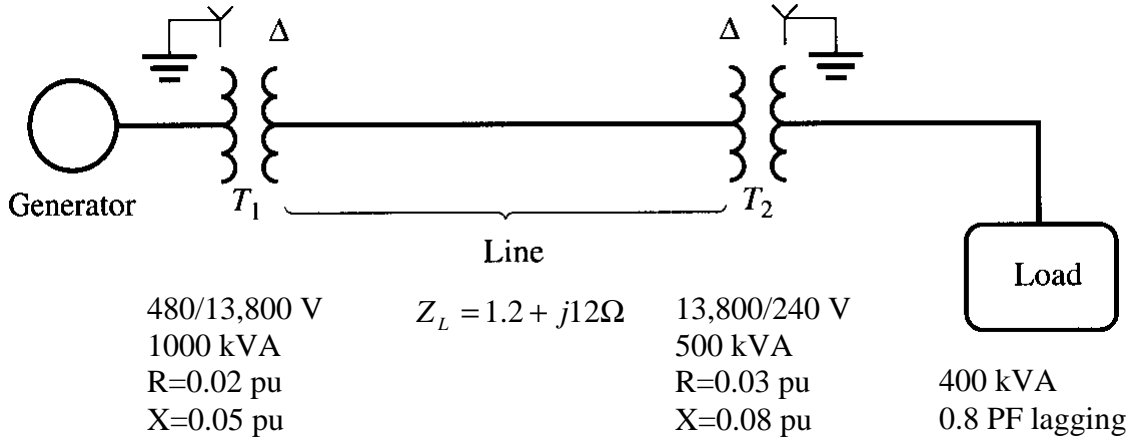**Problem No.3: (30 points)**

Consider a three-phase power system as shown below:



If the power base is chosen to be 1000 kVA, and the voltage base at the generator side to be 480 V. **Answer the following questions (please circle the right answers): You must show your steps. No credit will be given without your steps.**

a) What is the voltage base at load side?

- (i) 480 V                      (ii) 13,800 V                      **(iii) 240 V**                      (iv) 120 V

$$V_{b3} = 480 \times (13800 / 480) \times (240 / 13800) = 240V$$

b) ~~What is the power base at load side?~~

- (i) 1000 kVA**                      (ii) 500 kVA                      (iii) 400 kVA                      (iv) 320 kW

Power bases should be all the same for the whole system.

c) What is the per-unit value of line impedance at selected bases?

- (i) 5.21+j52.1                      **(ii) 0.0063+j0.063**                      (iii) 0.0021+j0.021                      (iv) 20.83+j208.3

$$Z_{b2} = (13800)^2 / 1000000 = 190.4\Omega, Z_{L,pu} = (1.2 + j12) / 190.4 = 0.0063 + j0.063$$

d) ~~What is the per-unit impedance of transformer T1 at selected bases?~~

- (i) 0.01+j0.025                      **(ii) 0.02+j0.05**                      (iii) 0.04+j0.1                      (iv) 0.08+j0.2

Bases are same as ratings. No need to transform.

e) What is the per-unit impedance of transformer T2 at selected bases?

- (i) 0.015+j0.04                      (ii) 0.03+j0.08                      **(iii) 0.06+j0.16**                      (iv) 0.12+j0.32

$$Z_{T2,new} = (0.03 + j0.08) \times (13800 / 13800)^2 \times (1000 / 500) = 0.06 + j0.16$$

f) ~~What is the per-unit value of the load power?~~

- (i) 0.32+j0.24**                      (ii) 0.32-j0.24                      (iii) 0.64+j0.48                      (iv) 0.64-j0.48

$$S_{load,pu} = (400 / 1000) \angle \cos^{-1}(0.8) = 0.32 + j0.24$$