
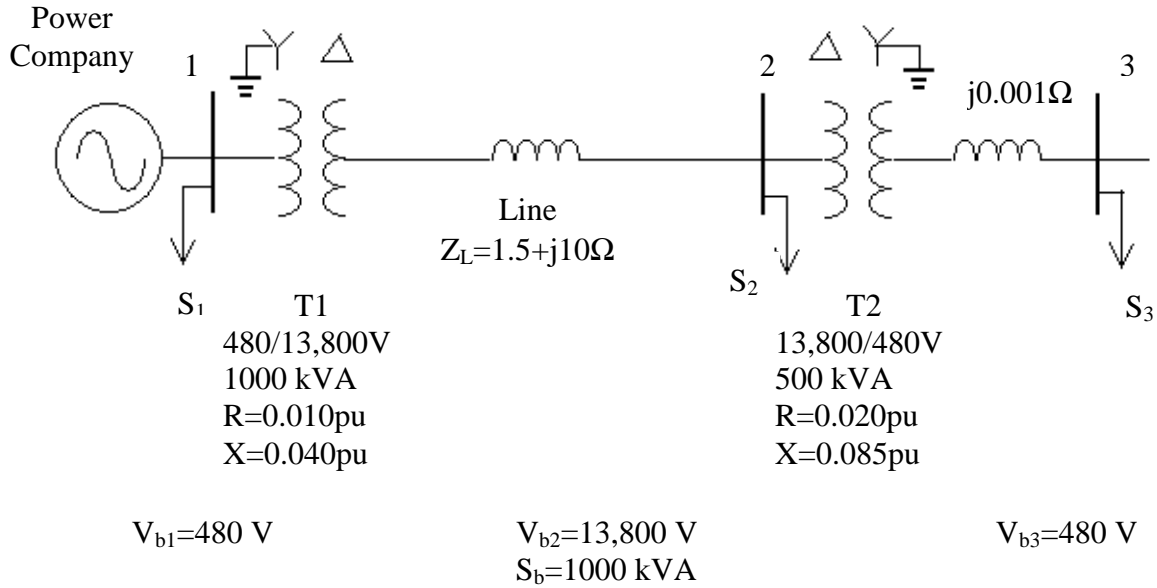


# EE341 Project Solution Part I: Matlab

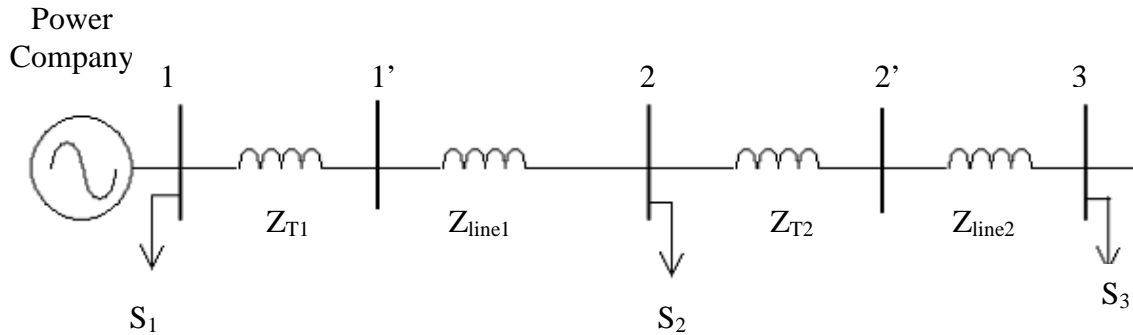

Compute the per-unit equivalent circuit:



$$Z_{b2} = \frac{(V_{b2} / \sqrt{3})^2}{S_b / 3} = \frac{V_{b2}^2}{S_b}$$


$$Z_{line1,pu} = \frac{Z_{line1}}{Z_{b2}}$$

$$Z_{b3} = \frac{V_{b3}^2}{S_b}$$


$$Z_{line2,pu} = \frac{Z_{line2}}{Z_{b3}}$$

$$Z_{T2,new} = Z_{T2,old} \left( \frac{V_{b,old}}{V_{b,new}} \right)^2 \frac{S_{b,new}}{S_{b,old}} = (.02 + j.085) \left( \frac{13800}{13800} \right)^2 \frac{1000}{500} = .04 + j.17$$

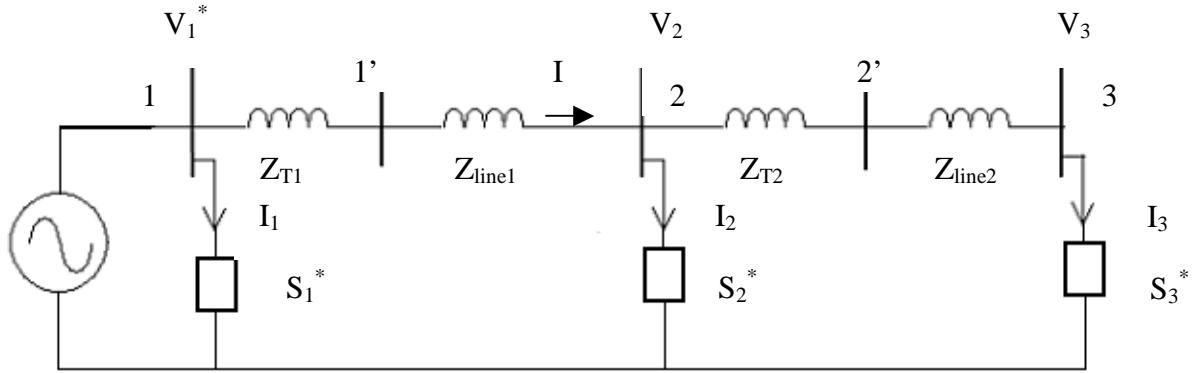**Problem (a): Compute  $V_2$  and  $V_3$**



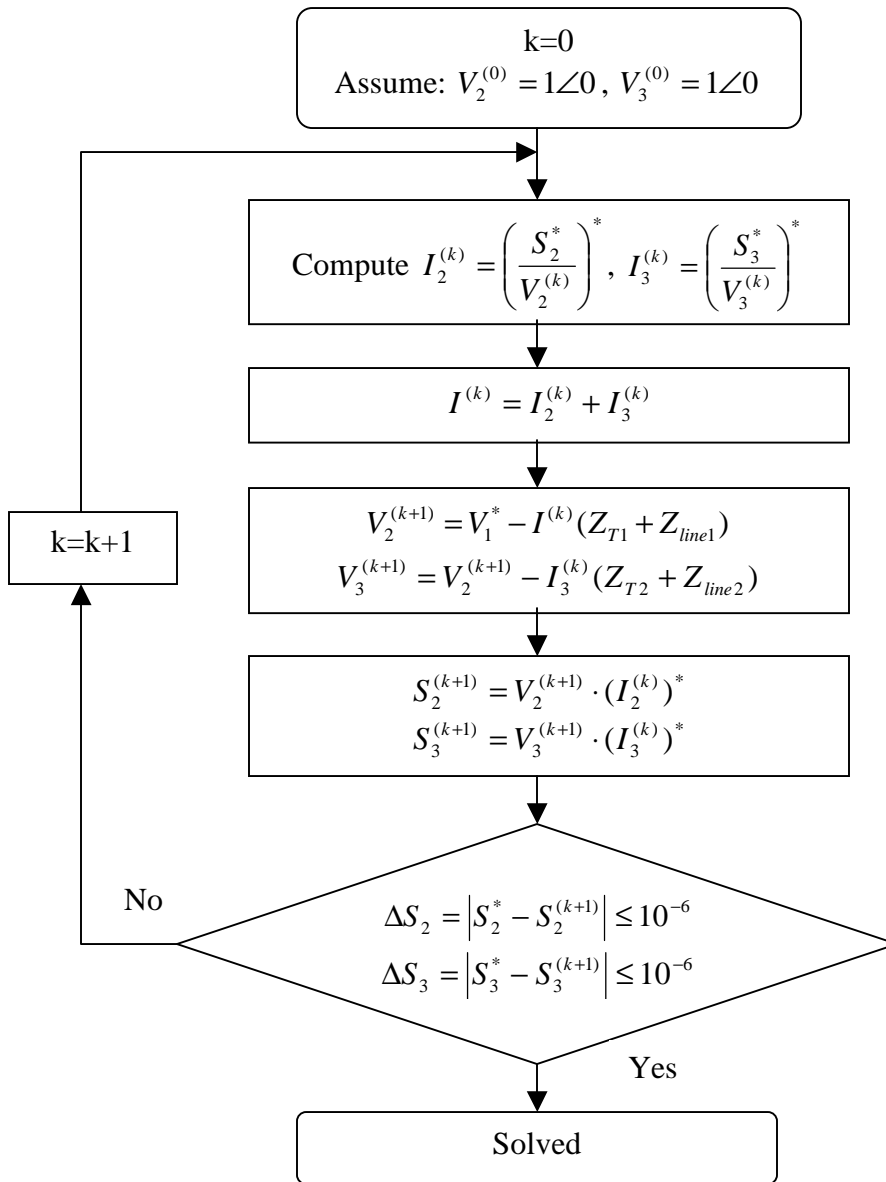Given:  $S_1^*, S_2^*, S_3^*, Z_{T1}, Z_{T2}, Z_{line1}, Z_{line2}, V_1^* = (460/480)\angle 0^\circ$



**Problem (b): Add reactive power ( $Q_{c2}$  and  $Q_{c3}$ ) to bus 2 and 3 to adjust  $V_2$  and  $V_3$**

