

EE682 – Group Project Design

Lecture #2 Inductor/Capacitor Design

Prof. Ali Keyhani

Boost DC/DC Converter Design

Inductor Design

For continuous mode ($\Delta I_L < 2I_{in}$)

$$t_1 = \left(\frac{1}{f}\right) \cdot \left(\frac{V_{out} + V_F - V_{in}}{V_{out}}\right)$$

$$\Delta I_L = \frac{1}{L} \cdot V_{in} \cdot t_1 \quad \text{and}$$

$$I_{max} = I_{in} + \frac{1}{2} \Delta I_L$$

(See Figure 2)

Inductor Design

For discontinuous mode ($\Delta I_L > 2I_{in}$)

$$t_1 = \sqrt{2I_{out} \cdot L \cdot \left(\frac{V_{out} + V_F - V_{in}}{f \cdot V_{in}^2} \right)}$$

$$t_2 = t_1 \cdot \left(\frac{V_{out} + V_F}{V_{out} + V_F - V_{in}} \right) \text{ and}$$

$$I_{max} = \frac{1}{L} \cdot V_{in} \cdot t_1$$

(See Figure 3)

Inductor Design

Assuming 15% current ripple:

$$\Delta I_L = 0.15 I_L = 0.15 I_{in} = 1.5 \text{ A}$$

$$\begin{aligned} L &= \frac{1}{f} (V_{out} + V_F - V_{in}) \left(\frac{V_{out} + V_F}{V_{in}} \right) \frac{1}{\Delta I_L} \\ &= \frac{1}{20 \times 10^3} \times (48 + 0.7 - 24) \times \frac{48 + 0.7}{24} \times \frac{1}{0.15 \times 10} \text{ H} \\ &= 406 \mu\text{H} \end{aligned}$$

Inductor Design – MTE Co. Products

DC AMPS	INDUC. mH	CATALOG No.	DC AMPS	INDUC. mH	CATALOG No.	DC AMPS	INDUC. mH	CATALOG No.
1	35.00	1RB001	40	0.50	40RB001	200	0.12	200RB001
1	60.00	1RB002	40	0.75	40RB002	200	0.21	200RB002
1	80.00	1RB003	40	1.00	40RB003	200	0.40	200RB003
2	10.00	2RB001	40	2.50	40RB004	200	0.50	200RB004
2	15.00	2RB002	50	0.625	50RB001	240	0.09	240RB001
2	20.00	2RB003	50	0.97	50RB002	240	0.25	240RB002
2	50.00	2RB004	50	1.35	50RB003	240	0.35	240RB003
4	5.00	4RB001	50	2.00	50RB004	300	0.08	300RB001
4	12.00	4RB002	62	0.32	62RB001	300	0.135	300RB002
4	15.00	4RB003	62	0.61	62RB002	300	0.32	300RB003
4	25.00	4RB004	62	0.67	62RB003	450	0.055	450RB001
9	2.00	9RB001	62	1.20	62RB004	450	0.11	450RB002
9	3.22	9RB002	62	1.50	62RB005	450	0.14	450RB003
9	7.50	9RB003	80	0.31	80RB001	450	0.25	450RB004
9	11.50	9RB004	80	0.40	80RB002	500	0.043	500RB001
12	1.00	12RB001	80	0.50	80RB003	500	0.09	500RB002
12	2.10	12RB002	80	0.75	80RB004	500	0.14	500RB003
12	4.00	12RB003	80	1.25	80RB005	500	0.19	500RB004
12	6.00	12RB004	92	0.20	92RB001	600	0.04	600RB001
18	0.65	18RB001	92	0.60	92RB002	600	0.11	600RB002
18	1.375	18RB002	92	1.00	92RB003	600	0.18	600RB003
18	2.75	18RB003	110	0.25	110RB001	700	0.044	700RB001
18	3.75	18RB004	110	0.30	110RB002	700	0.06	700RB002
18	6.00	18RB005	110	0.45	110RB003	700	0.15	700RB003
25	0.45	25RB001	125	0.11	125RB001	850	0.036	850RB001
25	1.00	25RB002	125	0.22	125RB002	850	0.065	850RB002
25	1.275	25RB003	125	0.50	125RB003	850	0.11	850RB003
25	1.75	25RB004	125	0.85	125RB004	1000	0.02	1000RB001
25	4.00	25RB005	150	0.15	150RB001	1000	0.042	1000RB002
32	0.85	32RB001	150	0.22	150RB002	1000	0.10	1000RB003
32	1.62	32RB002	150	0.32	150RB003			
32	2.68	32RB003	150	0.65	150RB004			

Inductor Design

Select product:


18RB001, $650\mu\text{H} > 406\mu\text{H}$, 18A

Peak current:

$$\begin{aligned}
 I_{\max} &= I_{in} + \frac{1}{2} \Delta I_L = I_{in} + \frac{1}{2} \left(\frac{1}{f} \right) (V_{out} + V_F - V_{in}) \left(\frac{V_{in}}{V_{out} + V_F} \right) \frac{1}{L} \\
 &= 10 + \frac{1}{2} \frac{1}{20 \times 10^3} (48 + 0.7 - 24) \left(\frac{24}{48 + 0.7} \right) \frac{1}{650 \times 10^{-6}} \text{ A} \\
 &= 10 + 0.468 \text{ A} = 10.468 \text{ A}
 \end{aligned}$$


$$10.468 \text{ A} < 15 \text{ A} = I_{D\max}$$

Capacitor Design

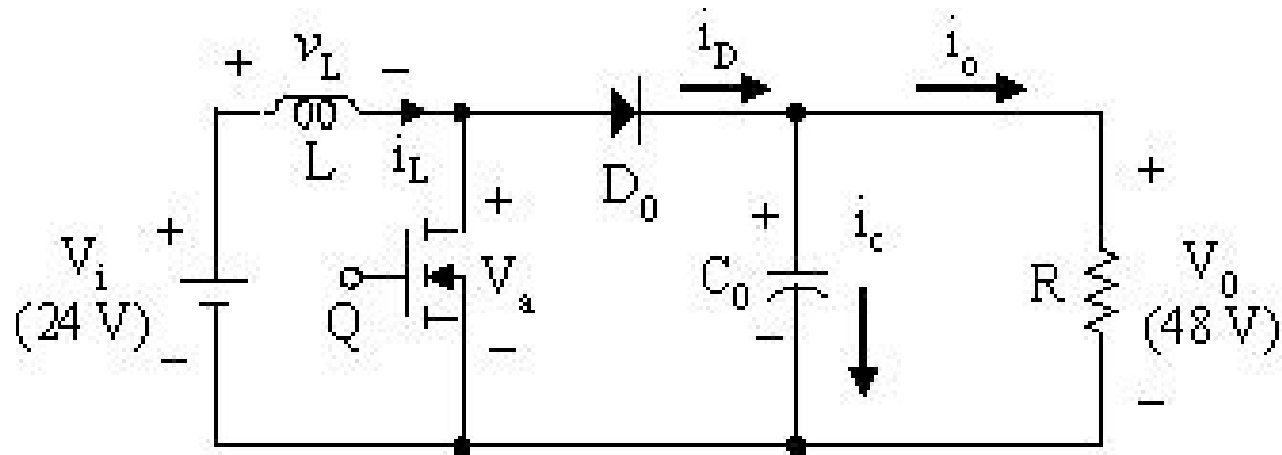

A conventional boost converter

Capacitor Design

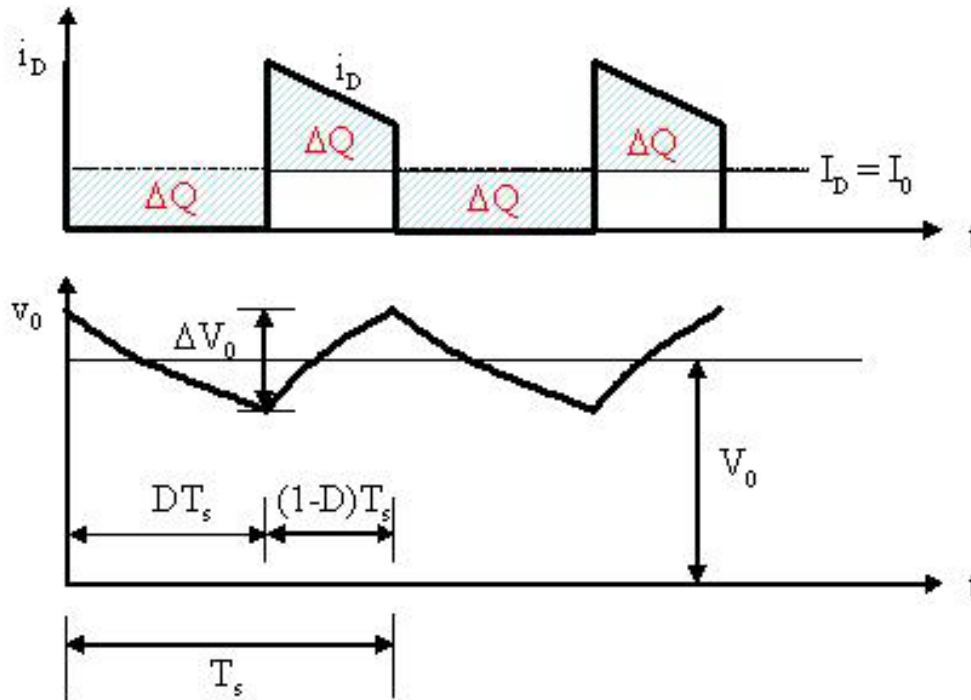

Output voltage ripple

Capacitor Design: Capacitance Calculation

Assume the diode current (i_D) is a square wave form

- Peak diode current:

$$I_{D,peak} = \frac{I_0}{D} = \frac{I_0}{0.5} = 10 \text{ A}$$

(Where $D = 0.5$, $I_0 = P/V_0 = 240/48 = 5 \text{ A}$)

- RMS diode current:

$$I_{D,rms} = I_{D,peak} \cdot \sqrt{D} = 10 \cdot \sqrt{0.5} = 7.07 \text{ A}$$

- RMS capacitor current

$$I_{c,rms} = \sqrt{I_{D,rms}^2 - I_0^2} = \sqrt{7.07^2 - 5^2} = 5 \text{ A}$$

Capacitor Design: Capacitance Calculation

- Output voltage ripple:

$$\Delta V_0 = \frac{\Delta Q}{C} = \frac{I_{c,rms} DT_s}{C}$$

- Capacitance

$$\therefore C = \frac{\Delta Q}{\Delta V_0} = \frac{I_{c,rms} DT_s}{\Delta V_0} = \frac{5 \cdot 0.5}{48 \times 10^{-3} \times 20 \times 10^3} = 2600 \mu F$$

Where, $D = 0.5$, $T_s = 1/(20 \times 10^3)$ sec, $I_{c,rms} = 5$ A, $\Delta V_0 = 48$ mV.

Capacitor Design: Supplier Selection

- ◆ Our Final Specifications:
 - Rated output voltage $> 48 \text{ V}$
 - Rated ripple current $> 5 \text{ A}$
 - Capacitance $> 2600 \mu\text{F}$

Capacitor Design: How to choose the type

- ◆ Considerations of designers:
 - Cost, Permissible temperature, Size, and ESR, etc

- ◆ Factors for Cost:
 - Materials
 - Rated voltage
 - Capacitance
 - Maximum permissible ripple currents
 - Maximum permissible temperature
 - ESR (Equivalent Series Resistance)

Capacitor Design: Supplier Selection

List of Aluminum Electrolyte Capacitors

Series		Applications	Load life Time (Hrs)	Miniature	Standard type	Low impedance	Long life	Solvent-proof	Terminal type	Rated voltage range (Vdc)	Capacitance range (μF)	
Screw-Bolt Terminal Type	General Purpose	SME	General	85°C 2000hrs	●				Screw	10~250	560~680,000	
		KMH	General, wide temp.	105°C 2000hrs	●		●		Screw	10~400	180~680,000	
	For Inverter	RWA	High ripple	85°C 2000hrs	●				Screw	350, 400	270~10,000	
		RWF	High ripple, long life	85°C 5000hrs				●	Screw	350~450	2,700~15,000	
	Special Application	PH	For Photo Flash	5~35°C 5,000 times						Pin/	330	165~2,000
		DH	For Welding	40°C 1,000,000 times						Screw	315, 475	100~330

(Manufactured by Sam Young Electronics Co.)

* Please refer to class note for more list

- Our selection: KMH Series for General Purpose


Capacitor Design: Supplier Selection

Data Sheet of KMH Series

PERMISSIBLE RIPPLE CURRENT

Frequency Multiplying Factor

Rated Voltage (VDC)	Case Diameter (mm)	Frequency(Hz)				
		60	120	300	1K	10K~
10~50	Φ30 ~ Φ89	0.95	1.00	1.03	1.05	1.09
63	Φ35	0.90	1.00	1.06	1.10	1.08
	Φ50 ~ Φ89	0.95	1.00	1.03	1.05	1.09
100	Φ35	0.82	1.00	1.12	1.22	1.30
	Φ50	0.90	1.00	1.06	1.10	1.18
	Φ63.5 ~ Φ89	0.95	1.00	1.03	1.05	1.09
160~250	Φ35	0.80	1.00	1.19	1.34	1.46
	Φ50 ~ Φ63.5	0.81	1.00	1.14	1.26	1.36
	Φ76 ~ Φ89	0.82	1.00	1.12	1.22	1.30
315~400	Φ35 ~ Φ89	0.80	1.00	1.19	1.34	1.46

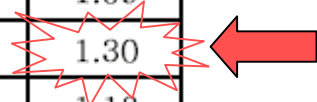

- **Our Selection:** – Rated output voltage: 100 V
 (Overvoltage due to parasite inductance)
 – Mutiplying factor: 1.3 ($f_s = 20$ kHz)

Capacitor Design: Supplier Selection

Rating of KMH Series

VDC μF	100(2A)			160(2C)			200(2D)			250(2E)		
2,700	A6	3.5	0.10	A10	3.3	0.15	A12	3.6	0.15	C10	3.5	0.20
3,300	A8	4.2	0.10	A12	3.8	0.15	C8	4.1	0.15	C12	4.2	0.20
3,900	A8	4.2	0.12	8	3.8	0.20	C10	4.9	0.15	C12	4.6	0.20
4,700	A10	5.0	0.12	C10	4.6	0.20	D10	5.3	0.20	D12	5.7	0.20
5,600	A10	5.4	0.12	C10	5.1	0.20	D10	5.8	0.20	D12	6.3	0.20

▲ Tan δ

▲ Permissible Ripple Current(Arms / 105°C, 120Hz)

▲ Case Code

- **Final Selection:** 100 V/3900 μF /4.2 A
 - Output voltage: 100 V > 48 V
 - Capacitance: 3900 μF > 2600 μF (Due to the effect of ESR)
 - Maximum permissible ripple current: $4.2 \times 1.3 = 5.46$ Arms > 5 A