

EE682
Fuel Cell Energy
Processing Systems
Spring 2003

Prof. Ali Keyhani

Class Notes: DC/DC Boost Converter Design

Fuel Cells

DC/DC Converters

Inverters

Mechatronics Laboratory
Department of Electrical Engineering
The Ohio State University

CHAPTER 5 Boost Converter Design

5.1 Introduction

The **Boost Converter** converts an input voltage to a higher output voltage. It is also named the step-up converter. Boost converters are used in fuel cell/battery powered devices, where the load side electronic circuit requires a higher operating voltage than the source can supply.

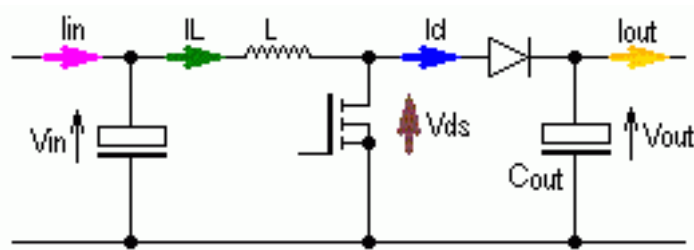


Figure 1 A topology of boost DC/DC converter

The transistor works as a switch which is turned on and off by a pulse-width-modulated control voltage. The ratio between on-time and the period t_1/T is called the *Duty Cycle*.

For theoretical analysis it will be assumed that the transistor is simplified as an ideal switch and the diode has no forward voltage drop. The diode will take into account a forward voltage drop $V_F = 0.7V$.

During the on-time of the transistor, the voltage across L is equal to V_{in} and the current I_L increases linearly. When the transistor is turned off, the current I_L flows through the diode and charges the output capacitor. The function of the boost converter can also be described in terms of energy balance: During the on-phase of the transistor, energy is loaded into the inductor. This energy is then transferred to the output capacitor during the blocking phase of the transistor.

The output voltage is always larger than the input voltage. Even if the transistor is not switched on and off the output capacitor charges via the diode until $V_{\text{out}} = V_{\text{in}}$. When the transistor is switched the output voltage will increase to higher levels than the input voltage.

- The Boost Converter is not short circuit proof, because there is inherently no switch-off device in the short-circuit path.

A distinction is drawn between **discontinuous** and **continuous** conducting mode depending on whether the inductor current I_L reduces to zero during the off-time or not. With the help of Faraday's Law the continuous mode and steady state conditions can be established.

$$\Delta I_L = \left(\frac{1}{L}\right) V_{\text{in}} \cdot t_1 = \left(\frac{1}{L}\right) (V_{\text{out}} - V_{\text{in}}) (T - t_1)$$

From this it follows that:

$$V_{\text{out}} = V_{\text{in}} \cdot \frac{T}{(T - t_1)}$$

- For continuous mode the output voltage is dependent on the duty cycle and the input voltage, it is independent of the load.

In discontinuous mode, the inductor current I_L will go to zero during every period. At the moment when the inductor current becomes zero, i.e. t_2 , the voltage V_1 jumps to the value of V_{out} because in this case $V_L = 0$. The drain-source capacitance in parallel with the diode-junction capacitance forms a resonant circuit with the inductance L . This is stimulated by the voltage jump across the diode. The voltage V_1 then oscillates and fades away.

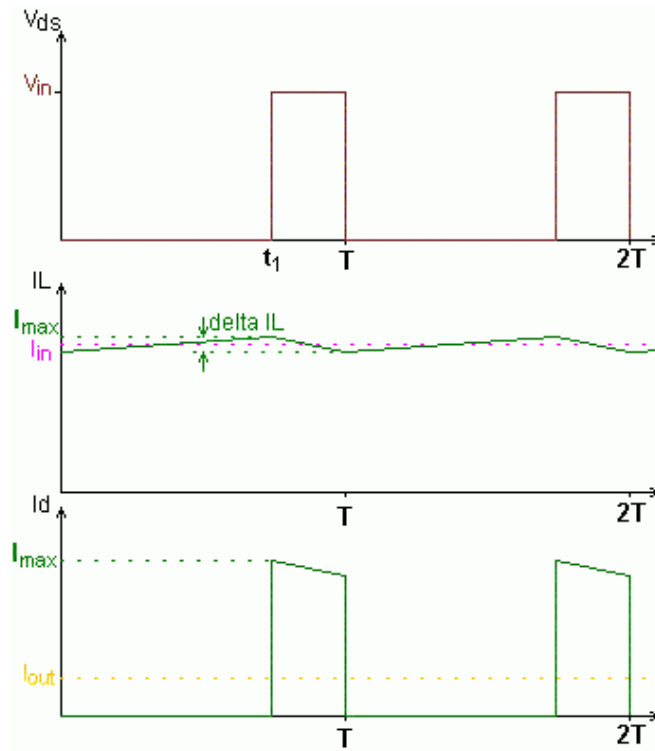


Figure 2 Continuous conducting mode (CCM)

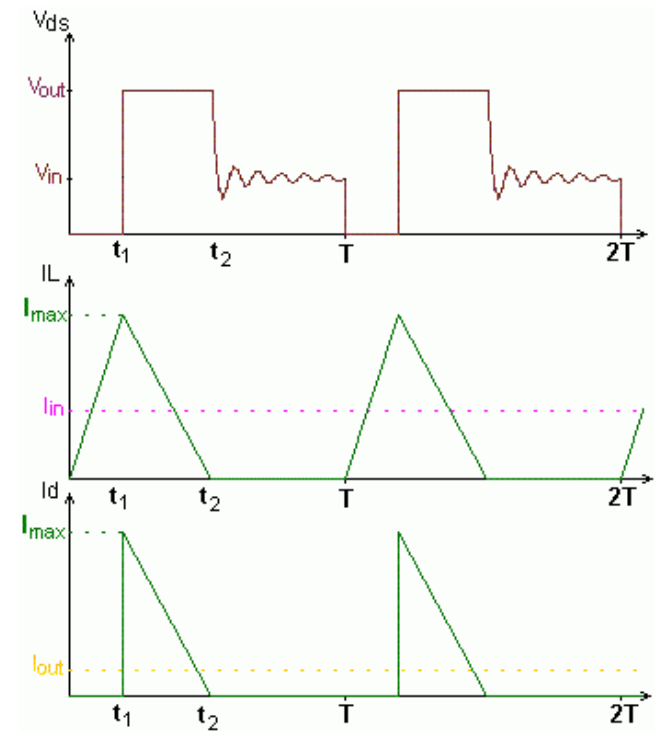


Figure 3 Discontinuous conducting mode

5.2 Power Switch Design

5.2.1 Select a power switch

BJTs (bipolar junction transistor), power MOSFETs (metal-oxide-semiconductor field effect transistors), and IGBT (insulated gate bipolar transistors) are commonly used controllable power switches (turned on/off by control signals).

BJTs and MOSFETs have characteristics that complement each other in some respects. BJTs have lower conduction losses in the ON state, especially in devices with larger blocking voltages, but have longer switching times, especially at turn-off. MOSFETs can be turned on and off much faster, but their ON state conduction losses are larger, especially in devices rated for higher blocking voltages (a few hundred volts and greater). These observations have led to attempts to combine BJTs and MOSFETs monolithically on the same silicon wafer to achieve a circuit or even perhaps a new device that combines the best qualities of both types of devices.

These attempts have led to the development of the IGBT, which is becoming the device of choice in most new applications.

In this section, design procedure will be discussed based on the difference between BJTs and MOSFETs. The methodology of using IGBT will be conceptually the same.

The criteria for choosing a power switch are the voltage and current ratings and the switching frequency. Generally, BJTs can be used for more highly rated applications than MOSFETs as shown in Figure 4.

MOSFETs have higher switching frequency than BJTs. Higher frequency in power electronic circuits leads to smaller inductors and capacitors in size and weight and therefore is desired. The related details will be given in the inductor and capacitor design sections below.

BJTs are driven by base drive current I_B . The ON state base current $I_{B(sat.)}$ can be large especially in large current applications, which is not desired. MOSFETs are driven by gate-source voltage V_{GS} and consumes little current. High base current leads to high loss, more complicated circuit, and more thermal concerns.

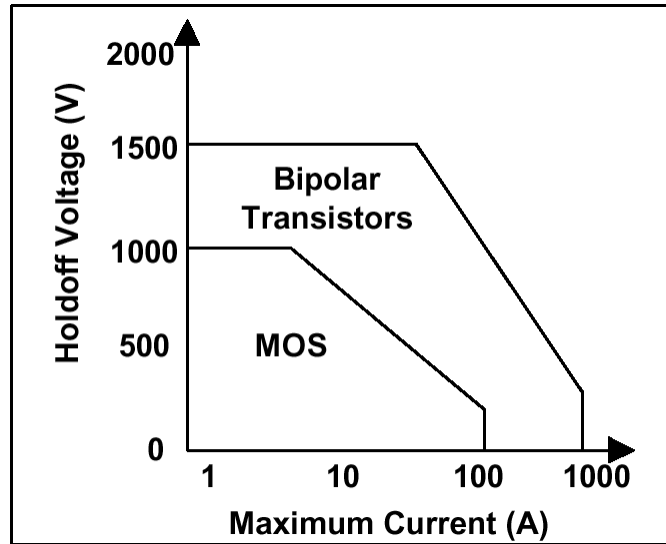


Figure 4 Voltage and current ratings for BJTs and power MOSFETs

The power switch selection and design procedures will be illustrated by the following design example.

Design requirement:

A 240-watt DC/DC boost converter with $V_{in}=24V$ and $V_{out}=48V$.

Design:

Based on the circuit topology shown in Figure 1, assuming large inductance and small current ripple, the peak transistor current should be close to the average inductor current (i.e., the input current):

$$I_{in} = P/V_{in} = 240W/24V = 10A$$

Based on this current capability requirement, considering some safety margin, two candidate transistors are chosen for comparison, one is BJT 2N6547

<http://www.semi-tech-inc.com/categories.php>

<http://www.electronica.ro/catalog/semiconductors.html>

the other is power MOSFET HUFA75307D3

http://www.fairchildsemi.com/collateral/powermosfets_sg.pdf

both of which satisfy the voltage and current requirement in that, for 2N6547, $I_C=15A > 10A$ and $V_{CE}=400V > 48V$, and for HUFA75307D3, $I_D=15A > 10A$ and $V_{DS}=55V > 48V$.

However, from Figure 5, it can be observed that the base current needs to be as high as 3.0A to saturate the collector which is undesirable. A BJT must work at saturation region (ON state) or cutoff region (OFF state) to be a power switch. A MOSFET is voltage driven and the threshold voltage for HUFA75307D3 is 4V and the maximum gate-source voltage $V_{GSmax}=20V$. Therefore a TTL logic +5V or MOSFET logic +15V circuit can be used to drive this MOSFET, which is easy for digital implementation.

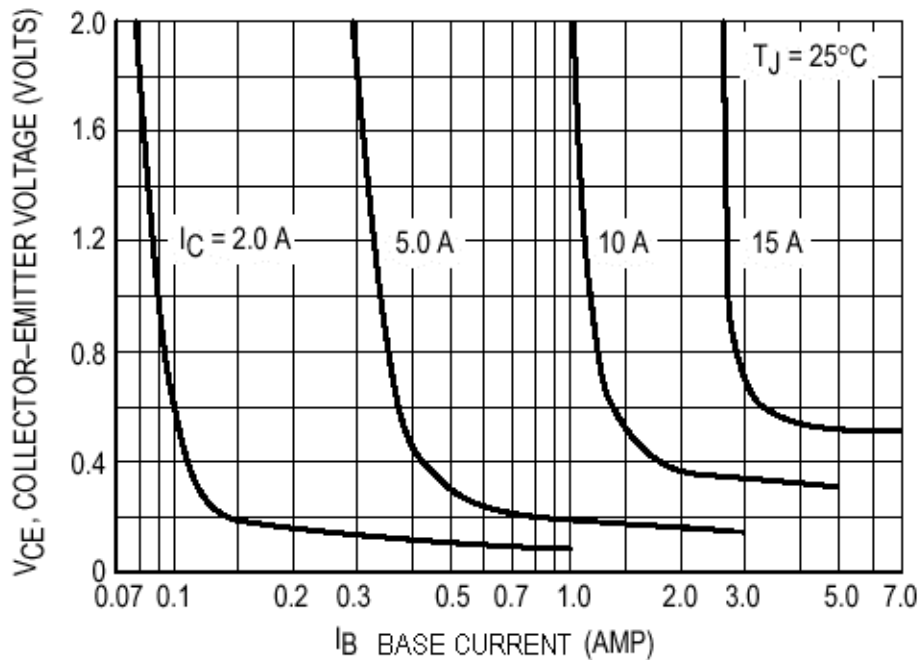


Figure 5 Collector Saturation Region of 2N6547

Transient performances of these two devices need to be compared also. The rise time and fall time of 2N6547 are $t_r=1.0\mu s$ and $t_f=1.5\mu s$ for inductive load, while those of HUFA75307D3 is $t_r=40ns$ and $t_f=45ns$ respectively. Therefore, the power MOSFET HUFA75307D3 can be used in much higher switching frequency.

Based on the above analysis, the power MOSFET HUFA75307D3 defeats the BJT 2N6547 in performance and becomes the solution. Before the circuit is implemented, the thermal issue needs to be addressed.

The switching loss can be calculated as follows

$$P_{loss} = \frac{W_{loss}}{T} = \frac{1}{T} (W_{loss_ON} + W_{loss_OFF}) = \frac{V_{ds} I_d}{2T} (t_{ON} + t_{OFF})$$

$$= \frac{48 \times 10}{2 \times \frac{1}{20 \times 10^3}} (60 + 100) \times 10^{-9} = 0.768 \text{ W}$$

The ON-state loss can be calculated as follows:

$$t_1 = \frac{1}{f} \left(\frac{V_{out} + V_F - V_{in}}{V_{out}} \right) = \frac{1}{20 \times 10^3} \left(\frac{48 + 0.7 - 24}{48} \right) \text{ sec} = 25.73 \mu\text{s}$$

$$P_{ON_loss} = \frac{W_{ON_loss}}{T} = \frac{1}{T} (I_D^2 r_{DS(ON)} t_1)$$

$$= \frac{1}{20 \times 10^3} (15^2 \times 0.075 \times 25.73 \times 10^{-6}) = 8.684 \text{ W}$$

Therefore the overall loss $P_{loss} = P_{SW_loss} + P_{ON_loss} = 9.452 \text{ W} < P_D = 45 \text{ W}$ (see the datasheet), where P_D is the heat dissipation capacity of the MOSFET. From the data sheet, the maximum thermal resistance from junction-to-sink is 3.3°C/W . Therefore, the junction-to-sink temperature different is

$$\Delta T_{js} = R_{\theta js} \times P_{loss} = 3.3^\circ\text{C/W} \times 9.452 \text{ W} = 31.2^\circ\text{C}$$

According to the data sheet, the maximum operating temperature is $T_{jmax} = 175^\circ\text{C}$. Therefore, with right heat sink, the MOSFET will be safe. Assuming 50% duty ratio, the transient thermal behavior can be calculated based on the normalized maximum transient thermal impedance in Figure 6 (the top curve):

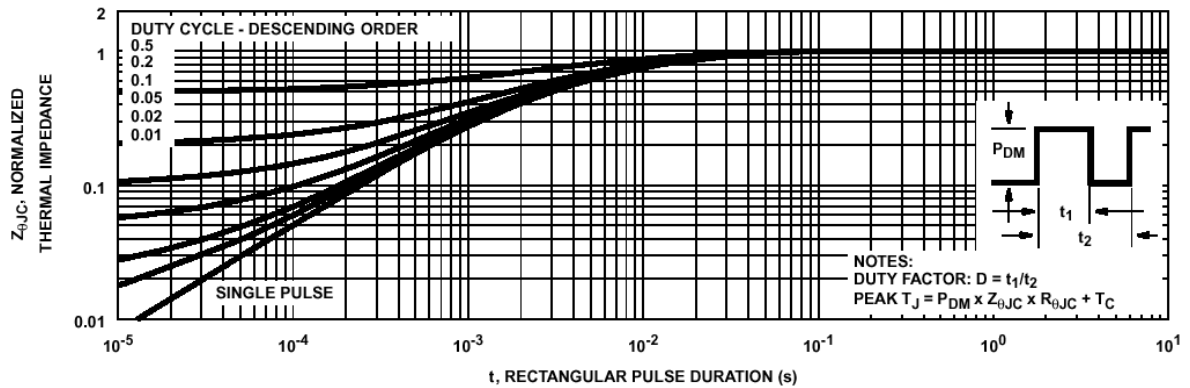


Figure 6 Normalized maximum transient thermal impedance of HUFA75307D3

$$\Delta T_{JC}(t) = P_{loss} Z_{\theta JC(50\%)}(t) R_{\theta JC}$$

$$\Delta T_{JC}(10\mu s) = P_{loss} Z_{\theta JC(50\%)}(10\mu s) R_{\theta JC} = 9.452 \text{ W} \times 0.5 \times 3.3^\circ \text{ C/W} = 15.60^\circ \text{ C}$$

$$\Delta T_{JC}(100\mu s) = P_{loss} Z_{\theta JC(50\%)}(100\mu s) R_{\theta JC} = 9.452 \text{ W} \times 0.53 \times 3.3^\circ \text{ C/W} = 16.53^\circ \text{ C}$$

$$\Delta T_{JC}(1 \text{ ms}) = P_{loss} Z_{\theta JC(50\%)}(1 \text{ ms}) R_{\theta JC} = 9.452 \text{ W} \times 0.63 \times 3.3^\circ \text{ C/W} = 19.65^\circ \text{ C}$$

$$\Delta T_{JC}(10 \text{ ms}) = P_{loss} Z_{\theta JC(50\%)}(10 \text{ ms}) R_{\theta JC} = 9.452 \text{ W} \times 0.85 \times 3.3^\circ \text{ C/W} = 26.51^\circ \text{ C}$$

$$\Delta T_{JC}(100 \text{ ms}) = P_{loss} Z_{\theta JC(50\%)}(100 \text{ ms}) R_{\theta JC} = 9.452 \text{ W} \times 1 \times 3.3^\circ \text{ C/W} = 31.2^\circ \text{ C} = \Delta T_{JC}(\infty)$$

5.3 Inductor Design and Current Ripple Calculation

Given the following operating conditions:

V_{in_min} , V_{in_max} , V_{out} , I_{out} and f , where f is the switching frequency.

Using these parameters, then a **proposal for L** can be obtained:

$$L = \left(\frac{1}{f} \right) \cdot (V_{out} + V_F - V_{in_min}) \cdot \left(\frac{V_{in_min}}{V_{out} + V_F} \right) \cdot \left(\frac{1}{\Delta I_L} \right)$$

where $V_F = 0.7 \text{ V}$ (Diode Forward-voltage) and 15% current ripple is assumed, i.e.,

$$\Delta I_L = 0.15 I_{in} = 0.15 I_{out} \left(\frac{V_{out} + V_F}{V_{in_min}} \right)$$

For the calculation of the curve-shapes, i.e. the peak current I_{max} , two cases have to be distinguished, i.e. *continuous conducting mode* and *discontinuous conducting mode*:

$$\Delta I_L = \left(\frac{1}{f} \right) \cdot (V_{out} + V_F - V_{in}) \cdot \left(\frac{V_{in}}{V_{out} + V_F} \right) \cdot \left(\frac{1}{L} \right) \text{ and}$$

$$I_{in} = I_{out} \cdot \left(\frac{V_{out} + V_F}{V_{in}} \right)$$

From this it follows that:

- a. For $\Delta I_L < 2I_{in}$ the converter is in continuous mode and it follows that:

$$t_1 = \left(\frac{1}{f}\right) \cdot \left(\frac{V_{out} + V_F - V_{in}}{V_{out}}\right)$$

$$\Delta I_L = \frac{1}{L} \cdot V_{in} \cdot t_1 \text{ and}$$

$$I_{max} = I_{in} + \frac{1}{2} \Delta I_L$$

- b. For $\Delta I_L > 2I_{in}$ the converter is in discontinuous mode and it follows that:

$$t_1 = \sqrt{2I_{out} \cdot L \cdot \left(\frac{V_{out} + V_F - V_{in}}{f \cdot V_{in}^2}\right)}$$

$$t_2 = t_1 \cdot \left(\frac{V_{out} + V_F}{V_{out} + V_F - V_{in}}\right) \text{ and}$$

$$I_{max} = \frac{1}{L} \cdot V_{in} \cdot t_1$$

For the above design example, the required inductance can be calculated as follows:

$$\begin{aligned} L &= \frac{1}{f} (V_{out} + V_F - V_{in}) \left(\frac{V_{out} + V_F}{V_{in}}\right) \frac{1}{\Delta I_L} \\ &= \frac{1}{20 \times 10^3} \times (48 + 0.7 - 24) \times \frac{48 + 0.7}{24} \times \frac{1}{0.15 \times 10} \text{ H} \\ &= 406 \mu\text{H} \end{aligned}$$

Based on the inductor manufacturer MTE Corporation catalog in

Table 1, considering the DC current capacity and some safety range, the type 18RB001 should be chosen, whose current capacity is $18A > 10A$ and inductance is $650\mu H > 406\mu H$.

The peak transistor current I_{\max} can be calculated as follows assuming continuous conducting mode (CCM)

$$\begin{aligned}
 I_{\max} &= I_{in} + \frac{1}{2}\Delta I_L = I_{in} + \frac{1}{2}\left(\frac{1}{f}\right)(V_{out} + V_F - V_{in})\left(\frac{V_{in}}{V_{out} + V_F}\right)\frac{1}{L} \\
 &= 10 + \frac{1}{2}\frac{1}{20 \times 10^{-3}}(48 + 0.7 - 24)\left(\frac{24}{48 + 0.7}\right)\frac{1}{650 \times 10^{-6}} \text{ A} \\
 &= 10 + 0.468 \text{ A} = 10.468 \text{ A}
 \end{aligned}$$

$I_{\max} = 10.468 \text{ A} < 15 \text{ A}$, therefore the current capacity of the MOSFET meets the peak requirement.

Table 1 MTE Corporation power magnetic components – DC inductors

DC AMPS	INDUC. mH	CATALOG No.	DC AMPS	INDUC. mH	CATALOG No.	DC AMPS	INDUC. mH	CATALOG No.
1	35.00	1RB001	40	0.50	40RB001	200	0.12	200RB001
1	60.00	1RB002	40	0.75	40RB002	200	0.21	200RB002
1	80.00	1RB003	40	1.00	40RB003	200	0.40	200RB003
			40	2.50	40RB004	200	0.50	200RB004
2	10.00	2RB001	50	0.625	50RB001	240	0.09	240RB001
2	15.00	2RB002	50	0.97	50RB002	240	0.25	240RB002
2	20.00	2RB003	50	1.35	50RB003	240	0.35	240RB003
2	50.00	2RB004	50	2.00	50RB004			
4	5.00	4RB001	62	0.32	62RB001	300	0.08	300RB001
4	12.00	4RB002	62	0.61	62RB002	300	0.135	300RB002
4	15.00	4RB003	62	0.67	62RB003	300	0.32	300RB003
4	25.00	4RB004	62	1.20	62RB004			
			62	1.50	62RB005	450	0.055	450RB001
9	2.00	9RB001	80	0.31	80RB001	450	0.11	450RB002
9	3.22	9RB002	80	0.40	80RB002	450	0.14	450RB003
9	7.50	9RB003	80	0.50	80RB003	450	0.25	450RB004
9	11.50	9RB004	80	0.75	80RB004			
			80	1.25	80RB005	500	0.043	500RB001
12	1.00	12RB001	92	0.20	92RB001	500	0.09	500RB002
12	2.10	12RB002	92	0.60	92RB002	500	0.14	500RB003
12	4.00	12RB003	92	1.00	92RB003	500	0.19	500RB004
12	6.00	12RB004						
18	0.65	18RB001	110	0.25	110RB001	600	0.04	600RB001
18	1.375	18RB002	110	0.30	110RB002	600	0.11	600RB002
18	2.75	18RB003	110	0.45	110RB003	600	0.18	600RB003
18	3.75	18RB004						
18	6.00	18RB005	125	0.11	125RB001	700	0.044	700RB001
			125	0.22	125RB002	700	0.06	700RB002
25	0.45	25RB001	125	0.50	125RB003	700	0.15	700RB003
25	1.00	25RB002	125	0.85	125RB004			
25	1.275	25RB003				850	0.036	850RB001
25	1.75	25RB004	150	0.15	150RB001	850	0.065	850RB002
25	4.00	25RB005	150	0.22	150RB002	850	0.11	850RB003
			150	0.32	150RB003			
32	0.85	32RB001	150	0.65	150RB004	1000	0.02	1000RB001
32	1.62	32RB002				1000	0.042	1000RB002
32	2.68	32RB003				1000	0.10	1000RB003

5.4 Design Tips

- The larger the chosen value of the inductor L , the smaller the current ripple ΔI_L . However this results in a physically larger and heavier inductor.
- Choose ΔI_L so that it is not too big. The suggestions proposed by us have adequately small current ripple along with physically small inductor size. With a

larger current ripple, the voltage ripple of the output voltage V_{out} becomes clearly bigger while the physical size of the inductor decreases marginally.

- The higher the chosen value of the switching frequency f , the smaller the size of the inductor. However the switching losses of the transistor also become larger as f increases.
- The smallest possible physical size for the inductor is achieved when $\Delta I_L = 2I_{in}$ at V_{in_min} . However, the switching losses at the transistors are at their highest in this state.

5.5 Capacitor Design

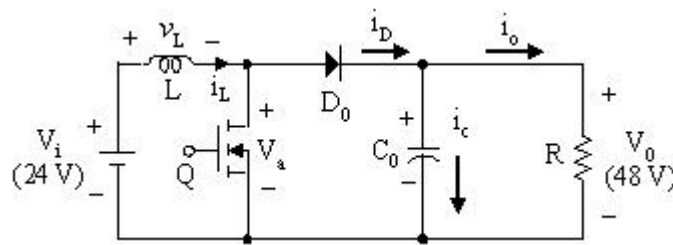


Figure 7 A conventional boost converter

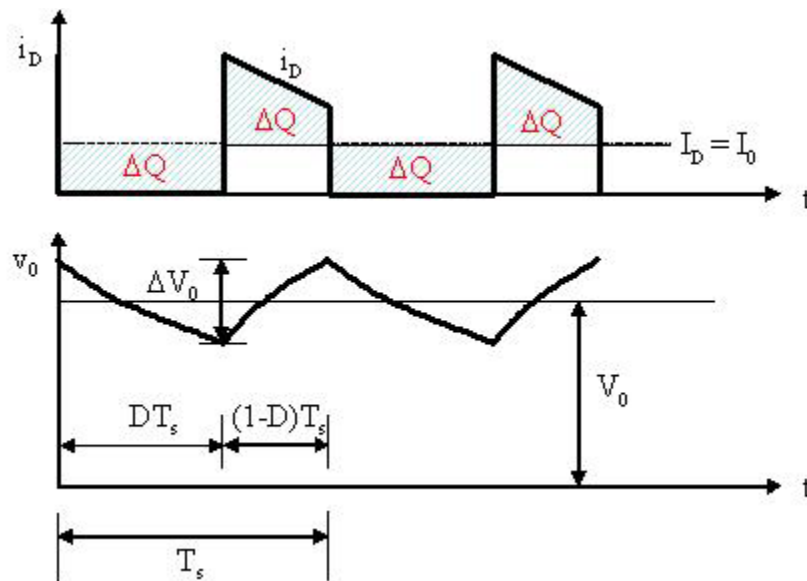


Figure 8 Output voltage ripple

Figure 1 and Figure 1 show a conventional boost converter and the output voltage ripple and diode current, respectively. Assuming that the diode current (i_D) is a square wave form, we can calculate the peak diode current ($I_{D, peak}$) for a duty ratio of 0.5

$$I_{D, peak} = \frac{I_0}{D} = \frac{I_0}{0.5} = 10 \text{ A}$$

where $I_0 = P/V_0 = 240/48 = 5 \text{ A}$ and the RMS diode current ($I_{D, rms}$) is

$$I_{D, rms} = I_{D, peak} \cdot \sqrt{D} = 10 \cdot \sqrt{0.5} = 7.07 \text{ A}$$

Therefore, the RMS capacitor current ($I_{c, rms}$) is given by

$$I_{c, rms} = \sqrt{I_{D, rms}^2 - I_0^2} = \sqrt{7.07^2 - 5^2} = 5 \text{ A}$$

Also, the output voltage ripple can be obtained using the following equation

$$\Delta V_0 = \frac{\Delta Q}{C} = \frac{I_{c, rms} D T_s}{C}$$

Putting the values below into the above equation, the capacitance is

$$D = 0.5, T_s = 1/(20 \times 10^3) \text{ sec}, I_{c, rms} = 5 \text{ A}, \Delta V_0 = 48 \text{ mV}.$$

$$\therefore C = \frac{\Delta Q}{\Delta V_0} = \frac{I_{c, rms} D T_s}{\Delta V_0} = \frac{5 \cdot 0.5}{48 \times 10^{-3} \times 20 \times 10^3} = 2600 \mu F$$

Therefore, the capacitor should be selected based on the rated voltage, the rated ripple current, and the capacitance calculated above. Finally, we chose the rated voltage (100 V) considering over-voltage by a parasite inductance, the rated ripple current (at least 5 A), and the capacitance (at least 2600 μF).

Next, we have to choose the supplier that manufactures the capacitors with the above specifications. In this case, we choose the Aluminum Electrolyte Capacitor manufactured by Sam Young Electronics Co., and the list of products is given below.

Table 2 List of Aluminum Electrolyte Capacitors

LIST OF PRODUCTS

● MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS

Series		Applications	Load life Time (Hrs)	Miniature	Standard type	Low impedance	Long life	Solvent-proof	Terminal type	Rated voltage range (Vdc)	Capacitance range (μF)	
Surface mount	General Purpose	MV	5.5 ~ 10.5mm max.height	85°C 1000~2000hrs	●			●	SMD	4~50	0.1~1,000	
		MVG	5.5 ~ 6.0 mm max.height, downsized	85°C 2000hrs	●			●	SMD	4~50	0.1~220	
		MVK	5.5 ~ 10.5 mm max.height	105°C 1000~2000hrs		●		●	●	SMD	6.3~50	0.1~1,000
		MVY	5.5 ~ 10.5 mm max.height, Low Imp	105°C 1000~2000hrs			●	●	●	SMD	6.3~35	4.7~470
	Bi-Polar	MV-BP	5.5 mm max.height, Bi-polar	85°C 2000hrs					●	SMD	4~50	0.1~47
		MVK-BP	6.0 mm max.height, Bi-polar	105°C 1000hrs				●	●	SMD	6.3~50	0.1~47
Miniature	Low Profile	SRE	5mm height	85°C 2000hrs		●			Radial	4~50	0.1~330	
		SRA	7mm height	85°C 2000hrs		●			Radial	4~63	0.1~220	
		GSA (NEW)	7mm height, downsized	85°C 2000hrs	●					Radial	6.3~50	0.1~220
		KRE	5mm height, Wide temp	105°C 1000hrs		●	●		●	Radial	4~50	0.1~100
		KMA	7mm height	105°C 1000hrs		●	●		●	Radial	4~63	0.1~150
		SR	9~16mm height	85°C 2000hrs	●					Radial	4~50	22~1,000
	General Purpose	SHL	General	85°C 2000hrs	●	●				Radial	6.3~450	0.1~15,000
		MHA (NEW)	High capacitance	85°C 2000hrs	●					Radial	160~450	1~820
		KMG	General	105°C 1000~2000hrs	●	●			●	Radial	6.3~450	0.1~15,000
		NHA (NEW)	High capacitance	105°C 1000~2000hrs	●					Radial	160~450	1~680
	Low Leakage	SRA-LL	Height 7mm	85°C 2000hrs	●					Radial	6.3~50	0.1~100
		LL	General	85°C 2000hrs		●				Radial	6.3~100	0.1~4,700
	Bi-polar	SRE-BP	5mm height	85°C 1000hrs	●					Radial	4~50	0.1~47
		SRA-BP	7mm height	85°C 2000hrs	●					Radial	6.3~50	0.1~47
		SHL-BP	General	85°C 2000hrs		●				Radial	6.3~250	0.47~6,800
		KMG-BP	General, Wide temp	105°C 1000hrs		●		●	●	Radial	6.3~250	0.47~6,800
		SSP	Speaker Network	85°C 2000hrs		●				Radial	25~63	1~100
		SSA	Horizontal deflection	85°C 1000hrs		●				Radial	25, 50	2.2~10
		KSA	Horizontal deflection	105°C 1000hrs				●	●	Radial	25, 50	2.2~10

	Low E.S.R	KXL	Low Imp., General	105°C 1000~2000hrs	●	●	●	Radial	6.3~50	10~10,000
		NXA	Low Imp., Long life	105°C 2000~5000hrs		●	●	Radial	6.3~35	4.7~15,000
		LXV	Low Imp., Long life	105°C 2000~5000hrs		●	●	Radial	6.3~50	18~15,000
		LXZ	Low Imp., Long life, Downsized	105°C 2000~5000hrs		●	●	Radial	6.3~35	33~18,000
		NXB	Ultra Low Imp., Long life,	105°C 2000~5000hrs		●	●	Radial	6.3~100	3.3~6,800
	High - Reliability	KMF	High ripple	105°C 2000hrs	●	●	●	Radial	160~450	3.3~330
		KMX	Long life, High ripple	105°C 5000hrs	●	●	●	Radial	160~450	3.3~330
		LXA	Long life	105°C 5000hrs~7000hrs			●	Radial	10~63	0.47~4,700
	Special Application	AHS	Audio grade, downsized	85°C 2000hrs	●			Radial	10~100	0.1~10,000
		PHL	For photo flash	5~35°C 5000 times				Radial	330	60~200

● LARGE SIZED ALUMINUM ELECTROLYTIC CAPACITORS

Series		Applications	Load life Time (Hrs)	Miniature	Standard type	Low impedance	Long life	Solvent-proof	Terminal type	Rated voltage range (Vdc)	Capacitance range (μF)
PCB Terminal Type	General Purpose	SMH	General	85°C 2000hrs	●				Pin	100~500	56~82,000
		RDA	Miniature	85°C 2000hrs	●				Pin	160~450	68~2,700
		KMH	General, Wide temp	105°C 2000hrs	●		●		Pin	16~450	56~47,000
		TDA	Miniature	105°C 2000hrs	●		●		Pin	160~450	56~2,200
		SLT	20mm height	85°C 2000hrs	●				Pin	160~400	47~560
		KLT	20mm height	105°C 2000hrs	●		●		Pin	160~400	47~560
	Special Application	LXG	Miniature long life	105°C 5000hrs	●		●		Pin	10~400	56~47,000
		KLG	No spark with DC overvoltage	105°C 2000hrs	●				Pin	200, 400	47~1,500
		DL	General Audio	85°C 2000hrs	●	●			Pin	50~100	3,300~22,000
Screw-Bolt Terminal Type	General Purpose	AHS	Hi-Fi Audio Miniature	85°C 2000hrs	●				Pin	50~100	3,300~22,000
		SME	General	85°C 2000hrs	●				Screw	10~250	560~680,000
	For Inverter	KMH	General, wide temp.	105°C 2000hrs	●		●		Screw	10~400	180~680,000
		RWA	High ripple	85°C 2000hrs	●				Screw	350, 400	270~10,000
	Special Application	RWF	High ripple, long life	85°C 5000hrs			●		Screw	350~450	2,700~15,000
		PH	For Photo Flash	5~35°C 5,000 times					Pin/	330	165~2,000
DH	For Welding	40°C 1,000,000 times					Screw	315, 475	100~330		


In general, the price of capacitors is determined by the order of rated voltage, capacitance, maximum permissible ripple currents, maximum permissible temperature, and ESR (Equivalent Series Resistance). Therefore, designers have to choose the optimal type that can satisfy the requirements such as cost, permissible temperature, size, and ESR, etc. In this case, we selected KMH series used for General Purpose from the above catalog.

The below table shows only the information required for selection of our capacitor in full data sheets of KMH series. From “table of permissible ripple current”, we have to consider a factor by switching frequency and case diameter when we calculate the maximum permissible currents. So, we selected $\Phi 35$ of rated voltage 100 V, and we have to multiply a factor (1.3) by the permissible ripple current (from table of “rating of KMH series”) because the switching frequency is 20 kHz.

Table 3 Data sheet of KMH Series

KMH Series

●
105°C 2,000Hrs assured



- Non-slovent proof.
- Wide Temperature Range

KME

→

KMH

Downsized

SPECIFICATIONS

Item	Characteristics										
Rated Voltage Range	10 ~ 100 V _{DC}	160~ 400 V _{DC}									
Operating Temperature Range	-40 ~ + 105 °C	-25 ~ + 105 °C									
Capacitance Tolerance	±20% (M) (at 20 °C ,120 Hz)										
Leakage Current	I = 0.02CV (μA) or 3mA, whichever is smaller. Where, I:leakage current(μA) C:Nominal capacitance(μF) V:Rated voltage(V _{DC}) (at 20 °C,5 minutes)										
Dissipation Factor (Tanδ)	Tanδ shall not exceed the values shown in the RATINGS. (at 20 °C,120Hz)										
Temperature Characteristics (Capacitance change)	<table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <tr> <td style="font-size: 0.8em;">Rated Voltage(VDC)</td> <td style="font-size: 0.8em;">10~100</td> <td style="font-size: 0.8em;">160~400</td> </tr> <tr> <td style="font-size: 0.8em;">Z(-25°C)/Z(20°C)</td> <td style="font-size: 0.8em;">-</td> <td style="font-size: 0.8em;">≥ 0.7</td> </tr> <tr> <td style="font-size: 0.8em;">Z(-40°C)/Z(20°C)</td> <td style="font-size: 0.8em;">≥ 0.6</td> <td style="font-size: 0.8em;">-</td> </tr> </table> (at 120Hz)		Rated Voltage(VDC)	10~100	160~400	Z(-25°C)/Z(20°C)	-	≥ 0.7	Z(-40°C)/Z(20°C)	≥ 0.6	-
Rated Voltage(VDC)	10~100	160~400									
Z(-25°C)/Z(20°C)	-	≥ 0.7									
Z(-40°C)/Z(20°C)	≥ 0.6	-									
Load Life	The following specifications shall be satisfied when capacitors are restored 20°C after the rated working voltage applied for 2,000 hours at 105 °C. Capacitance change ≤ ± 20% of the initial value Tanδ ≤ 200% of the initial specified value Leakage current ≤ The initial specified value										

PERMISSIBLE RIPPLE CURRENT

Frequency Multiplying Factor

Rated Voltage (VDC)	Case Diameter (mm)	Frequency(Hz)				
		60	120	300	1K	10K~
10~50	Φ30 ~ Φ89	0.95	1.00	1.03	1.05	1.09
63	Φ35	0.90	1.00	1.06	1.10	1.08
	Φ50 ~ Φ89	0.95	1.00	1.03	1.05	1.09
100	Φ35	0.82	1.00	1.12	1.22	1.30
	Φ50	0.90	1.00	1.06	1.10	1.18
	Φ63.5 ~ Φ89	0.95	1.00	1.03	1.05	1.09
160~250	Φ35	0.80	1.00	1.19	1.34	1.46
	Φ50 ~ Φ63.5	0.81	1.00	1.14	1.26	1.36
	Φ76 ~ Φ89	0.82	1.00	1.12	1.22	1.30
315~400	Φ35 ~ Φ89	0.80	1.00	1.19	1.34	1.46



RATINGS OF KMH Series

VDC μF	100(2A)			160(2C)			200(2D)			250(2E)		
180												
220												
270										A5	0.8	0.15
330							A5	0.9	0.15	A5	0.9	0.15
390							A5	1.0	0.15	A5	1.0	0.15
470							A5	1.1	0.15	A5	1.1	0.15
560				A5	1.2	0.15	A5	1.2	0.15	A5	1.2	0.15
680				A5	1.3	0.15	A5	1.3	0.15	A6	1.4	0.15
820				A5	1.4	0.15	A5	1.4	0.15	A8	1.6	0.15
1,000				A5	1.6	0.15	A6	1.7	0.15	A8	1.6	0.20
1,200				A6	1.9	0.15	A6	1.9	0.15	A8	1.8	0.20
1,500				A6	2.1	0.15	A8	2.3	0.15	A10	2.1	0.20
1,800	A5	2.7	0.10	A8	2.5	0.15	A8	2.5	0.15	A12	2.5	0.20
2,200	A5	3.0	0.10	A8	2.8	0.15	A10	2.5	0.15	A12	2.5	0.20
2,700	A6	3.5	0.10	A10	3.3	0.15	A12	3.6	0.15	C10	3.5	0.20
3,300	A8	4.2	0.10	A12	3.8	0.15	C8	4.1	0.15	C12	4.2	0.20
3,900	A8	4.2	0.12	8	3.8	0.20	C10	4.9	0.15	C12	4.6	0.20
4,700	A10	5.0	0.12	C10	4.6	0.20	D10	5.3	0.20	D12	5.7	0.20
5,600	A10	5.4	0.12	C10	5.1	0.20	D10	5.8	0.20	D12	6.3	0.20
6,800	A12	5.8	0.15	C12	6.1	0.20	D12	6.9	0.20	E12	7.7	0.20
8,200	C8	6.4	0.15	D10	7.0	0.20	D12	7.6	0.20	E12	8.4	0.20
10,000	C10	7.8	0.15	D12	8.4	0.20	E12	9.3	0.20	E14	10.0	0.20
12,000	C12	9.3	0.15	E10	9.4	0.20	E12	10.2	0.20	F14	11.9	0.20
15,000	C12	10.4	0.15	E12	11.4	0.20	E12	10.2	0.20	F14	11.9	0.20
18,000	D10	10.4	0.20	E14	13.4	0.20	F14	13.1	0.25			
22,000	D12	12.5	0.20	F14	14.5	0.25						
27,000	E12	13.7	0.25	F14	16.0	0.25						
33,000	E12	15.2	0.25									
39,000	E14	16.1	0.30									
47,000	F14	19.3	0.30									
56,000	F14	21.1	0.30									



▲ Tanδ

▲ Permissible Ripple Current(Arms / 105°C, 120Hz)

▲ Case Code

Based on the above table (“Rating of KMH Series”) and our requirements, even if we can choose any capacitor above 3300 $\mu\text{F}/4.2\text{ A}$ in 100 V rated voltage, we selected a 3900 $\mu\text{F}/4.2\text{ A}$ because we have to consider ESR.

– **Capacitance:** 3900 μF > 2600 μF

– **Maximum permissible ripple current:** $4.2 \times 1.3 = 5.46\text{Arms}$ > 5 A

Therefore, our design is reasonable by conditions above.

Bibliography

1. N. Mohan, W. P. Robbin, and T. Undeland, Power Electronics: Converters, Applications, and Design, 2nd Edition, 1995.
2. Hoft, R., Semiconductor Power Electronics, Van Nostrand Reinhold, 1986.
3. Design of switch mode power supplies,
http://henry.fbe.fh-darmstadt.de/smpps_e/smpps_e.asp