

# EE682 – Group Project Design

Prof. Ali Keyhani

Lecture on Design of a Static Switching

# Design Steps

1. Select a switching transistor;
2. Analyze to determine maximum steady state and transient device voltage and current over expected range of operating conditions;
3. Thermal analysis to establish the worst-case device junction temperature
4. Study transistor data sheet
  - Only worst-case data are published
  - Contacting application engineers of device manufacturers

# Low Frequency Design


## 1. Switching losses are small

- This is the case for static switch, choppers, buck converters
- Switching device is on and off for a short period

# Example
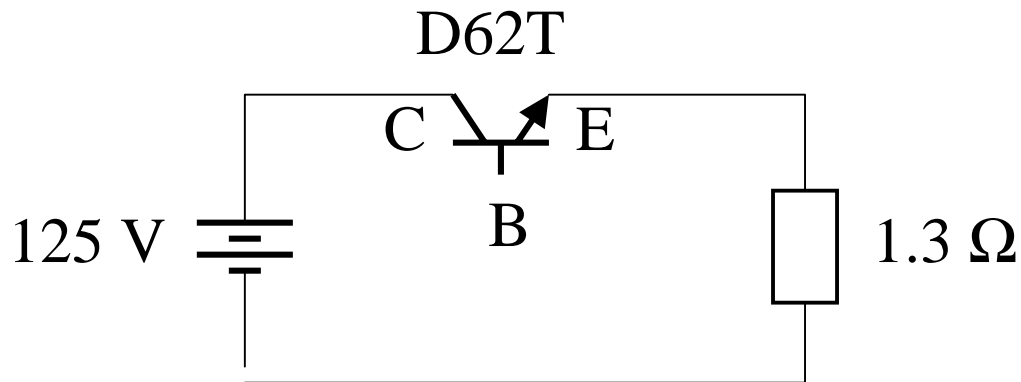
## Requirements:

- Supply voltage 125 V
- Load  $R = 1.3 \Omega$



Transistor selection:

D62T: 400-500 V switch, frequency of switching = 100 kHz

Is this a good selection?

# Example

No → It is not economical. Since D62T can switch of 400-500V.

However → It is a good choice since the thermal losses are low due to operating at 125 V.

## Assumptions:


- Off-state losses are small;
- Base drive losses are not very small, but they are considerable smaller than that of on-state;
- Base driver losses are neglected;
- Switch is on for a long time.

# Assumptions

1. No second breakdown limitation
2. Negligible off-state losses
3. Negligible base drive losses
4.  $V_{CE(sat)} = 1.2 \text{ V}$ ,  $I_{B1} = 20 \text{ A}$

$I_{B1}$  is the on-state drive current (see data sheets) with junction temperature of  $150^\circ\text{C}$

## On-state Circuit

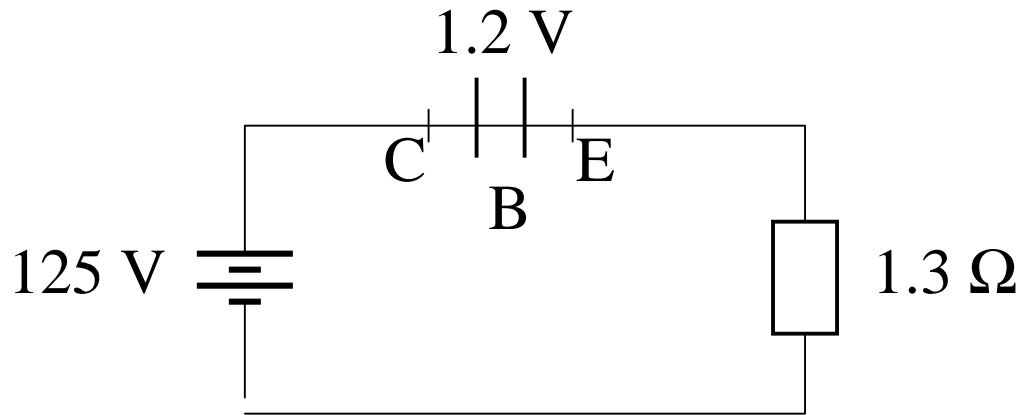

Continuous on-state losses ( $P_T$ ) in the switch is

$$P_T = \frac{125 - 1.2}{1.3} \times 1.2 = 114.28W$$

# On-state Circuit

From data sheet, the thermal resistance from junction-to-sink for double-sided cooling is  $0.14 \text{ }^\circ\text{C/W}$

The junction-to-sink temperature different is

$$\Delta T_{js} = R_{\theta js} \times P_T = 0.14 \times 114.28 = 16^\circ \text{C}$$



# Temperature rise

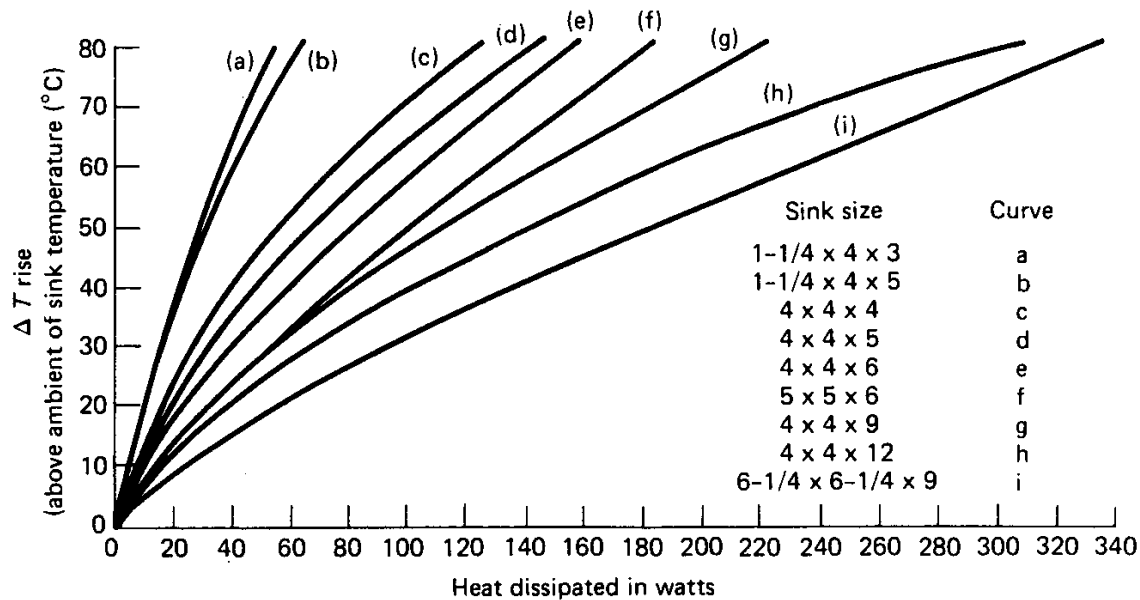


Fig. 2P-2. Standard heat sink ratings\* for natural convection—aluminum extrusion. \*Zinc-chromate converse coating. (From Westinghouse. Used with permission)

Fig 2P-2 indicates that with two of the smaller heat sinks, curve (b) for double-sided cooling, the sink-to-ambient temperature rise would be approximately 80°C with 114.28-W dissipation in switch.

# Temperature rise



Therefore with an ambient temperature of 54°C, the junction temperature ( $T_j$ ) is

$$\begin{aligned} T_j &= T_A + \Delta T_{js} + \Delta T_{sA} \\ &= 54^\circ + 16^\circ + 80^\circ = 150^\circ C \end{aligned}$$

$$T_j \leq 150^\circ C \quad \text{Design OK.}$$
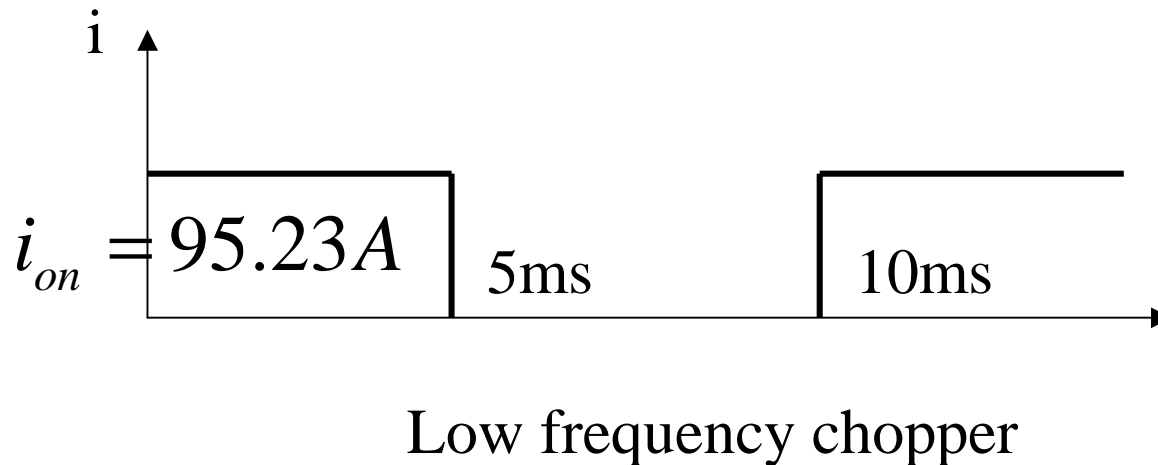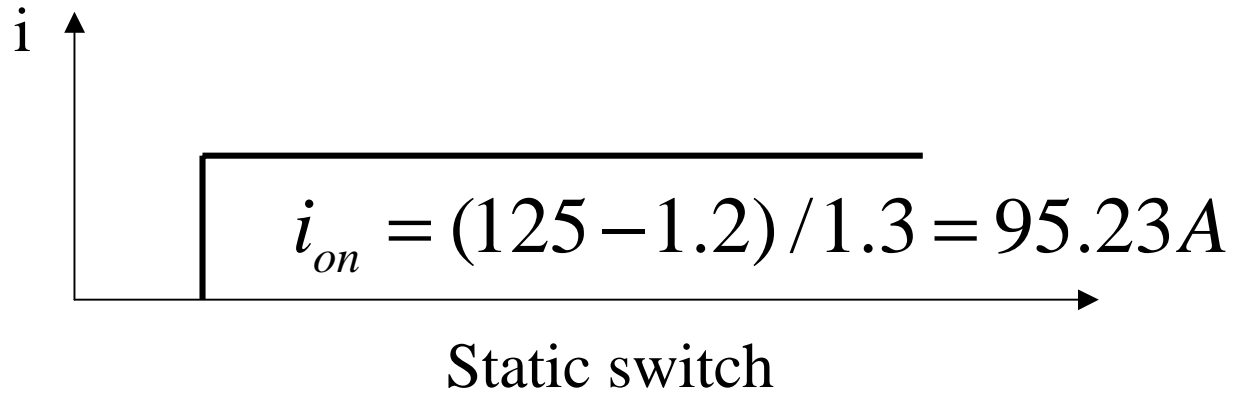
# Switching Losses

Assume an on-period of 10 ms and a 50-percent duty cycle.



# Switching Losses

The switching losses for chopper is

$$P_T = V_{CE(sat)} \times I_{on} \times \frac{t_{on}}{T}$$
$$= 1.2 \times 95.23 \times \frac{1}{2} = 57.14W$$

The junction-to-sink “average” temperature is


$$\Delta T_{js} = R_{\theta js} \times P_T = 0.14 \times 57.4 = 8^\circ C$$

# Transient Variation of Junction Temperature


Calculation of the transient variation of junction temperature:

A step-input of power equal to the on-state loss occurs at the beginning of each switching period, and an equal but negative step-input of power takes place at the end of each on-interval.
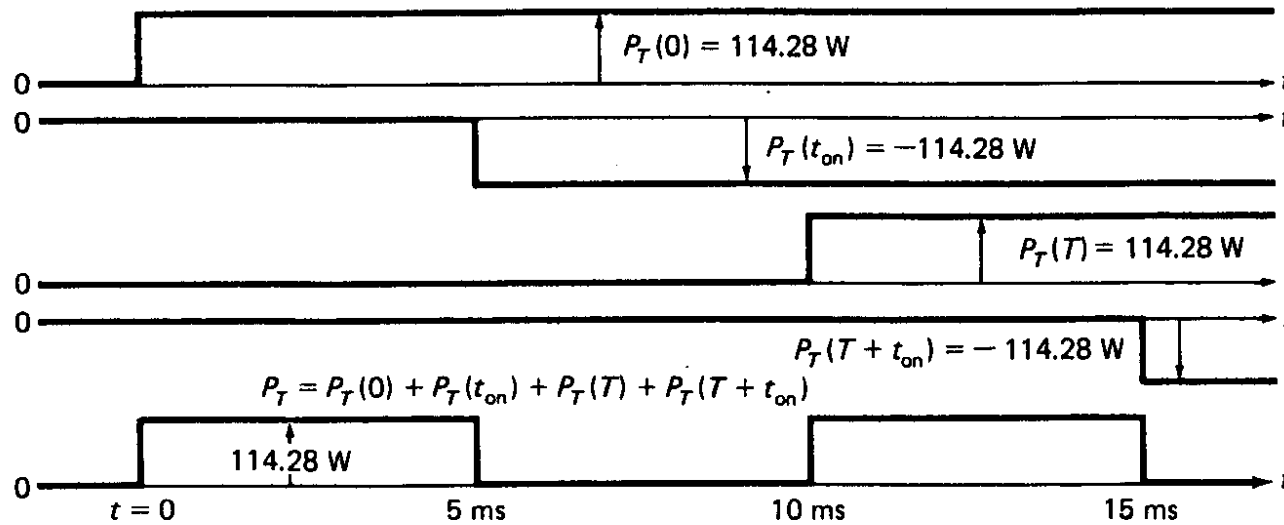
# Transient Variation of Junction Temperature



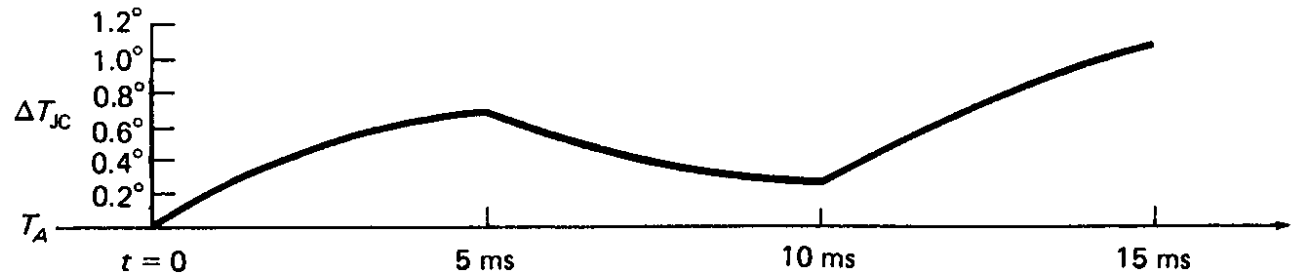(a) Equivalent step-function representation of transistor dissipation.



(b) Transient variation in  $\Delta T_{JC}$

Fig. 2-15. Initial variation in  $\Delta T_{JC}$ . (a) Equivalent step-function representation of transistor dissipation; (b) transient variation in  $\Delta T_{JC}$ .

# Transient Variation of Junction Temperature

The initial transient variation in the junction temperature, which is calculated as:

$$\begin{aligned}\Delta T_{jC(1ms)} &= Z_{\theta jC(1ms)} \times 114.28W \\ &= 0.003^\circ C / W \times 114.28W = 0.34^\circ C\end{aligned}$$

$$\begin{aligned}\Delta T_{jC(3ms)} &= Z_{\theta jC(3ms)} \times 114.28W \\ &= 0.0045^\circ C / W \times 114.28W = 0.51^\circ C\end{aligned}$$

## Transient Variation of Junction Temperature

$$\Delta T_{jC(5ms)} = 0.006^\circ C / W \times 114.28W = 0.69^\circ C$$

$$\begin{aligned}\Delta T_{jC(8ms)} &= [Z_{\theta jC(8ms)} - Z_{\theta jC(3ms)}] \times 114.28W \\ &= (0.0075 - 0.0045)^\circ C / W \times 114.28W = 0.34^\circ C\end{aligned}$$

$$\begin{aligned}\Delta T_{jC(10ms)} &= [Z_{\theta jC(10ms)} - Z_{\theta jC(5ms)}] \times 114.28W \\ &= (0.0085 - 0.006)^\circ C / W \times 114.28W = 0.29^\circ C\end{aligned}$$

Fig 2-15 (b) shows the transient temperature.

The steady state junction temperature may be obtained by continuously the process till reaching steady state.