

Lecture # 5C

EE740

A. Kayhani

Derivation of LTC Transformer PI-Model
(No phase shifter)

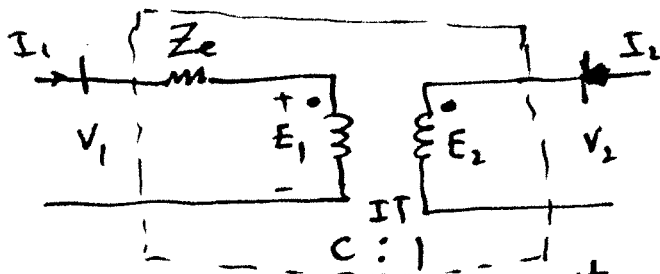


Fig. 1 P.U. Eq. circuit
LTC Trans.

Note $E_1 = CE_2$
 $I_1 = -\frac{C}{I_2}$

where $a = \frac{N_1}{N_2}$, $b = \frac{V_{b1}}{V_{b2}}$, $C = \frac{a}{b}$, C is real no-phase shifter

Assume two-port network

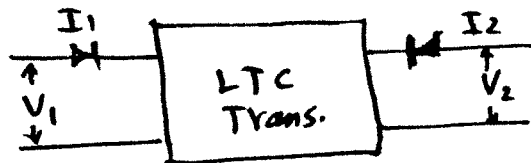


Fig. 2

$$I_1 = y_{11} V_1 + y_{12} V_2$$

where $y_{21} = y_{12}$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

The above equation can be represented by

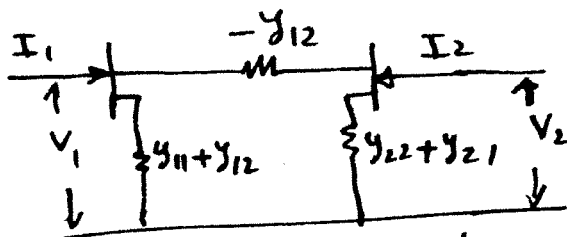


Fig. 3 PI-Eq. circuit
for LTC Trans (No-phase shifter)

The parameters of Fig. 3 can be calculated in the following way:

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{Z_e} = Y_e$$

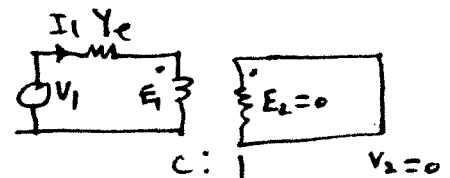


Fig. 1 when $V_2 = 0$


$V_2 = 0$, $E_2 = 0 \Rightarrow E_1 = 0$

$$V_1 = I_1 Z_e \Rightarrow I_1 = \frac{V_1}{Z_e}$$

Therefore $g_{11} = Y_e = \frac{1}{Z_e}$

$$g_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

With $V_1=0$, Fig. 1 is

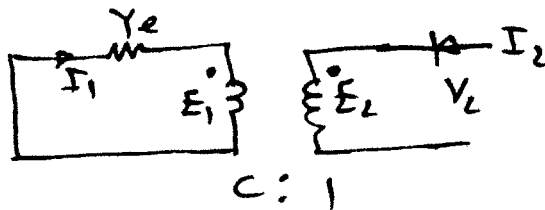

$$E_1 = c E_2 \quad E_2 = V_2 \quad \therefore E_1 = c V_2$$

$$I_1 = -E_1 Y_e$$


To cal. g_{12} , we need to cal. I_1 in terms of V_2

$$I_1 = -c V_2 Y_e \quad \therefore g_{12} = \frac{I_1}{V_2} = -c Y_e$$

To cal. g_{21} , we need to short V_2 .

$$g_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

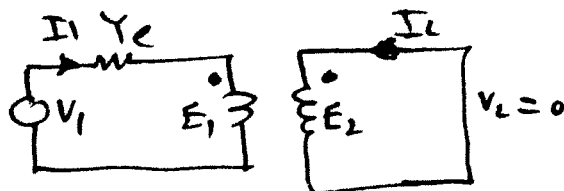With $V_2=0$, Fig. 1 can be represented as:



$$V_2=0, \therefore E_2=0 \quad \therefore E_1=0$$

$$V_1 = I_1 Z_e = \frac{I_1}{Y_e} \quad \text{or} \quad I_1 = V_1 Y_e$$

$$I_2 = -c I_1$$


To cal. y_{21} , we need to cal. I_2 in terms of V_1

$$I_2 = -c V_1 Y_e \quad \therefore \quad y_{21} = \frac{I_2}{V_1} = -c Y_e$$

To cal. y_{22} , we need to short V_1 (i.e. $V_1 = 0$)

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

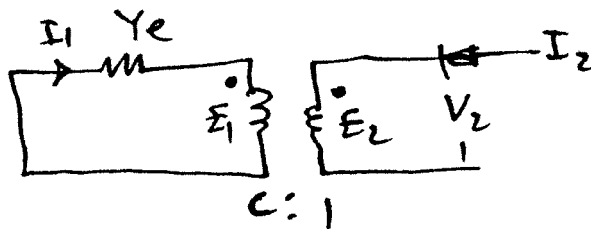With V_1 shorted, Fig. 1 can be represented as:



$$V_2 = E_2, \quad E_1 = c E_2 \text{ or } E_1 = c V_2$$

$$I_1 = -Y_e E_1$$

Substitute for E_1 . $I_1 = -Y_e c V_2$

$$I_2 = -c I_1$$

Substitute for I_1 from the above

$$I_2 = -c (-Y_e c V_2) = c^2 Y_e V_2$$

$$y_{22} = \frac{I_2}{V_2} = c^2 Y_e$$

4

Recall our PI EQ. CKT for LTC transformer

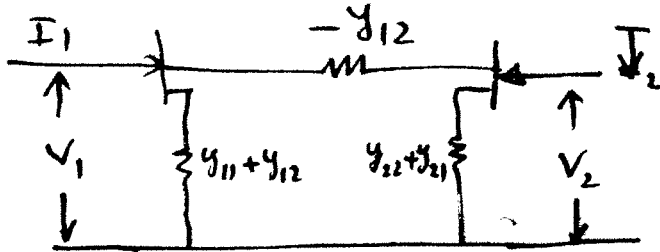


Fig. 4 P.U. PI EQ. Circuit
For LTC Trans

where $y_{12} = y_{21} = -c Y_e$ $Y_e = \frac{1}{Z_e}$

$$y_{11} = Y_e$$

$$y_{22} = c^2 Y_e$$

Therefore, the parameters of Fig. 4 are as follows:

$$y_{11} + y_{12} = Y_e + (-c Y_e) = Y_e(1 - c)$$

$$y_{22} + y_{21} = c^2 Y_e + (-c Y_e) = Y_e(c^2 - c)$$


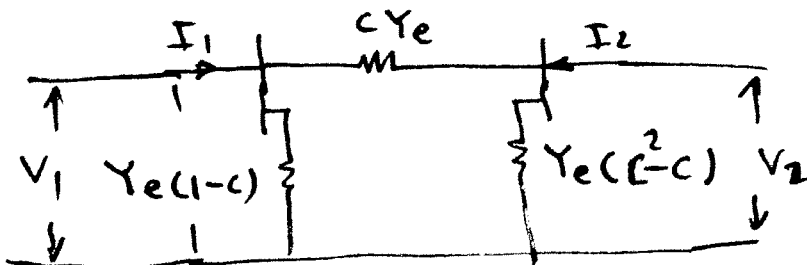
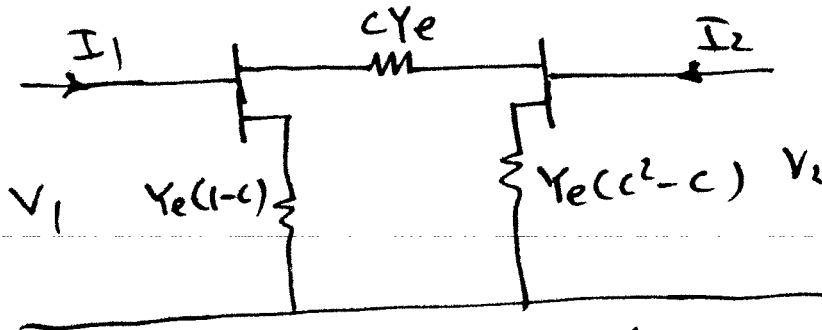



Fig. 5 P.U. PI EQ. Circuit
For LTC Trans

Summary

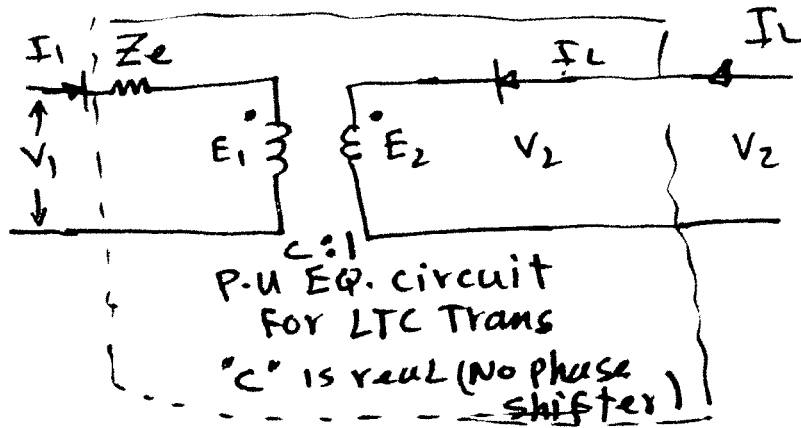

PI EQ. circuit
For LTC Trans.
"c" is real No phase shifter)

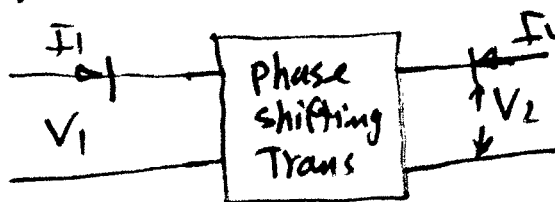Note: For phase shifting transformers c is complex and $y_{12} \neq y_{21}$. We can not synthesize an equivalent circuit with real R, L, c elements. However, we may represent the phase shifting transformer in our network impedance diagram as a two-port network with two inputs and outputs.



$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$