

Z-BUS Lecture #2

EE740
Zbus Lecture #17

Summary Zbus impedance matrix building Algorithms

1. Addition of a branch (radial line) from bus "p" to bus "q"

$$Z_{BUS \text{ old}} \quad n \times n$$

$$Z_{qi} = Z_{pi}$$

$$i = 1, 2, \dots, n+1$$

$$i \neq q$$

$$Z_{qq} = Z_{pp} + \bar{z}_{pq} \quad \text{or} \quad Z_{qq} = Z_{pp} + \bar{z}_{pq}$$

$$Z_{BUS \text{ new}} \quad (n+1) \times (n+1)$$

q: Added bus


p: existing bus "p"
(but not the ref. bus)

2. Addition of a branch from ref. bus (i.e. ground bus "0") to bus "q"

$$Z_{qi} = 0$$

$$Z_{qq} = \bar{z}_{pq}$$
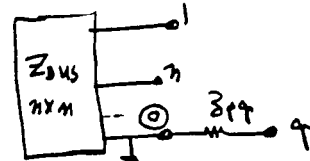
$$Z_{BUS \text{ new}} \quad (n+1) \times (n+1)$$



3. Addition of a branch from bus "q" to reference bus "0"

$$Z_{qq} = \bar{z}_{pq}$$

4. Addition of a link (loop) from bus "q" to ref. bus "0"

step 1. Add a link from bus "q" to fictitious bus "l"

$$Z_{BUS \text{ with } l} \rightarrow (n+1) \times (n+1)$$

$$Z_{li} = -Z_{qi} \quad i = 1, 2, \dots, n+1 \quad i \neq l$$

step 2. $Z_{ll} = -Z_{ql} + \bar{z}_{pq}$
Eliminate bus "l"

$$Z_{BUS \text{ without } l} = Z_{nn} - Z_{nl} Z_{ll}^{-1} Z_{ln}$$

5. Addition of a link from bus "p" to bus "q".

Step 1: Add a link from bus "p" to bus "l"

$$Z_{li} = Z_{pi} - Z_{qi} \quad \begin{matrix} i=1, 2, \dots, n+1 \\ i \neq l \end{matrix}$$

$$Z_{ll} = Z_{pl} - Z_{ql} + Z_{pp}$$

or $Z_{ll} = Z_{pp} + Z_{qq} - 2Z_{pq} + Z_{pp}$

Step 2: Eliminate the bus "l"

$$Z_{BUS \text{ with } l} = \begin{bmatrix} Z_{nn} & Z_{nl} \\ Z_{ln} & Z_{ll} \end{bmatrix}$$


$$Z_{BUS \text{ without } l} = Z_{nn} - Z_{nl} Z_{ll}^{-1} Z_{ln}$$

\downarrow \downarrow \downarrow \downarrow
 $n \times n$ $n \times 1$ 1×1 $1 \times n$

Power system modeling

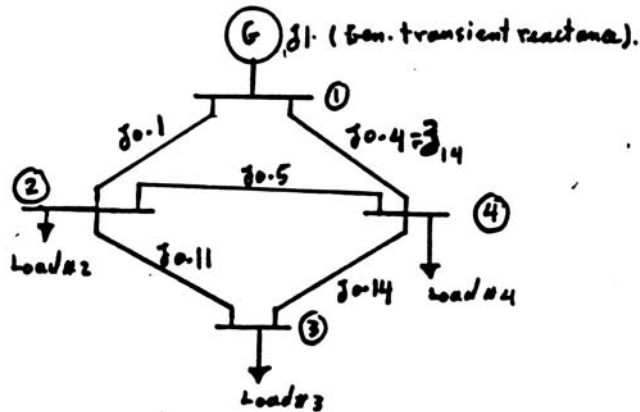1.8. Example. 1 Z_{BUS} Impedance matrix model using Z_{BUS} Algorithm.


Consider the single-line diagram of a balanced system.



Comments:

- Z_{BUS} matrix models are generally used for short circuit studies. For short circuit studies:
 - Loads are either neglected or the constant load impedance models are used.
 - The generators are represented by their transient or sub-transient reactances
 - Line charging capacitances could be represented but they are omitted.

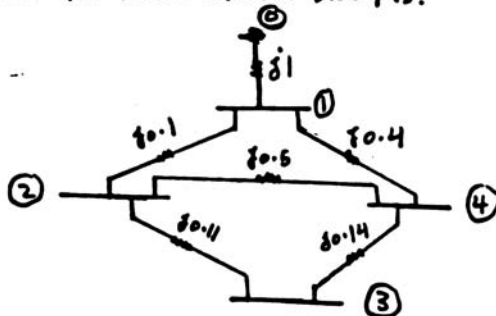Z_{BUS} model for short circuit study is:



(2)

4

(3)

Power system modeling

8-Example 1. Z_{bus} . Cont.

• Radial line from bus ② to bus ① (operator j is omitted)


$$Z_{bus} = 1 \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$



• Radial line from bus ② to bus ①

$$Z_{bus} = \frac{1}{2} \begin{bmatrix} 1 & 2 \\ 1 & 1 \end{bmatrix} \quad \begin{array}{l} Z_{pi} = Z_{pj} \\ p=1 \quad q=2 \\ Z_{21} = Z_{12} = 1 \\ Z_{11} = Z_{22} = 1 \end{array} \quad l=1,2$$

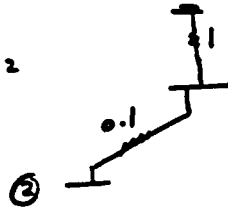
$$Z_{11} = Z_{22} + 3R_{1,2} = 1 + 0.1 = 1.1$$



• Radial line from bus ② to bus ④


$$Z_{bus} = \frac{1}{4} \begin{bmatrix} 1 & 2 & 4 \\ 1 & 1 & 1 \\ 1 & 1.1 & 1.1 \\ 1 & 1.1 & 1.6 \end{bmatrix}$$

↓
1.1 + 0.5 = 1.6

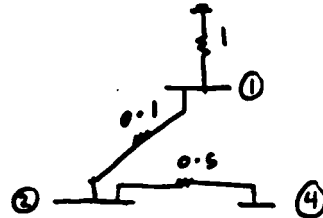

• Link from bus ④ to bus ①
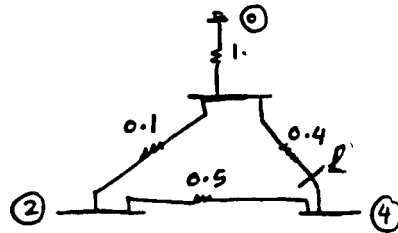
$$Z_{bus} = \frac{1}{4} \begin{bmatrix} 1 & 2 & 4 & L \\ 1 & 1 & 1 & 0 \\ 1 & 1.1 & 1.1 & -0.1 \\ 1 & 1.1 & 1.6 & -0.6 \\ 0 & -0.1 & -0.6 & 1 \end{bmatrix} \rightarrow \begin{array}{l} 1-1=0 \\ 1-1.1=-0.1 \\ 1-1.6=-0.6 \end{array}$$



$$Z_{LL} = Z_{11} + Z_{44} - 2Z_{14} + 3R_{1,4}$$

$$Z_{LL} = 1 + 1.6 - 2(1.1) + 0.4 = 1$$

$$Z_{Li} = Z_{pi} - Z_{qi} \quad p=1, q=4 \quad l=1,2,4$$

$$Z_{L1} = Z_{11} - Z_{41} = 1 - 1 = 0$$

$$Z_{L2} = Z_{12} - Z_{42} = 1 - 1.1 = -0.1$$

$$Z_{L4} = Z_{14} - Z_{44} = 1 - 1.6 = -0.6$$

~~27~~ 5

Power system modeling

8. Example 1. Z_{BUS} cont.

• Eliminate bus L

$$Z_{BUS} = \begin{matrix} & \begin{matrix} 1 & 2 & 4 & L \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 4 \\ L \end{matrix} & \begin{bmatrix} 1 & 1 & 1 & 0 \\ 1 & 1.1 & 1.1 & -0.1 \\ 1 & 1.1 & 1.6 & -0.6 \\ 0 & -0.1 & -0.6 & 1 \end{bmatrix} \end{matrix} \quad n \times m$$

$$Z_{BUS(\text{without } L)} = Z_{nn} - Z_{nl} Z_{ll}^{-1} Z_{ln}$$

$$Z_{BUS(\text{without } L)} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1.1 & 1.1 \\ 1 & 1.1 & 1.6 \end{bmatrix} - \begin{bmatrix} 0 \\ -0.1 \\ -0.6 \end{bmatrix} [1] \begin{bmatrix} 0 & -0.1 & -0.6 \end{bmatrix}$$

$$Z_{BUS(\text{without } L)} = \begin{matrix} & \begin{matrix} 1 & 2 & 4 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 4 \end{matrix} & \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1.09 & 1.04 \\ 1 & 1.04 & 1.24 \end{bmatrix} \end{matrix}$$

• Radial line from bus ③ to bus ②


$$Z_{BUS} = \begin{matrix} & \begin{matrix} 1 & 2 & 4 & 3 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 4 \\ 3 \end{matrix} & \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & 1.09 & 1.04 & 1.09 \\ 1 & 1.04 & 1.24 & 1.04 \\ 1 & 1.09 & 1.04 & 1.2 \end{bmatrix} \end{matrix}$$

$p=2$
 $q=3$

$$Z_{11} = Z_{11} + \delta = Z_{11} + \delta$$


$$Z_{21} = 1.09 + 0.11$$

$$Z_{33} = 1.20$$

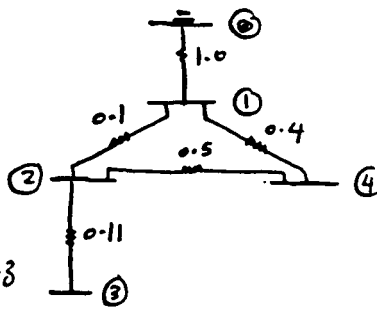

• Link from bus ③ to bus ④
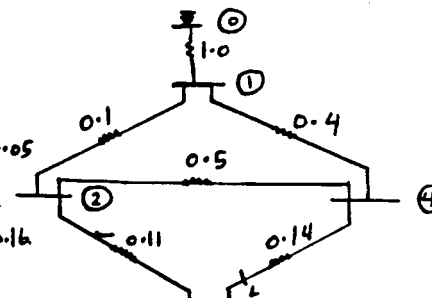
$$Z_{BUS} = \begin{matrix} & \begin{matrix} 1 & 2 & 4 & 3 & L \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 4 \\ 3 \\ L \end{matrix} & \begin{bmatrix} 1 & 1 & 1 & 1 & 0 \\ 1 & 1.09 & 1.04 & 1.09 & -0.05 \\ 1 & 1.04 & 1.24 & 1.04 & 0.2 \\ 1 & 1.09 & 1.04 & 1.2 & -0.16 \\ 0 & -0.05 & 0.2 & -0.04 & 0.5 \end{bmatrix} \end{matrix}$$



(38) 6

Power system Modeling


Example 1. Z_{BUS} Cont.

• Eliminate the bus 'L'

$$Z_{BUS} = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 1 & 1 & 1 & 1 \\ & 1-j0.5 & 1-j0.6 & 1-j0.7 \\ & & 1-j1.6 & 1-j1.4 \\ & & & 1-j1.5 \end{bmatrix} \end{matrix}$$

symmetric

Example #2.

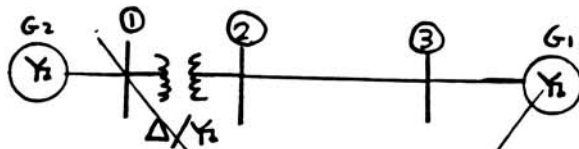

Given data:


For both generators.

$$Y = \begin{bmatrix} 0 & 1 & 2 \\ 10 & 0 & 0 \\ 0 & 10 & 0 \\ 0 & 0 & 10 \end{bmatrix}$$

Transformer:

$$y^o = 4$$

$$y^i = y^2 = 10 \Rightarrow$$

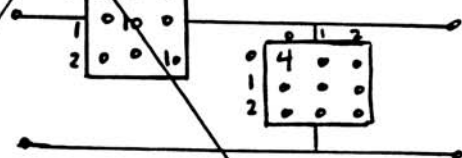

Transmission Line:

$$Z^{abc} = \begin{bmatrix} a & b & c \\ 0.3 & 0.1 & 0.1 \\ 0.1 & 0.3 & 0.1 \\ 0.1 & 0.1 & 0.3 \end{bmatrix}$$

$$Y^{abc} = \begin{bmatrix} a & b & c \\ 4.5 & -1.5 & -1.5 \\ -1.5 & 4 & -1 \\ -1.5 & -1 & 3.5 \end{bmatrix} = [Z^{abc}]^{-1}$$

From this we find.

$$Z^{o12} = T_s^{-1} Z^{abc} T_s = \begin{bmatrix} 0 & 1 & 2 \\ 0.5 & 0 & 0 \\ 0 & 0.2 & 0 \\ 0 & 0 & 0.2 \end{bmatrix}$$

$$Y^{o12} = \begin{bmatrix} 0 & 1 & 2 \\ 2 & 0 & 0 \\ 0 & 5 & 0 \\ 0 & 0 & 5 \end{bmatrix}$$