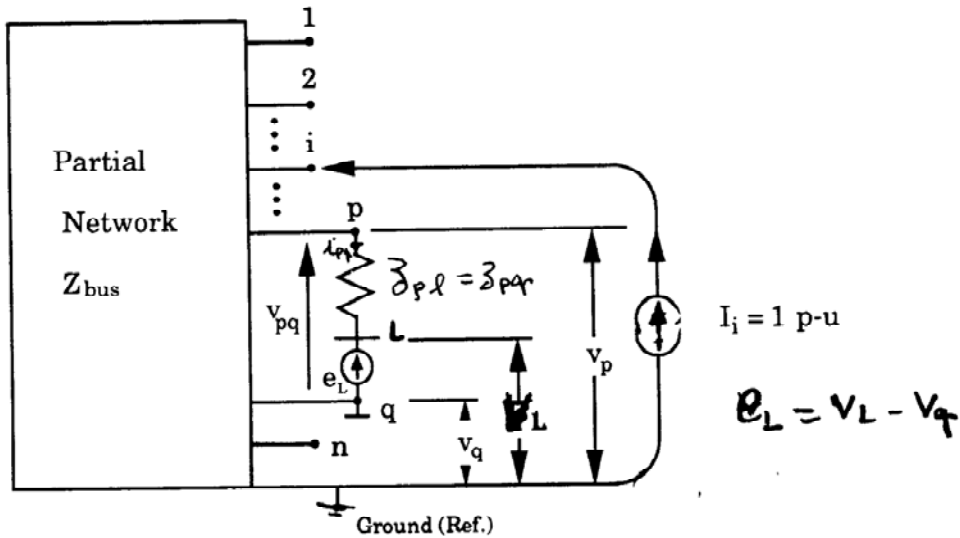


Z_{bus} impedance matrix algorithm

Addition of a link from ~~bus~~ existing bus "p" to the existing bus "q"



- Step 1. • Add a radial line from bus "p" to ~~bus~~ fictitious bus "l". This bus will be eliminated later.
 - Place a voltage source e_L between bus "l" and "q" such that $V_{pq} = 0$
 - Inject one amp at bus i ($I_i = 1$) and calculate the voltage at the lth node with respect to bus q.
- Step 2. Eliminate bus "l"

(B)

2

$$\begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_i \\ v_p \\ \vdots \\ v_q \\ v_n \\ e_L \end{bmatrix} = \begin{matrix} 1 \\ \vdots \\ p \\ \vdots \\ q \\ n \\ l \end{matrix} \begin{bmatrix} z_{11} & z_{1l} & z_{1p} & \dots & z_{1n} & z_{1l} \\ z_{21} & z_{2l} & z_{2p} & \dots & z_{2n} & z_{2l} \\ \vdots & \vdots & \vdots & \dots & \vdots & \vdots \\ z_{i1} & z_{il} & z_{ip} & \dots & z_{in} & z_{il} \\ z_{p1} & z_{pl} & z_{pp} & \dots & z_{pn} & z_{pl} \\ \vdots & \vdots & \vdots & \dots & \vdots & \vdots \\ z_{q1} & z_{ql} & z_{qp} & \dots & z_{qn} & z_{ql} \\ z_{n1} & z_{nl} & z_{np} & \dots & z_{nn} & z_{nl} \\ z_{l1} & z_{ll} & z_{lp} & \dots & z_{ln} & z_{ll} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ I_i = 1 \text{ A} \\ 0 \\ \vdots \\ 0 \\ 0 \end{bmatrix}$$

$$v_1 = z_{1i} I_i$$

$$v_2 = z_{2i} I_i$$

$$\vdots$$

$$v_i = z_{ii} I_i$$

$$\vdots$$

$$v_n = z_{ni} I_i$$

$$e_L = z_{li} I_i$$

$$\Rightarrow v_k = z_{ki} I_i \quad k=1, \dots, p, \dots, q, n$$

$$e_L = z_{li} I_i$$

note

$$e_L = v_{pq} - v_{pl} = v_p - v_q - v_{pl}$$
 since e_L is selected s.t. $l_{pq} = 0$, then the element \textcircled{p} to \textcircled{q} can be treated as a radial line

②

9

$$I_{pl} = I_{pq} = 0 = Y_{pl} V_{pl}$$

$$\therefore Y_{pl} = \frac{1}{Z_{pq}} \neq 0 \quad \therefore V_{pl} = 0$$

$$e_L = V_p - V_q$$

$$e_L = Z_{li} I_i \quad \text{since } I_i = 1 \quad Z_{li} = e_L$$

$$V_p = Z_{pi} I_i$$

$$Z_{pi} = V_p$$

$$V_q = Z_{qi} I_i$$

$$Z_{qi} = V_q$$

$$Z_{li} = Z_{pi} - Z_{qi}$$

$$i = 1, 2, \dots, n+1, i \neq l$$

The element Z_{ll} can be calculated by injecting a current at the l th bus with the bus q as reference and calculating the voltage at the l th bus with respect to bus q , $I_l = 1$, $I_i = 0$, $i = 1, \dots, n$

$$\begin{bmatrix} V_1 \\ \vdots \\ V_n \\ V_m \\ e_L \end{bmatrix} = \begin{matrix} P \\ \vdots \\ q \\ l \end{matrix} \begin{bmatrix} Z_{11} \\ \vdots \\ Z_{pq} \\ Z_{li} \end{bmatrix}$$

$$\begin{matrix} P \\ \vdots \\ q \\ l \end{matrix} \begin{bmatrix} Z_{1l} \\ Z_{2l} \\ \vdots \\ Z_{ll} \\ Z_{ll} \end{bmatrix} \begin{bmatrix} 0 \\ \vdots \\ 0 \\ I_l = 1 \end{bmatrix}$$

$$V_1 = Z_{1l} I_L$$

$$\vdots$$

$$V_n = Z_{nl} I_L$$

$$\vdots$$

$$e_L = Z_{ll} I_L$$

$$\Rightarrow \begin{cases} V_k = Z_{kl} I_L \\ e_L = Z_{ll} I_L \end{cases}$$

$$k = 1, \dots, n$$


①

The current in the element p-l is

$$I_{pl} = -I_l = -1$$

$$I_{pl} = y_{pq} V_{pl} = -1$$

$$V_{pl} = -\frac{1}{y_{pq}} = -Z_{pq}$$

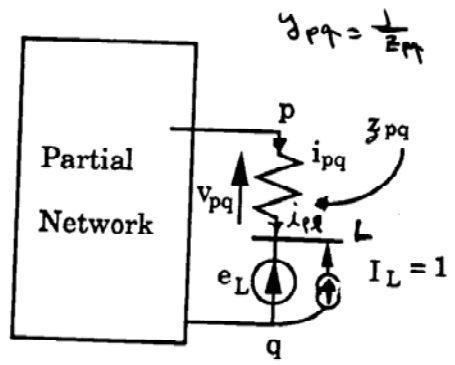

Recall

$$e_L = V_p - V_q - V_{pl}$$

↓

$$e_L = Z_{LL} I_L$$

$$V_p = Z_{pl} I_L$$

$$V_q = Z_{ql} I_L$$

$$V_{pl} = -Z_{pq}$$

$$Z_{LL} = Z_{pl} - Z_{ql} + Z_{pq}$$

Note $Z_{li} = Z_{pi} - Z_{ql}$

$$\therefore Z_{pl} = Z_{pp} - Z_{qp}$$

$$Z_{ql} = Z_{pq} - Z_{qq}$$

$$Z_{pl} - Z_{ql} = Z_{pp} - Z_{qp} - Z_{pq} + Z_{qq}$$

$$= Z_{pp} + Z_{qq} - 2Z_{pq}$$

$$\therefore Z_{LL} = Z_{pp} + Z_{qq} - 2Z_{pq} + Z_{pq}$$

(E)

Now, eliminate bus "l"

$$\begin{bmatrix} V_1 \\ \vdots \\ V_n \\ \hline V_l = 0 \end{bmatrix} = \begin{bmatrix} 1 \\ \vdots \\ n \\ \hline l \end{bmatrix} \underbrace{\begin{bmatrix} Z_{nn} & Z_{nl} \\ Z_{ln} & Z_{ll} \end{bmatrix}}_{Z_{\text{original bus}} (n+1) \times (n+1)} \begin{bmatrix} I_1 \\ \vdots \\ I_n \\ \hline I_l \end{bmatrix}$$

$$\begin{matrix} Z_{\text{bus (without } l)} \\ \downarrow \\ n \times n \end{matrix} = \begin{matrix} Z_{nn} \\ \downarrow \\ n \times n \end{matrix} - \begin{matrix} Z_{nl} \\ \downarrow \\ n \times l \end{matrix} \begin{matrix} Z_{ll}^{-1} \\ \downarrow \\ l \times l \end{matrix} \begin{matrix} Z_{ln} \\ \downarrow \\ l \times n \end{matrix}$$

(F) Example of bus elimination using Z_{BUS}

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Eliminate bus 3, i.e. $V_3 = 0$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 + Z_{13} I_3$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 + Z_{23} I_3$$

$$0 = Z_{31} I_1 + Z_{32} I_2 + Z_{33} I_3$$

$$I_3 = \frac{-(Z_{31} I_1 + Z_{32} I_2)}{Z_{33}}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 - \frac{Z_{13}}{Z_{33}} (Z_{31} I_1 + Z_{32} I_2)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 - \frac{Z_{23}}{Z_{33}} (Z_{31} I_1 + Z_{32} I_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} - \frac{Z_{13} Z_{31}}{Z_{33}} & Z_{12} - \frac{Z_{13} Z_{32}}{Z_{33}} \\ Z_{21} - \frac{Z_{23} Z_{31}}{Z_{33}} & Z_{22} - \frac{Z_{23} Z_{32}}{Z_{33}} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{aligned} Z_{\text{new}} &= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} - \begin{bmatrix} Z_{13} \\ Z_{23} \end{bmatrix} \begin{bmatrix} Z_{33} \end{bmatrix}^{-1} \begin{bmatrix} Z_{31} & Z_{32} \end{bmatrix} \\ &= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} - \begin{bmatrix} \frac{Z_{13}}{Z_{33}} \\ \frac{Z_{23}}{Z_{33}} \end{bmatrix} \begin{bmatrix} Z_{31} & Z_{32} \end{bmatrix} \end{aligned}$$

$$Z_{\text{new}} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} - \begin{bmatrix} \frac{Z_{13} Z_{31}}{Z_{33}} & \frac{Z_{13} Z_{32}}{Z_{33}} \\ \frac{Z_{23} Z_{31}}{Z_{33}} & \frac{Z_{23} Z_{32}}{Z_{33}} \end{bmatrix}$$

$$= \begin{bmatrix} Z_{11} - \frac{Z_{13} Z_{31}}{Z_{33}} & Z_{12} - \frac{Z_{13} Z_{32}}{Z_{33}} \\ Z_{21} - \frac{Z_{23} Z_{31}}{Z_{33}} & Z_{22} - \frac{Z_{23} Z_{32}}{Z_{33}} \end{bmatrix}$$