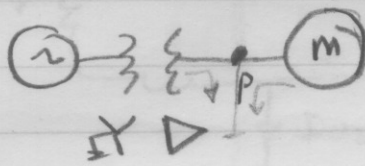


12.9 A generator supplies a motor through a Y- Δ transformer. The generator is connected to the Y side of the transformer. A fault occurs between the motor terminals and the transformer. The symmetrical components of the subtransient current in the motor flowing toward the fault are $I_{a1} = -0.8 - j2.6$ per unit, $I_{a2} = -j2.0$ per unit, and $I_{a0} = -j3.0$ per unit. From the transformer toward the fault $I_{a1} = 0.8 - j0.4$ per unit, $I_{a2} = -j1.0$ per unit, and $I_{a0} = 0$. Assume $X'_1 = X_2$ for both the motor and the generator. Describe the type of fault. Find (a) the prefault current, if any, in line a, (b) the subtransient fault current in per unit, and (c) the subtransient current in each phase of the generator in per unit.

solution



Fault occurs at P. The sum of I_{a1} from the transformer and the motor gives I_{a1} in the fault

The sum of I_{a1} toward from the motor and from trans. gives I_{a1} in the fault

$$I_{a1f} = I_{a1, \text{motor}} + I_{a1, \text{trans.}}$$

$$I_{a1f} = -0.8 - j2.6 + 0.8 - j0.4 = -j3.0$$


similarly

$$I_{a2f} = -j2.0 - j1.0 = -j3.0$$


$$I_{a0f} = -j3.0$$

since $I_{a1} = I_{a2} = I_{a0}$, then we have a single-line-to-ground fault.

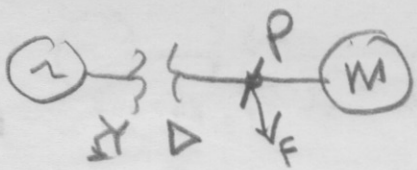The connection of the sequence network is:





2

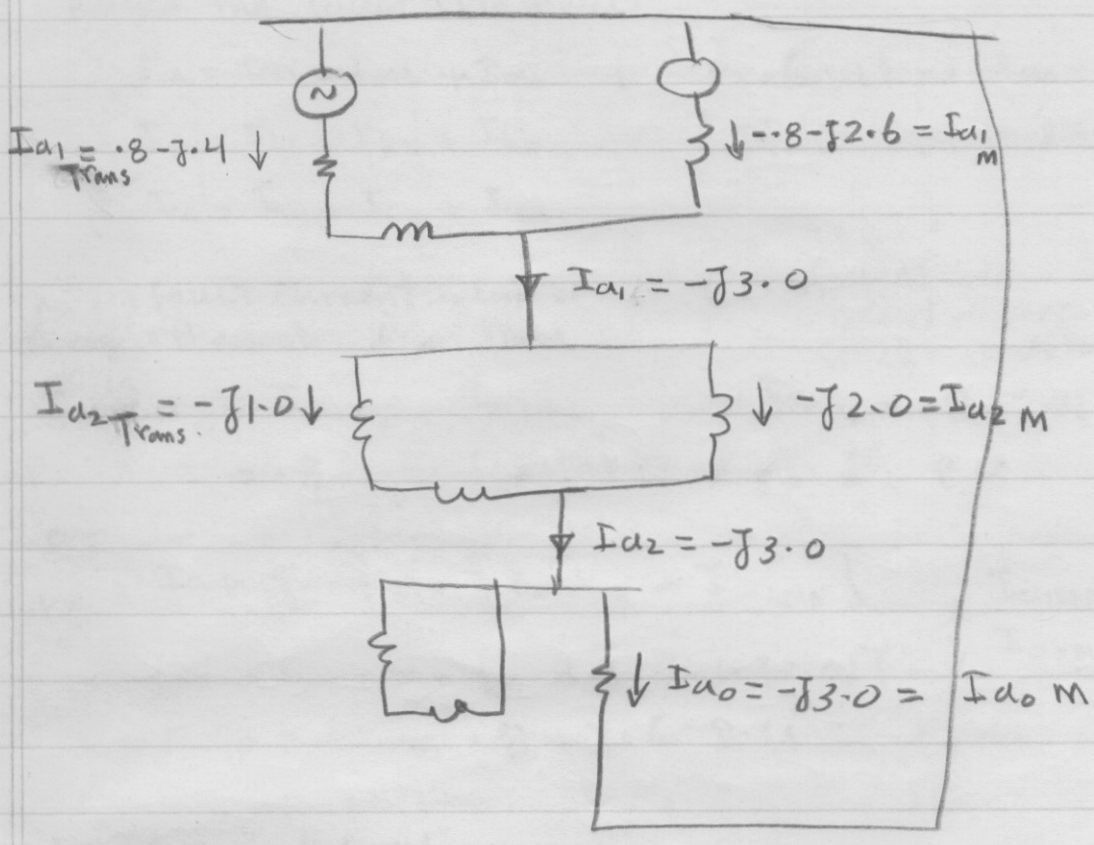

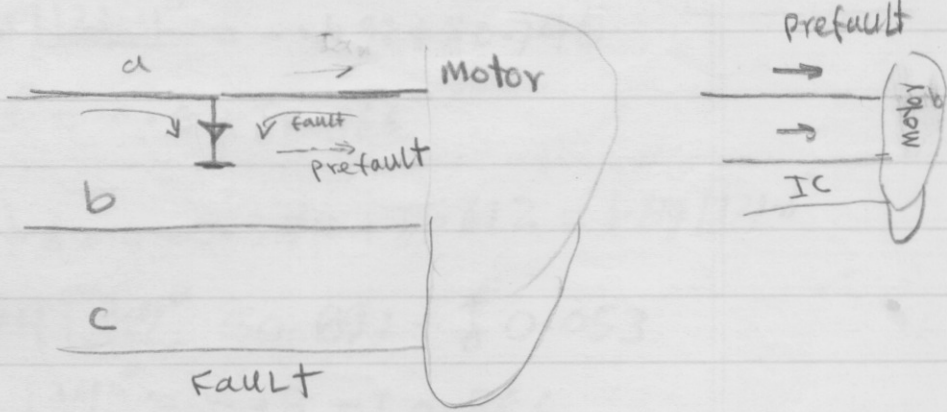a) currents are marked on the network diag.
 The division of the current due to the fault between the branches of the positive - sequence network is the same as between the branches of the negative sequence network since all x_1 values equal to x_2 values in corresponding branches.

The pre-fault current in the line a toward the motor is



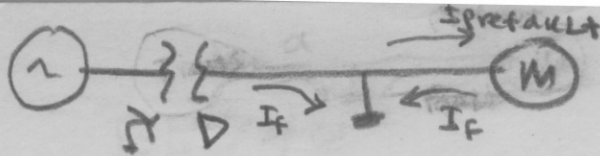

Before the fault (prefault)

$$I_a = I_{a1} + I_{a2} + I_{a0}$$

$$I_b = I_{b1} + I_{b2} + I_{b0}$$

$$I_c = I_{c1} + I_{c2} + I_{c0}$$

Prefault $\rightarrow I_{a0} = 0$

$I_{\text{prefault from trans}} = I_{\text{prefault Toward Motor}}$

The prefault current in line a toward the motor from trans

(prefault direction of current is opposite of the fault condition)

$$I_{a \text{ prefault}} = I_{a1TF} - I_{a2TF}$$

$$I_{a1TF} = 0.8 - j0.4, I_{a2TF} = -j1.0$$

$$\text{Prefault} = 0.8 - j0.4 - (-j1.0) = 0.8 + j0.6 \text{ p.u.}$$

or $I_{a \text{ prefault}} = -(-j0.8 - j2.6) = 0.8 + j0.6$

$$\text{Prefault } I_{a \text{ prefault}} = - [I_{a1MF} - I_{a2MF}], I_{a1MF} = -0.8 - j2.6$$

$$I_{a \text{ prefault}} = - [-0.8 - j2.6 - (-j2.0)]$$

$$I_{a2MF} = -j2.0$$

$$I_{a \text{ prefault}} = I_{a1} = 0.8 + j0.6 \text{ p.u.}$$

b) subtransient fault current

$$I_{af} = 3 I_{a1} = 3(-j3.0) = -j9.0 \text{ p.u.}$$

$$I_{af} = 3 I_{a1} = 3(-j3.0) = -j9.0 \text{ p.u.}$$

c) In the generator

$$I_{A1} = -j(0.8 - j0.4) = -0.4 - j0.8 = 0.894 \angle -116.6^\circ$$

$$I_{A2} = j(-j1.0) = 1.0 \angle 0^\circ, I_{A0} = 0$$

$$I_A = I_{A1} + I_{A2} = 0.6 - j0.8 = 1.0 \angle -53.1^\circ$$

$$I_{B1} = 0.894 \angle 123.4^\circ = -0.492 + j0.746$$

$$I_{B2} = 1.0 \angle 120^\circ = -0.5 + j0.866$$

$$I_B = I_{B1} + I_{B2} = -0.992 + j1.612 = 1.89 \angle 121.6^\circ$$

$$I_{C1} = 0.894 \angle 3.4^\circ = 0.892 + j0.053$$

$$I_{C2} = 1.0 \angle 240^\circ = -0.5 - j0.866$$

$$I_C = I_{C1} + I_{C2} = 0.392 - j0.813 = 0.903 \angle -64.3^\circ$$

$$I_{a1} = +j I_{A1}$$

$$I_{a2} = -j I_{A2}$$