

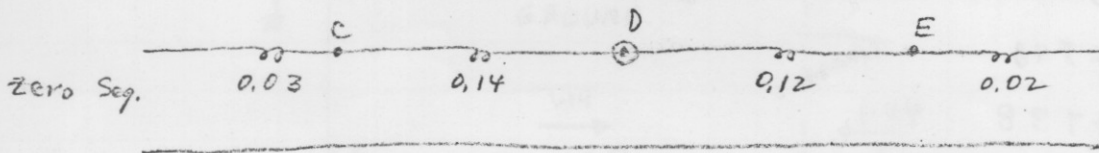
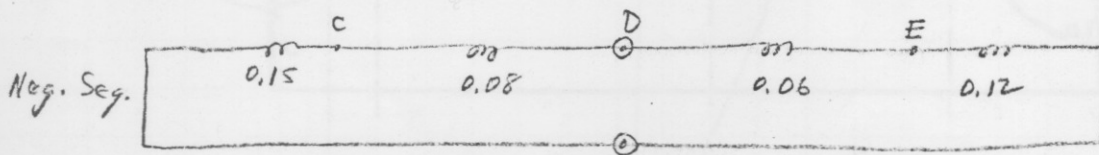
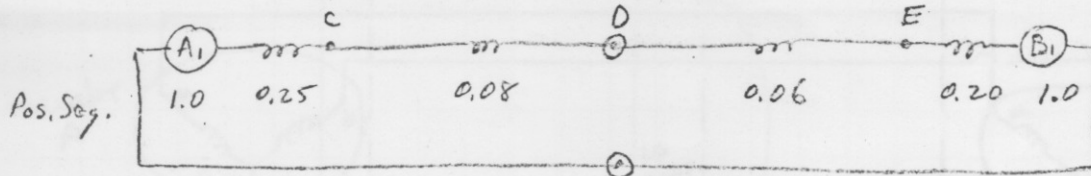
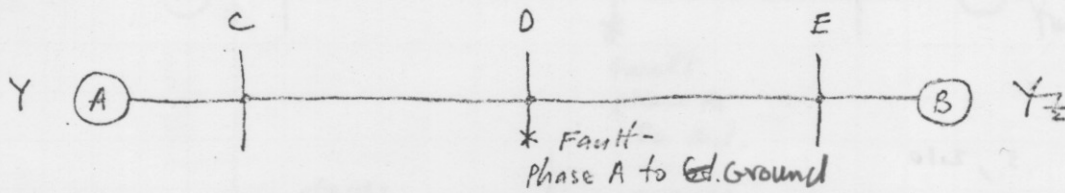
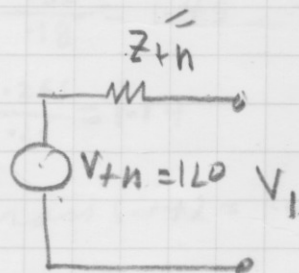



Single Line to Ground Fault.

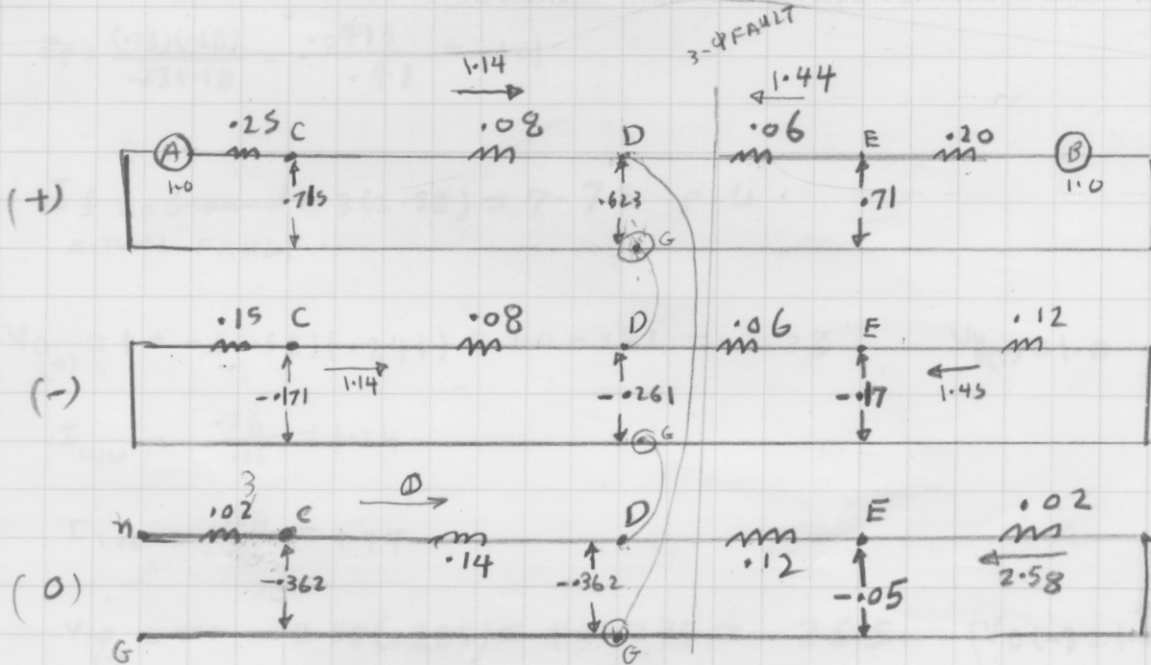

$$\begin{array}{r} .12 \\ .02 \\ \hline .14 \end{array}$$

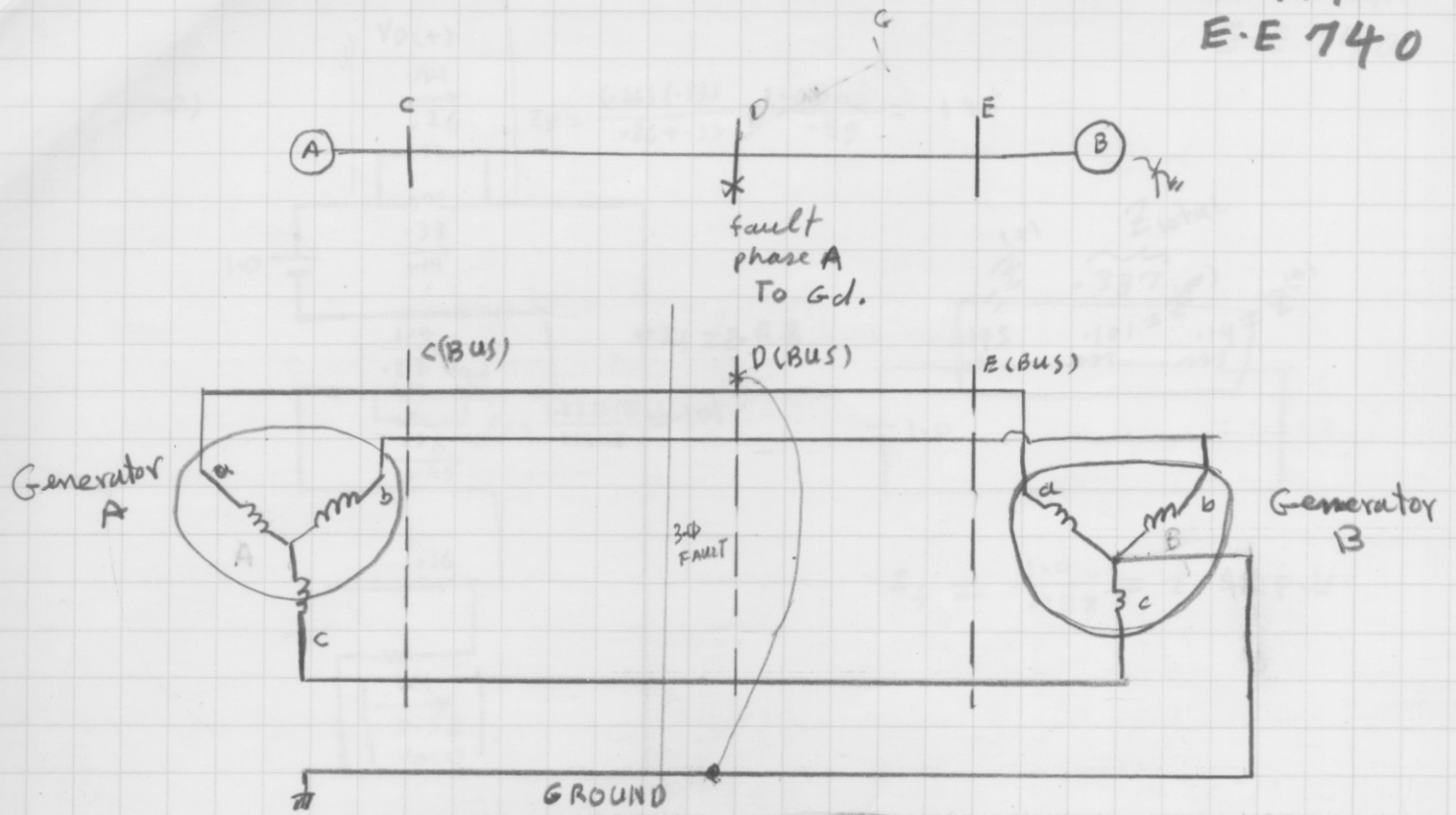- Find the actual phase voltages at the 3 buses. Show the phasor diagrams.
- Find actual generator line currents.
- Compare the currents in (b) with those for a 3-phase fault at bus D.



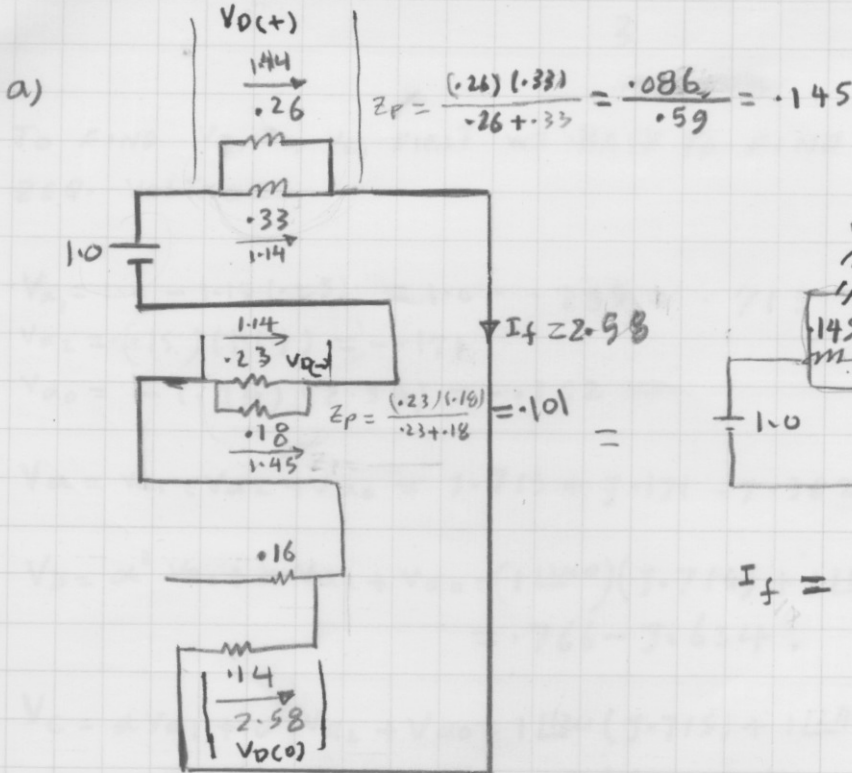

$$Z_p = \frac{(0.23)(0.16)}{0.23 + 0.16} = \frac{0.415}{0.41} = 0.101$$

$I_f \text{ to ground} = 3(2.58) = 7.75 \text{ p.u.}$
ACTUAL FAULT.

$$V_{D(+)} = 1.0 - (2.58)(0.241) = 1.0 - 0.62 = 0.38$$

$$V_{D(+)} = 1.0 - I_f (Z^0 + Z^-)$$

$\underbrace{\quad}_{0.241}$

$$I_{(0.33)} = \frac{0.38}{0.33} = 1.14$$

$$I_{(0.26)} = \frac{0.38}{0.26} = 1.44$$

$$V_{D(-)} = 1.0 - 2.58(0.205) = 1.0 - 0.529 = 0.471$$

$$V_{D(-)} = 1.0 - I_f (Z^0 + Z^+)$$

$\underbrace{\quad}_{0.205}$

$$I_{(0.18)} = \frac{0.265}{0.18} = 1.45$$

$$I_{(0.23)} = \frac{0.265}{0.23} = 1.14$$

(c) $V_{D(0)} = \text{drop across } (0.14) = 1.0 - (2.58)(0.246) = 1.0 - 0.635 = 0.365$

$$I_{(0.14)} = \frac{0.365}{0.14} = 2.58$$

$$V_{D(0)} = 1.0 - I_f (Z^+ + Z^-)$$

$\underbrace{\quad}_{0.246}$

TO FIND V_a, V_b, V_c FIRST WE HAVE TO FIND THE (+), (-), (0) ZEQ. VOLTAGES.

BUS
C

$$V_{a1} = 1.0 - 1.14(.25) = 1.0 - .285 = .715$$

$$V_{a2} = -(0.15)(1.14) = -.171$$

$$V_{a0} = -(0.14)(2.58) = -.362$$

.715
.533

$$V_a = V_{a1} + V_{a2} + V_{a0} = 1.715 + j.171 - j.362 = j.182$$

$$V_b = a^2 V_{a1} + a V_{a2} + V_{a0} = (1 \angle 240^\circ)(j.715) + 1 \angle 120^\circ(-j.171) + (-j.362) \\ = .766 - j.634$$

$$V_c = a V_{a1} + a^2 V_{a2} + V_{a0} = 1 \angle 120^\circ(j.715) + 1 \angle 40^\circ(-j.171) - j.362 \\ = -.766 - j.634$$

BUS D

$$V_{a1} = 1.0 - 1.14(.33) = 1.0 - .376 = .624$$

$$V_{a2} = -.171 - (1.14)(.08) = -.261$$

$$V_{a0} = -.362$$

$$V_a = V_{a1} + V_{a2} + V_{a0} = +j.624 - j.261 - j.362 = 0 \quad \left(\begin{array}{l} \text{IT IS SHORTED} \\ \text{TO GROUND} \\ \text{AND SHOULD} \\ \text{BE ZERO} \end{array} \right)$$

$$V_b = a^2 V_{a1} + a V_{a2} + V_{a0} = 1 \angle 240^\circ(j.624) + 1 \angle 120^\circ(-j.261) - j.362 \\ = +.766 - j.543$$

$$V_c = a V_{a1} + a^2 V_{a2} + V_{a0} \\ = 1 \angle 120^\circ(j.624) + 1 \angle 40^\circ(-j.261) + (-j.362)$$

$$V_c = -.766 - j.543$$

BUSE

$$V_{a1} = 1.0 - (.2)(1.44) = 1.0 - .288 = .71$$

$$V_{a2} = -(0.12)(1.45) = -.174$$

$$V_{a0} = -(0.02)(2.58) = -.0516$$

d) CONT.
BUS E


$$V_a = V_{a1} + V_{a2} + V_{a0} = 7.71 - 7.174 - 7.05 \\ = 7.487$$

$$V_b = a^2 V_{a1} + a V_{a2} + V_{a0} = 1 \angle 240^\circ (7.71) + (1 \angle 120^\circ)(-7.17) + (-7.05) \\ = -0.766 - j.32$$

$$V_c = a V_{a1} + a^2 V_{a2} + V_{a0} = (1 \angle 120^\circ)(7.71) + 1 \angle 240^\circ (-7.17) + (-7.05) \\ = -0.766 - j.32$$

to Ground Fault.

BUS C BUS D

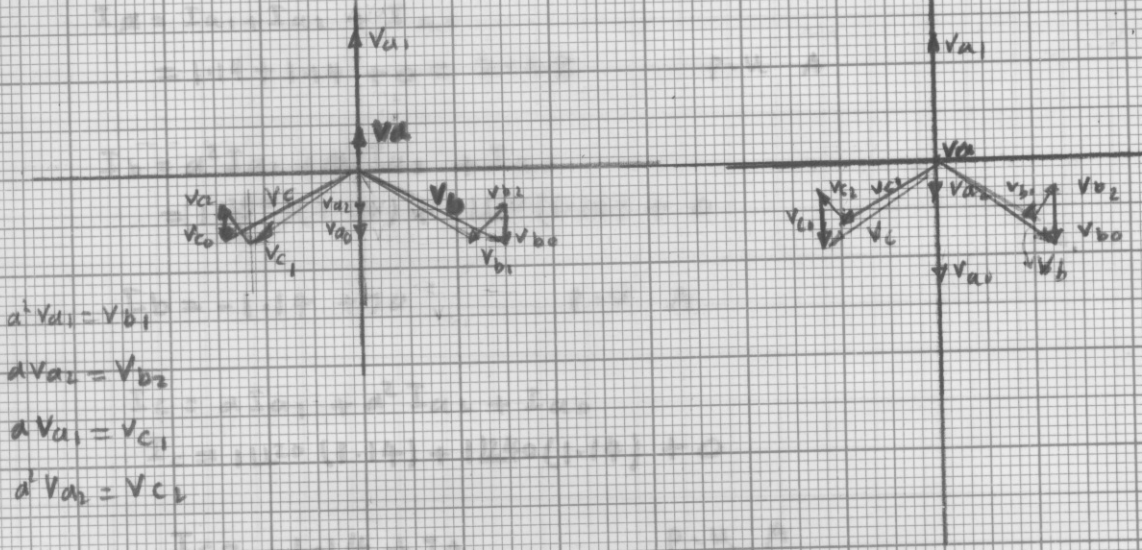


$$a^1 V_{a1} = V_{b1}$$

$$a^2 V_{a2} = V_{b2}$$

$$a^0 V_{a3} = V_{c1}$$

$$a^1 V_{a3} = V_{c2}$$

BUS E

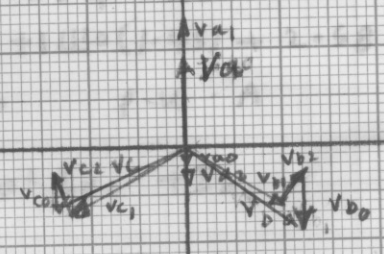

b) TO FIND THE ACTUAL GENERATOR LINE CURRENTS FIRST WE HAVE
TO FIND POSITIVE, NEGATIVE AND ZERO SEQ. CURRENTS.

GEN. A

$$I_a = I_{a1} + I_{a2} + I_{a0}$$

$$= 1.14 + 1.14 + 0 = 2.28 \quad \text{P.U. A}$$

$$I_b = a^2 I_{a1} + a I_{a2} + I_{a0}$$

$$= (1 \angle 240^\circ)(1.14) + 1 \angle 120^\circ(1.14) + 0$$

$$I_b = -1.14 + j0 \quad \text{P.U. A}$$

$$I_c = a I_{a1} + a^2 I_{a2} + I_{a0}$$

$$I_c = 1 \angle 120^\circ(1.14) + 1 \angle 40^\circ(1.14) + 0$$

$$I_c = -1.14 + j0 \quad \text{P.U. A}$$

GEN. B

$$I_a = I_{a1} + I_{a2} + I_{a0}$$

$$I_a = 1.44 + 1.45 + 2.58 = 5.47 \quad \text{P.U. A}$$

$$I_b = a^2 I_{a1} + a I_{a2} + I_{a0}$$

$$= 1 \angle 240^\circ(1.44) + 1 \angle 120^\circ(1.45) + 2.58$$


$$= 1.14 + j0 \quad \text{P.U. A}$$

$$I_c = a I_{a1} + a^2 I_{a2} + I_{a0}$$

$$I_c = 1 \angle 120^\circ(1.44) + 1 \angle 240^\circ(1.45) + 2.58$$

$$I_c = 1.14 + j0 \quad \text{P.U. A}$$

c) 3- ϕ FAULT

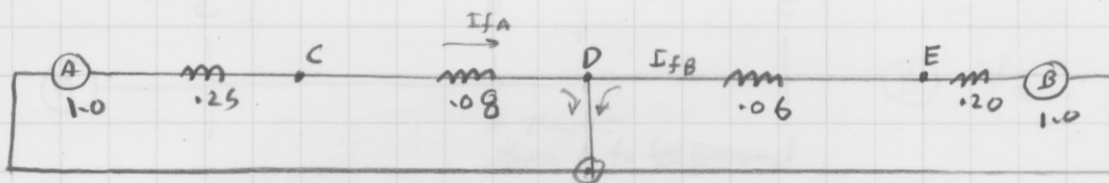

$$I_{fA} = \frac{1.0}{0.33} = 3.03 \text{ A.PU}$$

$$I_{fB} = \frac{1.0}{0.26} = 3.85 \text{ A.PU}$$

$$I_{fT} = 3.85 + 3.03 = 6.88 \text{ P.U. A}$$

$$I_{L-G} = 1.14$$

$$I_{BL-G} = 1.44$$

$$I_{fL-G} = 2.58$$

Max values

2.28

5.47

7.75

$$3.03 > 2.28$$


but -

$$5.47 > 3.85$$

3- ϕ FAULT CURRENT IS GREATER THAN SINGLE-LINE TO GROUND.

Not always -

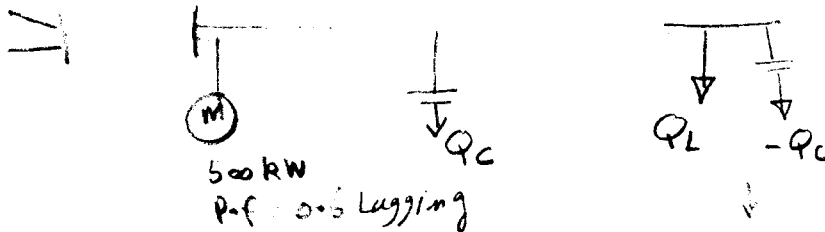- 2.8 An industrial plant consisting primarily of induction motor loads absorbs 500 kW at 0.6 power factor lagging. (a) Compute the required kVA rating of a shunt capacitor to improve the power factor to 0.9 lagging. (b) If a synchronous motor rated 500 hp and at unity power factor is added to the plant instead of the capacitor, calculate the resulting power factor. Assume constant voltage. (1 hp = 0.747 kW)



$$a) \quad P_L = VI \cos \theta = S \cos \theta \quad S_L = P_L + jQ_L$$

$$\theta = \cos^{-1}(\text{P.f.}) = \cos^{-1}(0.6) = 53.13^\circ$$

$$S_L = \frac{P_L}{\cos \theta} = \frac{500 \text{ kW}}{0.6} = 833.33 \text{ kVA}$$

$$Q_L = VI \sin \theta = 833.33 \sin(53.13^\circ) = 666.7 \text{ kvars}$$

After capacitor is in service

$$P_L = VI \cos \theta$$

$$\cos \theta = 0.9 \quad \theta = 25.84^\circ$$

$$500 = S_{\text{new}} (0.9)$$


$$S_{\text{new}} = \frac{500}{0.9} = 555.56 \text{ kVA}$$

$$Q_{\text{new}} = S_{\text{new}} \sin \theta$$

$$Q_{\text{new}} = 555.56 \sin(25.84^\circ) = 242.2 \text{ kvar}$$

$$Q_{\text{new}} = -Q_C + Q_L$$
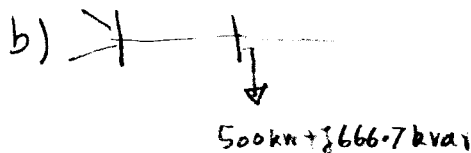
$$Q_C = 666.7 - 242.2 = 424.5 \text{ kVA}$$




$$P_M = \frac{500 \times 0.747}{0.9} = 415 \text{ kW}$$

$$S_{\text{net}} = 500 + 415_{\text{kW}} + j666.7_{\text{kvar}} = 914.44 + j666.7_{\text{kVA}}$$

$$\cos^{-1} \frac{666.7}{914.44}$$

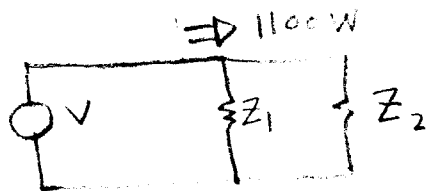
- (2.9) The real power delivered by a source to two impedances, $Z_1 = 3 + j4 \Omega$ and $Z_2 = 10 \Omega$, connected in parallel, is 1100 W. Determine (a) the real power absorbed by each of the impedances and (b) the source current.



$$Y_1 = \frac{1}{Z_1} = \frac{1}{3 + j4} = \frac{1}{5 \angle 53.13^\circ}$$

$$Y_1 = 0.2 \angle -53.13^\circ = 0.12 - j0.16$$
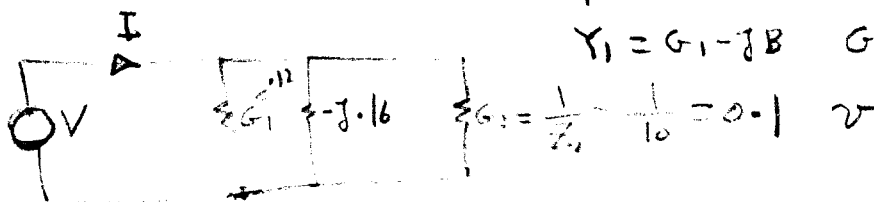
$$Y_1 = G_1 - jB \quad G_1 = 0.12 \text{ S}$$



$$G_2 = \frac{1}{Z_2} = \frac{1}{10} = 0.1 \text{ S}$$

a) $P = V^2 (G_1 + G_2) \quad V = \sqrt{\frac{P}{(G_1 + G_2)}} = \sqrt{\frac{1100}{0.12 + 0.1}} =$
 $V = 70.71 \text{ V}$


$$P_1 = V^2 G_1 = (70.71)^2 (0.12) = 600 \text{ W}$$

$$P_2 = V^2 G_2 = (70.71)^2 (0.10) = 500 \text{ W}$$


b) $Y_{eq} = Y_1 + Y_2 = (0.12 - j0.16) + 0.1 = 0.22 - j0.16$

$$I_s = V Y_{eq} = (70.71) (0.2720) = 19.23 \text{ A}$$

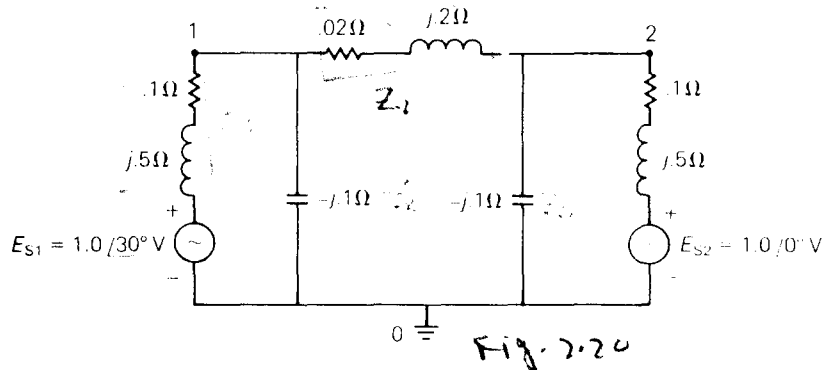2.11) For the circuit shown in Figure 2.20, convert the voltage sources to equivalent current



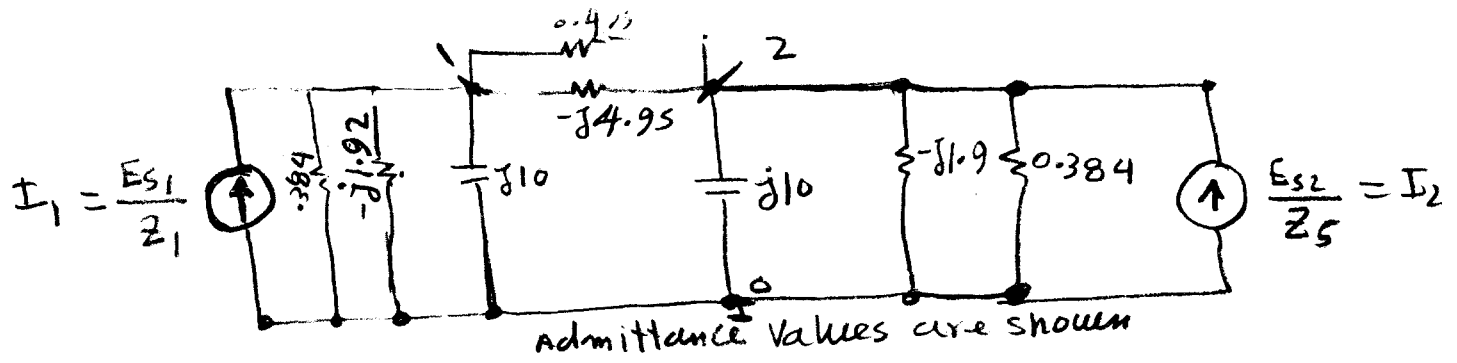sources and write nodal equations in matrix format using bus 0 as the reference bus. Do not solve the equations.



$$Y_1 = \frac{1}{Z_1} = \frac{1}{0.1 + j5} = G_1 - jB_1 = 0.384 - j1.72$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{0.02 + j2} = G_2 - jB_2 = 0.495 - j4.95$$

$$Y_3 = \frac{1}{Z_3} = j10 \quad Y_4 = \frac{1}{Z_4} = j10$$


$$Y_5 = \frac{1}{Z_5} = \frac{1}{0.1 + j5} = 0.384 - j1.92$$

$$I_1 = 1.96 \angle -48.6^\circ$$

$$I_2 = 1.96 \angle -78.69^\circ$$

$$\begin{bmatrix} +0.8796 + j3.12 \\ -0.495 + j4.95 \end{bmatrix} \begin{bmatrix} V_{10} \\ V_{20} \end{bmatrix} = \begin{bmatrix} 1.961 \angle -48.69^\circ \\ 1.961 \angle -78.69^\circ \end{bmatrix}$$

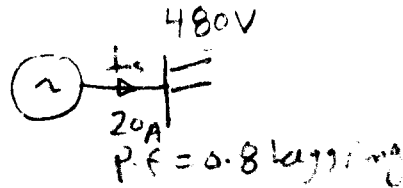- 2.16 A three-phase 25-kVA, 480-V, 60-Hz alternator, operating under balanced steady-state conditions, supplies a line current of 20 A per phase at a 0.8 lagging power factor and at rated voltage. Determine the power triangle for this operating condition.




$$S_{3\phi} = \sqrt{3} V_{LL} I_L \angle \cos^{-1}(P.f) = \sqrt{3} (480)(20) \angle \cos^{-1}(0.8)$$


$$= 16.627 \times 10^3 \angle 36.87^\circ = 13.3 \times 10^3 + j9.976 \times 10^3$$

$$P_{3\phi} = \text{Re}\{S_{3\phi}\} = 13.3 \text{ kW delivered}$$
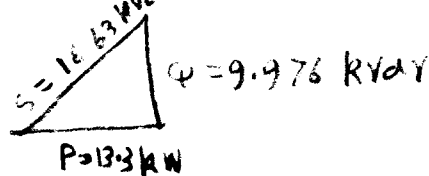
$$Q_{3\phi} = \text{Im}\{S_{3\phi}\} = 9.976 \text{ kVAR delivered}$$



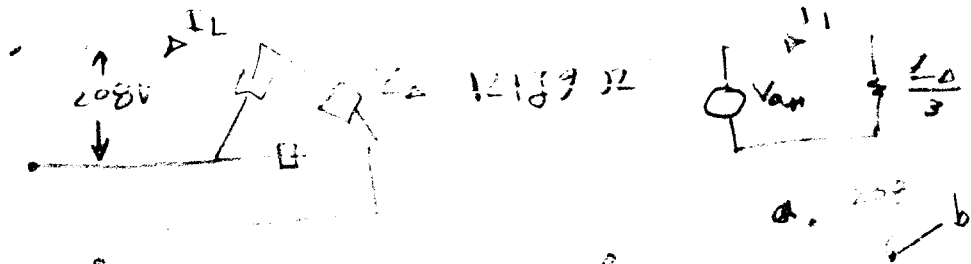- 2.17 A balanced Δ -connected impedance load with $(12 + j9)\Omega$ per phase is supplied by a balanced three-phase 60-Hz, 208-V source. (a) Calculate the line current, the total real and reactive power absorbed by the load, the load power factor, and the apparent load power. (b) Sketch a phasor diagram showing the line currents, the line-to-line source voltages, and the Δ -load currents. Assume positive sequence and use V_{ab} as the reference.



$$V_{an} = \frac{208 \angle -30^\circ}{\sqrt{3}} \quad Z_Y = \frac{Z_\Delta}{3} = 4 + j3 = 5 \angle 36.87^\circ \Omega$$

$$V_{an} = 120.1 \angle -30^\circ$$

$$I_a = \frac{V_{an}}{Z_Y} = \frac{120.1 \angle -30^\circ}{5 \angle 36.87^\circ} = 24.02 \angle -66.87^\circ$$

$$S_{3\phi} = 3 V_{an} I_a^* = 3(120.1 \angle -30^\circ)(24.02 \angle 66.87^\circ)$$

$$S_{3\phi} = 8654 \angle 36.87^\circ = 6923 + j5192$$




$$P_{3\phi} = 6923 \text{ W} \quad Q_{3\phi} = 5192 \quad \left. \vphantom{P_{3\phi}} \right\} \text{ absorbed by the load}$$

$$S_{3\phi} = |S_{3\phi}| = 8654 \text{ VA}$$

(5)

2.17 cont.

b)

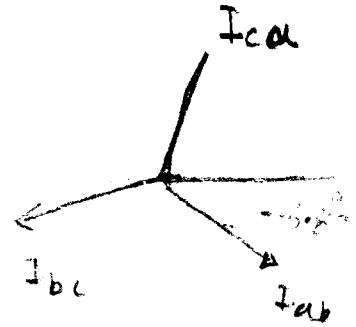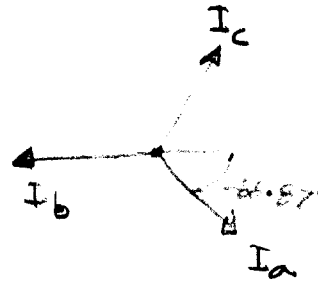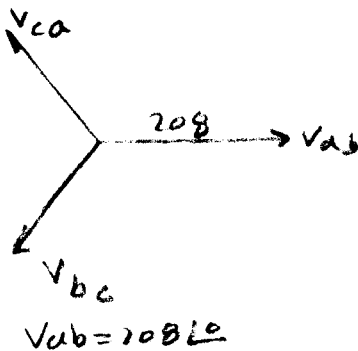

$$I_a = 24.02 \angle -66.87^\circ \quad I_a = \sqrt{3} I_{AB} \angle -30^\circ$$

$$I_{AB} = \frac{I_a}{\sqrt{3} \angle -30^\circ} = \frac{24.02 \angle -66.87^\circ}{\sqrt{3} \angle -30^\circ}$$

$$I_{AB} = 13.88 \angle -36.87^\circ$$

- (2.18) Two balanced Y-connected loads, one drawing 10 kW at 0.8 p.f. lagging and the other 15 kW at 0.9 p.f. leading, are connected in parallel and supplied by a balanced three-phase Y-connected, 480-V source. (a) Determine the source current. (b) If the load neutrals are connected to the source neutral by a zero-ohm neutral wire through an ammeter, what will the ammeter read?

$$P_{3\phi} = S_{3\phi} \cos \theta$$

$$P_{11} + jQ_{12} \quad P_{22} - jQ_{22}$$

$$S_{3\phi 1} = \frac{10 \times 10^3}{0.8} = 12.500 \text{ kVA} \quad S_{2\phi 2} = \frac{15 \times 10^3}{0.9} = 16.67 \text{ kVA}$$

$$\theta_1 = \cos^{-1}(0.8) = 36.86^\circ \quad \theta_2 = \cos^{-1}(0.9) = 25.84^\circ$$


$$Q_1 = S_{3\phi 1} \sin \theta_1 = 7.498 \quad S_T = P_1 + P_2 + j(Q_1 - Q_2)$$

$$Q_2 = S_{2\phi 2} \sin \theta_2 = 7.265$$

$$S_T = 25 \text{ kW} + j \cdot 233 \text{ kVar}$$

$$|I_s| = \frac{S_T}{\sqrt{3} V_{LL}} = \frac{25.00 \times 10^3}{\sqrt{3} (480)} = 30.07 \text{ A}$$

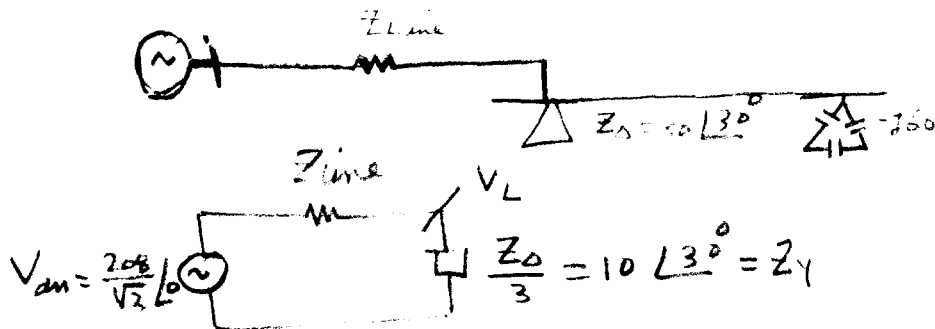- 2.19 Three identical impedances $Z_\Delta = 30/30^\circ \Omega$ are connected in Δ to a balanced three-phase 208-V source by three identical line conductors with impedance $Z_L = (0.8 + j0.6) \Omega$ per line. (a) Calculate the line-to-line voltage at the load terminals. (b) Repeat part (a) when a Δ -connected capacitor bank with reactance $(-j60) \Omega$ per phase is connected in parallel with the load.




$$V_{an} = V_{an} \frac{Z_Y}{Z_Y + Z_{line}} = \frac{208 \angle 0^\circ}{\sqrt{3}} \frac{10 \angle 30^\circ}{10 \angle 30^\circ + (0.8 + j0.6)}$$

$$= \frac{(120.09)(10 \angle 30^\circ)}{9.46 + j5.6} = \frac{1200.9 \angle 30^\circ}{10.99 \angle 30.62^\circ} = 109.3 \angle -0.62^\circ \text{ V}$$

Load voltage: $V_{AB} = \sqrt{3} (109.3) = 189.3 \text{ V (line-to-line)}$

b)

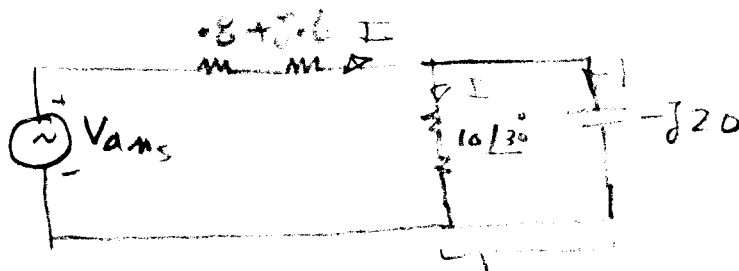

$$Z_{eq} = 10 \angle 30^\circ \parallel (-j20) = \frac{200 \angle -60^\circ}{8.66 - j15}$$

$$Z_{eq} = 11.547 \angle 0^\circ \Omega$$


$$V_{an_L} = V_{an_s} \frac{Z_{eq}}{Z_{eq} + Z_{line}}$$

$$= \frac{(120.09)(11.547)}{12.347 + j0.6} = \frac{1386.7}{12.362 \angle 2.78^\circ}$$

$$V_{an_L} = 112.2 \angle -2.78^\circ$$


The load voltage is $V_{AB} = \sqrt{3} (112.2) = 194.3 \text{ V (line-to-line)}$

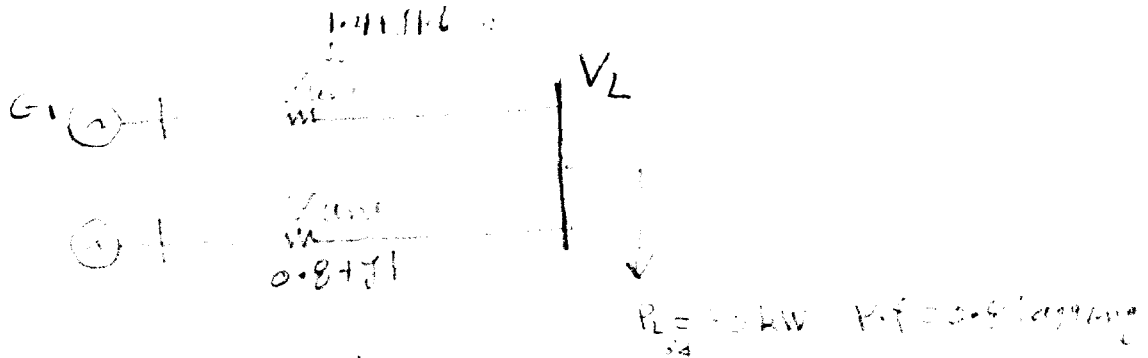2.20) Two three-phase generators supply a three-phase load through separate three-phase lines. The load absorbs 30 kW at 0.8 p.f. lagging. The line impedance is $(1.4 + j1.6) \Omega$ per phase between generator G1 and the load, and $(0.8 + j1) \Omega$ per phase between generator G2 and the load. If generator G1 supplies 15 kW at 0.8 p.f. lagging, with a terminal voltage of 460 V line-to-line, determine: (a) the voltage at the load terminals; (b) the voltage at the terminals of generator G2; and (c) the real and reactive power supplied by generator G2. Assume balanced operation.



$P_{G1} = 15 \text{ kW}$ P.F. = 0.8 lagging

$V_{L1} = 460 \text{ (L-L)}$

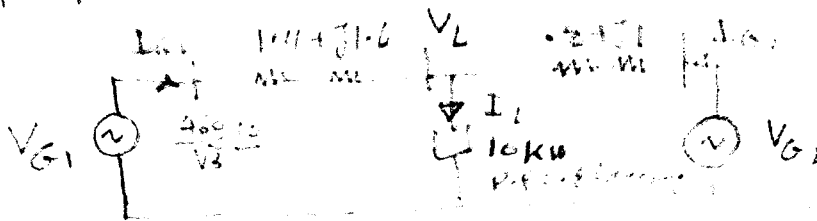

$$I_{G1} = \frac{P_{G1}}{\sqrt{3} (V_{G1-L-L}) (P.F.)} = \frac{15 \times 10^3}{(1.73)(460)(0.8)} = 23.53 \angle -36.87^\circ$$

$$V_{L_{per\ phase}} = V_{G1} - Z_{line} I_{G1} = 216.7 \angle -36.87^\circ$$

$$V_{L-L} = \sqrt{3} (216.7) = 375.7 \text{ V (L-L)}$$

b) $S_{L3\phi} = \frac{P_{L3\phi}}{P.F.} \angle \cos^{-1} P.F. = \frac{30 \times 10^3}{0.8} \angle -36.87^\circ$

$S_{L3\phi} = 37.5 \text{ kVA}$

$$I_L = \frac{37.5 \times 10^3 \angle -36.87^\circ}{\sqrt{3} (216.7) \angle -27.3^\circ} = 57.63 \angle -39.6^\circ \text{ A}$$

$I_L = 57.63 \angle -39.6^\circ \text{ A}$

$I_{G1} = I_L = 57.63 \angle -39.6^\circ \text{ A}$

$V_{G2} = V_L + Z_{line} I_L = 259.7 \angle -36.87^\circ$

c) $P_{G2} = 3 V_{G2} I_{G2} \cos \theta = 20.12 \text{ kW}$, $Q_{G2} = 13.4 \text{ kVAR}$

Solution set #2

3.3

Find the phase voltages V_{an} , V_{bn} , and V_{cn} whose sequence components are: $V_0 = 50 \angle 80^\circ$, $V_1 = 100 \angle 0^\circ$, $V_2 = 50 \angle 90^\circ$.

$$\begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 50 \angle 80^\circ \\ 100 \angle 0^\circ \\ 50 \angle 90^\circ \end{bmatrix}$$


$$= 50 \begin{bmatrix} 1 \angle 80^\circ + 2 \angle 0^\circ + 1 \angle 90^\circ \\ 1 \angle 80^\circ + 2 \angle 240^\circ + 1 \angle 210^\circ \\ 1 \angle 80^\circ + 2 \angle 120^\circ + 1 \angle 330^\circ \end{bmatrix} = 50 \begin{bmatrix} 2.174 + j1.985 \\ -1.692 - j1.247 \\ 2.0397 + j2.217 \end{bmatrix}$$

$$\begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} 147.2 \angle 42.4^\circ \\ 105.1 \angle 216.4^\circ \\ 110.9 \angle 88.97^\circ \end{bmatrix}$$

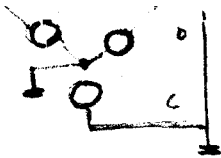3.4

One line of a three-phase generator is open-circuited, while the other two are short-circuited to ground. The line currents are $I_a = 0$, $I_b = 1000 \angle 150^\circ$, and $I_c = 1000 \angle 30^\circ$ A. Find the symmetrical components of these currents. Also find the current into the ground.

$$I_a = 0 \quad I_b = 1000 \angle 150^\circ \quad I_c = 1000 \angle 30^\circ$$



$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ 1000 \angle 150^\circ \\ 1000 \angle 30^\circ \end{bmatrix} = \frac{1000}{3} \begin{bmatrix} 1 \angle 150^\circ + 1 \angle 30^\circ \\ 1 \angle 270^\circ + 1 \angle 270^\circ \\ 1 \angle 150^\circ + 1 \angle 150^\circ \end{bmatrix}$$

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 333.3 \angle 90^\circ \\ 666.7 \angle 270^\circ \\ 333.3 \angle 90^\circ \end{bmatrix} \text{ A}$$

current into ground = $I_n = 3 I_0 = 1000 \angle 90^\circ$

3.5) Given the line-to-ground voltages $V_{ag} = 280/0^\circ$, $V_{bg} = 250/-110^\circ$, and $V_{cg} = 290/130^\circ$ volts, calculate (a) the sequence components of the line-to-ground voltages, denoted V_{Lg0} , V_{Lg1} , and V_{Lg2} ; (b) line-to-line voltages V_{ab} , V_{bc} , and V_{ca} ; and (c) sequence components of the line-to-line voltages V_{LL0} , V_{LL1} , and V_{LL2} . Also, verify the following general relation: $V_{LL0} = 0$, $V_{LL1} = \sqrt{3}V_{Lg1}/+30^\circ$, and $V_{LL2} = \sqrt{3}V_{Lg2}/-30^\circ$ volts.

a)

$$\begin{bmatrix} \tilde{V}_{Lg0} \\ \tilde{V}_{Lg1} \\ \tilde{V}_{Lg2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 280/0^\circ \\ 250/-110^\circ \\ 290/130^\circ \end{bmatrix}$$

$$= \begin{bmatrix} 5.039 \angle -57.6^\circ \\ 272.4 \angle 6.52^\circ \\ 27.82 \angle -76.05^\circ \end{bmatrix} \quad \text{V}$$

b)

$$\begin{bmatrix} \tilde{V}_{ab} \\ \tilde{V}_{bc} \\ \tilde{V}_{ca} \end{bmatrix} = \begin{bmatrix} \tilde{V}_{ag} - \tilde{V}_{bg} \\ \tilde{V}_{bg} - \tilde{V}_{cg} \\ \tilde{V}_{cg} - \tilde{V}_{ag} \end{bmatrix} = \begin{bmatrix} 280/0^\circ - 250/-110^\circ \\ 250/-110^\circ - 290/130^\circ \\ 290/130^\circ - 280/0^\circ \end{bmatrix}$$

$$= \begin{bmatrix} 434.6 \angle 32.73^\circ \\ 468.1 \angle -77.55^\circ \\ 516.6 \angle 154.5^\circ \end{bmatrix}$$

c)

$$\begin{bmatrix} \tilde{V}_{LL0} \\ \tilde{V}_{LL1} \\ \tilde{V}_{LL2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \tilde{V}_{ab} \\ \tilde{V}_{bc} \\ \tilde{V}_{ca} \end{bmatrix}$$

Note
 $\tilde{V}_{LL+} = \sqrt{3} \tilde{V}_{Lg+} \angle +30^\circ$
 $\tilde{V}_{LL-} = \sqrt{3} \tilde{V}_{Lg-} \angle -30^\circ$

$$\begin{bmatrix} \tilde{V}_{LL0} \\ \tilde{V}_{LL1} \\ \tilde{V}_{LL2} \end{bmatrix} = \begin{bmatrix} 0 \\ 471.8 \angle 36.58^\circ \\ 48.35 \angle -106.2^\circ \end{bmatrix} = \begin{bmatrix} 0 \\ \sqrt{3} \tilde{V}_{Lg1} \angle 30^\circ \\ \sqrt{3} \tilde{V}_{Lg2} \angle -30^\circ \end{bmatrix}$$

$$\tilde{V}_{LL1} = \sqrt{3} \tilde{V}_{Lg1} \angle 30^\circ = \sqrt{3} 272.4 \angle 6.58^\circ \angle 30^\circ = 471.8 \angle 36.58^\circ$$


$$\tilde{V}_{LL2} = \sqrt{3} \tilde{V}_{Lg2} \angle -30^\circ = \sqrt{3} 27.82 \angle -76.05^\circ \angle -30^\circ = 48.35 \angle -106.2^\circ$$

(3)

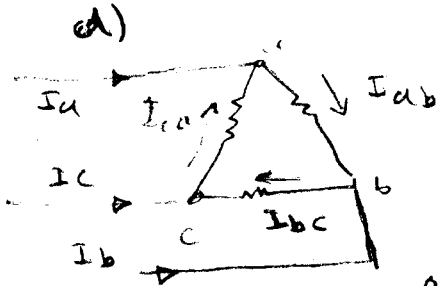3.6

Section 3.2

The currents in a Δ load are $I_{ab} = 10/0^\circ$, $I_{bc} = 15/-90^\circ$, and $I_{ca} = 20/90^\circ$ A. Calculate (a) the sequence components of the Δ -load currents, denoted $I_{\Delta 0}$, $I_{\Delta 1}$, $I_{\Delta 2}$; (b) the line currents I_a , I_b , and I_c , which feed the Δ load; and (c) sequence components of the line currents I_{L0} , I_{L1} , and I_{L2} . Also, verify the following general relation: $I_{L0} = 0$, $I_{L1} = \sqrt{3}I_{\Delta 1}/-30^\circ$, and $I_{L2} = \sqrt{3}I_{\Delta 2}/+30^\circ$ A.



$$\begin{bmatrix} I_{\Delta 0} \\ I_{\Delta 1} \\ I_{\Delta 2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$

$$\begin{aligned} I_{ab} &= 10 \angle 0^\circ \\ I_{bc} &= 15 \angle -90^\circ \text{ A} \\ I_{ca} &= 20 \angle 90^\circ \end{aligned}$$

$$\begin{bmatrix} I_{\Delta 0} \\ I_{\Delta 1} \\ I_{\Delta 2} \end{bmatrix} = \begin{bmatrix} 3.727 \angle 26.56^\circ \\ 13.47 \angle -3.55^\circ \\ 6.821 \angle 187.0^\circ \end{bmatrix}$$

b)

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} I_{ab} - I_{ca} \\ I_{bc} - I_{ab} \\ I_{ca} - I_{bc} \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ - 20 \angle 90^\circ \\ 15 \angle -90^\circ - 10 \angle 0^\circ \\ 20 \angle 90^\circ - 15 \angle -90^\circ \end{bmatrix} = \begin{bmatrix} 22.36 \angle -63.43^\circ \\ 18.03 \angle 236.3^\circ \\ 35 \angle 90^\circ \end{bmatrix}$$

c)

$$\begin{bmatrix} I_{L0} \\ I_{L1} \\ I_{L2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 0 \\ 23.32 \angle -33.56^\circ \\ 11.81 \angle 217^\circ \end{bmatrix} = \begin{bmatrix} 0 \\ \sqrt{3} \tilde{I}_{\Delta 1} \angle -30^\circ \\ \sqrt{3} \tilde{I}_{\Delta 2} \angle 30^\circ \end{bmatrix}$$

$$\begin{aligned} \hat{I}_{L1} &= \sqrt{3} \tilde{I}_{\Delta 1} \angle -30^\circ = \sqrt{3} 13.47 \angle -3.55^\circ \times \angle -30^\circ \\ &= 23.47 \angle -33.56^\circ \checkmark \end{aligned}$$

Note:

"For a balanced Δ load"

$$\text{Positive sequence } \hat{I}_L^+ = \tilde{I}_\Delta^+ \angle -30^\circ$$

$$\text{Negative sequence } \hat{I}_L^- = \tilde{I}_\Delta^- \angle 30^\circ$$


$$\hat{I}_{L2} = \sqrt{3} \tilde{I}_{\Delta 2} \angle 30^\circ$$

$$\begin{aligned} &= (\sqrt{3}) 6.821 \angle 187.0^\circ \angle 30^\circ \\ &= 11.81 \angle 217^\circ \end{aligned}$$

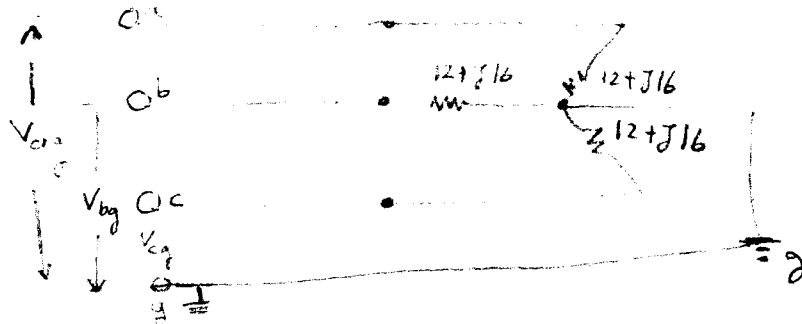(4)


3-7

The voltages given in Problem 3.5 are applied to a balanced-Y load consisting of $(12 + j16)$ ohms per phase. The load neutral is solidly grounded. Draw the sequence networks and calculate I_0 , I_1 , and I_2 , the sequence components of the line currents. Then calculate the line currents I_a , I_b , and I_c .



$$\begin{aligned} V_{ag} &= 280 \angle 0^\circ \text{ V} \\ V_{bg} &= 250 \angle -110^\circ \text{ V} \\ V_{cg} &= 290 \angle 130^\circ \text{ V} \end{aligned}$$

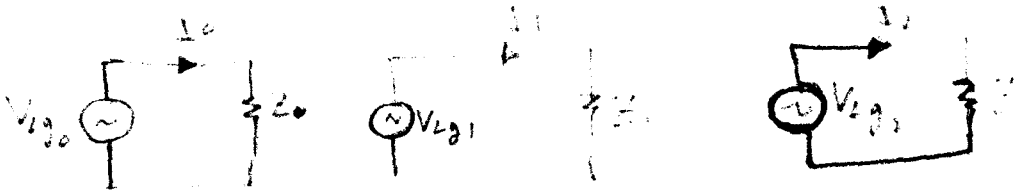From Prob. 3.5 $V_{Lg0} = 5.039 \angle -57.65^\circ$ $V_{Lg1} = 272.4 \angle 6.59^\circ$
 $V_{Lg2} = 21.82 \angle -16.05^\circ$ $Z_L = 12 + j16 = 20 \angle 53.13^\circ = Z_0 = Z_1 = Z_2$



$$\begin{aligned} I_0 &= \frac{V_{Lg0}}{Z_0} = \frac{5.039}{20 \angle 53.13^\circ} = 0.252 \angle -110.78^\circ \text{ A} & I_1 &= \frac{V_{Lg1}}{Z_1} = \frac{272.4}{20 \angle 53.13^\circ} = 13.62 \angle -46.58^\circ \text{ A} \\ I_2 &= \frac{V_{Lg2}}{Z_2} = \frac{21.82}{20 \angle 53.13^\circ} = 1.091 \angle -129.18^\circ \text{ A} \end{aligned}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0.252 \angle -110.78^\circ \\ 13.62 \angle -46.58^\circ \\ 1.091 \angle -129.18^\circ \end{bmatrix} = \begin{bmatrix} 14.0 \angle -53.13^\circ \\ 12.5 \angle -163.1^\circ \\ 14.5 \angle 76.37^\circ \end{bmatrix}$$


Since the source and load neutrals are connected

$$I_a = \frac{V_{ag}}{Z_Y} = \frac{280 \angle 0^\circ}{20 \angle 53.13^\circ} = 14.0 \angle -53.13^\circ \text{ A}$$

$$I_b = \frac{V_{bg}}{Z_Y} = \frac{250 \angle -110^\circ}{20 \angle 53.13^\circ} = 12.5 \angle -163.1^\circ \text{ A}$$

$$I_c = \frac{V_{cg}}{Z_Y} = \frac{290 \angle 130^\circ}{20 \angle 53.13^\circ} = 14.5 \angle 76.87^\circ \text{ A}$$

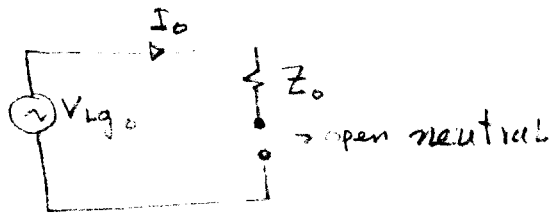3.8 Repeat Problem 3.7 with the load neutral open



$$I_0 = 0$$

$$I_1 = 13.62 \angle -46.54^\circ \text{ A}$$

$$I_2 = 1.391 \angle -129.18^\circ \text{ A}$$


From
Prob. 3.7

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ 13.62 \angle -46.54^\circ \\ 1.391 \angle -129.18^\circ \end{bmatrix} = \begin{bmatrix} 13.86 \angle -62.24^\circ \\ 12.35 \angle 195.9^\circ \\ 14.75 \angle 76.74^\circ \end{bmatrix}$$

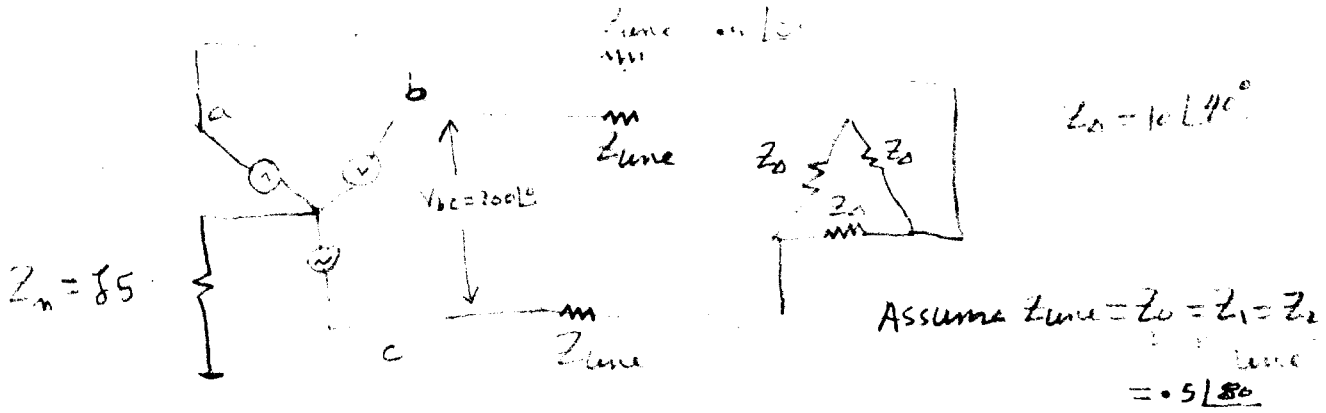
3.13

Section 3.4

A balanced-Y-connected generator with terminal voltage $V_{bc} = 200/0^\circ$ volts is connected to a balanced- Δ load whose impedance is $10/40^\circ$ ohms per phase. The line impedance between the source and load is $0.5/80^\circ$ ohm for each phase. The generator neutral is grounded through an impedance of $j5$ ohms. The generator sequence impedances are given by $Z_{g0} = j7$, $Z_{g1} = j15$, and $Z_{g2} = j10$ ohms. Draw the sequence networks for this system and determine the sequence components of the line currents.



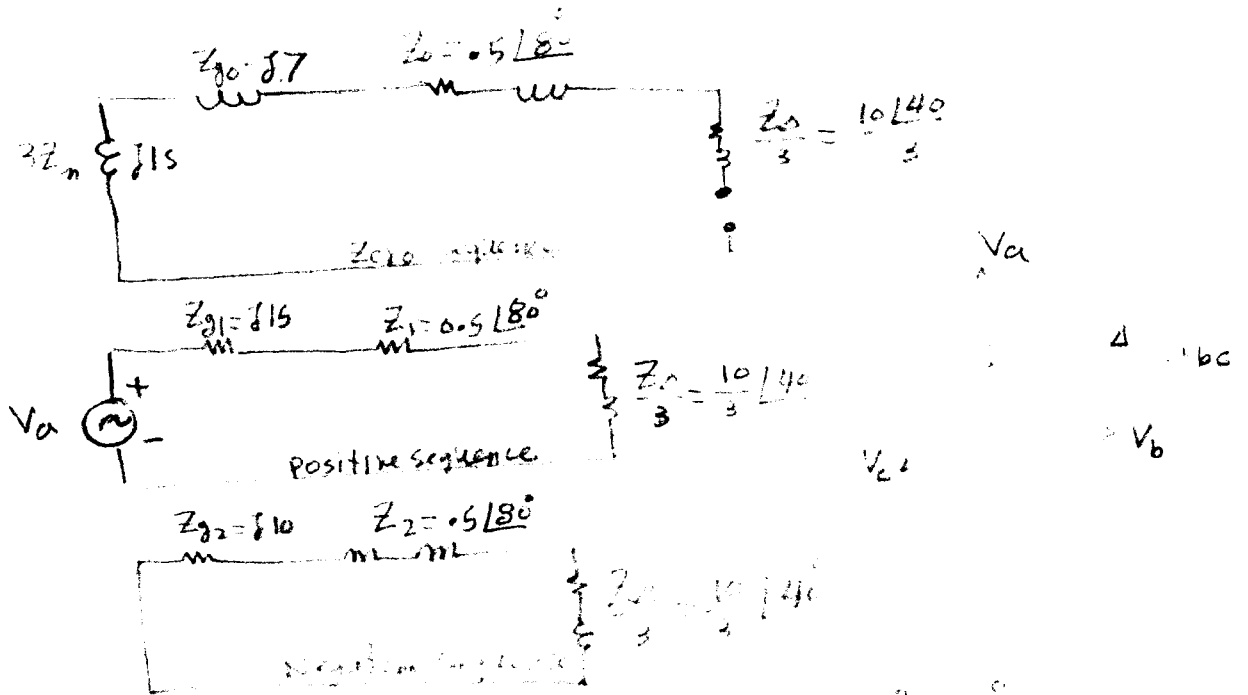
$Z_{g0} = j7, Z_{g1} = j15, Z_{g2} = j10$



$I_{line} = I_{line0} + I_{line1} + I_{line2} = \frac{V_a}{Z_{line} + Z_0} = \frac{200 \angle 90^\circ}{0.5 \angle 80^\circ + \frac{10 \angle 40^\circ}{3}} = 30.96 \angle 45.05^\circ$



(7)

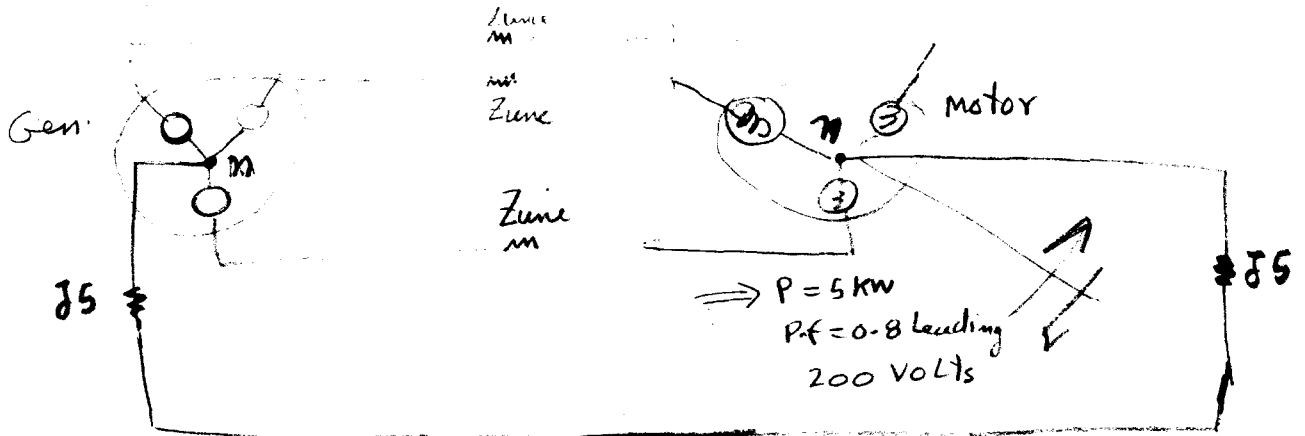3.14 In a three-phase system, a synchronous generator supplies power to a 200-volt synchronous motor through a line having an impedance of $0.5/80^\circ$ ohm per phase. The motor draws 5 kW at 0.8 p.f. leading and at rated voltage. The neutrals of both the generator and motor are grounded through impedances of $j5$ ohms. The sequence impedances of both machines are $Z_0 = j5$, $Z_1 = j15$, and $Z_2 = j10$ ohms. Draw the sequence networks for this system and find the line-to-line voltage at the generator terminals. Assume balanced three-phase operation.



Assume $Z_{line} = Z_0 = Z_1 = Z_2$

Solution

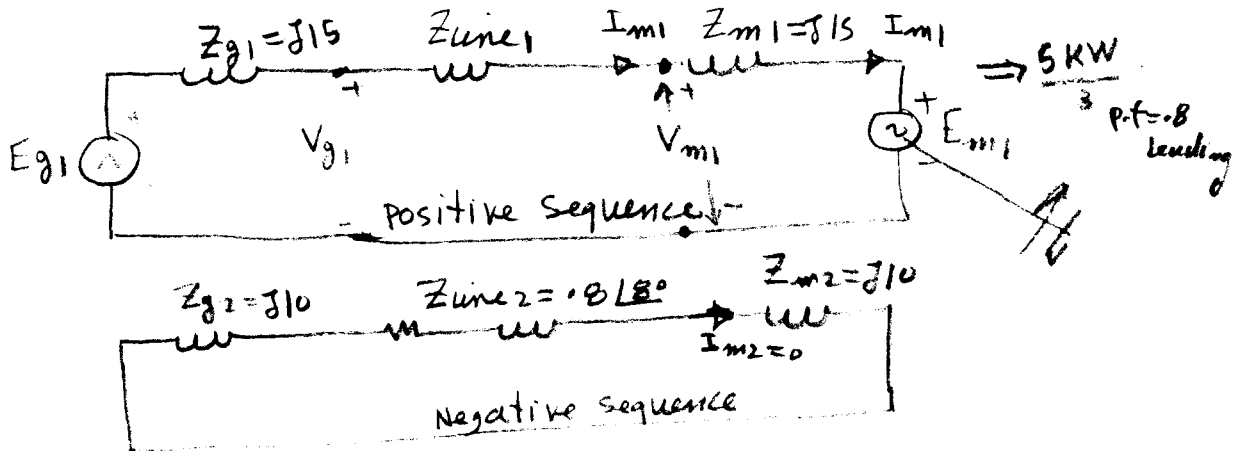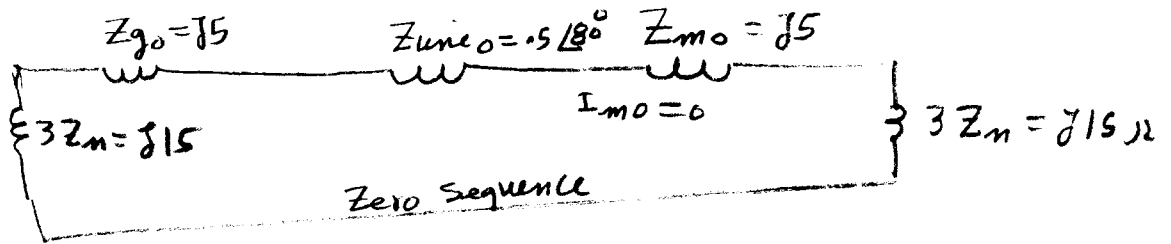

$$\tilde{V}_{gan} = \tilde{V}_{g1} = \tilde{V}_{m1} + \tilde{Z}_{line1} \tilde{I}_{m1}$$

$$I_{m1} = \frac{5000 \angle \cos^{-1} 0.8}{200 \sqrt{3} \angle 0.8} = 18.04 \angle 36.8^\circ$$

$$\tilde{V}_{gan} = \frac{200}{\sqrt{3}} \angle 0 + (0.5 \angle 80^\circ)(18.04 \angle 36.8^\circ) = 111.7 \angle 44.1^\circ$$


$$V_g = \sqrt{3} (111.7) = 193.5 \text{ V (line-to-line)}$$

Solution
Problem set #4


A. / CCY / CA

4.12 Consider the three single-phase two-winding transformers shown in Figure 4.32. The high-voltage windings are connected in Y. (a) For the low-voltage side, connect the windings in Δ , place the polarity marks, and label the terminals $a, b,$ and c in accordance with the American standard. (b) Relabel the terminals $a', b',$ and c' such that $V_{a'n}$ is 90° out of phase with $V_{a'n}$ for positive sequence.




Figure 4.32
Problem 4.12

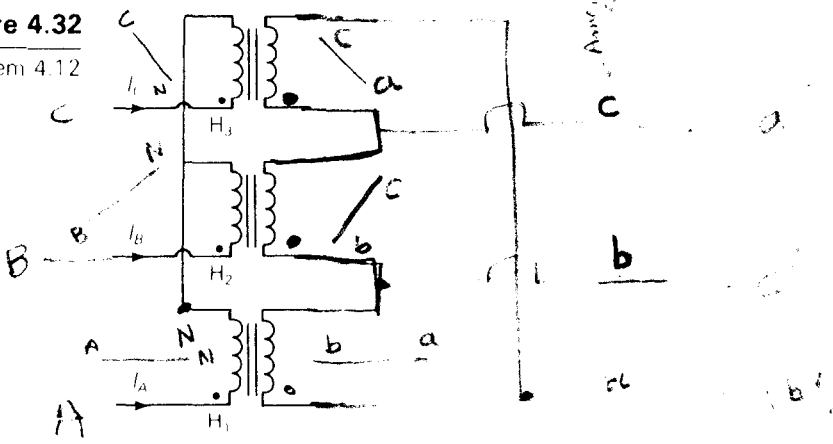

a)

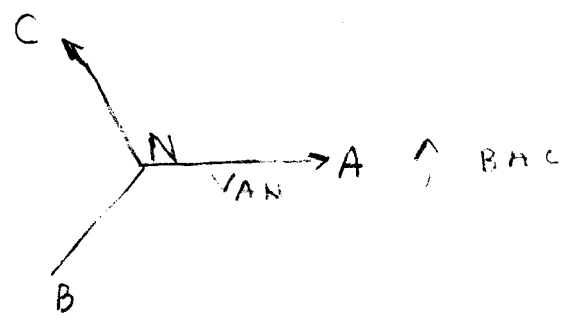

b)

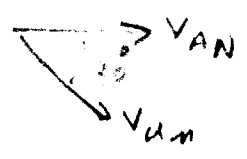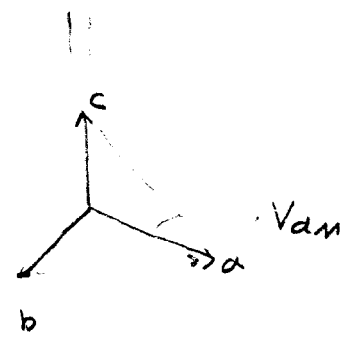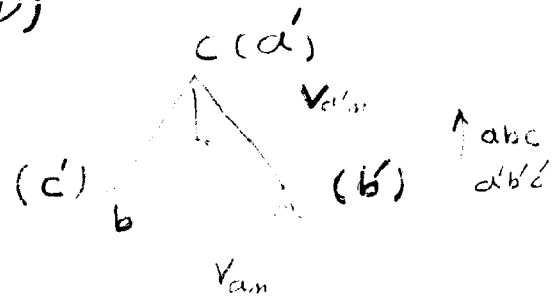


\hat{V}_{AN} lead \hat{V}_{an} by 30°

Problemset #4


2

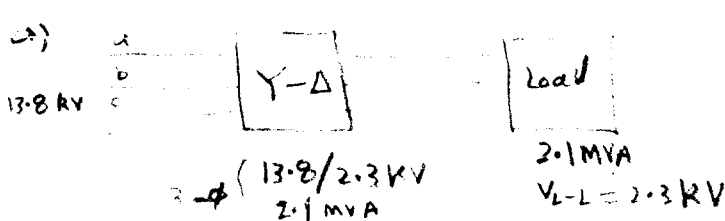4.13 Consider a bank of three single-phase two-winding transformers whose high-voltage terminals are connected to a three-phase, 13.8-kV feeder. The low-voltage terminals are connected to a three-phase substation load rated 2.1 MVA and 2.3 kV. Determine the required voltage, current, and MVA ratings of both windings of each transformer, when the high-voltage/low-voltage windings are connected (a) Y-Δ, (b) Δ-Y, (c) Y-Y, and (d) Δ-Δ.





$$\text{single-phase rating} = \frac{2.1}{3} = 0.7 \text{ MVA}$$
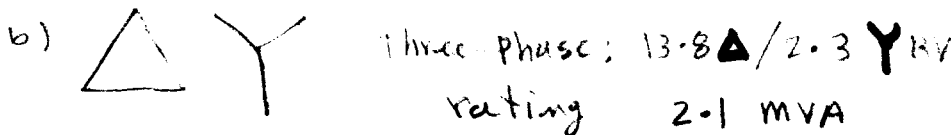
$$\text{Single-phase voltage rating} = \frac{13.8}{\sqrt{3}} / 2.3 \text{ kV}$$



$$\text{Single-phase rating: } \frac{2.1}{3} = 0.7 \text{ MVA}$$
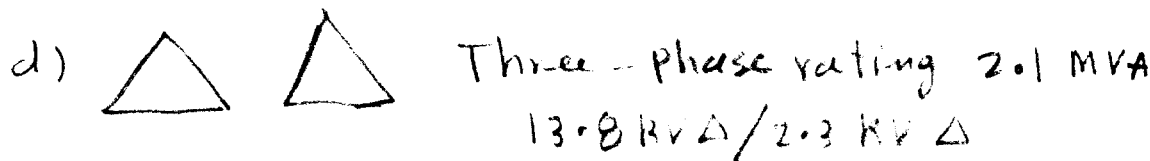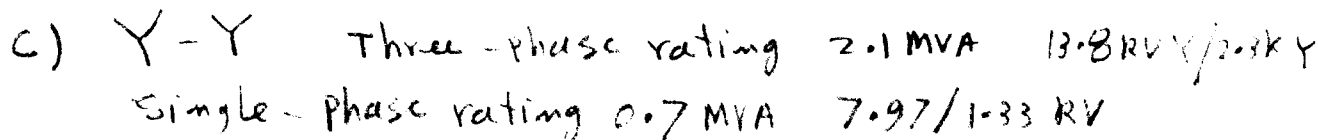
$$\text{Single-phase voltage rating } 13.8 \text{ kV} / \frac{2.3}{\sqrt{3}} \text{ OR } 13.8 / 1.33 \text{ kV}$$



$$\text{Single-phase rating: } 0.7 \text{ MVA } 13.8 / 2.3 \text{ kV}$$

Problem set #4

3


4.17 Consider the single-line diagram of the power system shown in Figure 4.33. Equipment ratings are:

generator 1:	1000 MVA, 18 kV, $X'' = 0.2$ per unit
generator 2:	1000 MVA, 18 kV, $X'' = 0.2$
synchronous motor 3:	1500 MVA, 20 kV, $X'' = 0.2$
3-phase Δ -Y transformers T_1, T_2, T_3, T_4 :	1000 MVA, 500 kV Y/20 kV Δ , $X = 0.1$
3-phase Y-Y transformer T_5 :	1500 MVA, 500 kV Y/20 kV Y, $X = 0.1$

Neglecting resistance, transformer phase shift, and magnetizing reactance, draw the positive-sequence reactance diagram. Use a base of 1000 MVA and 500 kV for the 50-ohm line. Determine the per-unit reactances.

Figure 4.33

Problems 4.17, 4.18, 4.19

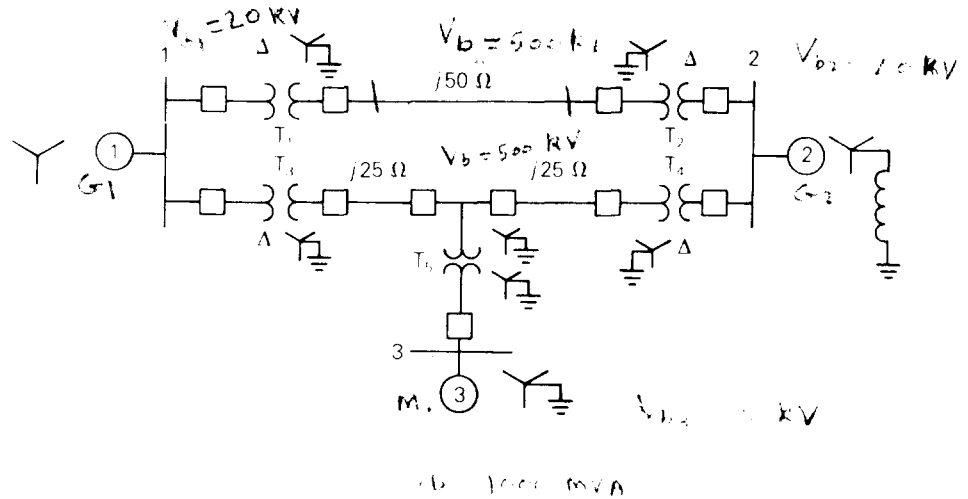

$$V_{b1} = \frac{18}{\sqrt{3}} \left(\frac{1000}{1000} \right) = 10.39 \text{ kV}$$

$$V_{b2} = \frac{18}{\sqrt{3}} \left(\frac{1000}{1000} \right) = 10.39 \text{ kV}$$

$$X''_{g1} = 0.2 \left(\frac{18}{20} \right)^2 \left(\frac{1000}{1000} \right) = 0.162 \text{ p.u.}$$

$$X''_{g2} = X''_{g1} = 0.162 \text{ p.u.}$$

$$X''_{m3} = 0.2 \left(\frac{20}{20} \right)^2 \left(\frac{1000}{1500} \right) = 0.1333 \text{ p.u.}$$

$$X_{T1} = X_{T2} = X_{T3} = X_{T4} = 0.10 \text{ p.u.}$$

$$X_{T5} = 0.1 \left(\frac{20}{20} \right)^2 \left(\frac{1000}{1500} \right) = 0.06667 \text{ p.u.}$$

$$Z_{base 500} = \frac{(500)^2}{1000} = 250 \text{ } \Omega$$


$$X_{line 50} = \frac{50}{250} = 0.2 \text{ p.u.}$$

$$X_{line 25} = \frac{25}{250} = 0.1 \text{ p.u.}$$

Problem Set #4

4

4.17 cont.

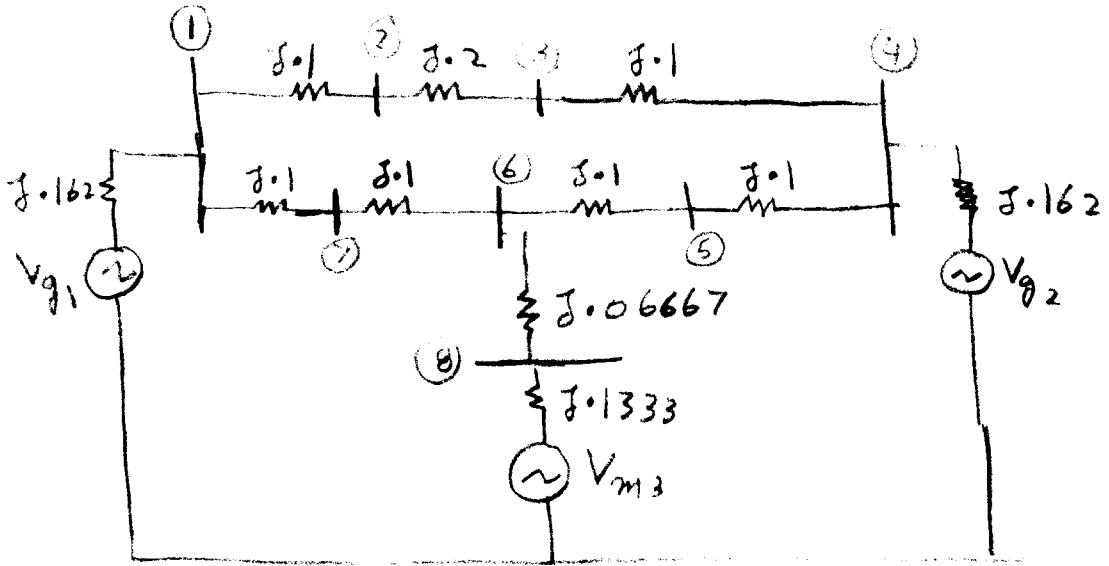


Set #4


5

4.19 Draw the zero-sequence reactance diagram for the power system shown in Figure 4.33. The zero-sequence reactance of each generator and of the synchronous motor is 0.05 per unit based on equipment ratings. Generator 2 is grounded through a neutral reactor of 0.06 per unit on a 100-MVA, 18-kV base. The zero-sequence reactance of each transmission line is assumed to be three times its positive-sequence reactance. Use the same base as in Problem 4.17.

Figure 4.33
Problems 4.17, 4.18, 4.19

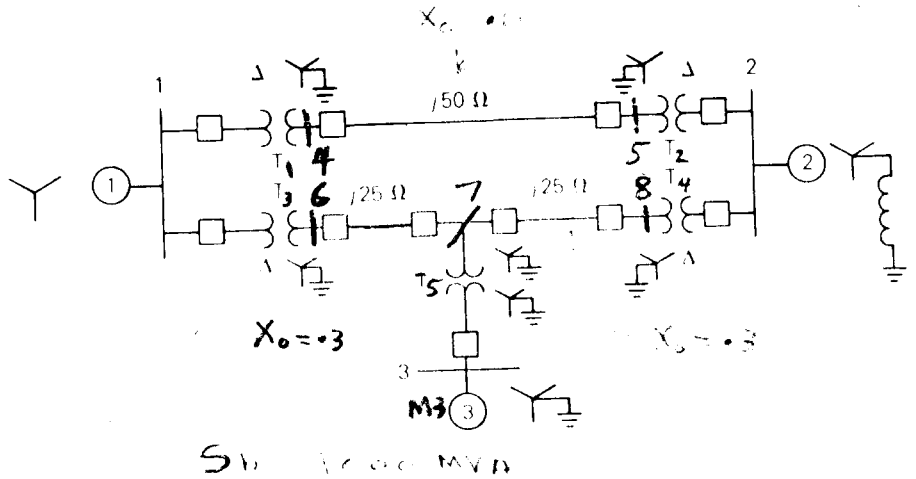

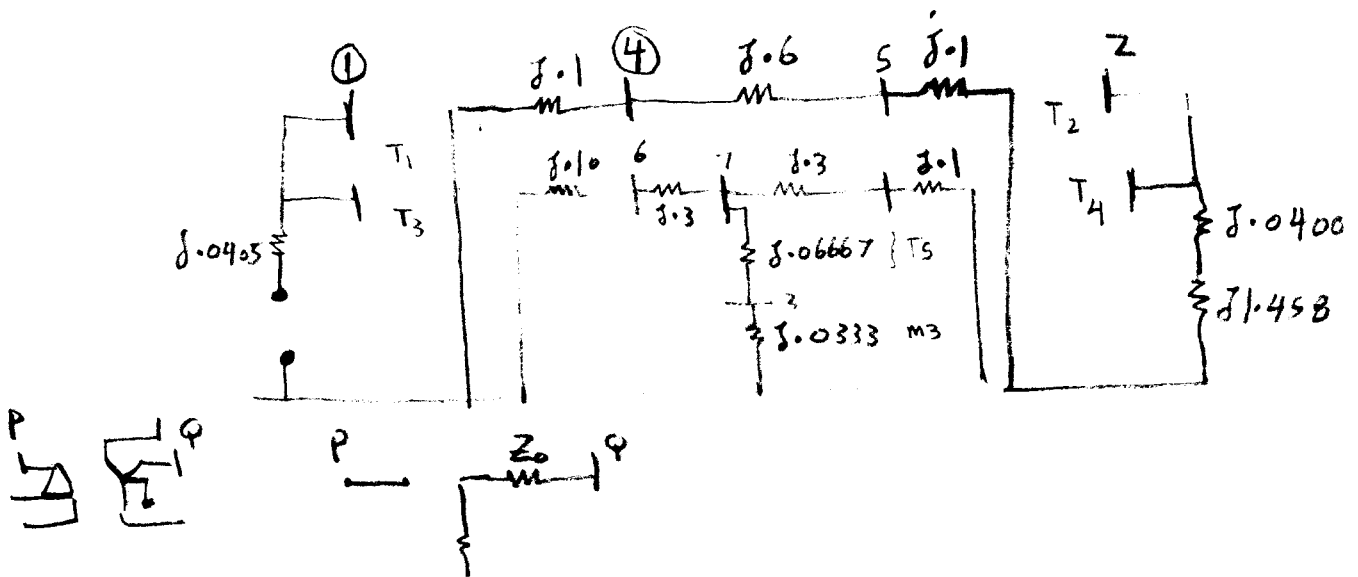$X_{T1-0} = X_{T2-0} = X_{T3-0} = X_{T4-0} = 0.1$ $X_{T5-0} = 0.06667$
 $X_{g1-0} = (0.05) \left(\frac{18}{20} \right)^2 = 0.0405 \text{ p.u.} = X_{g2-0}$
 $X_{m3-0} = (0.05) \left(\frac{1000}{1500} \right) = 0.0333 \text{ p.u.}$
 $X_{n2} = (0.06) \left(\frac{18}{20} \right) \left(\frac{1000}{100} \right) = 0.486 \text{ p.u.}$ $3X_{n2} = 1.458 \text{ p.u.}$




Problem set #4

i.

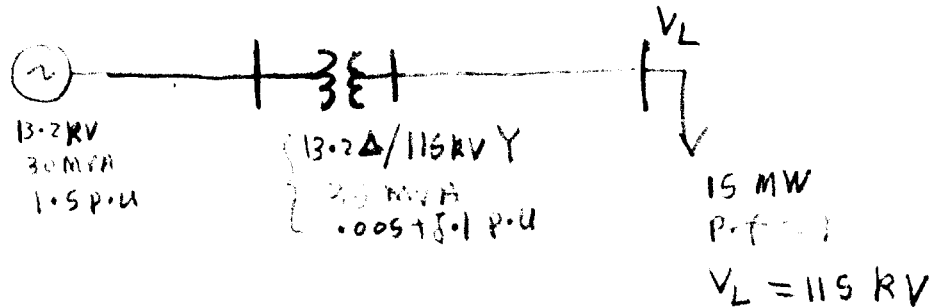4.21


A 30-MVA, 13.2-kV three-phase generator, which has a positive-sequence reactance of 1.5 per unit on the generator base is connected to a 35-MVA, 13.2Δ/115 Y-kV step-up transformer with a series impedance of $(0.005 + j0.1)$ per unit on its own base. (a) Calculate the per-unit generator reactance on the transformer base. (b) The load at the transformer terminals is 15 MW at unity power factor and at 115 kV. Choosing the transformer high-side voltage as the reference phasor, draw a phasor diagram for this condition. (c) For the condition of part (b), find the transformer low-side voltage and the generator internal voltage behind its reactance. Also compute the generator output power and power factor.



a) $S_{U_{new}} = 35 \text{ MVA}$


$X_{T_{new}} = 1.5 \left(\frac{13.2}{13.2} \right)^2 \left(\frac{35}{30} \right) = 1.75 \text{ p.u.}$

P.U. Eq. CRT

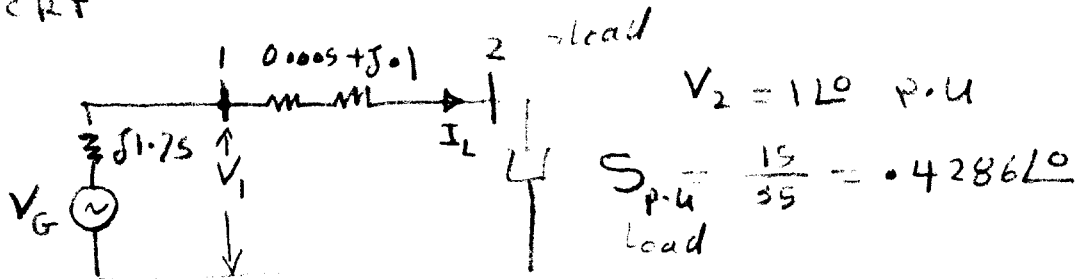

V_1 = Generator terminal voltage

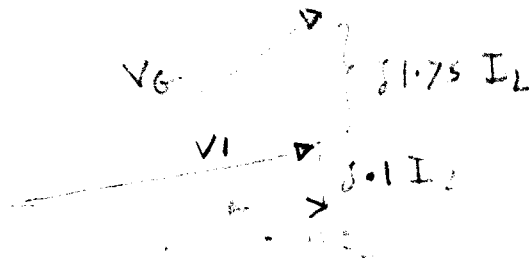$I_L = \frac{S}{V_2} = \frac{0.4286 \text{ L}^0}{1.0} = 0.4286 \text{ L}^0$



7

4.21 cont.

$$V_1 = I_L (\cdot 009 + j \cdot 1) I_L + V_2$$

$$V_1 = 0.4286 \angle 0^\circ (\cdot 009 + j \cdot 1) + 1 \angle 0^\circ = 1.0021 \angle 0.12^\circ$$

$$V_G = I_L (j 1.75 + \cdot 009 + j \cdot 1) + V_2$$

$$V_G = 1.793 \angle 0.067^\circ \text{ p.u.}$$

$$V_{\text{actual}} = (1.0021)(13.2) = 13.23 \text{ kV}$$

$$V_G = (1.793)(13.2) = 23.67 \text{ kV}$$




$$S_1 = (V_1 I_L^*) = 0.4295 \angle -0.12^\circ \text{ p.u.}$$

$$S_{\text{actual}} = (S_1) \times S_b = 15.03 \text{ MW} + j \cdot 0.3 \text{ Mvars}$$

$$\text{p.f.} = \cos(0.12^\circ) = 0.999 \text{ lagging}$$

Section 4.6

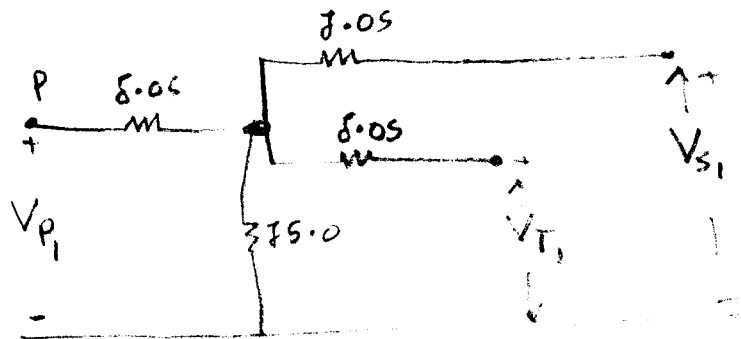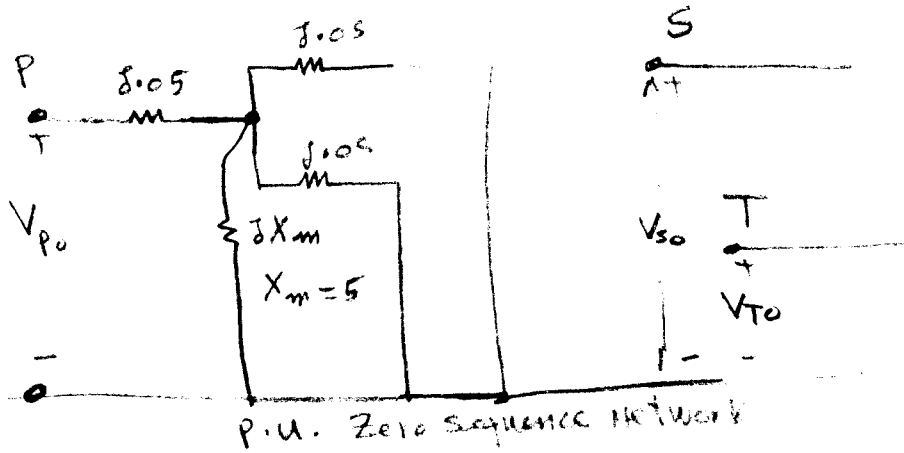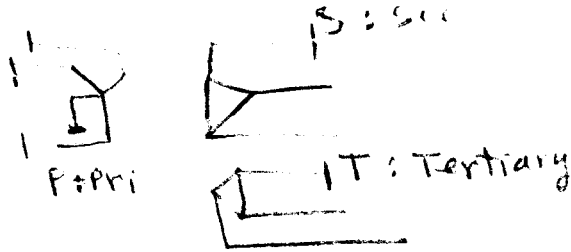4.22 A single-phase three-winding transformer has the following parameters: $Z_1 = Z_2 = Z_3 = 0 + j0.05$, $G_c = 0$, and $B_m = 0.2$ per unit. Three identical transformers, as described, are connected with their primaries in Y (solidly grounded neutral) and with their secondaries and tertiaries in Δ . Draw the per-unit sequence networks of this transformer bank.



Per unit positive (or negative) Sequence Network