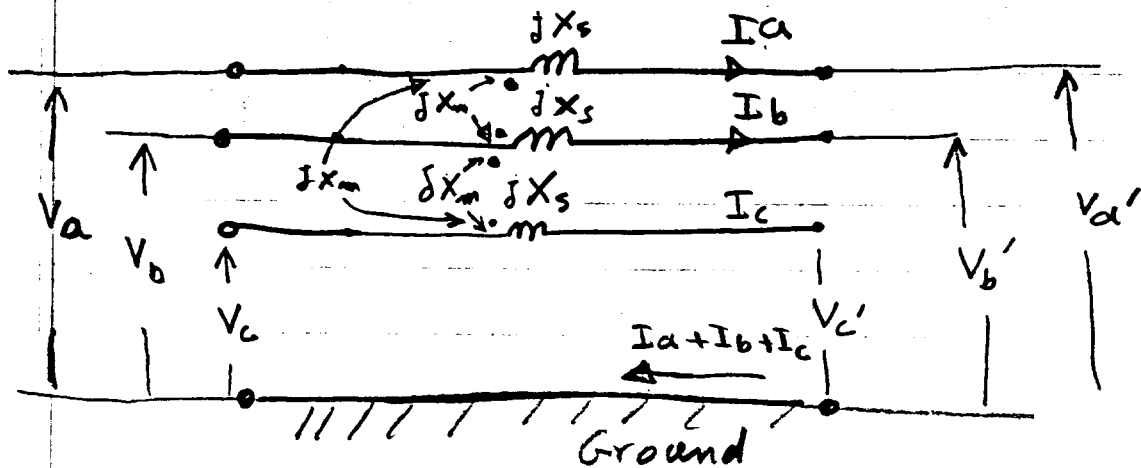


Sequence Impedances of 3- ϕ balanced transmission lines



$$\begin{aligned} V_a &= jX_s I_a + jX_m I_b + jX_m I_c + V_a' \\ V_b &= jX_s I_b + jX_m I_a + jX_m I_c + V_b' \\ V_c &= jX_s I_c + jX_m I_a + jX_m I_b + V_c' \end{aligned}$$

In matrix notation

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} - \begin{bmatrix} V_a' \\ V_b' \\ V_c' \end{bmatrix} = j \begin{bmatrix} X_s & X_m & X_m \\ X_m & X_s & X_m \\ X_m & X_m & X_s \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\begin{bmatrix} V_{abc} \\ V_{abc} \end{bmatrix} - \begin{bmatrix} V_{abc}' \\ V_{abc}' \end{bmatrix} = j \begin{bmatrix} Z^{abc} \end{bmatrix} \begin{bmatrix} I_{abc} \\ I_{abc} \end{bmatrix} \quad \text{①}$$

Recall

$$\begin{bmatrix} V_{abc}^{abc} \end{bmatrix} = \begin{bmatrix} T_s \end{bmatrix} \begin{bmatrix} V_{0,1,2} \end{bmatrix} \quad \text{②}$$

$$\begin{bmatrix} I_{abc}^{abc} \end{bmatrix} = \begin{bmatrix} T_s \end{bmatrix} \begin{bmatrix} I_{0,1,2} \end{bmatrix} \quad \text{③}$$

(2)

Replace V_{abc} by Eq (2)

" I_{abc} by Eq (3)

$$[T_s][V_{012}] - [T_s][V'_{012}] = [Z_{abc}][T_s][I_{012}] \quad (4)$$

multiply (4) by T_s^{-1} and we get

$$\underbrace{[T_s]^{-1}}_I [T_s][V_{012}] - \underbrace{[T_s]^{-1}}_I [T_s][V'_{012}] = \underbrace{[T_s]^{-1}}_I [Z_{abc}] \underbrace{[T_s]}_I [I_{012}]$$

$$[V_{012}] - [V'_{012}] = [Z_{012}][I_{012}] \quad (A)$$

$$[Z_{012}] = [T_s]^{-1} [Z_{abc}] [T_s]$$

$$[Z_{012}] = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} X_s & X_m & X_m \\ X_m & X_s & X_m \\ X_m & X_m & X_s \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$[Z_{012}] = \frac{1}{3} \begin{bmatrix} (X_s + 2X_m) & (X_s + 2X_m) & X_s + 2X_m \\ (X_s - X_m) & (aX_s + (1+a^2)X_m) & (a^2X_s + (1+a)X_m) \\ (X_s - X_m) & (a^2X_s + (1+a)X_m) & (aX_s + (1+a^2)X_m) \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$Z_{012} = j \begin{bmatrix} X_s + 2X_m & 0 & 0 \\ 0 & X_s - X_m & 0 \\ 0 & 0 & X_s - X_m \end{bmatrix} \quad (5)$$

$$Z_0 = \text{Zero sequence impedance} = j(X_s + 2X_m)$$

$$Z_1 = \text{Positive sequence impedance} = j(X_s - X_m)$$

$$Z_2 = \text{Negative sequence impedance} = j(X_s - X_m)$$

Note some book use the notation '012' for (0, + -)

$$V_{abc} = [T_s] [V_{012}]$$

$$I_{abc} = [T_s] [I_{012}]$$

$$Z^{012} = Z^{0+-}$$

From Eq. (4)



$$\begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_0' \\ V_1' \\ V_2' \end{bmatrix} = j \begin{bmatrix} X_s + 2X_m & 0 & 0 \\ 0 & X_s - X_m & 0 \\ 0 & 0 & X_s - X_m \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

C

$$V_0^{\circ} - V_0^{\prime} = j (X_s + 2X_m) I_0^{\circ}$$

$$V_1^{\dagger} - V_1^{\prime} = j (X_s - X_m) I_1^{\dagger}$$
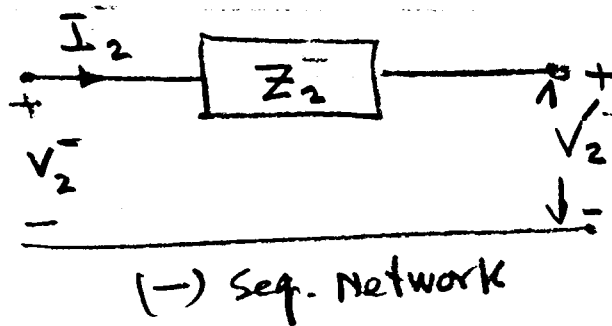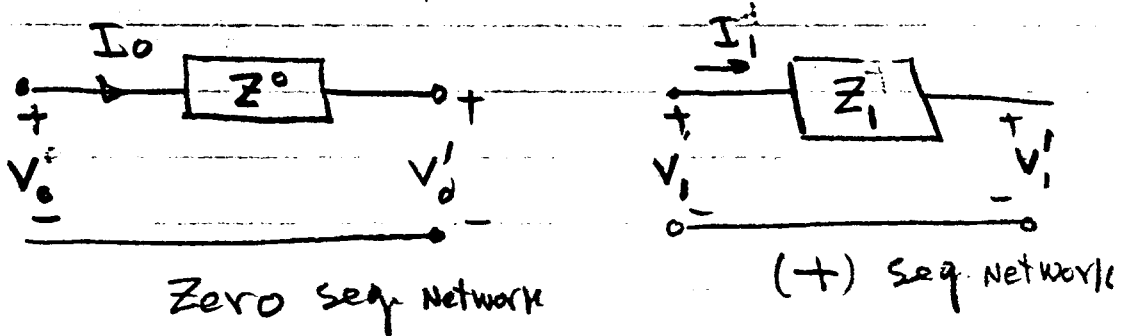
$$V_2^{-} - V_2^{\prime} = j (X_s - X_m) I_2^{-}$$



Power.

$$S_{3\phi} = V_a I_a^* + V_b I_b^* + V_c I_c^*$$

$$S_{3\phi} = [V_{abc}]^t [I_{abc}^*]$$

$$= \{ [T] [V_{012}] \}^t [T I_{012}^*]$$

C

$$S_{3\phi} = 3 [V_0^{\circ} I_0^{\circ*} + V_1^{\dagger} I_1^{\dagger*} + V_2^{-} I_2^{-*}]$$

$$= 3 [S_{012}]$$

