
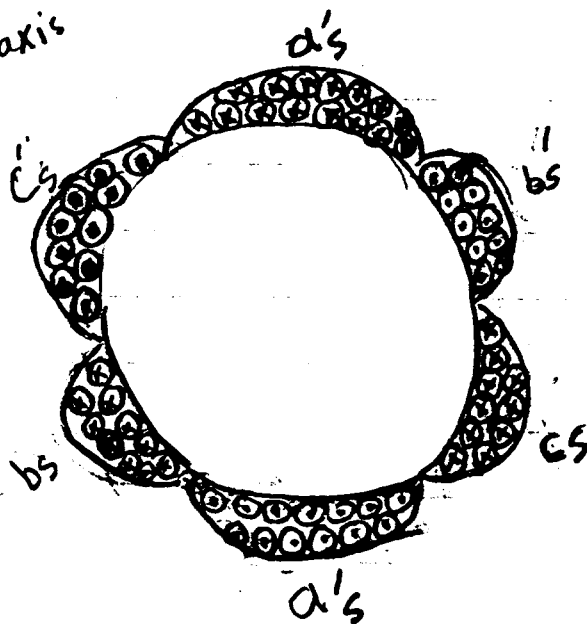
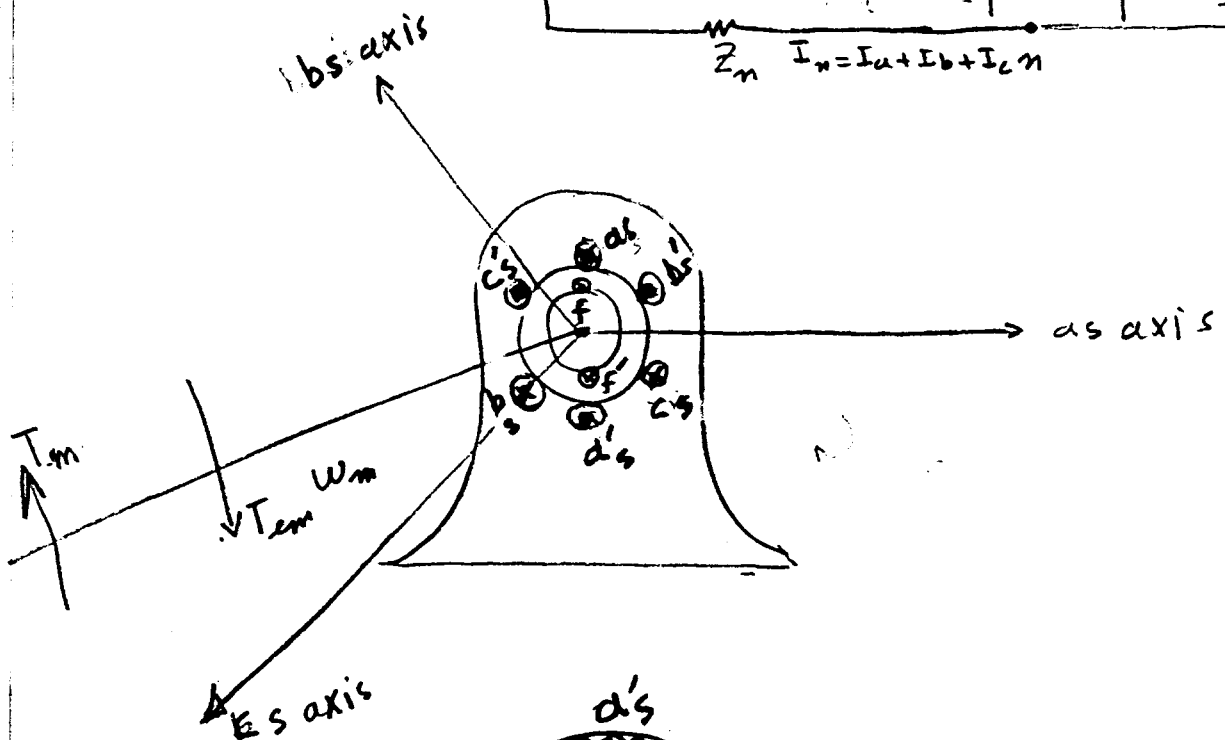


EE740
Lecture #1
Synchronous Machine Sequence Network. ①

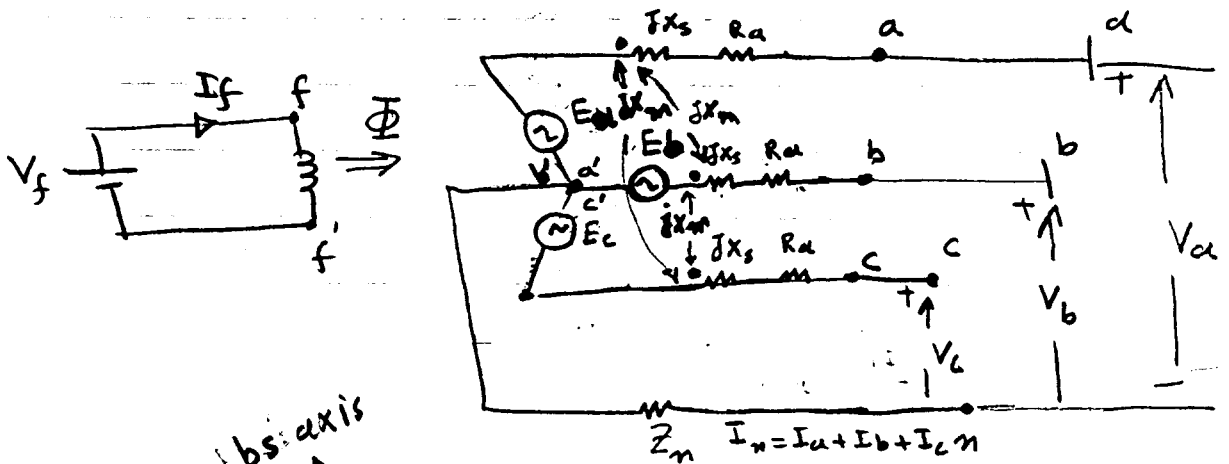Sequence networks for Synchronous Machine



Consider the steady state operation

- ω_m constant
- constant I_f
- No saturation
- balanced 3- ϕ windings located 120° apart.

$$E_a = (R_a + jX_s + Z_m)I_a + (jX_m + Z_m)I_b + (jX_m + Z_m)I_c + V_a$$

$$E_b = (R_a + jX_s + Z_m)I_b + (jX_m + Z_m)I_a + (jX_m + Z_m)I_c + V_b$$


$$E_c = (R_a + jX_s + Z_m)I_c + (jX_m + Z_m)I_a + (jX_m + Z_m)I_b + V_c$$

Balanced voltage set

$$E_a = E$$

$$E_b = a^2 E$$

$$E_c = a E$$

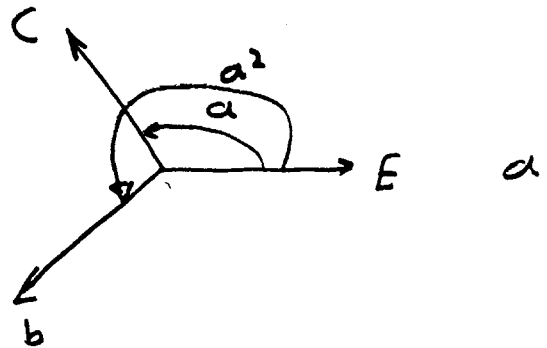

$$\text{Let } Z_s = R_a + jX_s + Z_m$$

$$Z_m = jX_m + Z_m$$

Then ① can be written as

$$\begin{bmatrix} E_a \\ E_b \\ E_c \end{bmatrix} = \begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} + \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \quad (4)$$

③

$$[E_{abc}] = [Z_{abc}] [I_{abc}] + [V_{abc}] \quad (5)$$

Recall

$$[E_{abc}] = [T_s] [E_{012}] \quad (6) \text{ or } E_{012} = T_s^{-1} E_{abc}$$

$$[I_{abc}] = [T_s] [I_{012}] \quad (7)$$

multiply Eq (5) by T_s^{-1} and replace I_{abc} with Eq. 7

$$[T_s]^{-1} [E_{abc}] = [T_s]^{-1} [Z_{abc}] [T_s] [I_{012}] + [T_s]^{-1} [V_{abc}]$$

observe that

$$\begin{bmatrix} E_0 \\ E_1 \\ E_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} E \\ a^2 E \\ a E \end{bmatrix} = \frac{E}{3} \begin{bmatrix} 0 \\ 3 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ E \\ 0 \end{bmatrix}$$

That is, for a balanced set of voltages

$$E_0 = 0$$

$$E_1 = E$$

$$E_2 = 0$$

(10)

Recall

$$[T]^{-1} [V_{abc}^{abc}] = [V_{012}^{0+-}]$$

$$[T_s]^{-1} [Z_{abc}^{abc}] = [Z_{012}^{0+-}] = \begin{bmatrix} Z_0^0 & 0 & 0 \\ 0 & Z_1^+ & 0 \\ 0 & 0 & Z_2^- \end{bmatrix} //$$

where $Z_0 = Z_{ogen} + 3Z_m$

$$Z_{ogen} = R_a + j(X_s + 2X_m)$$

$$Z_1^+ = Z_s - Z_m = R_a + j(X_s - X_m) \quad (12)$$

$$Z_2^- = Z_s - Z_m = R_a + j(X_s - X_m)$$

Therefore Eq. 8 can be written as

$$\begin{bmatrix} 0 \\ E \\ 0 \end{bmatrix} = \begin{bmatrix} Z_0^0 & 0 & 0 \\ 0 & Z_1^+ & 0 \\ 0 & 0 & Z_2^- \end{bmatrix} \begin{bmatrix} I_0^0 \\ I_1^+ \\ I_2^- \end{bmatrix} + \begin{bmatrix} V_0^0 \\ V_1^+ \\ V_2^- \end{bmatrix}$$

$$Z_0^0 I_0^0 + V_0^0 = 0$$

$$E = Z_1^+ I_1^+ + V_1^+$$

$$Z_2^- I_2^- + V_2^- = 0$$