

HW #3

EE743

A. Keyhani

Problem 1. An iron-core transformer which has two windings is shown in Fig. 1. $N_1 = 50$ turns, $N_2 = 100$ turns, and $\mu_r = 4000$. Calculate L_{12} , L_{m1} and L_{m2} and polarity of coupled coils with appropriate dots.

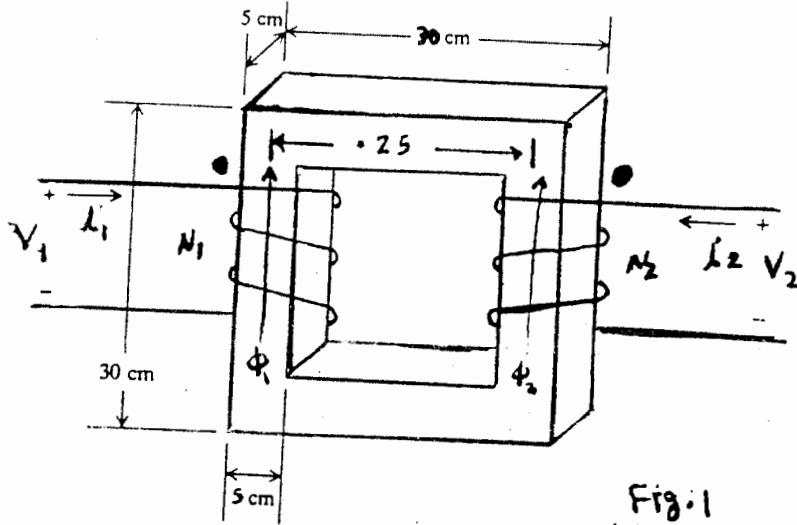


Fig. 1

Solution

$$R_m = \frac{l}{\mu_i A} \quad \mu_i^{-1} \mu_i = \mu_0 \mu_{ri} = (4000)(4\pi \times 10^{-7})$$

$$A = (0.05)(0.05) = 0.0025 \text{ m}^2$$

$$l = 4(0.30 - 0.05) = 4(0.25) = 1 \text{ m}$$


$$R_m = 79,577 \text{ H}^{-1}$$

$$L_{12} = \frac{N_1 N_2}{R_m} = \frac{(50)(100)}{79,577} = 0.0628 \text{ H}$$

$$L_{m1} = \frac{N_1^2}{R_m} = \frac{50^2}{79,577} = 0.0314 \text{ H}$$

$$L_{m2} = \frac{N_2^2}{R_m} = \frac{100^2}{79,577} = 0.1257 \text{ H}$$

Equivalent circuit model:

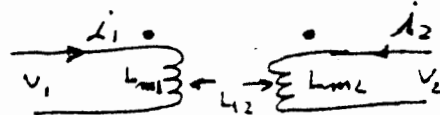

—|—

Problem 2. Two coupled coils have the following parameters:

$$r_1 = 10 \text{ } (\Omega), \quad L_{\ell 1} = 0.1 L_{11}, \quad r_2 = 2.5 \text{ } (\Omega), \quad L_{\ell 2} = 0.1 L_{22},$$


$$L_{11} = 100 \text{ (mH)}, \quad N_1 = 100 \text{ turns}, \quad L_{22} = 25 \text{ mH}, \quad N_2 = 50 \text{ turns}$$

Develop an equivalent T circuit with (a) Winding 1

as the reference winding and (b) Winding (2) as reference

winding.

(P.6)

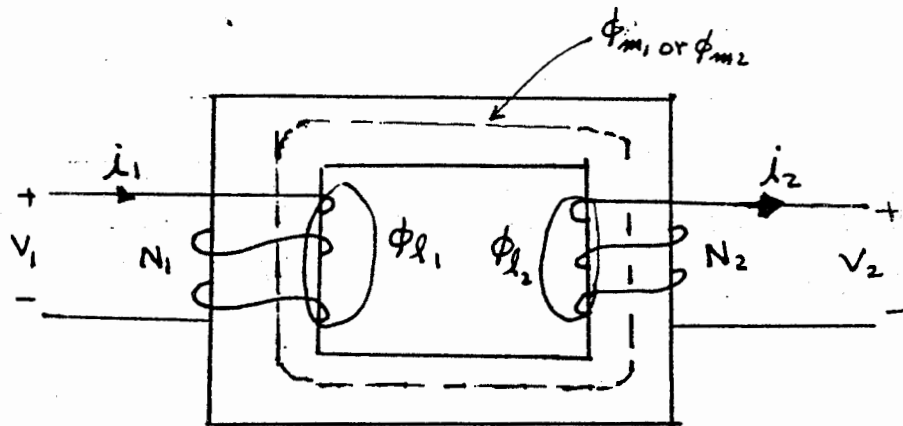

$$\Phi_1 = \phi_{\ell 1} + \phi_{m1} + \phi_{m2} = \frac{N_1 i_1}{\mathcal{R}_{\ell 1}} + \frac{N_1 i_1}{\mathcal{R}_m} + \frac{N_2 i_2}{\mathcal{R}_m}$$

$$\lambda_1 = N_1 \Phi_1 = \frac{N_1^2}{\mathcal{R}_{\ell 1}} i_1 + \frac{N_1^2}{\mathcal{R}_m} i_1 + \frac{N_1 N_2}{\mathcal{R}_m} i_2$$

Define

$$L_{11} = \frac{N_1^2}{\mathcal{R}_{\ell 1}} + \frac{N_1^2}{\mathcal{R}_m} = L_{\ell 1} + L_{m1}$$

Similarly,


$$L_{22} = L_{\ell 2} + L_{m2}$$

$$L_{m1} = L_{11} - L_{\ell 1} = 100 - 0.1(100) = 90 \text{ (mH)}$$

$$L_{\ell 2} = 0.1 L_{22} = 0.1(25 \text{ mH}) = 2.5 \text{ (mH)}$$

$$L'_{\ell 2} = \left(\frac{N_1}{N_2}\right)^2 L_{\ell 2} = \left(\frac{100}{50}\right)^2 (2.5 \times 10^{-3}) = 10 \text{ (mH)}$$
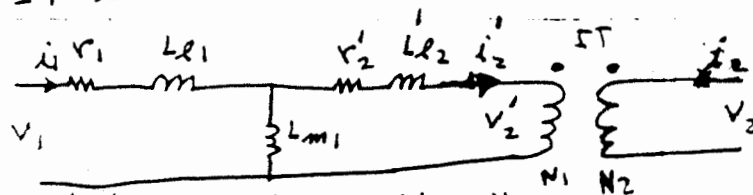
$$r'_2 = \left(\frac{N_1}{N_2}\right)^2 r_2 = 10 \text{ } \Omega$$



'T' Equivalent circuit with winding 1 as a reference.


Problem 2 cont. b)

$$L_{22} = L_{l2} + L_{m2} \quad L_{l2} = 0.1 \quad L_{22} = 0.1(25) = 2.5 \text{ (mH)}$$

$$L_{m2} = L_{22} - L_{l2} = 25 - 2.5 = 22.5 \text{ (mH)}$$

$$L'_{l1} = \left(\frac{N_2}{N_1}\right)^2 L_{l1} = \left(\frac{50}{100}\right)^2 (10 \times 10^{-3}) = 2.5 \text{ (mH)}$$
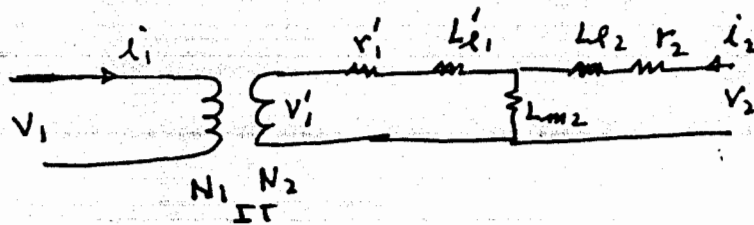
$$r'_1 = \left(\frac{N_2}{N_1}\right)^2 r_1 = \left(\frac{50}{100}\right)^2 (10) = 2.5 \text{ (}\Omega\text{)}$$



Equivalent circuit with
Winding 2 as a reference.

- Problem 3. Two coupled coils have the following parameters: $r_1 = 10 \Omega$, $L_{l1} = 0.1 L_{11}$, $r_2 = 2.5 \Omega$, $L_{l2} = 0.1 L_{22}$, $L_{11} = 100 \text{ (mH)}$, $N_1 = 100$ turns, $L_{22} = 25 \text{ (mH)}$, $N_2 = 50$ turns. Develop a coupled coil equivalent circuit and compare with its T equivalent circuit.

Solution: Recall

$$\Phi_1 = \phi_{l1} + \phi_{m1} + \phi_{m2} = \frac{N_1 i_1}{\mathcal{R}_{l1}} + \frac{N_1 i_1}{\mathcal{R}_m} + \frac{N_2 i_2}{\mathcal{R}_m}$$

$$\lambda_1 = N_1 \Phi_1 = \frac{N_1^2}{\mathcal{R}_{l1}} i_1 + \frac{N_1^2}{\mathcal{R}_m} i_1 + \frac{N_1 N_2}{\mathcal{R}_m} i_2$$

Define self inductance

$$L_{11} = \frac{N_1^2}{\mathcal{R}_{l1}} + \frac{N_1^2}{\mathcal{R}_m} = L_{l1} + L_{m1}$$

$$L_{12} = \frac{N_1 N_2}{\mathcal{R}_m}$$

$$\lambda_2 = N_2 \Phi_2 = \frac{N_2^2}{\mathcal{R}_{l2}} i_2 + \frac{N_2^2}{\mathcal{R}_m} i_2 + \frac{N_1 N_2}{\mathcal{R}_m} i_1$$

define

$$L_{22} = \frac{N_2^2}{\mathcal{R}_{l2}} + \frac{N_2^2}{\mathcal{R}_m} = L_{l2} + L_{m2}$$

$$L_{21} = \frac{N_1 N_2}{\mathcal{R}_m}$$

$$\boxed{L_{21} = L_{12}}$$

and also

$$L_{m2} = \frac{N_2^2}{\mathcal{R}_m}$$

$$\frac{L_{21}}{L_{m2}} = \frac{N_1 N_2}{\mathcal{R}_m} \times \frac{\mathcal{R}_m}{N_2^2} = \frac{N_1}{N_2}$$

$$L_{21} = \frac{N_1}{N_2} L_{m2} = \frac{N_2}{N_1} L_{m1}$$

$$\lambda_1 = L_{11} i_1 + L_{12} i_2$$

$$\lambda_2 = L_{21} i_1 + L_{22} i_2$$

Problem 3 cont.

$$L_{\cancel{2}1} = L_{11} - L_{l1} = 100 - 0.1(100) = 90 \text{ (mH)}$$


$$L_{l2} = 0.1 L_{22} = 0.1 (25 \text{ mH}) = 2.5 \text{ (mH)}$$

$$L_{m2} = L_{22} - L_{l2} = 25 - 0.1(25) = 22.5 \text{ (mH)}$$


$$L_{l1} = 0.1 L_{11} = 0.1(100) = 10 \text{ (mH)}$$

$$L_{21} = \frac{N_1}{N_2} L_{m2} = \frac{100}{50} (22.5) = 45 \text{ (mH)}$$
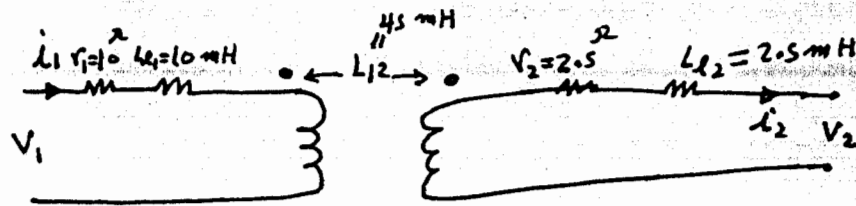
$$L_{12} = \frac{N_2}{N_1} L_{m1} = \frac{50}{100} (90) = 45 \text{ (mH)}$$




coupled coil equivalent circuit.

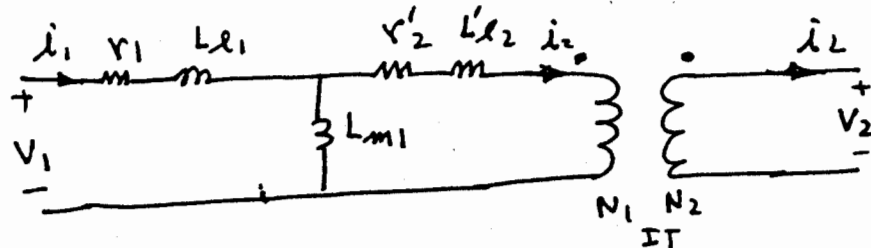

"T" Equivalent circuit
with winding "1" as a reference.

Problem 4. Consider a two-winding transformer with (P-12)
 an "T" equivalent circuit model. Assume $r_1 = 6 \Omega$, $L_{m1} = 263.9$
 (mH), $L_{l1} = 13.5$ (mH), $r_2 = 5 \Omega$, $L_{l2} = 13.5$ mH. Compute the
 transient response of the transformer winding 1 current
 $i_1(t)$, assuming the windings are initially unexcited and
 winding "2" is open-circuited. Assume a) when the switch
 is closed, the sinusoidal input voltage is at its maximum value,
 b) the input voltage is at its zero crossing point. ($\omega = 377$ rad/sec
 and $V_{max} = \sqrt{2} 110$ volts)

Solution

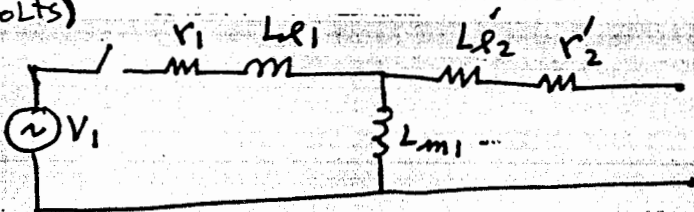

$$V_1 = r_1 i_1 + \frac{d\lambda_1}{dt}, \quad \lambda_1 = (L_{l1} + L_{m1}) i_1 = L_{11} i_1$$

$$V_1 = r_1 i_1 + L_{11} \frac{di_1}{dt}, \quad i_1 = i_{tr} + i_{ss}, \quad i_{tr} = k e^{-r_1/L_{11} t}$$

a) $V_1 = \sqrt{2} 110 \cos \omega t = \sqrt{2} V_s \cos \omega t$

$$i_{ss} = \frac{\sqrt{2} V_s}{|Z|} \cos(\omega t - \phi), \quad \phi = \tan^{-1} \frac{\omega L_{11}}{r_1}$$

$$i_1 = k e^{-r_1/L_{11} t} + \frac{\sqrt{2} V_s}{|Z|} \cos(\omega t - \phi)$$

where

at $t=0$ $i_1(0) = 0$, thus

$$k = -\frac{\sqrt{2} V_s}{|Z|} \cos(-\phi)$$

b) $V_1 = \sqrt{2} V_s \sin \omega t$

$$i_1 = k e^{-r_1/L_{11} t} + \frac{\sqrt{2} V_s}{|Z|} \sin(\omega t - \phi)$$

where

at $t=0$ $i_1(0) = 0$, thus

$$k = -\frac{\sqrt{2} V_s}{|Z|} \sin(-\phi) = \frac{\sqrt{2} V_s}{|Z|} \sin \phi$$

Problem 4) For part a)

$$Z = \sqrt{(6)^2 + [(377)(13.5 + 263.9) \times 10^{-3}]^2} = 104.75 \Omega$$

$$\phi = \tan^{-1} \frac{(377)(13.5 + 263.9) \times 10^{-3}}{6} = -86.7^\circ$$

$$K = -\frac{\sqrt{2} 110}{104.75} \cos(-86.7^\circ) = -0.085$$

$$\frac{R_1}{L_1} = \frac{6}{0.2774} = 21.6$$

$$i_1(t) = -0.085 e^{-21.6t} + 1.48 \cos(377t - 86.7^\circ) \text{ A}$$

For part b)

$$K = +\frac{\sqrt{2} 110}{104.75} \sin(86.7^\circ) = 1.48$$

$$i_1(t) = 1.48 e^{-21.6t} + 1.48 \sin(377t - 86.7^\circ) \text{ A}$$

Problem 5. Consider the elementary electromagnet shown in Fig. 1. Assume that the cross-sectional area of the stationary and movable member is the same and $A_i = A_g = 4 \text{ cm}^2$. Assume $l_i = 20 \text{ cm}$, $N = 500$ and $\mu_{ri} = 1000$. a) Derive an expression for the magnetizing inductance $L_m(x)$. b) Compute the value of the magnetizing inductance when $x = 1 \text{ mm}$.

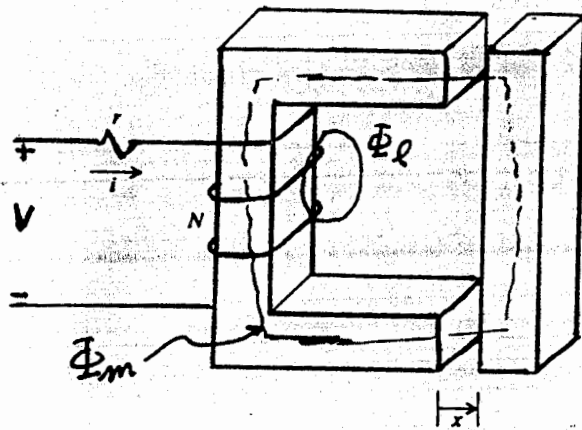


Fig. 1 Elementary electromagnet

Solution.

$$v = ri + \frac{d\lambda}{dt}$$

flux linkage

$$\lambda = N\Phi \quad , \quad \Phi = \Phi_l + \Phi_m$$

$$\Phi_l = \frac{Ni}{\mathcal{R}_l} \quad \Phi_m = \frac{NI}{\mathcal{R}_m}$$

$$\lambda = \left(\frac{N^2}{\mathcal{R}_l} + \frac{N^2}{\mathcal{R}_m} \right) i \quad L_l (\text{leakage}) = \frac{N^2}{\mathcal{R}_l}$$

magnetizing inductance

$$L_m = \frac{N^2}{\mathcal{R}_m}$$

reluctance of the magnetizing path

$$\mathcal{R}_m = \mathcal{R}_i + 2\mathcal{R}_g$$

R_i : total reluctance of the magnetic material of the stationary and movable members.

R_g : Reluctance of the air gaps.

$$R_i = \frac{l_i}{\mu_{ri} \mu_0 A_i}, \quad R_g = \frac{x}{\mu_0 A_g}$$

Assume $A_g = A_i$

$$R_m = \frac{1}{\mu_0 A_i} \left(\frac{l_i}{\mu_{ri}} + 2x \right)$$

$$\lambda_m = N \Phi_m = \frac{N^2}{R_m} i \quad L_m = \frac{N^2}{R_m}$$

$$L_m = \frac{N^2}{\left(\frac{1}{\mu_0 A_i} \right) \left(\frac{l_i}{\mu_{ri}} + 2x \right)} = L_m(x)$$

$$L_m(x) = \frac{(N^2 \mu_0 A_i / 2)}{\left(\frac{l_i}{2 \mu_{ri}} \right) + x} = \frac{K}{K_0 + x}$$

$$K = \frac{N^2 \mu_0 A_i}{2} = \frac{(500)^2 4\pi \times 10^{-7} \times 4 \times 10^{-4}}{2} = 2\pi \times 10^{-5}$$

$$K_0 = \frac{l_i}{2 \mu_{ri}} = \frac{20 \times 10^{-2}}{2(1000)} = 10^{-4}$$

$$L_m(x) = \frac{2\pi \times 10^{-5}}{10^{-4} + x} \quad (\text{H})$$

$$L_m(10^{-3}) = \frac{2\pi \times 10^{-5}}{10^{-4} + 10^{-3}} = 57.09 \text{ mH}$$

$$L_m(0) = \frac{2\pi \times 10^{-5}}{10^{-4}} = 62.8 \text{ mH}$$



- 9 -