



$$V_{GS} = V_{GS} + v_{in}(t)$$

$$= DC + AC$$

NONLINEAR!

$$\frac{V_{DD} - V_{OUT}}{R_L} = I_Q = f(V_{GS}, V_{OUT}) \quad DC$$

solve for  $V_{OUT}$  either triode or active eqn.

usually NOT 2.5V, but close VARIES with temp.

1st ORDER

add  $v_{in}(t)$  use TAYLOR expansion, take time VARYING  $v_{in}(t), v_{out}(t)$

out of NONLINEAR FUNCTIONS, WORRY ABOUT REGION OF VALIDITY!

NONLINEAR DIFF. EQU.

$$\frac{V_{DD} - V_{OUT} - v_{out}}{R_L} = f(V_{GS} + v_{in}, V_{OUT} + v_{out}) + C_L \frac{dv_{out}}{dt}$$

$$= I_Q + v_{in} \frac{\partial f}{\partial V_{GS}} + v_{out} \frac{\partial f}{\partial V_{DS}} + C_L \dot{v}_{out}$$

$$\frac{V_{DD} - V_{OUT}}{R} - \frac{v_{out}}{R_L} = I_Q + g_m v_{in} + \frac{v_{out}}{r_{DS}} + C_L \dot{v}_{out}$$

DC operating point zero order eqn.

$$\frac{V_{DD} - V_{OUT}}{R_L} = I_Q(V_{GS}, V_{OUT})$$

DON'T FORGET  $C_{gs} = \left. \frac{\partial Q}{\partial V_{GS}} \right|_{Q \text{ POINT}}$

1st ORDER LINEAR EQUATION.

$$0 = g_m v_{in} + v_{out} \left( \frac{1}{r_{DS}} + \frac{1}{R_L} \right) + C_L \dot{v}_{out}$$

ZERO & FIRST ORDER

solve both (sequentially), then combine back for total ANSWER.