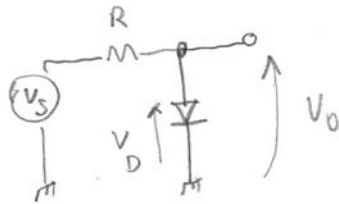


SMALL SIGNAL MODEL (PERTURBATION THEORY FOR
 FIRST DIODE CIRCUITS, SOLVING NONLINEAR DIFF EQU.)
 THEN TRANSISTOR CIRCUITS



$$V_0 = V_D$$

$$I_D = I_s \exp(V_D/V_T)$$

$$\text{LET } V_s = \text{DC} + v_{in} = 5V + v_{in}$$

$$v_{in} \text{ is AC, } A \sin \omega t$$

KCL at V_0 NODE:
$$\frac{5 + v_{in} - V_D}{R} = I_D = I_s \exp(V_D/V_T)$$

LET $V_D = V_D + v_d = \text{DC} + \text{AC}$
$$I_D = I_s \exp\left(\frac{V_D}{V_T}\right) \cdot \exp(v_d/V_T)$$

(USE v_d vs V_D FOR BETTER NOTATION)
$$= I_B \exp(v_d/V_T)$$

$$\frac{5 + v_{in} - V_D - v_d}{R} = I_B \exp(v_d/V_T) = I_B + I_B \frac{v_d}{V_T} \quad \text{when } \frac{v_d}{V_T} \ll 1$$

DIVIDE INTO TWO EQUS. (AND TWO CIRCUITS) I_B is DIODE DC CURRENT
 ONE DC, ONE AC (LINEAR, SMALL SIGNAL)


$$\frac{5 - V_D}{R} = I_B \quad \frac{v_{in} - v_d}{R} = \frac{v_d}{r_d} \quad r_d = \frac{V_T}{I_B} \quad v_d = \frac{r_d}{r_d + R} v_{in}$$

⚡ SOLVE FOR V_D , THUS $I_B \Rightarrow$ FIND r_d , SOLVE AC EQU. FOR v_d

$$V_0 = V_D$$

①

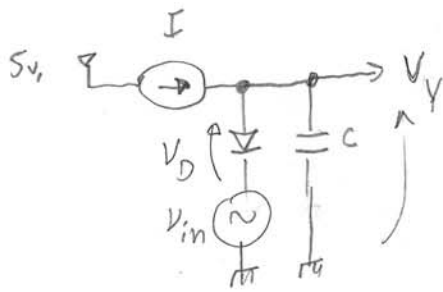NEED C, L, etc, to actually get NONLINEAR DIFF EQU.



USE \$V_Y\$ vs \$V_D\$ FOR SMALL SIGNAL NOTATION

$$I_D = I_S \exp(V_D/V_T)$$

$$I = I_S \exp(V_D/V_T) + C \frac{dV_Y}{dt} \quad \text{KCL at } V_Y$$

$$v_{in} + V_D = V_Y \quad \text{KVL}$$

USE SMALL SIGNAL APPROACH FOR EACH KCL, KVL, THEN SOLVE DC & AC CIRCUITS SEPERATELY! SOLVE DC FIRST (WHY?)

$$\text{KCL} \left\{ \begin{aligned} I &= I_S \exp[(V_D + v_d)/V_T] + C \frac{d(V_Y + v_y)}{dt} = I_B + \frac{v_d}{r_d} + C \frac{d v_y}{dt} \\ I_B &= I_S \exp V_D/V_T \text{ as before: DC eqn. } I = I_B \end{aligned} \right.$$

$$\text{AC eqn. } 0 = v_d/r_d + C \frac{d v_y}{dt}$$


$$\text{KVL } v_{in} + V_D + v_d = V_Y + v_y$$

$$\text{DC eqn } V_D = V_Y$$

$$\text{AC eqn. } v_{in} + v_d = v_y$$

$$\text{DC only } I = I_S \exp(V_D/V_T) \quad V_Y = V_D \quad \text{FIND } V_D, V_Y \text{ FOLLOW}$$

AC CIRCUIT

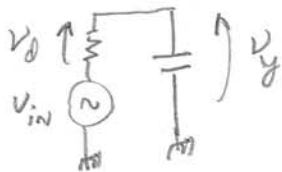

\$v_y\$ is a LOW PASS FILTER OF \$v_{in}\$

$$v_y = \frac{1/j\omega C}{1/j\omega C + r_d} v_{in} = \frac{v_{in}}{1 + j\omega r_d C}$$

(2)