



# L10 – additional State Machine examples

---



# States Machine Design

---

- Other topics on state machine design
  - Examples that are Equivalent
  - More one hot examples
  
- Ref: text Unit 15.4, 15.5, 15.8




# Equivalent State Machines

---

- So far have seen that equivalent states in the state table of a sequential machine are equivalent and can be removed.
- How about the equivalence between two sequential circuits?
  - *Two sequential circuits are equivalent if they are capable of doing the same work.*
 
# Equivalence of two machines

- Consider a sequential machine
  - (ref lect 6) – a machine to detect 101 results in a state graph of with state table




Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1
 
# Now consider a second machine

---


- Consider a machine to detect 010, the complement of the other machine.
- Not yet developed - A is starting state where any number of 1's has been received.


 
# State A and state B


□ State A is starting state.

- On a 1 stay there
- On a 0 go to state B



□ State B

 
- On a 0 stay there
- On a 1 now have 01 so go to C



# State C

 
## □ In state C

- On a 0 have 010 as last 3, output a 1 and go back to B.
- On a 1 have a 1 as last input and return to A


 
# Machine and state table

- Can generate a state table for this 010 sequential machine





Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	A	0	0
B	B	C	0	0
C	B	A	1	0


  
# Question

- Are the sequential circuits to detect 010 and 101 as the last 3 equivalent?



# Look at next state tables

- The tables for the two machines are and develop an equivalence implication table

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	A	0	0
B	B	C	0	0
C	B	A	1	0


S0			
S1			
S2			
	A	B	C

# Start on table

- Mark output incompatible states
  - S2-A,B,C    C-S0,S1,S2

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	A	0	0
B	B	C	0	0
C	B	A	1	0

 

# Now the other blocks

## □ Implied next states


Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	A	0	0
B	B	C	0	0
C	B	A	1	0

<i>S0</i>	S0-B S1-A	S0-B S1-C	X
<i>S1</i>	S2-B S1-A	S2-B S1-C	X
<i>S2</i>	X	X	X
	A	B	C

# Check implied next states

- On pass 1 remove
  - S1-C and S2-B

 

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

Pr state	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	A	0	0
B	B	C	0	0
C	B	A	1	0


# Check implied next states

□ On pass 2 remove

- S1-A
- Now all blocks are Xed


□ What does this tell us?

 - The machines are incompatible.
- To be compatible one block in each row and one block in each column need to be un-Xed and only one.
- If more than one – says machine incompatible or one or both not minimal


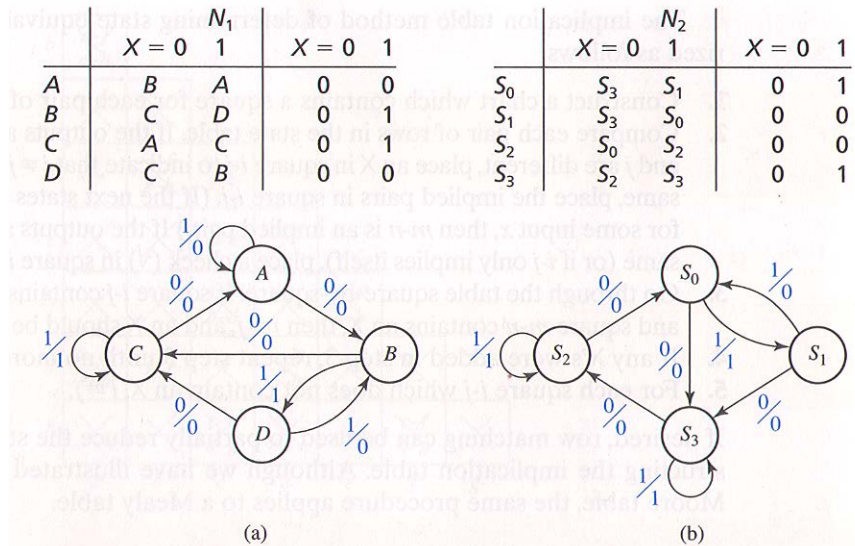
# An example

- State tables and state graphs of two sequential machines. Figure 15-6 from the text.
- Equivalent?





# Proving equivalence


---

- Again will use an implication table.
  - Only this time, it is the full square.
  - Along bottom are the states of one machine
  - Along the side are the states of the second.
- Start by removing output incompatible states.


 
# The equivalence implication table

- X squares where the outputs are incompatible
- Enter implied equivalence pairs for remaining states.



$S_0$	×	$C-S_3$ $D-S_1$	$A-S_3$ $C-S_1$	×
$S_1$	$B-S_3$ $A-S_0$	×	×	$C-S_3$ $B-S_0$
$S_2$	$B-S_0$ $A-S_2$	×	×	$C-S_0$ $B-S_2$
$S_3$	×	$C-S_2$ $D-S_3$	$A-S_2$ $C-S_3$	×
	A	B	C	D

(a)

# Step 2

- Go back through and remove the implied equivalence pairs that were Xed on the first pass. Continue until no further Xs are entered.
- If there is one square not Xed in each row and each column, the state machines are equivalent. (When both are minimal)
- Consider problem 15-17 in text Does this work if the state tables are of different size?

$s_0$	X	$C-S_3$ $D-S_1$	<del><math>A-S_3</math></del> <del><math>E-S_1</math></del>	X
$s_1$	<del><math>B-S_3</math></del> <del><math>A-S_0</math></del>	X	X	$C-S_3$ $B-S_0$
$s_2$	$B-S_0$ $A-S_2$	X	X	<del><math>C-S_0</math></del> <del><math>B-S_2</math></del>
$s_3$	X	<del><math>C-S_2</math></del> <del><math>D-S_3</math></del>	$A-S_2$ $C-S_3$	X
	A	B	C	D

(b)

# Problem 15.17

## □ The problem statement




15.17 Circuits  $N$  and  $M$  have the state tables that follow.

- Without first reducing the tables, determine whether circuits  $N$  and  $M$  are equivalent.
- Reduce each table to a minimum number of states, and then show that  $N$  is equivalent to  $M$  by inspecting the reduced tables.

$M$				$N$			
	$X = 0$	$1$		$X = 0$	$1$		
$S_0$	$S_3$	$S_1$	$0$	$A$	$E$	$A$	$1$
$S_1$	$S_0$	$S_1$	$0$	$B$	$F$	$B$	$1$
$S_2$	$S_0$	$S_2$	$1$	$C$	$E$	$D$	$0$
$S_3$	$S_0$	$S_3$	$1$	$D$	$E$	$C$	$0$
				$E$	$B$	$D$	$0$
				$F$	$B$	$C$	$0$

# Minimize Sx machine


□ Can it be reduced?

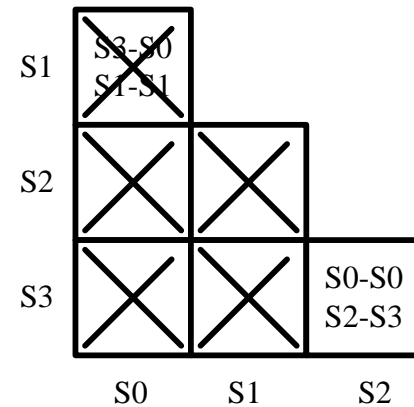  

□ YES
 
# Reduced machine

- States S2 and S3 are equivalent – in fact S2 is not reachable unless the machine comes up in that state at startup and it can never reach S2 again.



# Significance

- Now consider the equivalence implication table. What is the implication if S2 replaces state S2 and S3?

	A	B	C	D	E	F
S0	X	X	<del>S3 - E S1 - D</del>	<del>S3 - E S1 - C</del>	S3 - B S1 - D	S3 - B S1 - C
S1	X	X	S0 - E S1 - D	S0 - E S1 - C	<del>S0 - B S1 - D</del>	<del>S0 - B S1 - C</del>
S2	S0 - E S2 - A	S0 - F S2 - B	X	X	X	X
S3	S0 - E S3 - A	S0 - F S3 - B	X	X	X	X



# Incompletely Specified

---

- Incompletely Specified State Tables
  - State tables that contain don't cares.
  - Results in reduced logic
  
- Determining the best way to fill in the don't cares is another of the *n-p complete* problems.
- For this course do the most logical approach.



# One Hot

---

- CPLDs and FPGAs have a good number of F/Fs onboard. The F/Fs are there whether they are used or not, so a circuit with the minimum number of F/Fs is not the ultimate objective.
- For these devices the objective is to reduce the total number of logic cells used and the interconnection between cells.
- One hot encoding is one approach to have shorter signal paths and reduce logic cells.






# What is one hot?

---

- ❑ One hot is a method where a flip flop is used for each state in the state machine. A state machine with  $n$  states will require  $n$  flip flops in its realization.
- ❑ One hot realization is excellent for controllers that step through a set sequence of linear steps.
- ❑ Text gives example of a multiplier controller state graph which is not linear.
 
# The full circuit

- Desire  $Z=1$  when  $X_{-1} X_{-2} X_{-3}$  is 101.
- Simply construct the combinational logic with inputs from the F/F outputs.






# Compare the gates

---

- Traditional implementation for sequence detector (from text)
  - 2 F/Fs
  - 2 2-input AND gates
  - 1 INV
  
- One hot implementation
  - 3 F/Fs
  - 1 3-input AND gate

 
# Another example

- Design a circuit to detect when the value represents a BCD digit
- Could also detect when it is not a valid BCD digit, i.e., 10,11,12,13,14,15 which is
  - 1010,1011,1100,1101,1110,1111 or
  - 101x,11xx
  - As last 4 inputs


 
# BCD digit detector

- The logic
- In groups of 4
- Detect when
  - 101x
  - 11xx
- $Z=1$  valid BCD





# Lecture summary

---

- Have again looked at state machine equivalence.
- One hot encoding and it is interesting for many implementations.