



ALUs and Data Paths

Subtitle: How to design the data path of a processor.



Lecture overview

- General Data Path Design
- Design of a multifunction ALU



Design of ALUs and Data Paths

- Objective: Design a General Purpose Data Path such as the datapath found in a typical computer.
- A Data Path Contains:
 - Registers – general purpose, special purpose
 - Execution Units capable of multiple functions

ALU Operations

- Add ($A+B$)
- Add with Carry ($A+B+Cin$)
- Subtract ($A-B$)
- Subtract with Borrow ($A-B-Cin$)
- [Subtract reverse ($B-A$)]
- [Subtract reverse with Borrow ($B-A-Cin$)]
- Negative A ($-A$)
- Negative B ($-B$)
- Increment A ($A+1$)
- Increment B ($B+1$)
- Decrement A ($A-1$)
- Decrement B ($B-1$)
- Logical AND
- Logical OR
- Logical XOR
- Not A
- Not B
- A
- B
- Multiply Step or Multiply
- Divide Step or Divide
- Mask
- Conditional AND/OR (uses Mask)
- Shift
- Zero

A High Level Design

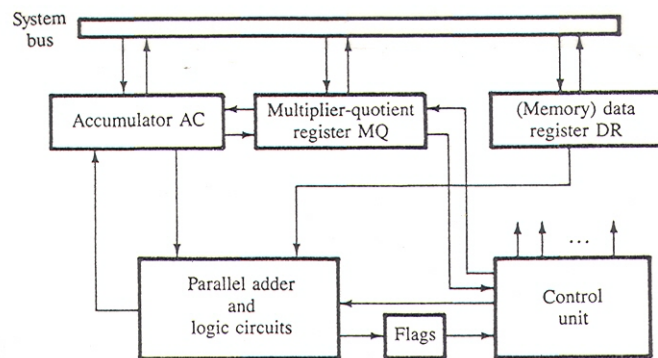


FIGURE 3.59
Structure of a basic fixed-point ALU.

The use typically made of these registers may be defined concisely as follows:

Addition:	$AC \leftarrow AC + DR$
Subtraction:	$AC \leftarrow AC - DR$
Multiplication:	$AC, MQ \leftarrow DR \times MQ$
Division:	$AC, MQ \leftarrow MQ \div DR$
AND:	$AC \leftarrow AC \wedge DR$
OR:	$AC \leftarrow AC \vee DR$
EXCLUSIVE-OR:	$AC \leftarrow AC \oplus DR$
NOT:	$AC \leftarrow \overline{AC}$

The AMD 2901 Bit Slice ALU


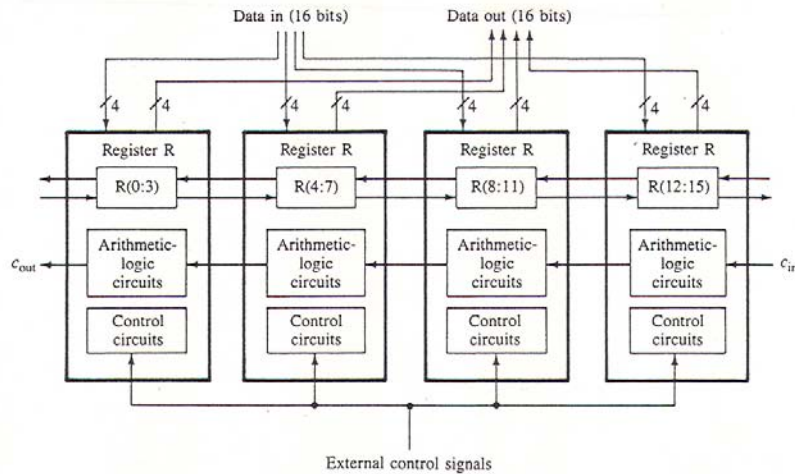


FIGURE 3.60
A 16-bit bit-sliced ALU composed of four 4-bit slices.

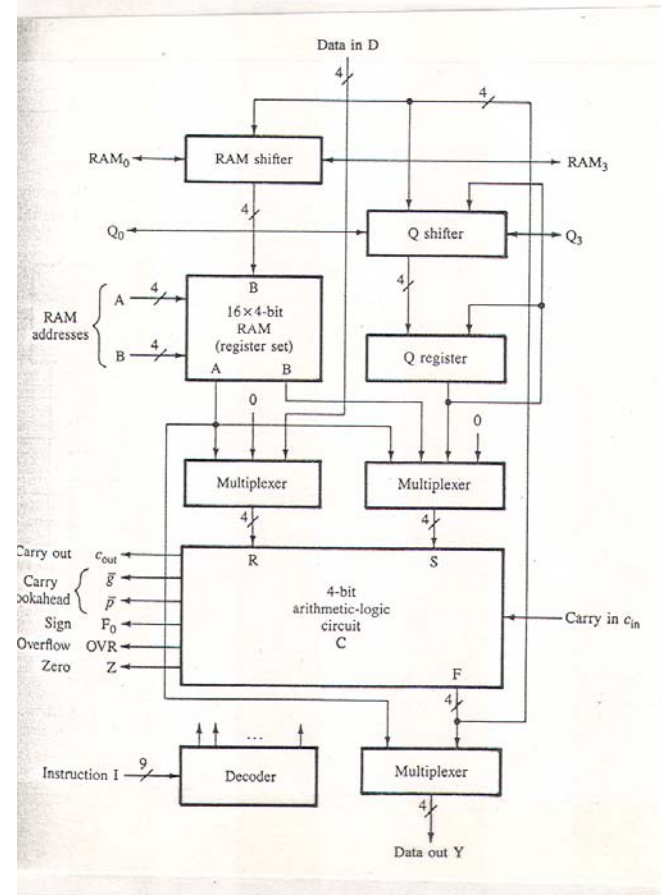

The Architecture

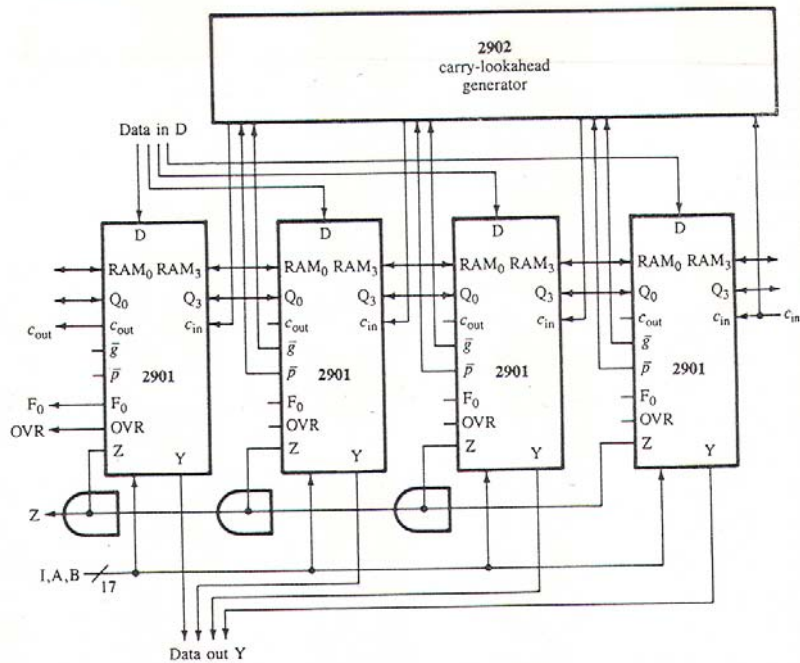


FIGURE 3.62
A 16-bit 4-slice array of 2901s employing carry lookahead.

ALU sources			ALU destinations and shifts		
$I_S = I_0 I_1 I_2$	R	S	$I_D = I_6 I_7 I_8$	Y	RAM(B) Q
000	RAM(A)	Q	000	F	— F
001	RAM(A)	RAM(B)	001	F	— —
010	0	Q	010	RAM(A)	F —
011	0	RAM(B)	011	F	F —
100	0	RAM(A)	100	F	$F \div 2$ $Q \div 2$
101	D	RAM(A)	101	F	$F \div 2$ —
110	D	Q	110	F	$2 \times F$ $2 \times Q$
111	D	0	111	F	$2 \times F$ —

$I_F = I_3 I_4 I_5$	ALU function
000	$R + S + C_{in}$
001	$S - R - C_{in}$
010	$R - S - C_{in}$
011	$R \vee S$ (OR)
100	$R \wedge S$ (AND)
101	$\bar{R} \wedge S$ (COMPLEMENT-AND)
110	$R \oplus S$ (EXCLUSIVE-OR)
111	$R \oplus \bar{S}$ (EXCLUSIVE-NOR)




Arithmetic Logic Circuits

□ The Brute Force Approach

□ A more modern approach

Arithmetic Logic Circuits


- The Brute Force Approach

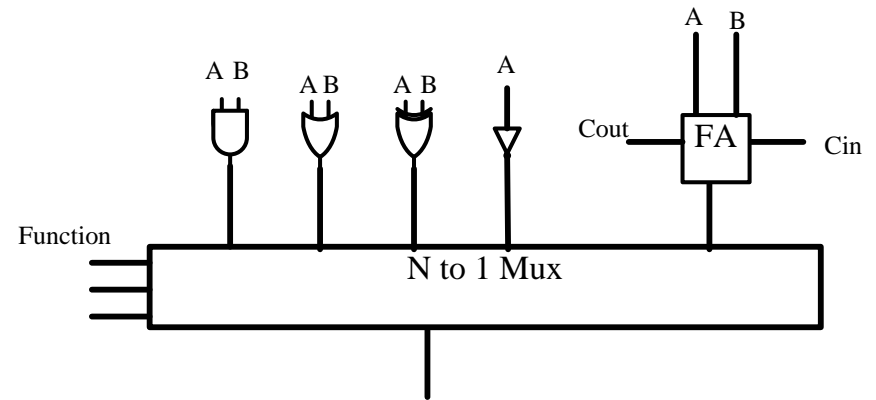

- A more modern approach

Arithmetic Logic Circuits


□ The Brute Force Approach

 

□ A more modern approach

A Generic Function Unit

 - Desire a generic functional unit that can perform many functions





- A 4-to-1 mux will perform all basic logic functions of 2 inputs

Low level implementation


At the implementation
Level the design can be
With transmission gates
Very important for VLSI
implementation

  Implementation has a total
Of 16 transistors.



Low level implementation

 - An implementation in pass gates (CMOS)
- When the control signal is a '1' the value will be transmitted
- Otherwise it is an open switch



A	B	A'	B'	G(A,B)	AB	A+B	AxorB
0	0	1	1	G0	0	0	0
0	1	1	0	G1	0	1	1
1	0	0	1	G2	0	1	1
1	1	0	0	G3	1	1	0

Lets look at Binary Addition

□ We can use this generic function unit construct a generic ALU.

□ For Binary Addition consider the following:

■ $SUM_i = A_i \text{ xor } B_i \text{ xor } C_i$

■ $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

An Alternative - Define two signals

- Equations for P and K
- $P_i = A_i \text{ xor } B_i$
- $K_i = A' B'$

- Now can reform equations into functions of P and K

P	K	A	B	Cin	Sum	Cout
0	1	0	0	0	0	0
0	1	0	0	1	1	0
1	0	0	1	0	1	0
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	0	1	0	1	0	1
0	0	1	1	0	0	1
0	0	1	1	1	1	1


New functions

- Using these definitions of P and K
- $SUM_i = P_i \text{ xor } C_i$
- $C_{i+1} = P_i C_i + P_i' K_i'$
- $\quad = P_i C_i + AB$

- You can use the generic functional blocks to generate P and K and then select the correct function for final output


A bit slice of the ALU

 - Slice starts out with a generic unit which can produce any function of inputs A_i and B_i to produce P
- Need another to produce K
- And a 3rd to generate the result
- And also need a dedicated unit to compute the carry out, the C_{i+1} term



Generation of the carry out

 - The carry chain is the critical path for arithmetic operations.
- A simple ripple carry circuit is shown here for the slice
- Actual implementation depend on the technology in which implemented.






Carry chain implementation

- CMOS – Manchester carry chain using precharge pulldown logic works well.
- ECL – Carry look-ahead circuitry works well as ECL allows for large fan-in wired OR gates.

Multibit implementation

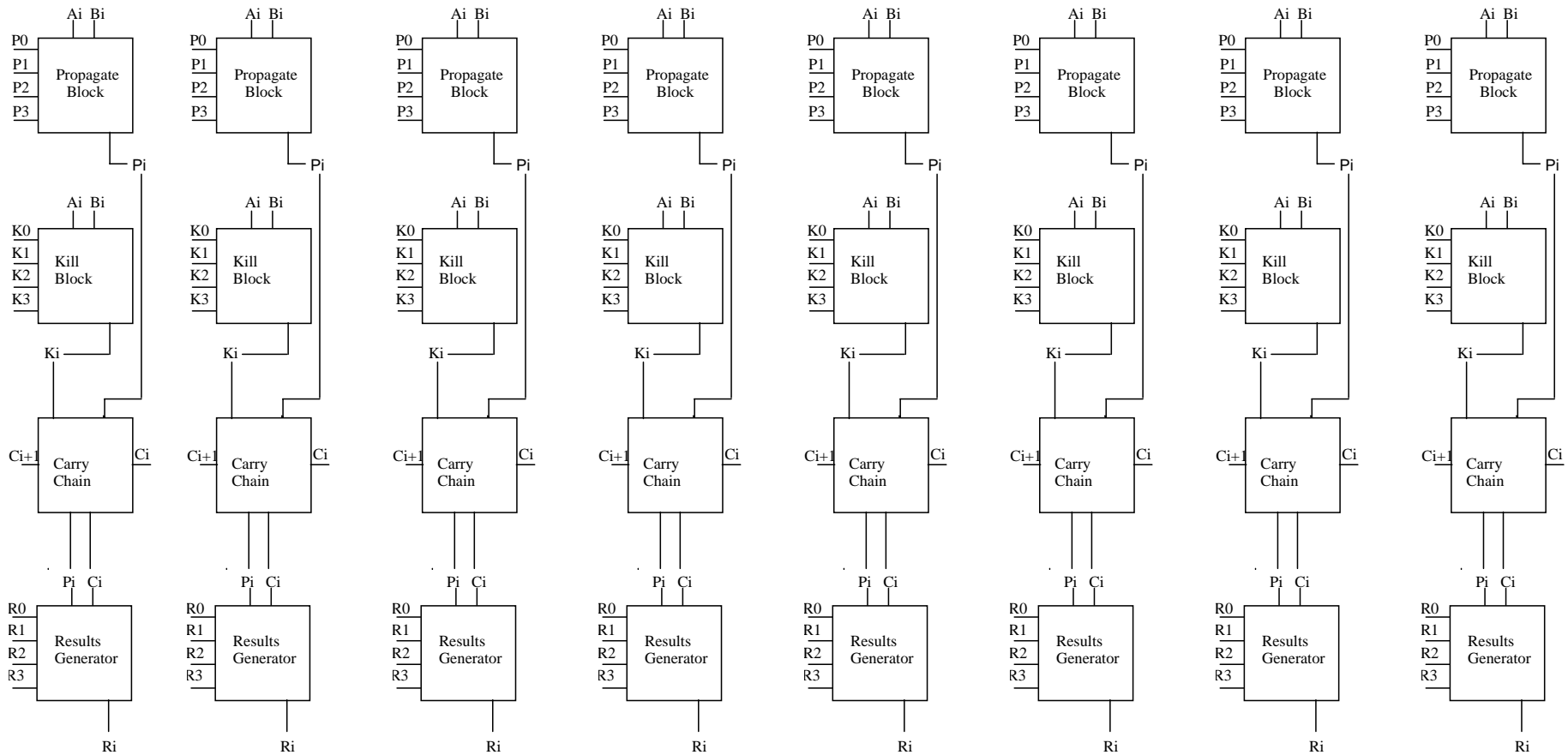

Function codes

A	B	A'	B'	G	0	NOR	A'B	A'	AB'	B'	XOR	NAND	AND	XNOR	B	A'+B	A	A+B'	OR	1
0	0	1	1	G ₀	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	1	0	G ₁	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	1	G ₂	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	G ₃	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

The G values for the various logic functions
 By setting the value of the G inputs the output is the
 Corresponding logic function of the data which comes in
 On the select inputs.

Binary Subtraction

- Much like addition but now choose

- $P = A \text{ xnor } B$

- $K = A B'$

- Diff

- $D = A \text{ xor } B \text{ xor } \text{Bin}$

- $= A \text{ xnor } B \text{ xnor } \text{Bin}$

- Borrow Out

- $\text{Bout} = P \text{ Bin} + P' K'$

P	K	A	B	Bin	Diff	Bout
1	0	0	0	0	0	0
1	0	0	0	1	1	1
0	0	0	1	0	1	1
0	0	0	1	1	0	1
0	1	1	0	0	1	0
0	1	1	0	1	0	0
1	0	1	1	0	0	0
1	0	1	1	1	1	1

The codes to have the ALU work

- Consider as we go to the sliced ALU
- Logic function done in the P generic unit
- Math used all the blocks

Function	P	K	R	Cin
A	12	---	12	---
A and B	8	--	12	---
OR	14	---	12	---
A + B + Cin	6	1	6	Cin
A+B	6	1	6	0
Incr A	12	3	6	1
A - B	9	4	9	0 or Bin

Multibit implementation

