



Project Step 1

Due Friday Apr 4th

A 4-to-1 mux.

The Unit to Model – A 4-to-1 Mux

□ Truth Table

  

This Unit Can perform any of the logic functions of 2 inputs



Project Step 1

- **Objective – Model the unit. Connect the data inputs, A and B to the Select inputs, the G inputs to the corresponding data lines.**
- **You will then have a “generic” logic unit that can perform any of the functions of two inputs.**

The 16 functions

□ The 16 functions are:

(note that the G values are Hex)

<u>G3</u>	<u>G2</u>	<u>G1</u>	<u>G0</u>	<u>Function</u>
□			0	zero
□			1	NOR
□			2	A'B
□			3	A'
□			4	AB'
□			5	B'
□			6	XOR
□			7	NAND
□			8	AND
□			9	XNOR
□			A	B
□			B	A' + B
□			C	A
□			D	A + B'
□			E	OR
□			F	one

How to model

- Model using a dataflow style
 - Concurrent signal assignment statement
 - `Y <= (A AND B OR C) NOR D;`
 - Conditional signal assignment statement (pp 207-209)
 - `Y <= '1' WHEN Q = "000" ELSE`
 - `A AND C WHEN Q = "001" ELSE ...`
 - Selected signal assignment statement (pp 272-275)
 - `WITH bit_vector_signal SELECT`
 - `Y <= '0' WHEN "0000"`
 - `'1' WHEN "0010" | "0011"`
 - `A WHEN OTHERS;`
- Note that all three of these are concurrent statements of the language.



The testbench

- In this assignment you are given the testbench which will stimulate your model by applying exhaustive testing.
- Copy the file `pr_step1.vhdl`
 - FROM the web page or from `~degroat/ee762_assign`
- The ENTITY is provided for you. Enter the architecture.



Simulate and get results

- Compile the file
- Simulate the design – generate both waveform and a listing of the results.
- Turn in
 - Copy of the code
 - Copy of the listing file
 - Copy of the waveform. **BE SURE TO GET THE ENTIRE SIMULATION.** Use zoom as appropriate. You will need to simulate for 5200 ns to run all the test cases.