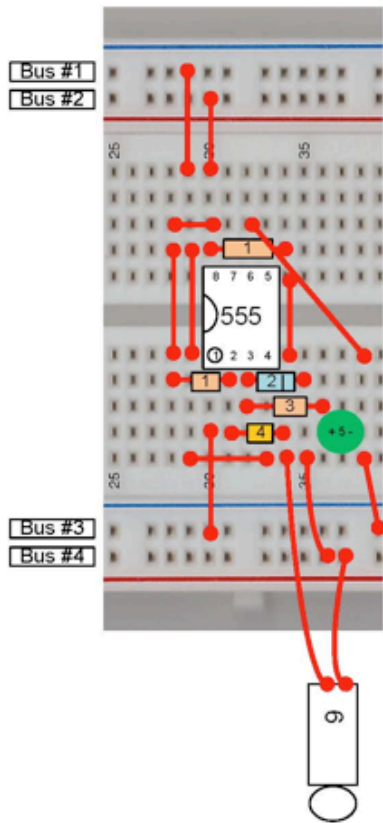


## QUIZ GAME CIRCUIT



- #1 – 10000Ω Resistor
- #2 – 4148 Diode (dark black line oriented on right)
- #3 – 470Ω Resistor
- #4 – 0.1 μF (microfarad) Capacitor
- #5 – Colored LED
- #6 – Push Button

- Bus #1 : Reset
- Bus #2 : +5 V
- Bus #3 : Ground
- Bus #4 : Trigger Line

## COMPONENT OVERVIEW

LED		Emits light when an electric current is applied in one direction
Diode		Allows electric current to flow in only one direction
Capacitors		Stores energy (like a charged battery)
Resistors		Prohibits the amount of electric current
555 Timer		Synchronizes the digital logic

### For LEDs and Capacitors:

- Long lead is positive (anode)
- Short lead is negative (cathode)




## RESISTOR COLOR CHART



Note: We are ignoring the 4<sup>th</sup> band for this experiment.

Color	1 <sup>st</sup> band	2 <sup>nd</sup> band	3 <sup>rd</sup> band (multiplier)
Black	0	0	$\times 10^0$
Brown	1	1	$\times 10^1$
Red	2	2	$\times 10^2$
Orange	3	3	$\times 10^3$
Yellow	4	4	$\times 10^4$
Green	5	5	$\times 10^5$
Blue	6	6	$\times 10^6$
Violet	7	7	$\times 10^7$
Gray	8	8	$\times 10^8$
White	9	9	$\times 10^9$

## DIGITAL LOGIC OVERVIEW

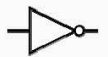Logic	Symbol	Boolean algebra	Truth table		
			INPUT	OUTPUT	
AND		A·B	A	B	A AND B
			0	0	0
			0	1	0
			1	0	0
			1	1	1
OR		A+B	A	B	A OR B
			0	0	0
			0	1	1
			1	0	1
			1	1	1
NOT		$\bar{A}$	A	NOT A	
			0	1	
			1	0	

For this experiment:

- Ground is represented by logic 0
- 5 Volts is represented by logic 1